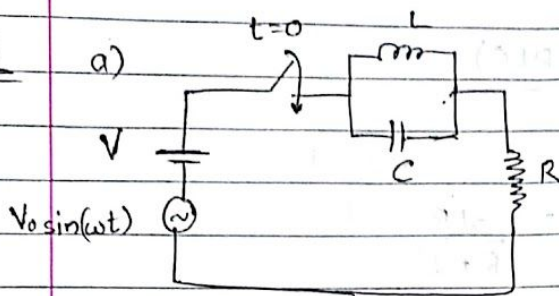


Assignment 7 solution

Q.1



For AC,

$$Z_s = R + sL \parallel \frac{1}{sC}$$

$$= R + \frac{L/C}{\frac{s^2 LC + 1}{sC}}$$


$$\therefore Z_s = \frac{R + sL + s^2 RLC}{1 + s^2 LC}$$

$$s = j\omega, \therefore Z_s = \frac{R + j\omega L + -\omega^2 RLC}{1 - \omega^2 LC}$$

$$i_{ac} = \frac{V_o \sin(\omega t)}{Z_s} \Rightarrow i_{ac} = \frac{V_o (1 - \omega^2 LC) \sin \omega t}{R(1 - \omega^2 LC) + j\omega L}$$

$$\text{for DC, } I_{dc} = \frac{V_o}{R} (1 - e^{-Rt/L} + e^{-t/Rc})$$

$$i = i_{ac} + I_{dc}$$

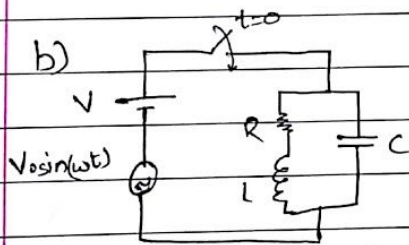

For AC,


$$Z_s = (R + j\omega L) \parallel \frac{1}{j\omega C}$$

$$= \frac{(R + j\omega L) / j\omega C}{j\omega RC + -\omega^2 LC + 1}$$

$$\therefore Z_s = \frac{R + j\omega L}{1 + j\omega RC - \omega^2 LC}$$

$$i_{ac} = \frac{V_o \sin(\omega t)}{Z_s} = \frac{V_o (1 + j\omega RC - \omega^2 LC) \sin(\omega t)}{R + j\omega L}$$

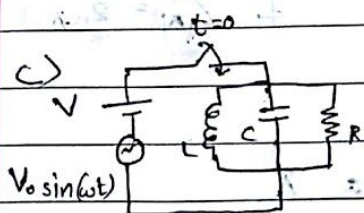
$$\text{for DC, } I_{dc} = \frac{V}{R} (1 - e^{-Rt/L})$$



$$Z_c = R \parallel j\omega L \parallel \frac{1}{j\omega C}$$

$$Z_s = \frac{j\omega LR}{R + j\omega L - \omega^2 RLC}$$
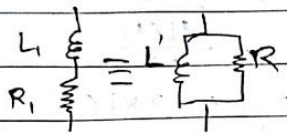
$$i_{ac} = \frac{V \sin(\omega t)(R + j\omega L - \omega^2 RLC)}{j\omega RL}$$



$$sL_1 + R_1 = \frac{sL'R'}{R' + sL'}$$

$$j\omega R'L_1 + -\omega^2 L'L_1 + R'R_1 + j\omega L'R_1 = j\omega L'R'$$

$$\therefore R'R_1 = \omega^2 L'L_1 \quad \& \quad \omega(R'L_1 + L'R_1) = L'R'$$


$$\therefore L' = L_1 \left[\frac{1 + R_1^2}{\omega^2 L_1^2} \right]$$

$$Q = \frac{\omega L_1}{R_1}$$

$$\therefore L' = L_1 \left[\frac{1 + \frac{1}{Q^2}}{\frac{1}{Q^2}} \right] \Rightarrow R' = R_1 Q^2 \left[\frac{1 + \frac{1}{Q^2}}{\frac{1}{Q^2}} \right]$$

Near resonance, Q is large. $\therefore L' \rightarrow L_1$ & $R' \rightarrow R_1 Q^2$
at $\omega_0 = \frac{1}{\sqrt{LC_1}}$, $Z_s = R_1 Q^2$

Q.2

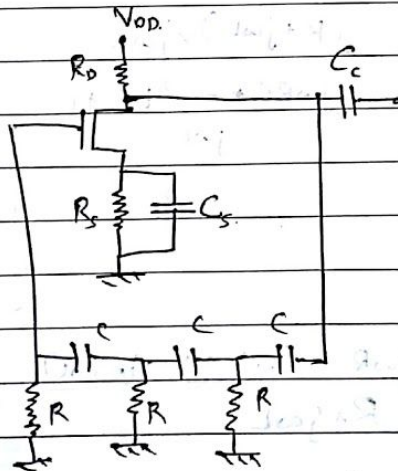

~~without feedback~~, the source of resistor will be shorted by the bypass capacitor.

$$\therefore \text{open-loop-gain} = -g_m R_0 = A$$

$$\beta = \left(\frac{R}{R + \frac{1}{j\omega C}} \right)^3 = \left(\frac{j\omega CR}{1 + j\omega CR} \right)^3$$

for Barkhausen criterion, $|A\beta| = 1$ & $\angle A\beta = 2n\pi$

phase shift by op-A is 180°

\therefore phase shift by β should be 180°

$$\text{phase shift by } \beta = \tan^{-1}\left(\frac{1}{\omega RC}\right) = \pi$$

$$\therefore \frac{1}{\omega R C} = \frac{1}{\sqrt{3}} \Rightarrow C = \frac{1}{\omega R \sqrt{3}}$$

$$\omega = 2\pi f = 2\pi \times 2\text{ kHz} \quad \& \quad R = 10\text{ k}\Omega$$

$$\therefore \underline{C = 4.6\text{ nF}}$$


Also, as $|A_{\beta}| = 1 \Rightarrow \frac{g_m R_D}{\left(1 + \omega^2 R^2 C^2\right)^{3/2}} = 1$

$$\therefore \frac{g_m R_D \omega^3 R^3 C^3}{\left(1 + \omega^2 R^2 C^2\right)^{3/2}} = 1 \Rightarrow \frac{g_m R_D}{\left(\left(\frac{1}{\omega R C}\right)^2 + 1\right)^{3/2}} = 1$$

$$\therefore \frac{g_m R_D}{\dots} = 8 \Rightarrow \underline{R_D = 800\ \Omega} \quad (\because g_m = 10\text{ mS})$$

Q3.

$$V_o = 10(1 - e^{-V_i})$$

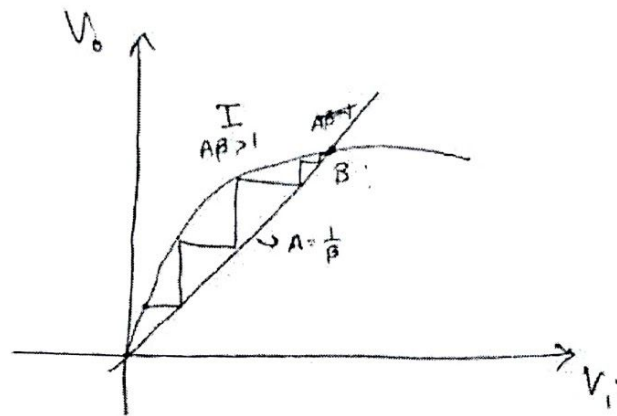


If a point is taken in Region I, because of the feedback the i/p will increase and so gain will decrease (clear from the graph)

Hence at B, the oscillation will become stable as Barkhausen criteria is satisfied. $\{ |AB| = 1 \}$

Hence B is a stable point (where $A = \frac{1}{B}$)

Q4.

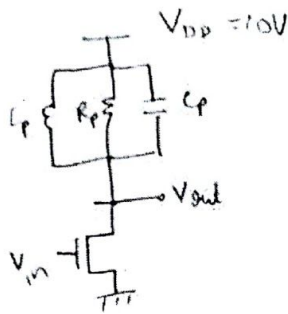

$$(V_{in})_{dc} = 4V \text{ (assumed)}$$

$$\text{Also assume } V_T = 1V$$

$$\Rightarrow V_{GS} - V_T = 3V$$

Clearly max amplitude of V_{in} can be 7V as above
that the saturation region does not exist.
Minimum amplitude is $\frac{V_{DD}}{2} = 5V$

$$A_{gain} = -g_m R_D$$

$$\Rightarrow 5 \leq (V_{in}) g_m R_D \leq 7$$

We take std. i/p of 5mV sin wt and $g_m = 10mS$

$$\Rightarrow 5 \leq (5m) g_m R_p \leq 7$$

$$\Rightarrow 1K \leq g_m R_p \leq 1.4K$$

$$100K\Omega \leq R_p \leq 140K\Omega$$