 


→ Combination of FSMs

- Easier debugging
- Modularity
- Smaller problem size

III CASCADE FORM




eg. 15-step counter using 3-step \times 5-step

$$\begin{aligned} \bullet \quad \delta((q^{(1)}, q^{(2)}), x) &= (\delta_1(q^{(1)}, x), \delta_2(q^{(2)}, \lambda(q^{(1)}, x))) \\ &\quad \text{For } nq \\ \bullet \quad \lambda((q^{(1)}, q^{(2)}), x) &= \lambda_2(q^{(2)}, \lambda_1(q^{(1)}, x)) \\ &\quad \text{For } y \end{aligned}$$

III Parallel FSMs


PARALLEL FORM

 

- $s[(q_1, q_2), x] = (s_1(q_1, x), s_2(q_2, x)) = nq[k]$


- $\lambda[(q_1, q_2), x] = f(\lambda_1(q_1, x), \lambda_2(q_2, x)) = y[k]$

eg Oscillatory cascade

 

No stable output

eg Cascade with uncertain output

 


Two possible stable outputs

- Hence, we avoid combinatorial logic loops.

IV D FLIP FLOP

A] SR Bistable

 


- Contains loop consisting of two NAND in series.
- Can store one bit (Q) at for given \bar{S}, \bar{R}

	\bar{S}	\bar{R}	Q	\bar{Q}	
x	0	0	1	1	useless
	0	1	1	0	{ forcing state \rightarrow Set
	1	0	0	1	\rightarrow Reset
	1	1	Q_{old}	\bar{Q}_{old}	holding state


15/3

 • For $(\bar{S}, \bar{R}) \equiv (0, 0)$, the circuit is entering an indeterminate. For any future input, we cannot know what value Q will take if we give $(\bar{S}, \bar{R}) \equiv (1, 1)$ just after $(0, 0)$





if both NAND gates have delay 1

 if NAND with \bar{S} has delay 0.1 instead of 1




5/3



→ Problems in our delay model

  

→ Inertial Delay Model

 If the input pulse width is narrower than the delay of the gate, it does not appear at the output.



  


Change in Q is swallowed by lower NAND gate


- How long should \bar{S} be made 1 to change both Q & \bar{Q} successfully

3

 B] → Level-triggered ~~D Flip Flop~~ (latch) Latch.



 
- When $CLK = 1$, $Q = D$ after a small delay
- When $CLK = 0$, Q holds its previous value.
- Hence, the negative edge of CLK is the sampling instant of D .
- When $CLK = 0$, Q holds value of D that was at negative edge of CLK .
- This is not a flip-flop because Q follows D all throughout CLK instead of just at positive edge.



- For correct sampling of D , value of D should not change in ' $S+H$ ' time. We cannot comment on final Q if it does.

→ $H = 0$

?

 


$$S = d_1 + d_2 + d_3$$

$$d_{0 \rightarrow Q} = d_1 + d_3 \quad \text{or} \quad d_4 + d_1 + d_2 + d_5$$


$$d_{CLK \rightarrow Q} = d_1 + d_2 \quad \text{or} \quad d_4 + d_1 + d_2$$

should be
 $\geq d_1 + d_2$

 

$$t_{CLK} - t_D \geq d_1 + d_2 \Rightarrow t_D \leq t_{CLK} - (d_1 + d_2)$$


$\geq d_1 + d_2$

 


$d_{CLK \rightarrow Q}$

- IF $D = 1$ when $CLK \uparrow$, upper (shorter) path.
0, lower (longer)

A Inverted clock latch.

 

 - Rising edge of CLK is now sampling edge.
- When CLK is low, Q follows D
- high, Q will become D at falling edge.




$$\begin{aligned}
 \rightarrow d_{D \rightarrow Q} &\equiv \text{same} \\
 t_H &= d_c \quad (\text{previous } H + d_c) \\
 S &= \text{previous } S - d_c \\
 d_{CLK \rightarrow Q} &= \text{previous} + d_c
 \end{aligned}$$

1 CLK

D


Q

Master - Slave Flip-flop

 

- When CLK is low, X follows D. Q is unchanged
high, Q X X
- There is no direct connection between D and Q.
- This behaves like a positive edge-triggered circuit.

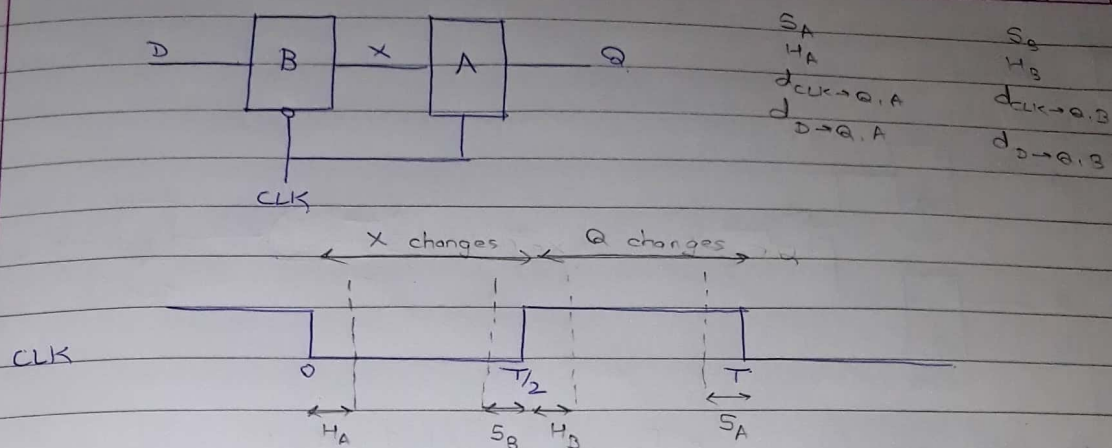20/3 • Sampling edge :- Master - Positive
Slave - Negative



- t_D = time at which D changes

IF we want D to appear at X, $t_D \leq \frac{T}{2} - S_B$

don't want " " " " later, $t_D \geq \frac{T}{2} + H_B$

- Changes in X :- (CLK is low)

- X changes earliest when CLK \downarrow :- $d_{CLK \rightarrow Q, B} \geq H_A$
- latest when CLK is low and

D updates latest :- $\frac{T}{2} - S_B + d_{D \rightarrow Q, B} \leq T$

- Changes in Q :- (CLK is high)


- Earliest, when CLK \uparrow :- $\frac{T}{2} + d_{CLK \rightarrow Q, A}$



- Latest :- Latest of X + $d_{D \rightarrow Q, A} = \frac{T}{2} - S_B + d_{D \rightarrow Q, B} + d_{D \rightarrow Q, A}$
 $\leq T - S_A$, as seen above


- No constraint on outputs (Q)

C] Retiming

 

For both circuits, $C[k+1] = A[k] \cdot B[k]$.

 - In left circuit, setup time of A & B for both flip flops is small
- In right circuit, the flip flop is larger



|||

