

BOOLEAN ALGEBRA

Page No.:

$$\{\Omega, +, \cdot, 0 \in \Omega, 1 \in \Omega, \sim\}$$

Additive identity Multiplicative identity Complement operator.

- If $a, b \in \Omega$, $a+b \in \Omega$, $a \cdot b \in \Omega$
- $a+b = b+a$ $a \cdot b = b \cdot a$
- $a+(b+c) = (a+b)+c$ $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
- $a \cdot (b+c) = a \cdot b + a \cdot c$
- $a+(b \cdot c) = (a+b) \cdot (a+c)$
- ② • $a+0 = a$ $a \cdot 1 = a$
- $\forall a$, there exist an \bar{a} , such that $a \cdot \bar{a} = 0$ and $a + \bar{a} = 1$

I IDENTITIES

1. $0, 1$ and \bar{a} Zero element, one element and complement of every element are unique.

$$0_1 + 0_2 = 0_1 \quad \because 0_2 \in \Omega$$

$$\text{Also } 0_1 + 0_2 = 0_2 \quad \because 0_1 \in \Omega$$

Hence proved.

2. $a \cdot a = a$, $a + \bar{a} = 1$

$$a + (\bar{a} \cdot 0) = (a + \bar{a}) \cdot (a + 0)$$

$$a = 1 \cdot (a + 0)$$

$$a = a + 0$$

$$a + \bar{a} = 1$$

$$(a + \bar{a}) \cdot a = a$$

$$a \cdot a = a$$

3. $1 + a = 1$ and $0 \cdot a = 0$

$$a + \bar{a} + a = 1 + a$$

$$= \bar{a} + a + a$$

$$= \bar{a} + a$$

$$= 1$$

Proof

For uniqueness of complement,

$$\bar{a}_1 = \bar{a}_1 \cdot 1 = \bar{a}_1(a + \bar{a}_2) = \bar{a}_1 \cdot a + \bar{a}_1 \cdot \bar{a}_2 = 0 + \bar{a}_1 \cdot \bar{a}_2 = \bar{a}_1 \cdot \bar{a}_2$$

Similarly, $\bar{a}_2 = \bar{a}_1 \cdot \bar{a}_2$
 $\bar{a}_1 = \bar{a}_2$

4 $a + \bar{a} \cdot b = a + b$

--- BODMAS is always followed

$$\begin{aligned} \text{LHS} &= (a + \bar{a}) \cdot (a + b) \\ &= 1 \cdot (a + b) \end{aligned}$$

5 De Morgan's Laws :- $\overline{a+b} = \bar{a} \cdot \bar{b}$

Show :- $(a+b) \cdot (\bar{a} \cdot \bar{b}) = 0$

$$(a+b) + (\bar{a} \cdot \bar{b}) = 1$$

$$\text{LHS} = a + \bar{a}\bar{b} + b + \bar{a}\bar{b}$$


$$= a + \bar{b} + b + \bar{a}$$

$$= 1$$

$$\overline{a \cdot b} = \bar{a} + \bar{b}$$

→ To define :- A function $f: A \rightarrow B$

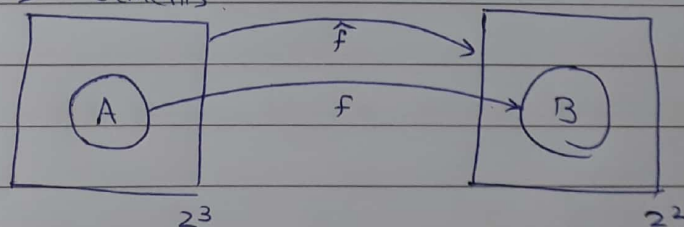If A has 7 elements and B has 3 elements, we do this by defining a function \hat{f} from a box of 2^3 elements to a box of 2^2 elements.



- A is encoded to a 2^3 box. B is encoded to a 2^2 box.
- Elements from 2^3 box not in A have arbitrary images of \hat{f} (does not matter)
- By encoding, Ω can be represent as a set of binary-string elements

Minimal = Atom?

Page No.:

Theorem Cardinality of Ω in Boolean algebra is a power of 2.

Proof {

Definition $a \leq b$, if $a \cdot b = a$

• $0 \leq a \quad \forall a$

• Minimal element: $(u) :- \nexists a \leq u \quad \forall a \neq u$

Only 0 and u are $\leq u$

Definition Atom: $\textcircled{1} a \neq 0$ and $a \cdot b = a$ or $a \cdot b = 0$

Theorem $|\Omega| \geq 2$

Theorem For any Ω , the set of atoms (A) is never empty.

Proof {

Theorem If $a \leq b$ and $b \leq c$, then $a \leq c$

$$ac = (abc) = ab = a$$

• Hence, there can never be a chain $a < b < c < d < a$

}

③

2/1

• In set algebra, $\leq \rightarrow \subseteq$ and atom

• Alternative definition of $u \leq v :-$

$$u \leq v \iff u + v = v$$

Proof

$$u \cdot v = u$$

$$u \cdot v + v = u + v$$

$$(u+1) \cdot v = u + v$$

$$\therefore v = u + v$$

Theorem $u < v \Rightarrow \bar{u} \cdot v \neq 0$

Proof Contradiction: $u < v$, but $\bar{u} \cdot v = 0$

$$u + \bar{u}v = u$$

$$u + v = u$$

$$\therefore v = u$$

Theorem A is the set of atoms and $p \in \Omega$

$$p = \sum_{\substack{a \in A \\ a \leq p}} a$$

- Any element of Ω can be constructed from atoms that are \leq that element

Proof

- Let $w = \sum_{\substack{a \in A \\ a \leq p}} a \Rightarrow w \leq p$

$$(a_1 + a_2)p = a_1p + a_2p = a_1 + a_2$$

$$\therefore a_1 + a_2 \leq p$$

- Suppose $w < p$

$$\Rightarrow \bar{w}p \neq 0$$

$$\therefore \exists a' \in A \text{ such that } a' \leq \bar{w}p$$

$$\therefore a' \leq p$$

Then a' should have been included in w already.

Contradiction

$$w = p$$

- There is a bijection between ^{subsets of A} all atoms and elements of Ω .
 - Every $p \in \Omega$ can be constructed from atoms
 - Every subset of A constructs some $p \in \Omega$.

Proof Let a_i and b_j be atoms such that $\sum a_i = \sum b_j$

$$a_i \cdot (\sum a_i) = a_i \cdot (\sum b_j)$$

$$\Rightarrow a_i = 0$$

Contradiction.

ie Hence, There is a bijection between 2^A and Ω

↑
Power set of A

- If $b \in \Omega \leftrightarrow A_b \in 2^A$ and $c \in \Omega \leftrightarrow A_c \in 2^A$
 then $b+c \leftrightarrow A_b \cup A_c$
 $b \cdot c \leftrightarrow A_b \cap A_c$
 $\bar{b} \leftrightarrow A_b^c$

- Hence, cardinality of Ω is a power of 2

}

- $\Omega = \{ \langle x_1, x_2, x_3, \dots, x_n \rangle \mid x_i \in \{0, 1\} \}$

④

CMOS Logic Gates



Page No.:

- 2-input XOR gate $\therefore (x+y)(\bar{x}+\bar{y})$


I CMOS INVERTER



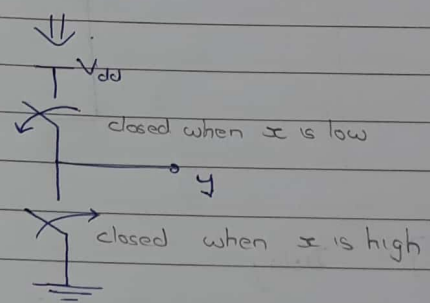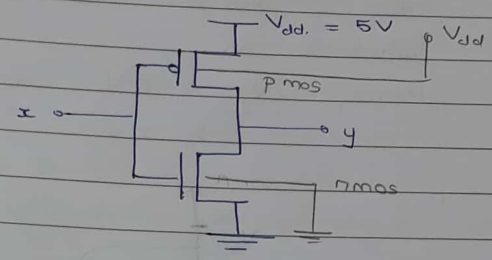
$y = V_{dd}$ when x is low
 $= 0$ when x is high



→ Ideal Inverter

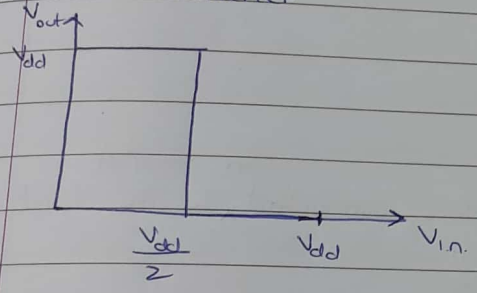


→ Actual characteristics

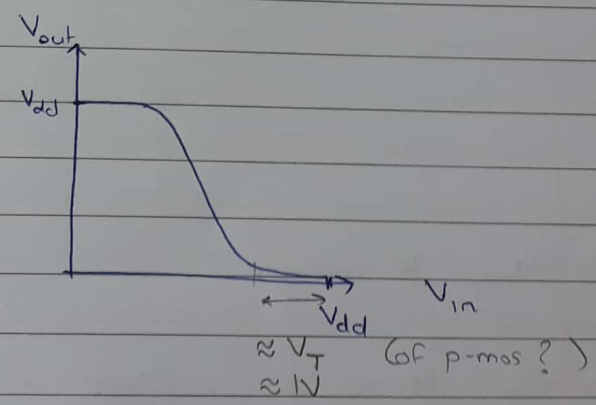

→ Undesirable characteristics

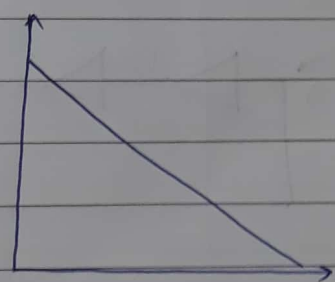
- Poor noise rejection.
- The transition time should be as small as possible.



A] Output characteristics

When we connect a load to 'y', current flows through it. There is also a (resistive) voltage drop across the transistor which is on.

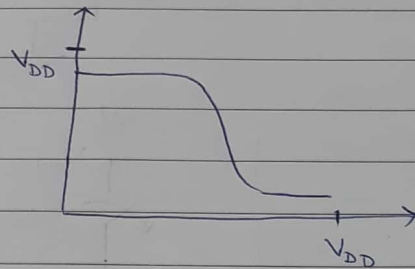Hence, $V_y < 5V$ when p-mos is on
 $> 0V$ n-mos.




B] Delay


When an inverter ~~is~~ has K inverters connected ^{in parallel} to its load,
 $\text{Delay } \tau = p + Kq$
 \uparrow comes from self-capacitance \leftarrow comes from capacitances of load inverters.

A How to measure?

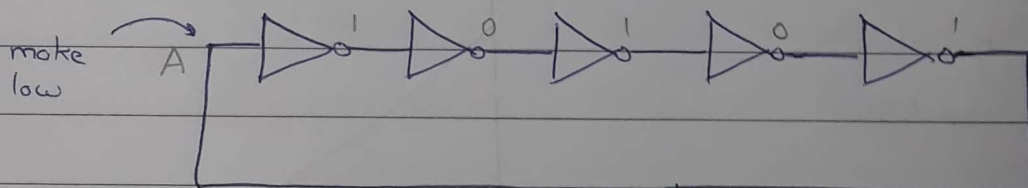- Use odd no. of inverters in series. Supply Low to first inverter.



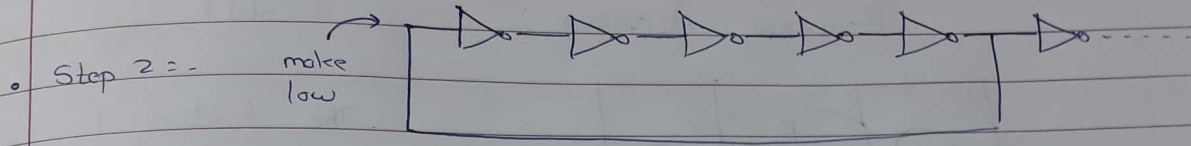V_A oscillates b/w high and low with period $10 \times (\text{Delay of one inverter})$
 $= 10(p + q)$




$$\text{New period} = 8(p+g) + 2(p+2g)$$

c] Current

Current is drawn only when ~~a~~ the inverter is switching.

(Contd.)

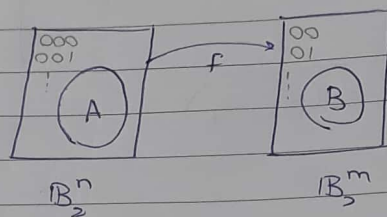

(Contd.)

$IB_2^n \rightarrow IB_2^m$

The function f has 'm' different functions, one to independently determine each output bit.

These functions are $IB_2^n \rightarrow IB_2$

$$\rightarrow B_2^n = \{ (x_1, x_2, x_3, \dots, x_n) \mid x_i \in \{0, 1\} \}$$

- $0, 1, x_1, x_2, \dots, x_n$ are 'formula's
- Production Rules :-

Rules used to produce new strings of formulas from given strings

eg $A \rightarrow (\sim A)$ Inverter

eg $A, B \rightarrow A + B$ OR

eg $A \cup B \rightarrow A \cdot B$ AND

- All 'legal' strings can be constructed from formulas using above rules
- eg $(x_1 + x_2) \cdot x_3$ is a legal string.

→ Minterms

eg	x_1	x_2	x_3	f (function)	Construct atoms m_1, m_2, m_3 such that $f = m_1 + m_2 + m_3$
	0	0	0	0	0 0 0
	0	0	1	1	0 0 1
	0	1	0	1	0 1 0
	0	1	1	0	0 1 1
	1	0	0	1	1 0 0
	1	0	1	0	1 0 1
	1	1	0	0	1 1 0
	1	1	1	0	1 1 1

$$\therefore f = \bar{x}_1 \bar{x}_2 x_3 + \bar{x}_1 x_2 \bar{x}_3 + x_1 \bar{x}_2 \bar{x}_3$$

- From 'n' formulas x_1, \dots, x_n , we can create infinite functions using production rules.

eg- $x_1 \cdot x_1 \cdot x_1 + x_1$ is also a function.

- No. of distinct functions we can create = 2^{2^n}

⑥

22/1

→ Any Boolean function can be written as

$$f = \sum_{\substack{a \in A \\ a \leq f}} a \quad \text{--- Union of atoms}$$

- By De Morgan's Law,

$$f = \prod_{\substack{a \in A \\ a \leq f}} \bar{a} \quad \text{--- Intersection of complements of atoms}$$

- If a is an atom, \bar{a} is a coatom.

→ If a_1 has formula m_1 and a_2 has formula m_2 , then $a_1 + a_2$ has formula $m_1 + m_2$.

Proof Truth table

→ The formulae $\bar{x}_1 \cdot (\bar{x}_2 \cdot x_3)$ and $(\bar{x}_1 \cdot \bar{x}_2) \cdot x_3$ evaluate to the same function, represented as $\bar{x}_1 \cdot \bar{x}_2 \cdot x_3$

→ In Boolean functional algebra

eg

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	0

$$f = \begin{matrix} 0 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{matrix} = \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2$$


'Sum-of-products'

$$\bar{f} = \begin{matrix} 1 & 0 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 0 & 0 \end{matrix} = \bar{x}_1 \bar{x}_2 + x_1 x_2$$


$$\Rightarrow f = (x_1 + x_2) \cdot (\bar{x}_1 + \bar{x}_2)$$

'Product-of-sums'

• Sum-of-products

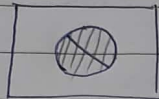

Product-of-sums

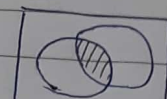

→ Minimization of formulae:-

• Use of Boolean Algebra.

eg $\bar{x}_1 \cdot x_2 + x_1 \cdot \bar{x}_2 = x_2$

$(\bar{x}_1 + x_2) \cdot (x_1 + \bar{x}_2) = x_2$


eg $x_1 x_2 + \bar{x}_1 x_3 + x_2 x_3 = x_1 x_2 + \bar{x}_1 x_3$

eg

x_1	x_2	f
0	0	0
0	1	1
1	1	1
1	0	1

$$f = \bar{x}_1 x_2 + x_1 x_2 + x_1 \bar{x}_2 \quad \text{--- (i)}$$
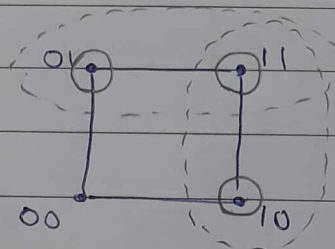
$$= x_2 + x_1 \bar{x}_2 = x_1 + x_2 \quad \text{--- (ii)}$$



— (i)

--- (ii)

SUM OF PRODUCTS MINIMIZATION

$$f = m_1 + m_2 + \dots + m_k \longrightarrow f = p_1 + p_2 + \dots + p_r \text{ where } r \leq k$$

Literals :-

eg $f = \underset{1}{x_1} \underset{2}{x_2} \underset{3}{x_3} + \underset{4}{\bar{x}_1} \underset{5}{x_2} \underset{6}{x_3}$ has 6 literals

- No. of 2-input gates required (except inverters) = (No. of literals) - 1


- By combining terms, no. of literals ↓

eg In above example, $f = \underset{1}{x_2} \underset{2}{x_3}$ --- requires 1 gate

• Start with 0 dimensional terms, combine them to form as many 1D squares as possible, combine those to form as many 2D squares as possible, and so on.

Q $f(x_1, x_2, x_3, x_4) = 1$ if binary no. $x_1x_2x_3x_4$ is prime
0 otherwise.

Meth K-Maps

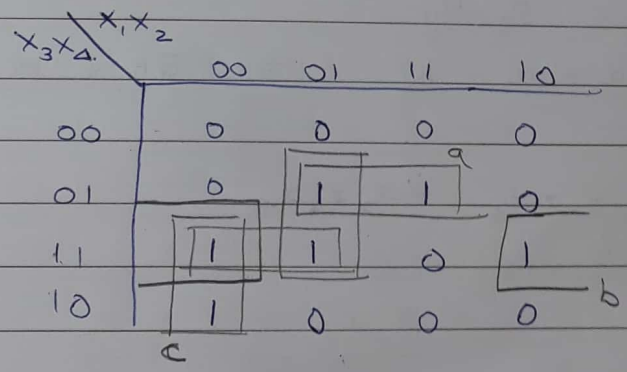

Step1 Recognize prime implicants - 2D squares that are essential
--- a, b, c

Step2 Now only one 1 remains - Use any one of two possible 2D squares containing this 1.

	0D	1D	2D
Meth 2 ✓ 2	0010	(2,3) 001_	No
✓ 3	0011	(3,7) 0_11	possible
✓ 5	0101	(3,11) _011	combinations
✓ 7	0111	(5,7) 01_1	No 1D used
✓ 11	1011	(5,13) _101	
✓ 13	1101	All 0D used	

- Combine those that differ in only one variable

Step 2	✓ 2	✓ 3	✓ 5	7	✓ 11	✓ 13
✓ (2,3)	x	x				
(3,7)		x		x		
✓ (3,11)		x			x	
(5,7)			x	x		
✓ (5,13)			x			x


Choose any one term for 7

25/1

→ Consensus Equality :-

$$\bar{a}b + ac + bc = \bar{a}b + ac$$


A] → 'Don't Care' Conditions

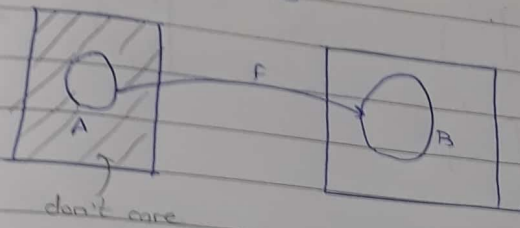

eg x_1, x_2, x_3, x_4 in binary from 0 to 9
 $f = 1$ if x_1, x_2, x_3, x_4 is odd
 $= 0$ otherwise

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00				d	
01		1	1	d	1
11		1	1	d	d
10				d	d

• 'Observability' Don't Cares

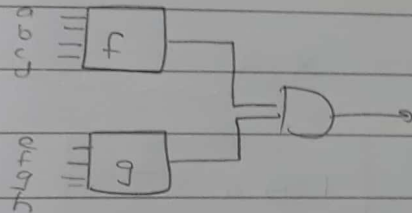


We don't care output of f when g produces zero


B] Shannon's Formula.

$$f(x_1, x_2, \dots, x_n) = x_1 \cdot \underbrace{f(1, x_2, \dots, x_n)}_{f_{x_1}} + \bar{x}_1 \cdot \underbrace{f(0, x_2, \dots, x_n)}_{f_{\bar{x}_1}}$$

Cofactors

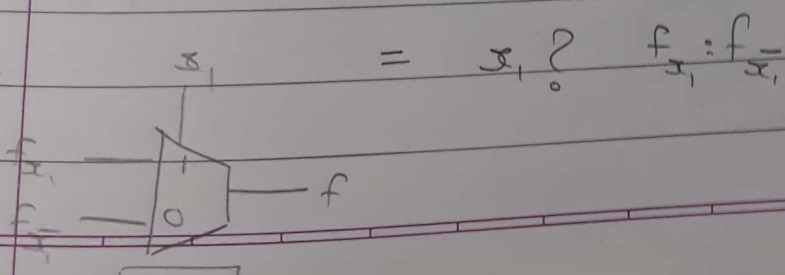

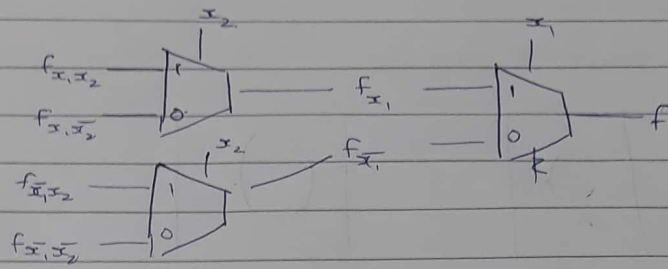Cofactors are simpler expressions than original function (one variable less)




2^n MUXes required

29/1


II UNIVERSAL GATES

= NAND, NOR, MUX

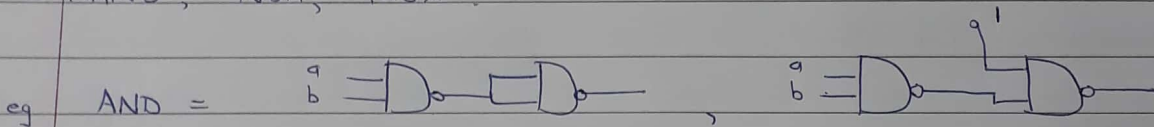

* $a \oplus b = a\bar{b} + \bar{a}b$ ----- XOR

Prove :: Associative, Commutative

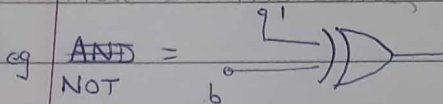

$1 \oplus a = \bar{a}$
$0 \oplus a = a$

eg $f_{x_1} \oplus f_{\bar{x}_1} = 1$ if $f(1, x_2, \dots, x_n) \neq f(0, x_2, \dots, x_n)$
 $= 0$ otherwise

This function gives '1' if value of x_1 is affecting the end result.

* $f_{x_1} + f_{\bar{x}_1} = 1$ if $\exists x_1$ such that $f(x_1, x_2, \dots, x_n) = 1$
 $= 0$ otherwise

'Existential Quantifier'

Page No.:

$$* f_x \cdot f_x = 1 \quad \text{if } \forall x, f(x_1, \dots, x_n) = 1$$

$$= 0 \quad \text{otherwise}$$

'Universal Quantifier'


$$* x_1 \oplus x_2 \oplus x_3 \oplus x_4 \dots \oplus x_n = 1 \quad \text{if odd no. of } x_i \text{'s are 1}$$

'Odd parity function'

eg $x_1 \oplus x_2 \oplus x_3 \oplus x_4$

$x_3 x_4$ \ $x_1 x_2$	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0

• Shannon's Decomposition :-

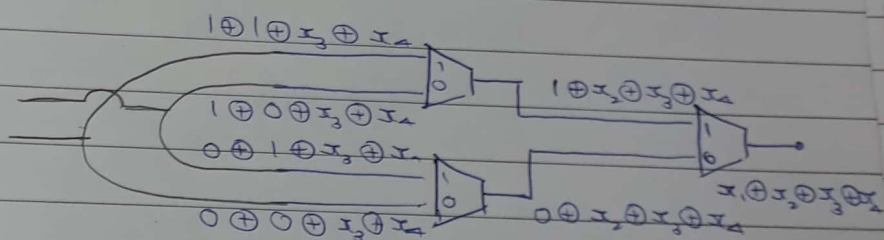

- Using logic gates, 2^n gates will be required. 😊
- Using Shannon's method (MUX), 2^n MUXes are required. 😊
where every MUX is built using constant no. of gates itself.

→ Minimization by factorization

$$1 \quad pq + pr = p(q+r)$$

$$2 \quad pq + pr + sq + sr = (p+s)(q+r)$$

$$* 3 \quad tr + uv = f$$

$$wt + rs = g$$

$$p+q = t$$

$$A \quad p\bar{q} + \bar{p}q = (p+q)(\bar{p}+\bar{q})$$

30/1

* We want to write $f = q \cdot g$

$$\text{eg } f = \bar{x}_1 x_2 + x_1 \bar{x}_2$$

$$g = x_1 + x_2$$

TFT

2

$x_1 x_2$	00	01	11	10
$g = (x_1 + x_2)$	0	X	X	X
	0	1	0	1

X = not possible
(consider as
don't care)


Choose prime implicants such that

we can take 'g' common --- don't choose verticle PI's


$$f = g\bar{x}_1 + g\bar{x}_2$$

$$= g(\bar{x}_1 + \bar{x}_2)$$


$$g = \bar{x}_1 + \bar{x}_2$$

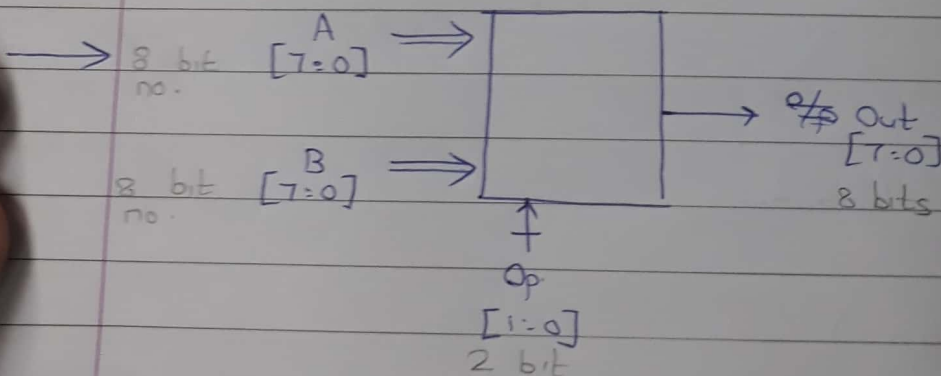

Op	Out
0	A + B
1	A - B
2	A > B
3	A == B

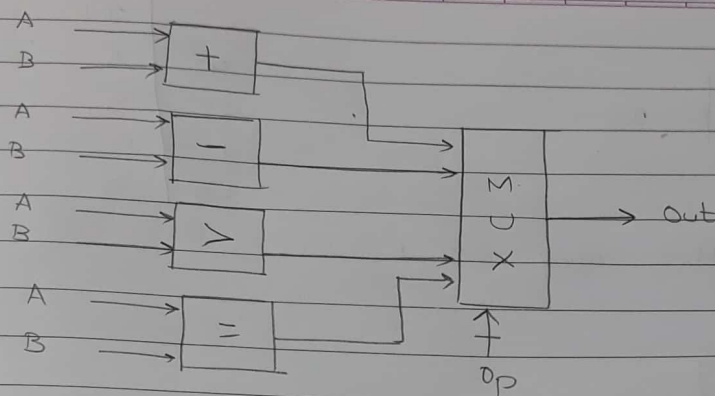


= Use XNOR gate

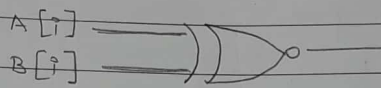


> We will check from most significant bit.


Make a cascade of 8 of the following

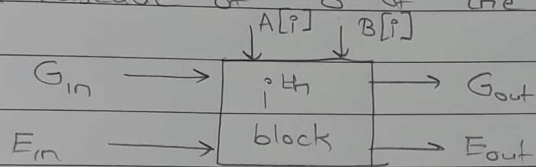

$G_{in}, G = 1 \Rightarrow$ Until now, $A[i] > B[i]$
 $E = 1 \Rightarrow$

+ Cascade of

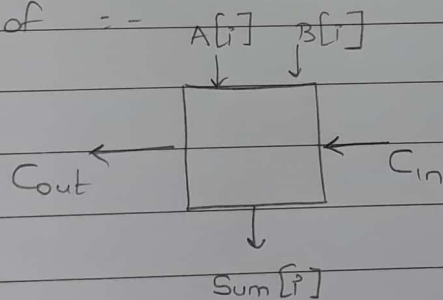

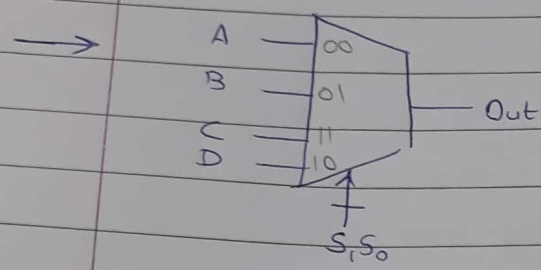

$S_1 S_0$	Out
00	A
01	B
11	C
10	D

Build 4:1 MUX using 2:1 MUXes

