

Register-Transfer-Level (RTL) descriptions

Madhav Desai

March 23, 2018

An FSM can be viewed as an algorithm

```
// inputs {a,b}, outputs {P,Q}, initial state phi
phi: if(input == a) then
    //  $Q(k) = 1, q(k+1) = s_a$ 
    Q = 1, $state := s_a
else
    Q = 1, $state := phi end if
s_a: if (input == a) then
    $state := s_aa
else if(input == b)
    $state := s_ab end if
s_aa:... etc ....
s_aab: if (input == b) then
    P = 1, $state := phi
else if(input == a)
    Q = 1, $state := s_aba
else
    Q = 1, $state := s_phi end if
```

An FSM for a counter down timer

```
// by default, Y = 0
rst: if(start)    then
    $state := s1
    else
    $state := s0
    end if
    ready := 1
s1: $state := s2
s2: $state := s3
s1023: Y = 1, $state := s0
```

for every state some variables are required and it gets multiplied

Too many states!

Introduce register (storage) variables and register transfers

```
// count is a register with 8 bits.
register count[9:0];
thread DCount {
  rst: if (start) then
    // x := y means  $x(k+1) = y(k)$ 
    count := 1023,
    // goto decr means
    //    $q(k+1) = \text{decr}$ 
    $state := decr
  else goto rst end if
  decr: if(count == 0) then
    // done = 1 means  $\text{done}(k) = 1$ 
    done = 1, $state := rst
  else
    count := count - 1, $state := decr
  end if
}
```

The control-path and the data-path in the RTL

A couple of points:

- ▶ Identify the transfers used in the RTL using output variables (or symbols).
- ▶ Identify the predicates used in the RTL using output variables (or symbols).
- ▶ The RTL algorithm can be thought of as two parts:
 - ▶ A pure Mealy machine (the control path).
 - ▶ The implementation of the transfers (the data path)

The data-path for the counter

- ▶ Introduce signals $T0$, $T1$ to indicate the transfers
 $count := 1023$ and $count := count - 1$.
- ▶ the data-path implements the two transfers as

$$count(k+1) \leq (T1(k)? \underset{\text{Text}}{count(k)-1} : (T0(k)? 1023 : count(k)))$$

and produces the status signal

$$S(k) = (count(k) == 0)$$

$t1 = 1 \text{ count} - 1$

$t1 = 0, t0 = 1. 1023$

$t1 = 0 \text{ count} k$

The data-path: implement using muxes, combinational circuits, registers

 


Figure : Datapath for the counter

Control path FSM

```
// by default
//      T0=T1=done=0 unless specified.
// by default, unless specified,
//      $state := next-statement-label
fsm DCount_control {
  rst: if (start) then
    T0 = 1, $state := decr
  else $state := rst end if
  decr: if(S) then
    done=1, $state := rst
  else
    T1 = 1, $state := decr
  end if
}
```

t1 =1 count-1

t0 = t1=0 countK

t1 = 0 , t0=1. 1023

Control path FSM

state	reset	start	S	next-state	T0	T1	done
_	1	_	_	rst	-	-	-
rst	0	0	_	rst	0	0	0
rst	0	1	_	decr	1	0	0
decr	0	_	0	decr	0	1	0
decr	0	_	1	rst	0	0	1

Advantages of separating Data/Control paths

- ▶ State complexity is clearly demarcated.
- ▶ Datapath resources are clearly defined.
- ▶ Verification problem is simpler.
- ▶ It is easy to estimate resources needed.

RTL Pseudo-code Convention

```
input start, incount[31:0]
output done
register count[31:0]
thread Main() {
    // default reset state.
    rst: if (start) then
        $state := work, done = '1',
        count := incount
    else
        $state := rst
    end if
    decr: if (count > 0) then
        count := count-1,
        $state := decr
    else
        done = 1, $state := rst
    end if
}
```

RTL Pseudo-code Convention

```
.. declare ins, outs, registers.  
.. define threads  
thread <thread-1> {  
    ..statements..  
}  
thread <thread-2> {  
    ..statements..  
}  
etc..
```

Going further: collections of RTL threads

- ▶ The concept of subroutines can be extended to RTL.
- ▶ Fork-join structures are a natural extension of subroutines, but which provide parallelism.
- ▶ Synchronized threads can be used to create deadlock free implementations of useful things (such as pipelines).

Subroutines

```
thread master {
A: if (...) then
    call=1, $state := W
else
    $state := A
end if
W: if (ret) then
    $state := R
else
    $state := W
end if
R: ....
}
```

```
thread slave {
  Idle:
    if (call) then
      $state := W
    else goto Idle end if
  W:
    if (finished) then
      ret = 1, $state := Idle
    else
      goto W
    end if
}
```

Fork-Join Structures

```
thread Master {  
A: if (...) then  
    call=1, $state := W  
else goto A end if  
W: if (retA and retB) then  
    $state := R  
else $state := W end if  
R: ....  
}
```

both the D flip flop will be used simultaneously

Text

```
thread Slave_1 {  
Idle: retA = 1  
    if (call) then  
        $state := W  
    else $state := Idle end if  
W: if (finished)  
    $state := Idle  
    else $state := W end if }  
thread Slave_2 {  
Idle: retB = 1  
    if (call) then $state := W  
    else goto Idle end if  
W: if (finished) then  
    $state := Idle  
    else $state := W end if }
```

Synchronized Threads

```
thread Peer_1 {  
  Working:  
    if (done-working) then  
      $state := Synch  
    else  
      $state := Working  
    end if  
  Synch:  
    SynchA = 1  
    if (SynchB) then  
      $state := Working  
    else  
      $state := Synch  
    end if  
}
```

```
thread Peer 2 {  
  Working:  
    if (done-working)  
      $state := Synch  
    else  
      $state := Working  
    end if  
  Synch:  
    SynchB = 1  
    if (SynchA) then  
      $state := Working  
    else  
      $state := Synch  
    end if  
}
```