

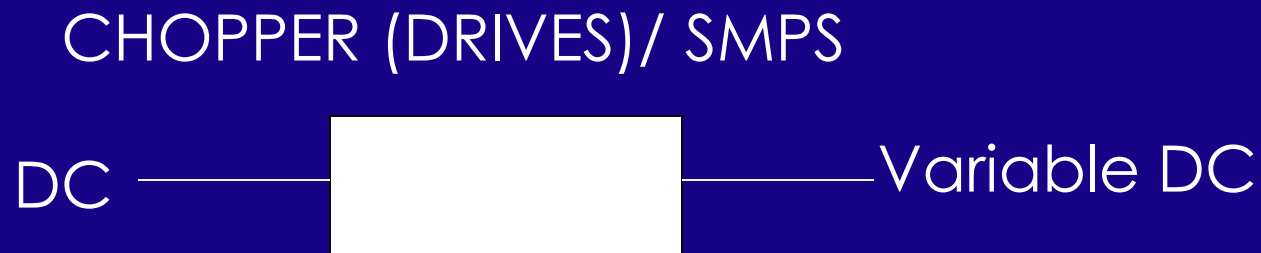


## Power Electronics circuits /Equipments


### 1.0 Classification

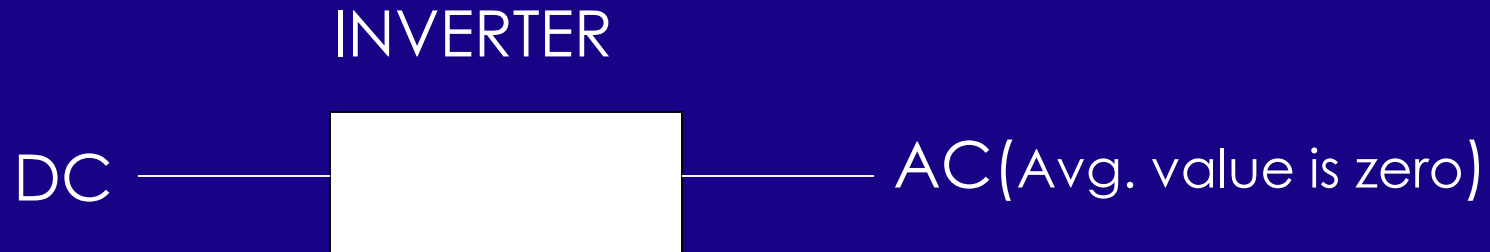

## PHASE CONTROLLER

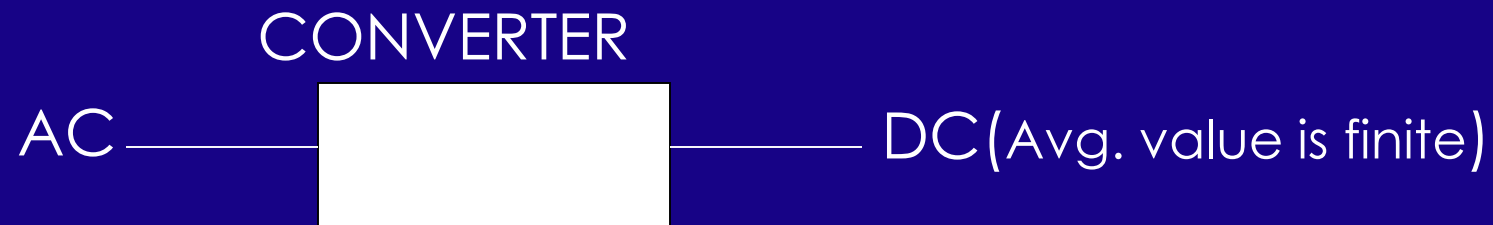

## CYCLO CONVERTER / MATRIX CONVERTER

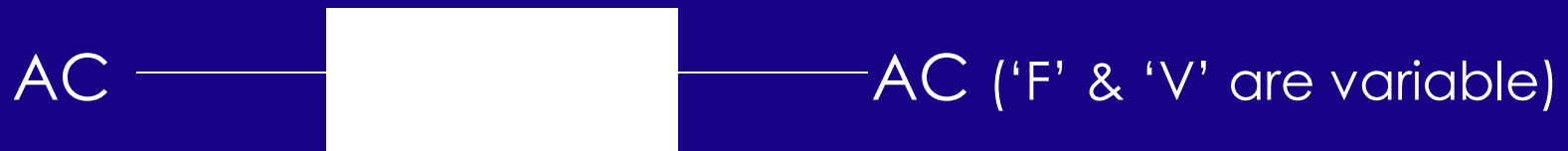

## 2. Converter

Assumptions: 1. All the devices and circuit components are ideal.  
2. Input is a pure sine wave.

### 2.1 Diode Circuits


- Uncontrolled Rectification

Let  $\alpha$  = the angle at which diode starts conducting.

$\beta$  = the angle at which diode stops conducting.

$\gamma$  = conduction angle =  $\beta - \alpha$

## 2.1.1 Half Bridge: R-Load

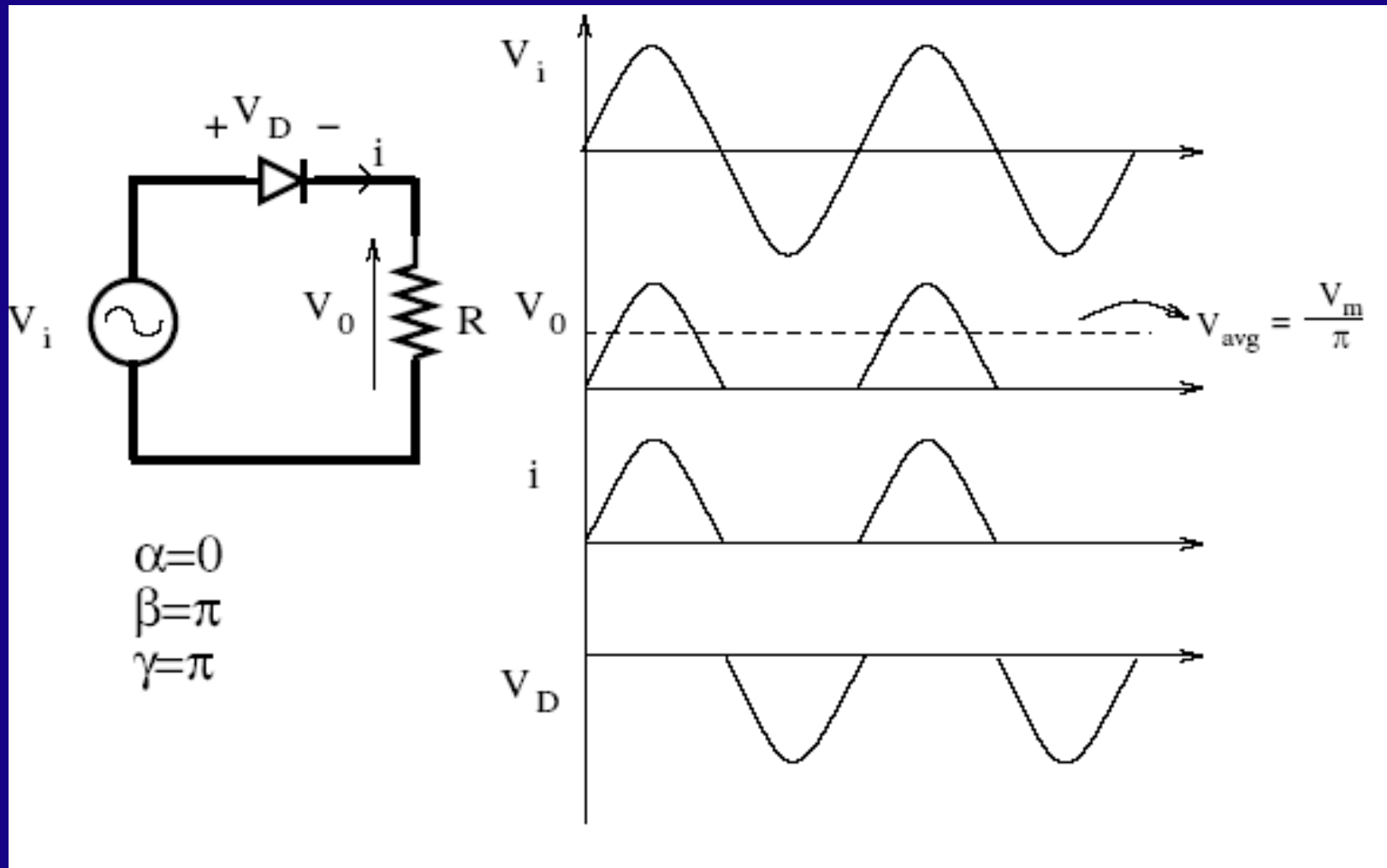

$$V_i = V_m \sin \omega t = Ri = V_0$$

$$i = \frac{V_m}{R} \sin \omega t, \quad i = I_{\max} \text{ at } \omega t = \pi/2$$

$$V_{\text{avg}} = V_m / \pi$$


$$V_{\text{rms}} = V_m / 2$$

$$V_{\text{ripple}} = \sqrt{(V_{\text{rms}}^2 - V_0^2)}$$

→ Measure of AC component in  $V_0$

$$\text{Ripple Factor} = V_{\text{ripple}} / V_0 = 1.21$$

## 2.1.2 Half Bridge: L-Load

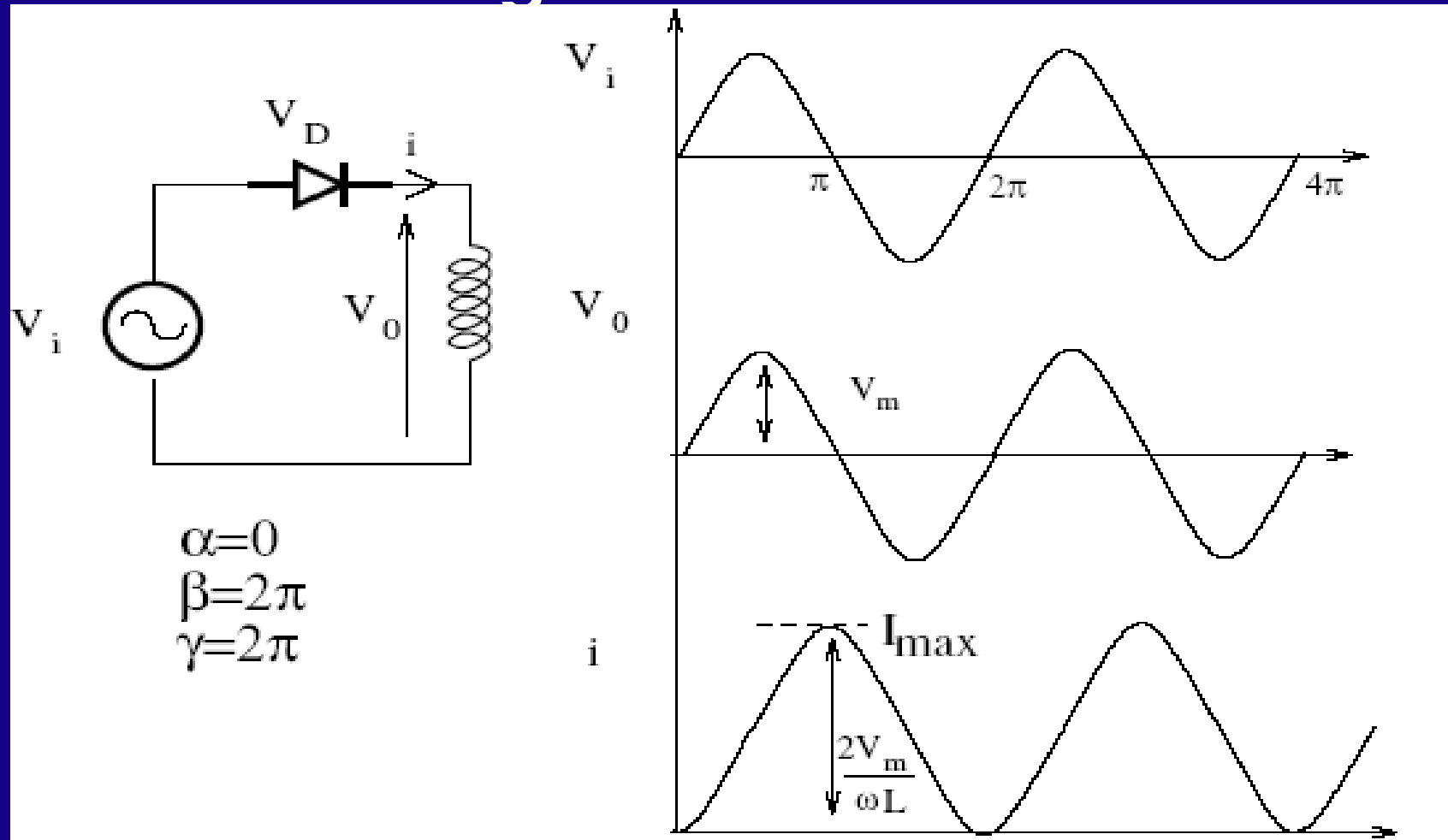



$$V_i = L \frac{di}{dt} = V_m \sin \omega t, \quad i = I_{\max} \quad \text{at} \quad \omega t = \pi$$


$$i = \frac{V_m}{\omega L} (1 - \cos \omega t)$$

$$V_0 = V_i = V_m \sin \omega t$$

$$V_{\text{avg}} = 0$$

$$\text{Power delivered to load} = V_{\text{avg}} I_{\text{avg}} = 0$$

## 2.1.2 Half Bridge: R-L-Load

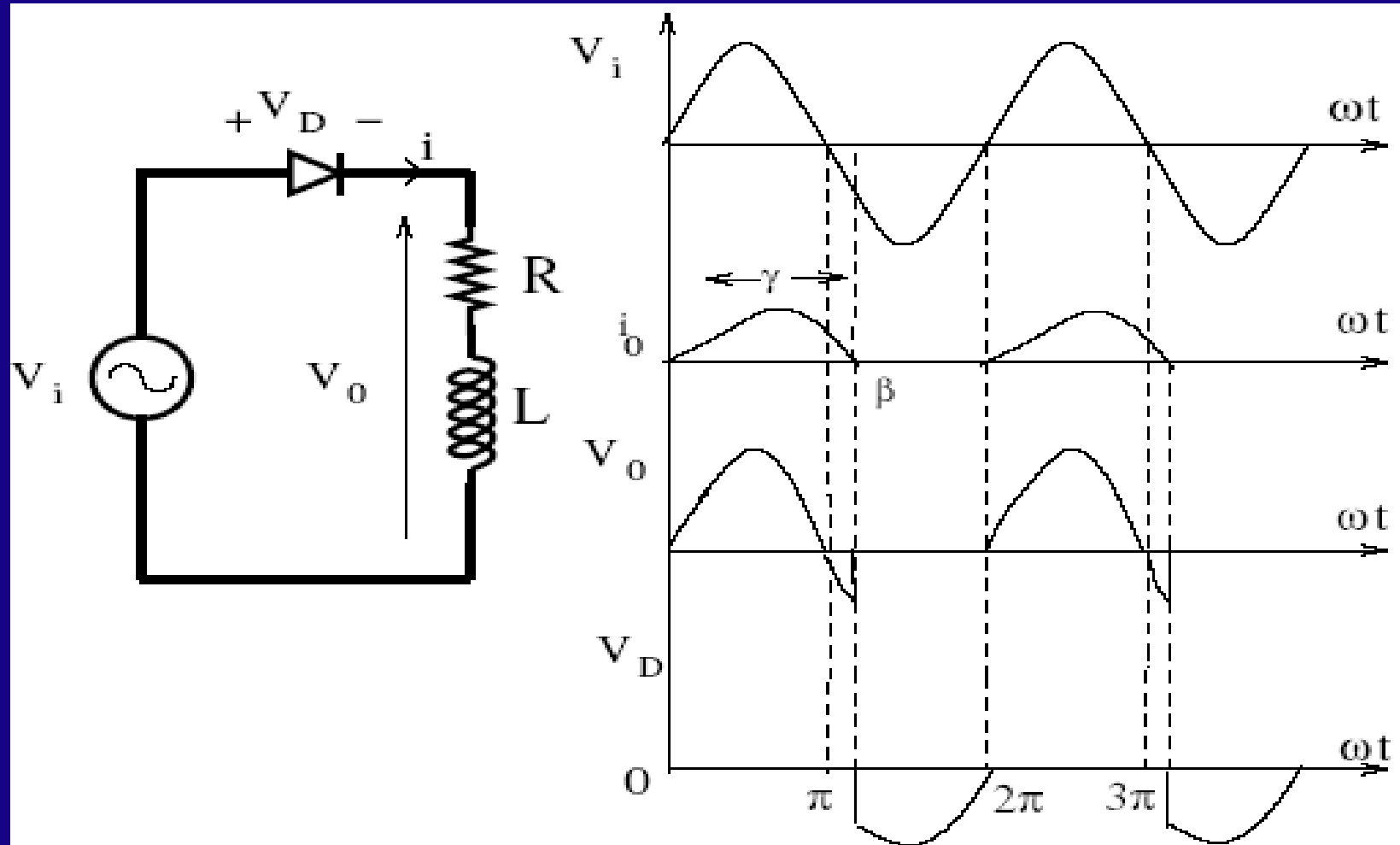



$$Ri + L \frac{di}{dt} = V_m \sin \omega t$$

$$i = \frac{V_m}{Z} [\sin(\omega t - \phi) + k_1 e^{-\frac{Rt}{L}}]$$

$$\text{where } Z = \sqrt{R^2 + \omega L^2} \text{ \& } \phi = \tan^{-1} \frac{\omega L}{R}$$

$$\text{At } \omega t = 0, i = 0$$

$$\therefore i = \frac{V_m}{Z} [\sin(\omega t - \phi) + \sin(\phi) e^{-\frac{Rt}{L}}] \quad 0 < \omega t < \beta$$

$$i = i_{\max} \quad \pi/2 < \omega t < \pi$$

$$V_0 = Ri_{\max}$$

$$V_{\text{avg}} = \frac{V_m}{2\pi} (1 - \cos \beta)$$

## Observation:

- $\gamma$  increases with increase in 'L'.
- Avg.  $V_0$  decreases with increase in 'L'.

What is the significance of  $\gamma$  ?

Or why should the current be continuous in the load ?

Consider a DC motor driving a load


$$\text{Developed Torque} = k I_F I_a = T_e$$

$$J \frac{d\omega}{dt} + B\omega + T_L = T_e$$

$$\frac{d\omega}{dt} = [T_e - T_L] / J$$

At Steady state  $\frac{d\omega}{dt} = 0$

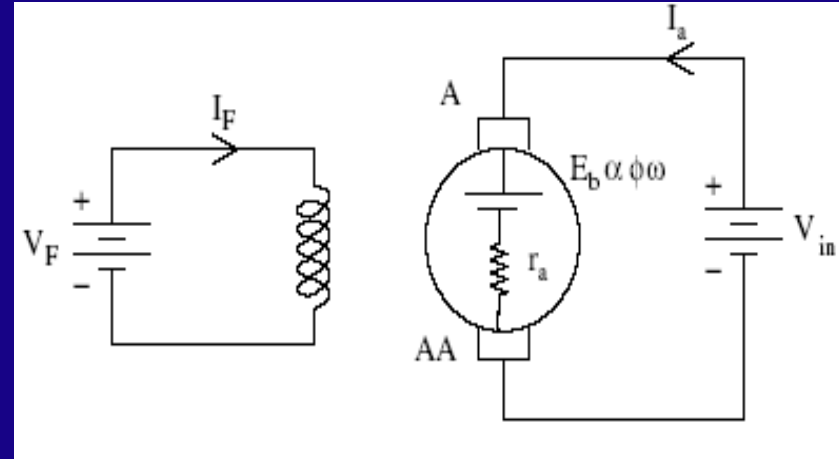Possible only if  $T_e$  is constant  $\Rightarrow$  if  $I_a$  and  $I_F$  are constant.




If  $I_a = 0$ ,  $T_e = 0$

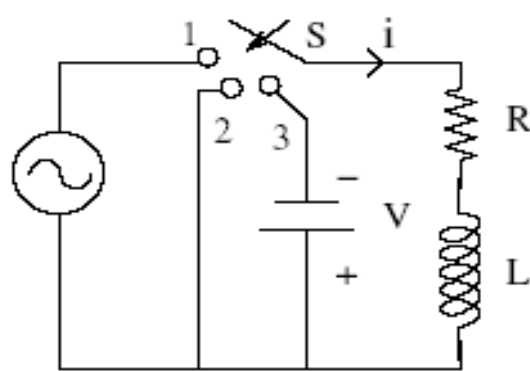
**Speed will PULSATE**

⇒ **Always desirable to have finite  $I_a$  if not constant ' $I_a$ '.**


⇒ **Just increasing ' $L$ ' is not a solution ( $\gamma$  increases with increasing ' $L$ ', but avg.  $V_0$  decreases.)**




S is closed to position 1

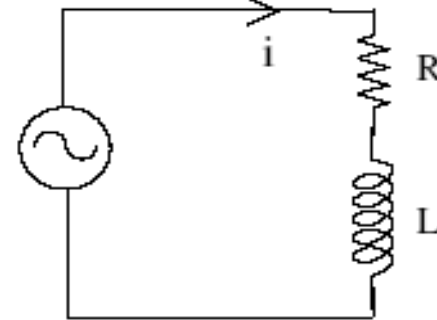

S is closed to position 2

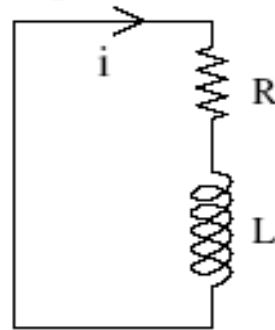

S is closed to position 3

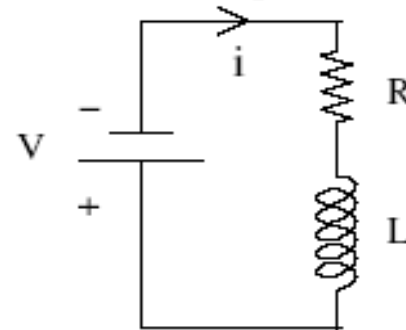

$$Ri + L \frac{di}{dt} = 0$$

$i$  decays slowly


$V_0 = \text{constant with } \uparrow \beta$

$$Ri + L \frac{di}{dt} = -V$$

$i$  decays very fast

$V_0 \downarrow$  with  $\uparrow \beta$


## 2.1.4 Freewheeling Diode

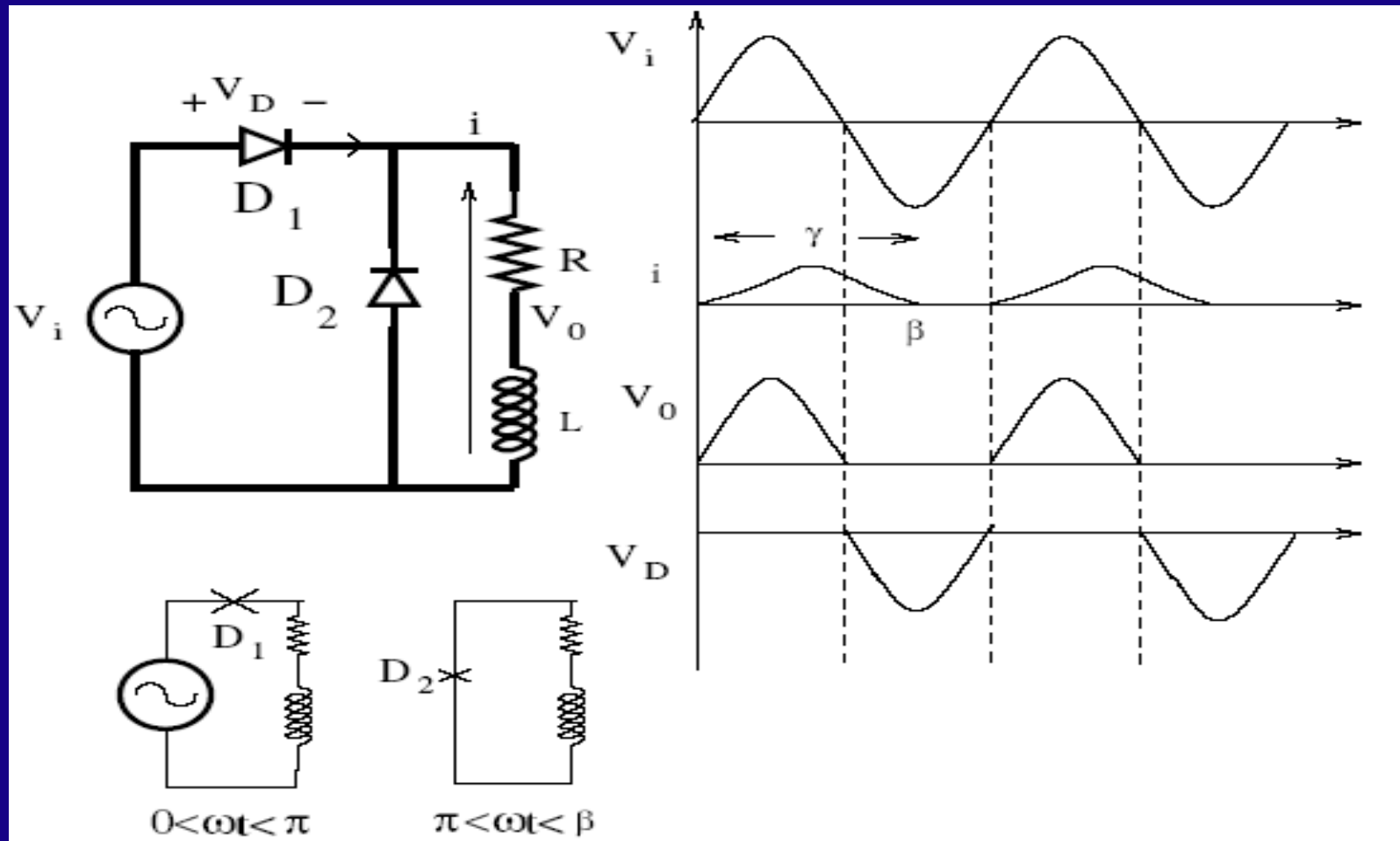



## 2.1.5 Load is R-L-E

- Case – 1:  $L=0$

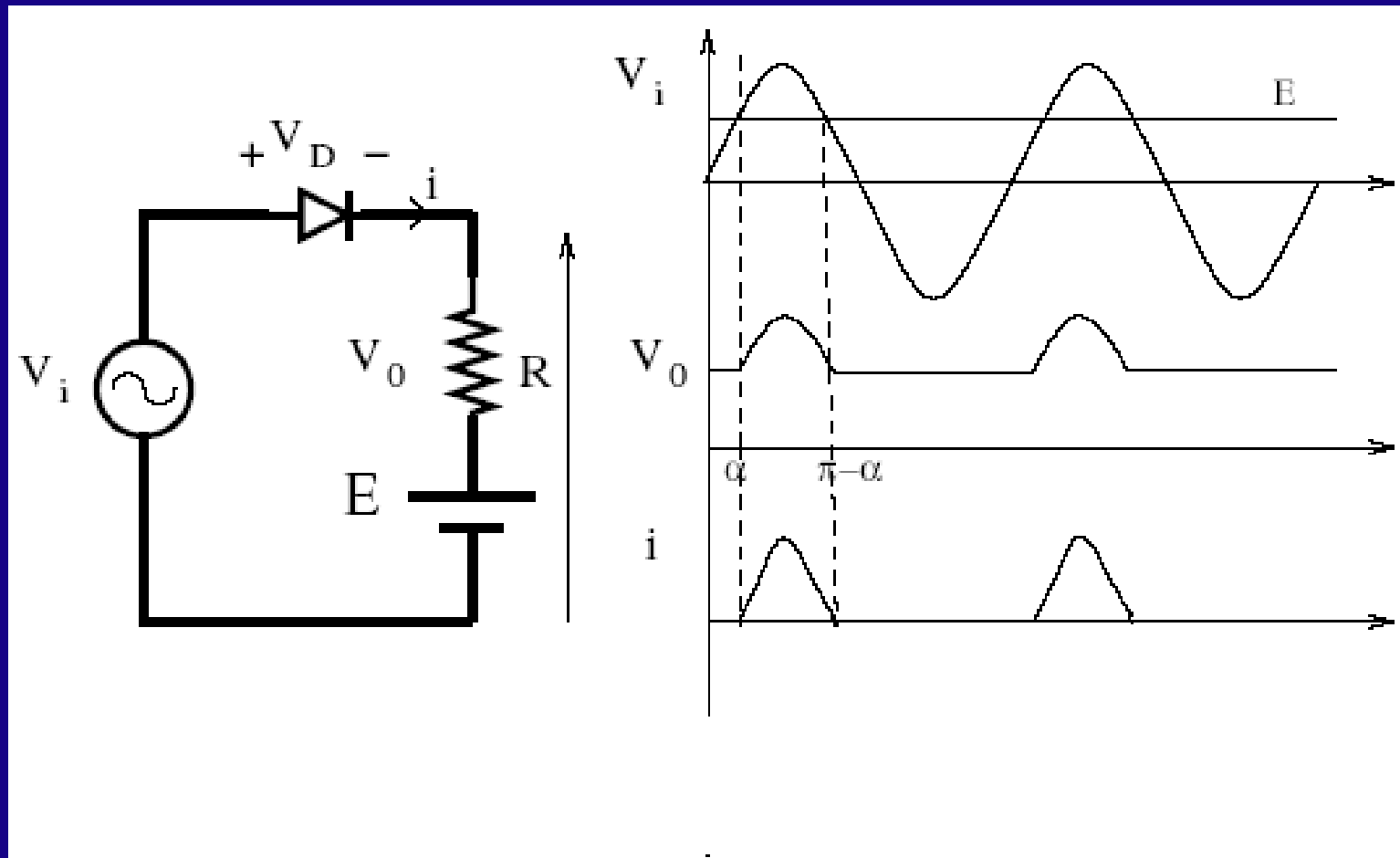

Diode can conduct when  $V_m \sin \omega t = E$

$$\alpha = \omega t = \sin^{-1}\left(\frac{E}{V_m}\right)$$

When diode is ON,  $V_0 = V_i$

When diode is OFF,  $V_0 = E$


Applying KVL,  $V_i = Ri + E$

$$i = [V_m \sin \omega t - E]/R$$

Diode turns off at  $\beta = \pi - \alpha$

$$i = I_{\max} \text{ at } \omega t = \pi/2$$

## Case – 2: $R=0$

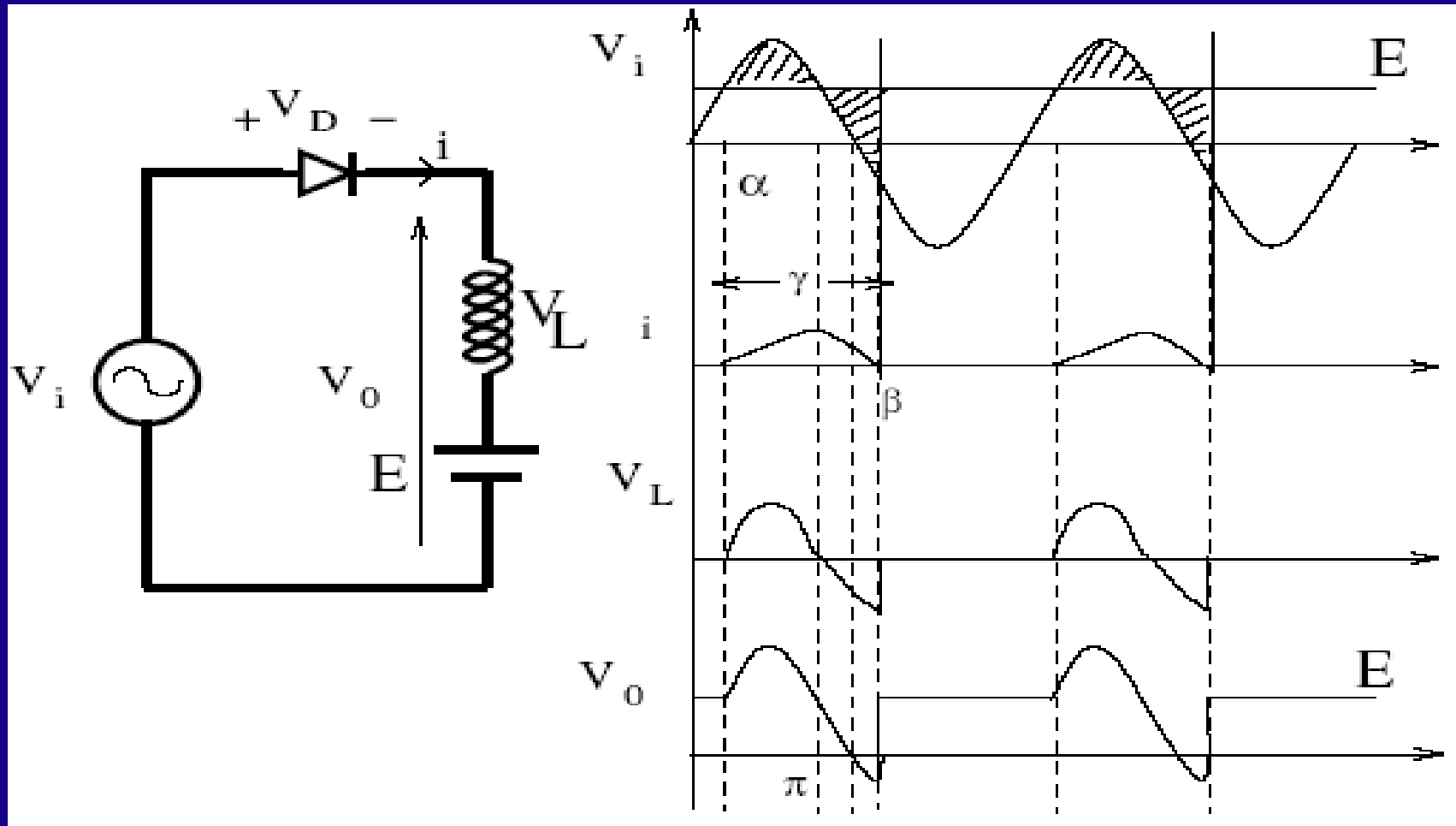

$$\alpha = \omega t = \sin^{-1}\left(\frac{E}{V_m}\right)$$

when diode is ON,  $V_i = L \frac{di}{dt} + E$

'i' starts  $\uparrow$  beyond  $\alpha$

$$i = I_{\max} \text{ at } \pi - \alpha$$

$$i = I_{\max}, \frac{di}{dt} = 0$$

$$V_i = E \text{ at } \omega t = \pi - \alpha$$


$$V_o = E, \text{ for } 0 < \omega t < \alpha$$

$$V_o = V, \text{ for } \alpha < \omega t < \gamma$$

$$V_o = E, \text{ for } \gamma < \omega t < 2\pi + \alpha$$

$$i = 0 \text{ at } \beta \text{ when } +ve L \frac{di}{dt} = -ve L \frac{di}{dt}$$

## Case – 3: R-L-E Load

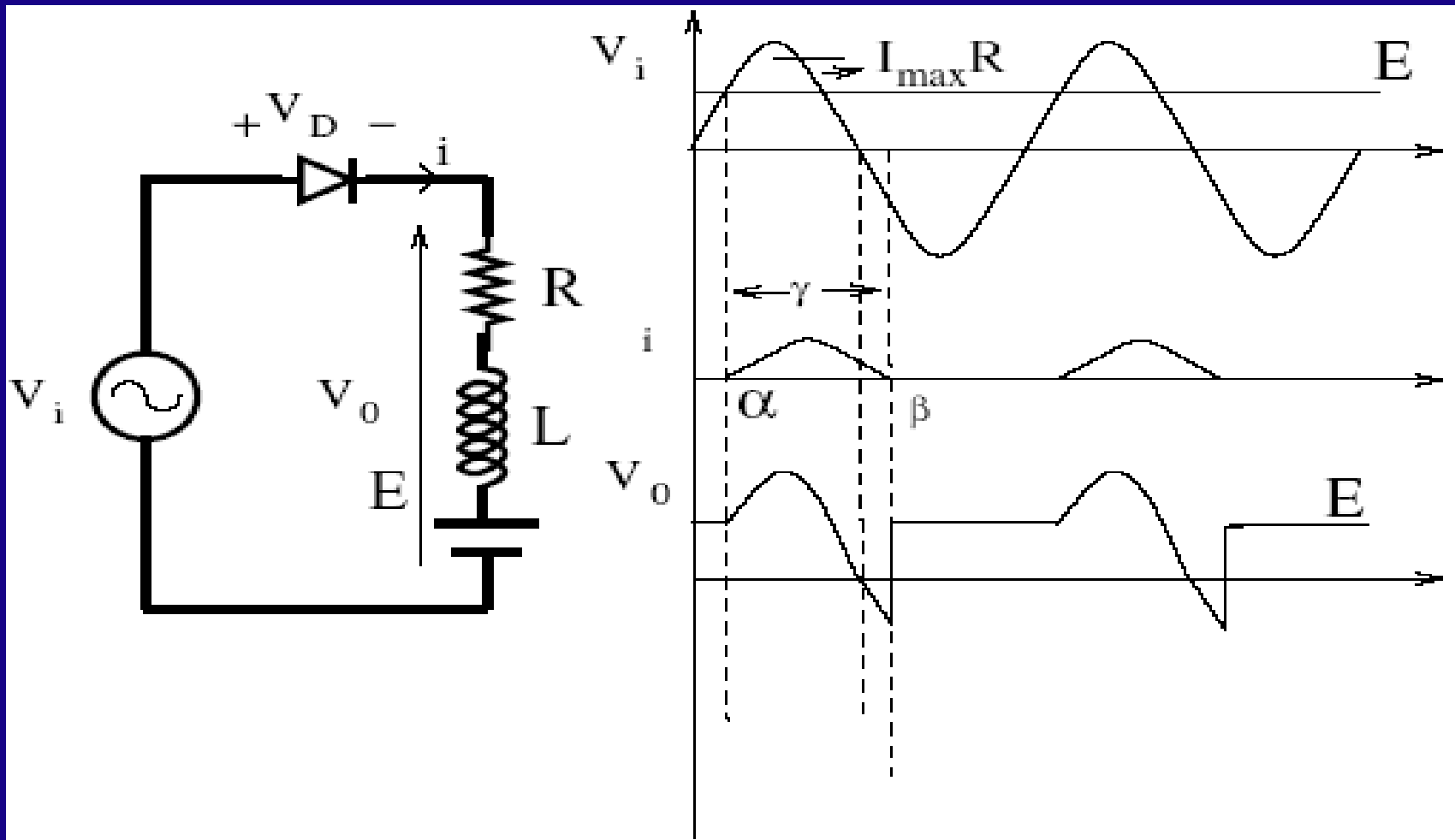

$$\alpha = \omega t = \sin^{-1}\left(\frac{E}{V_m}\right)$$

$$V_i = Ri + E + L \frac{di}{dt}$$

$$i = I_{\max},$$


$$\pi / 2 < \omega t < \pi - \alpha$$

$$V_i = E + RI_{\max}$$

$$\therefore L \frac{di_{\max}}{dt} = 0$$



## Case – 4: R,L, Freewheel Diode

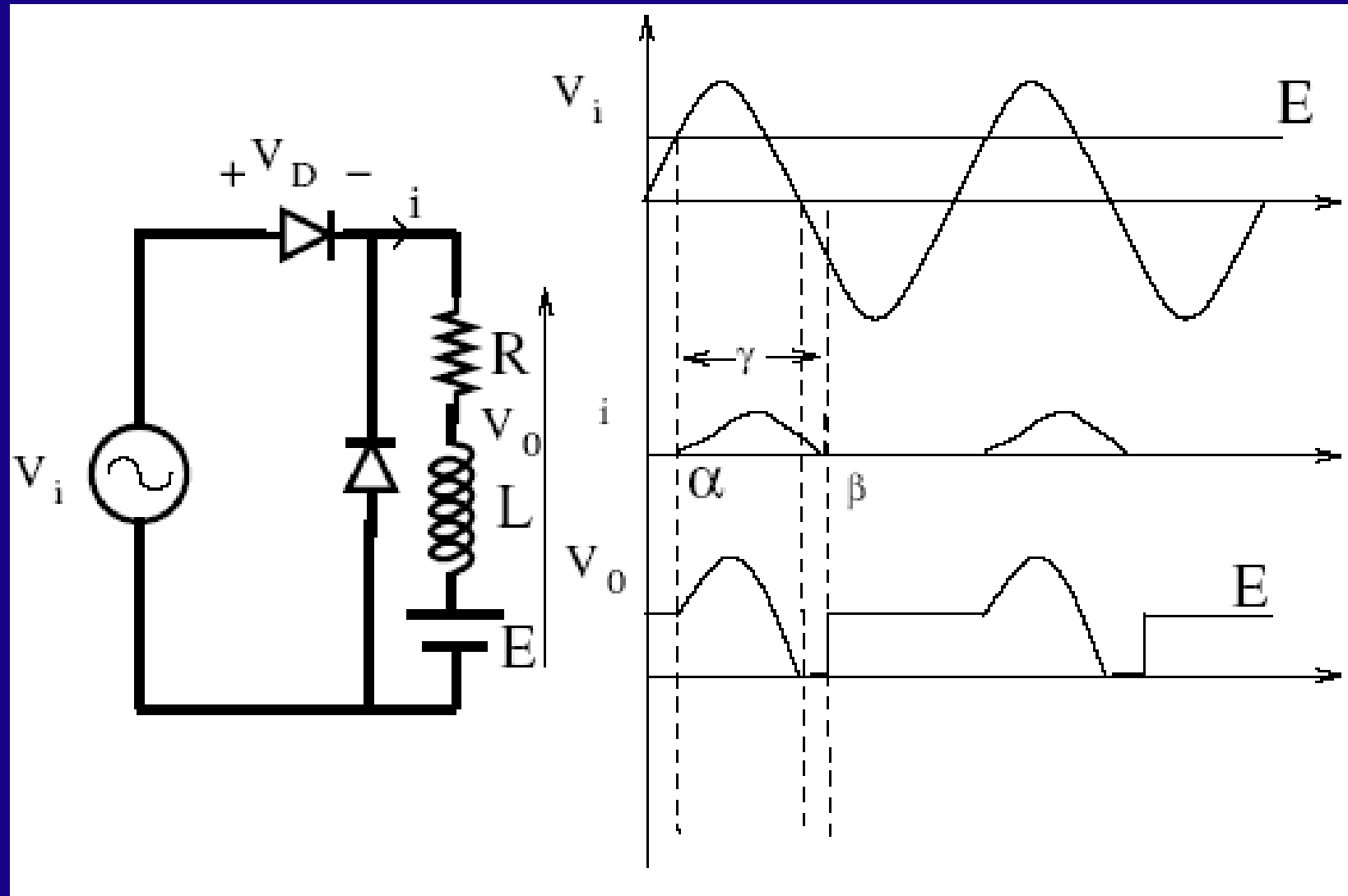


–ve voltage can not appear across the load

For  $\pi < \omega t < \beta$ , 'i' starts flowing through freewheeling diode.

$V_0 = 0$ ,      beyond  $\beta$ ,  $V_0 = E$

Observations

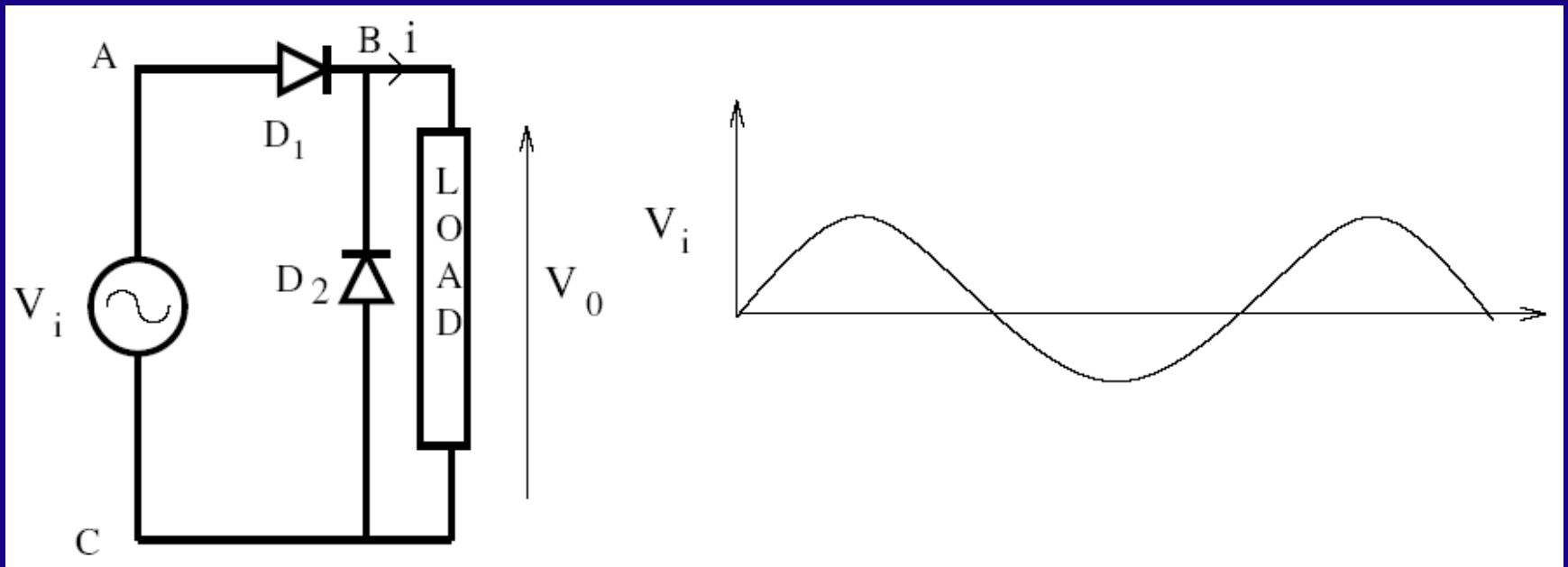- when diode is OFF,  $V_0$  depends on Load
- when diode is ON,  $V_0 = V_i$



Assume that the load current is continuous

Either  $D_1$  or  $D_2$  should be ON

In +ve half  $D_1$  is ON,  $D_2$  can not conduct.

Proof:

Potential of Pt. A  $>$  Potential of Pt. C

Assume  $D_2$  is ON

Potential of Pt. C = Potential of Pt. B

Potential of Pt. A  $>$  Potential of Pt. B

+ve voltage across  $D_1$  is not possible

Assumptions is wrong.

$\therefore$  If 'i' is continuous in the +ve half  $D_1$  conducts and during -ve half  $D_2$  conducts.

$\Rightarrow$  Independent of type of load

## Conclusions

- $\gamma \uparrow$  with load 'L'.
- For diode to conduct  $V_D = 0$ ,  
 $V_A$  potential need not be +ve.
- Use of freewheeling diode  $\uparrow \gamma$ .
- If 'i' is discontinuous & load is R-L-E

$$\text{then } \alpha = \sin^{-1}\left(\frac{E}{V_m}\right)$$

- If 'i' is continuous,  $\alpha = 0$ ,

independent of load  $\Rightarrow$  due to  $L \frac{di}{dt}$