
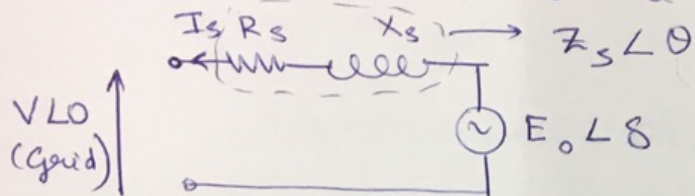


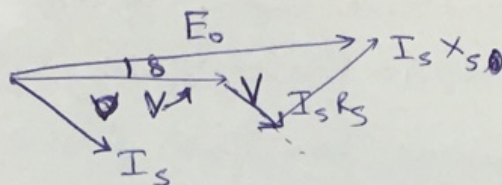Q-1) Find Q supplied by Synchronous Machine when connected to the Grid.



$\delta > 0$ for Generator Action

$\vec{I}_s \neq \vec{I}$



$$\vec{I}_s = \frac{E_0 \angle \delta - V \angle 0}{Z_s \angle \theta} = \frac{E_0 \angle (\delta - \theta) - V \angle -\theta}{Z_s}$$

$$= \left[\frac{E_0}{Z_s} \cos(\delta - \theta) - \frac{V}{Z_s} \cos \theta \right] + j \left[\frac{E_0}{Z_s} \sin(\delta - \theta) + \frac{V}{Z_s} \sin \theta \right]$$

$$VA = V I_s = \frac{V}{Z_s} \left(\underbrace{\left[E_0 \cos(\delta - \theta) - V \cos \theta \right]}_{\text{Power } W} + j \underbrace{\left[E_0 \sin(\delta - \theta) + V \sin \theta \right]}_{\text{Reactive power } VA_r}$$

$$Z_s = (R_s + jX_s)$$

$$\Rightarrow P = \frac{V}{Z_s} \left(\frac{V}{R_s + jX_s} \right) \left[E_0 \cos(\delta - \theta) - V \cos \theta \right]$$

if $X_s \gg R_s \Rightarrow \theta = \pi/2$: Approximation

$$P = \frac{V}{X_s} [E_0 \sin \delta] = \frac{E_0 V}{X_s} \sin \delta \quad (\text{per phase})$$

$$Q = \left[E_0 \sin(\delta - \theta) + V \sin \theta \right] \frac{V}{(R_s + jX_s)}$$

total power = 3P
With Approximation

Again, per phase


$$\approx (-E_0 \cos \delta + V) \times \frac{V}{X_s} = \frac{V^2 - VE_0 \cos \delta}{X_s}$$

OR -ve of this depending on convention

Q2) Expression for power Generated by Salient Pole Machine (Different from power transferred)

$X_{dg} \rightarrow$ Direct Axis

$X_{qg} \rightarrow$ Quadrature axis

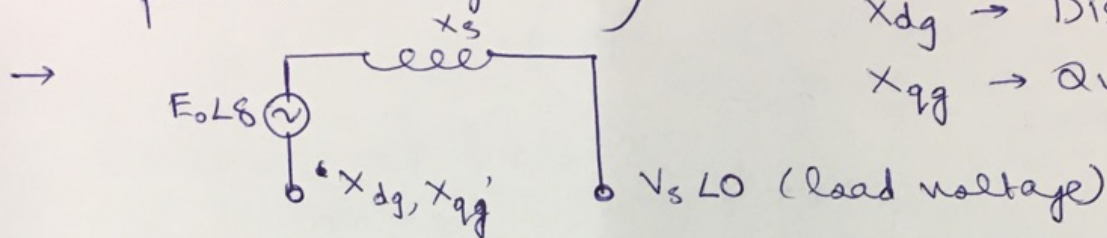


\rightarrow Total Reactance along direct axis $= X_d = X_{dg} + X_s$

\rightarrow Total Reactance along quadrature axis $= X_q = X_{qg} + X_s$

Neglect Armature Resistances.

Armature Current has both direct & quadrature components

Phasor Diagram:

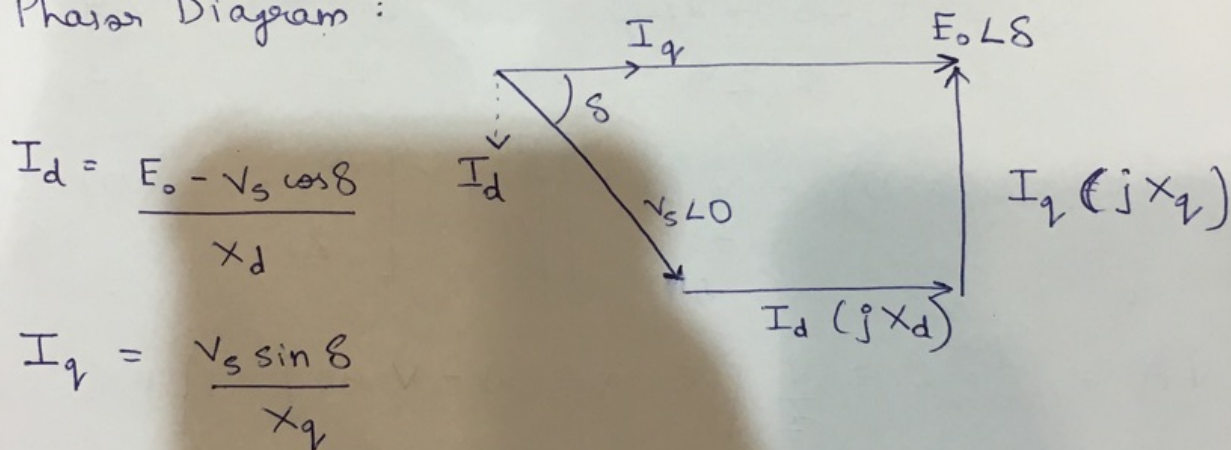

Total power delivered by E_0 to V_s

$$= (V_s \sin \delta) I_d + (V_s \cos \delta) I_q$$


$$= (V_s \sin \delta) \left[\frac{E_0 - V_s \cos \delta}{X_d} \right] + V_s \cos \delta \left(\frac{V_s \sin \delta}{X_q} \right)$$

$$= \frac{E_0 V_s \sin \delta}{X_d} + V_s^2 \cos \delta \sin \delta \left(\frac{X_d - X_q}{X_d X_q} \right)$$

$$= \frac{E_0 V_s \sin \delta}{X_d} + V_s^2 \left(\frac{X_d - X_q}{2 X_d X_q} \right) \sin 2\delta$$

4.3.18




AC-DC Converter

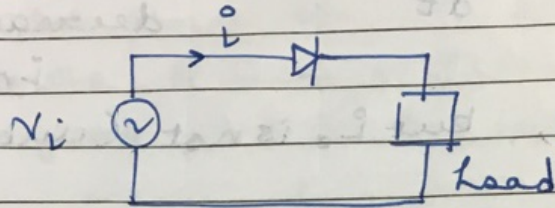

Half wave uncontrolled rectification

→ HW uncontrolled rectification


RLC type load
 $\rightarrow E$ in PE

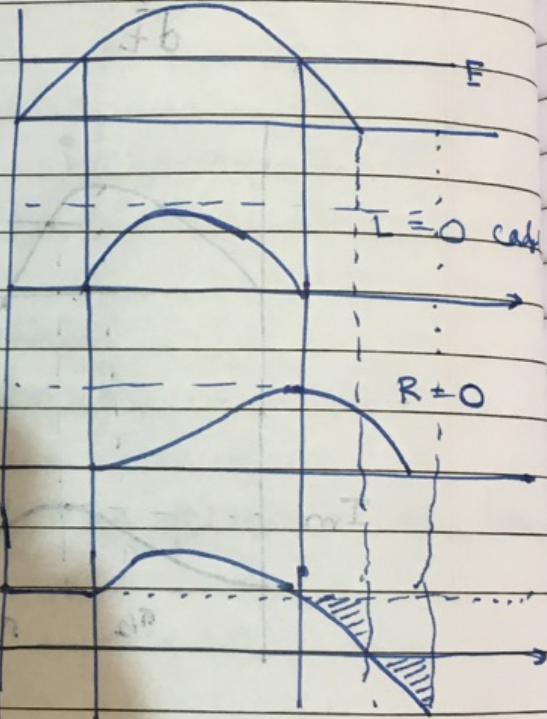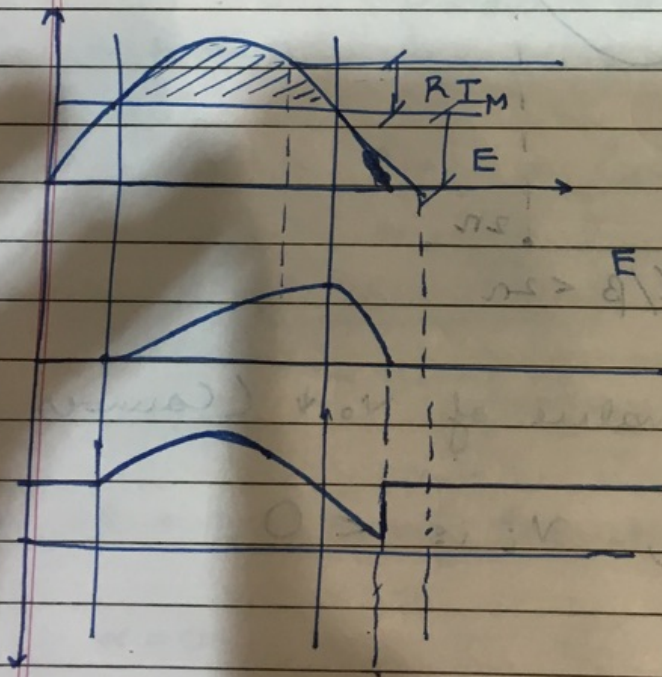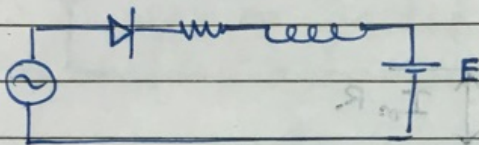



→ Problem with HW Rectification

- Source I has a DC component, this will flow in transformer secondary, limits Magnetic headroom that transformer has.

- only works at low power.

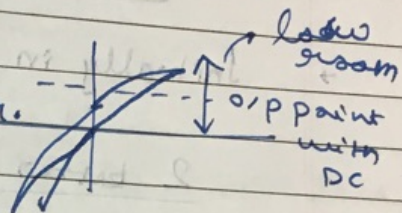

→ DC Motor speed control

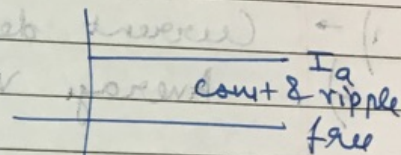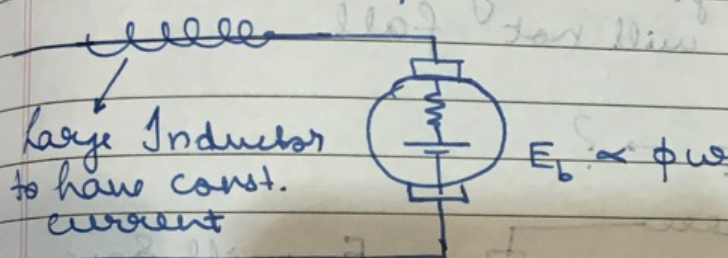


$$\frac{d\psi}{dt} = \frac{E_b - I_a R_a}{L}$$

- Cost of larger Inductor: Conduction period \uparrow
 $\Rightarrow V_o \downarrow$ (Average value last lecture)

- I_a - Should remain almost k

↓
Connect a large value of L

↓
As $L \uparrow$, $V_a \downarrow$

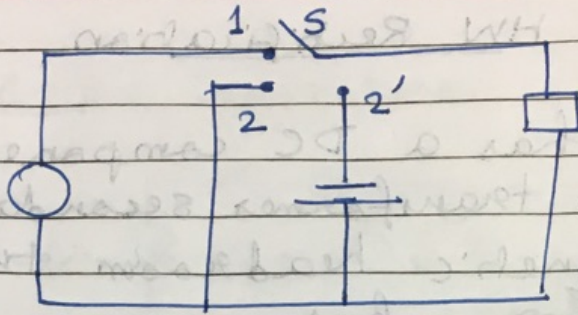


Initially in 1 \rightarrow transfer to 2 or 2'

2 better than 2'


- 1) \rightarrow Current decays slowly
- 2) Average V_o will not fall

Short DC M/c \rightarrow ?

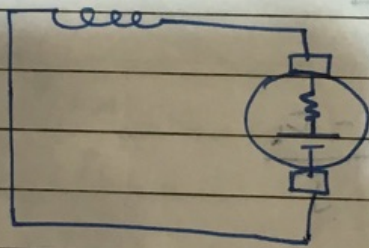


E_b will source & current may Reverse

prevent this by ...

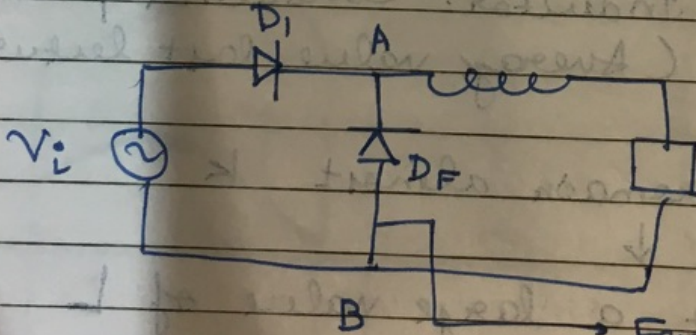

Free wheel diode

o/g CRB

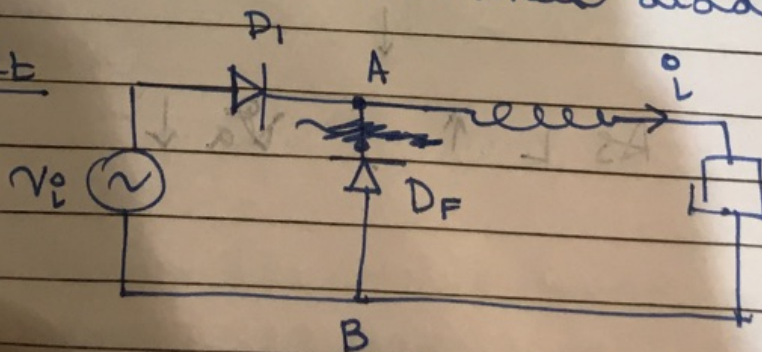

→ Assume i_L is cont. (Somehow)



General load $\rightarrow RLE$

→ Diode D_1 starts to conduct at zero crossing independent of the type of load.

→ $\frac{di}{dt}$ may be $-ve$ ($< VL$)

→ D_F cannot conduct in the half (Since D_1 is F.B & inconsistency)


$\frac{di}{dt} < 0$

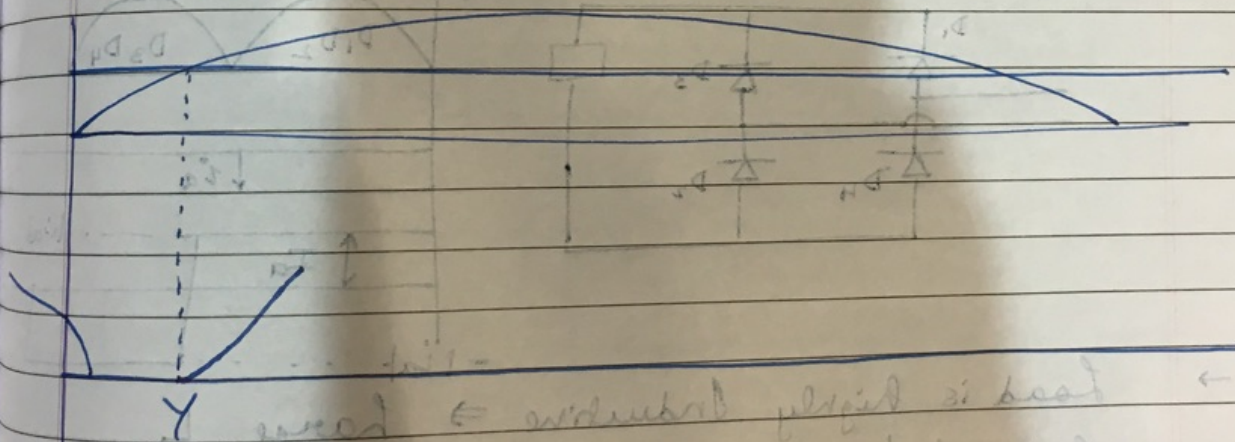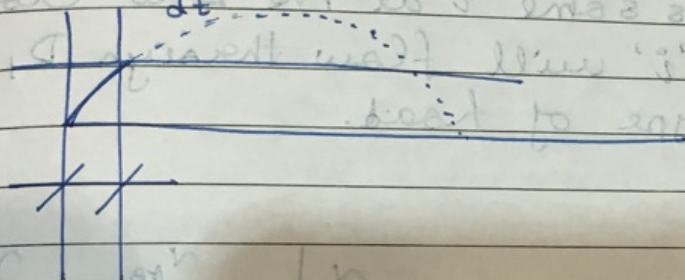


if $R=0$, $\frac{di}{dt}$ starts becoming $+ve$ at Y

→ Before that current may fall to 0

→ Current will start rising at Y


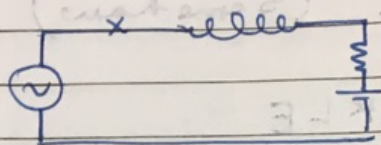


Condition

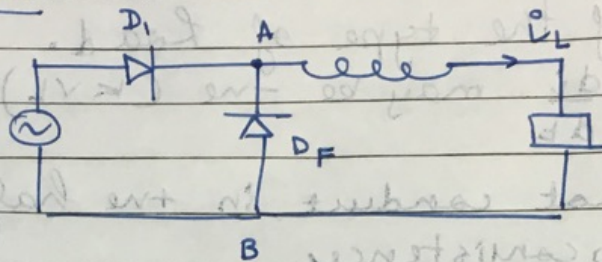

If there is some i at the zero crossing
 \Rightarrow This ' i ' will flow through D_1
 Indep. of type of load.

Full Wave

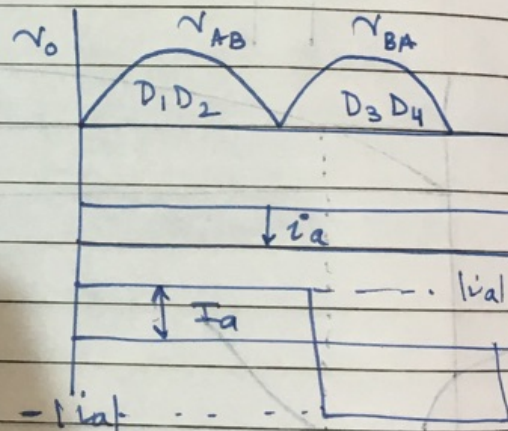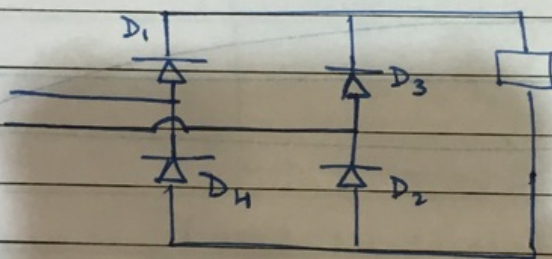


\rightarrow Load is highly Inductive \Rightarrow large L
 connected in series \Rightarrow DC link current
 is high & Ripple free

\rightarrow Source Current

$D_1 D_2 \rightarrow \text{Load} = \text{Source}$

$D_3 D_4 \rightarrow \text{Load} = -ve \text{ of Source}$

Power supplied by source

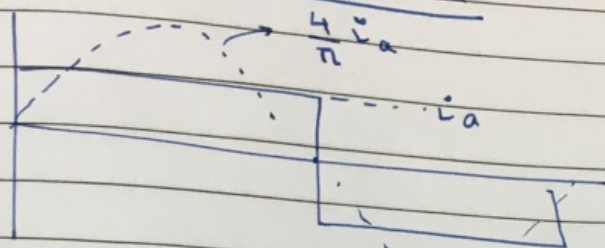

I_1 → Fund. component in square wave
 $V_e = 0 = \phi$, Displacement Angle
 $\cos \phi$, " Factors

→ New power factor Definition.

Any power term with 0 avg → Reactive power
 ⇒ $\sin \omega t \sin 3\omega t + \dots$ etc term
 $\sin \omega t \sin 5\omega t \dots$

$$= \frac{\text{Power}}{VA} = \frac{V_{RMS} I_1 \cos \phi}{V_{RMS} I_a} \rightarrow 1$$

$$= \frac{I_1}{I_a} = \left[\frac{4}{\pi \sqrt{2}} \right]$$