

Review

1. Buck, Boost, Buck – Boost & Cuk' Inverter → No isolation

⇒ $|V_{DC}|$ & $|V_0|$ can not be greatly different

⇒ Use a transformer & do not allow it to saturate

Close 'S' for 'DT' duration:


' i_1 ' enters the dot in the primary.

$i_2 = 0$, because of D_2

∴ $i_1 = i_m$ source supplying as the magnetising current,

↑ linearly with time.

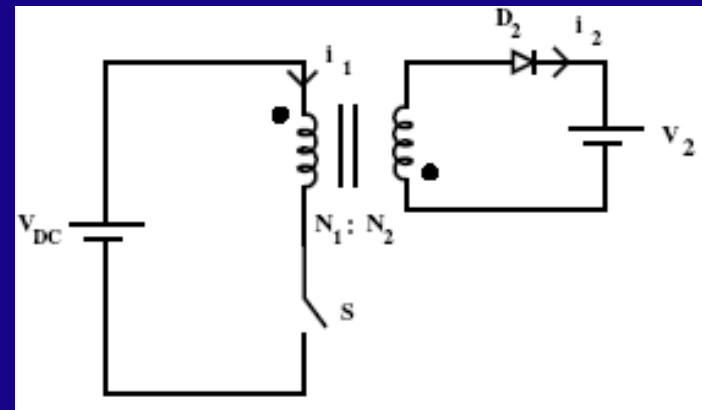' ϕ ' in the core also ↑ linearly with time.



Open 'S'

\Rightarrow ' ϕ ' in the core must be continuous

\therefore ' ϕ ' due to i_2 should be in the same direction as that due to i_1 (they are not produced at the same time).

$\Rightarrow \therefore i_2$ also enters the ' \bullet '



i_1 & i_2 will flow simultaneously when 'S' is opened.

\Rightarrow No path for i_m

\Rightarrow 'V' spike across 'S'

\Rightarrow Instead of feeding power to another 'V' source, connect a parallel combination of C & R


\Rightarrow Fly back converter

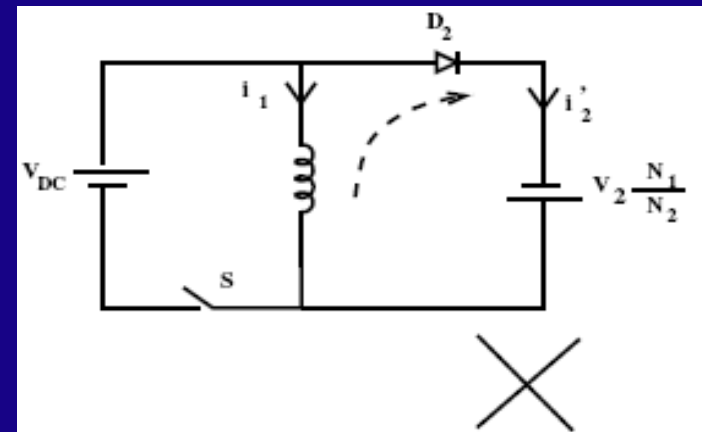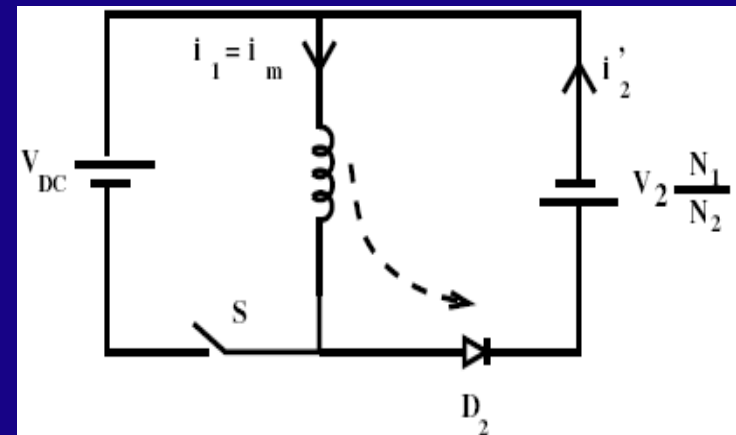

FLYBACK CONVERTER :

Freewheeling diode also known as flywheel diode.

Very popular upto 200 W.

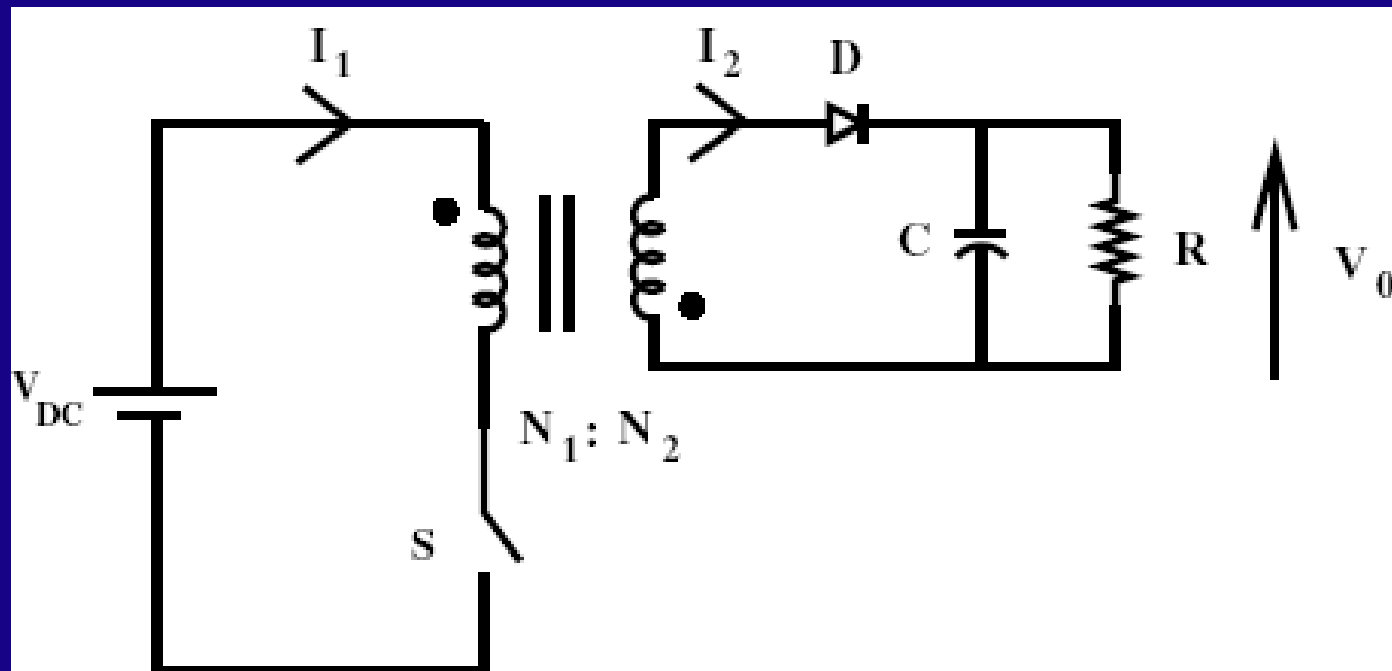

Close S :

Current enters the dotted terminal.

I_2 should leave the dot in the secondary.


⇒ Not possible due to D

$\therefore I_2 = 0 \quad \therefore I_1 = I_s = i_m \rightarrow$ only the magnetizing 'I'.

i_1 & $\therefore \phi \uparrow$ linearly.

'C' supplies power to the load.

'V' across $N_1 = V_{DC}$ ('•' is + ve)

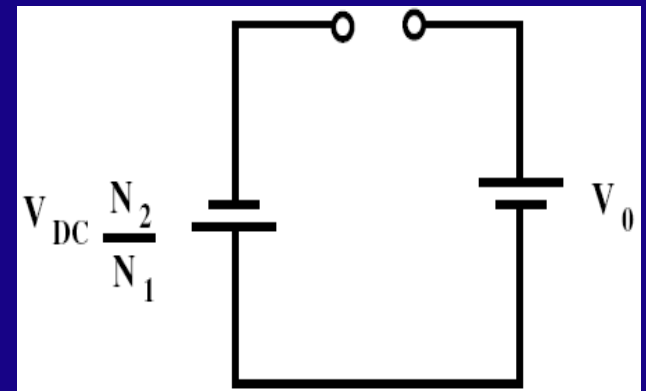

\therefore 'V' induced in secondary $= V_{DC} \frac{N_2}{N_1}$ ('•' is + ve)

Open S :

' ϕ ' in the core must be continuous.

$\Rightarrow i_2$ will flow in the sec. in such a way that direction of ' ϕ ' due to i_1 is same




$\Rightarrow i_2$ enters the dot in secondary

\Rightarrow Stored energy is transferred to the load



$\Rightarrow i_2$ may or may not become zero

$\Rightarrow i_2 \neq 0$ just prior to turn ON of 'S'

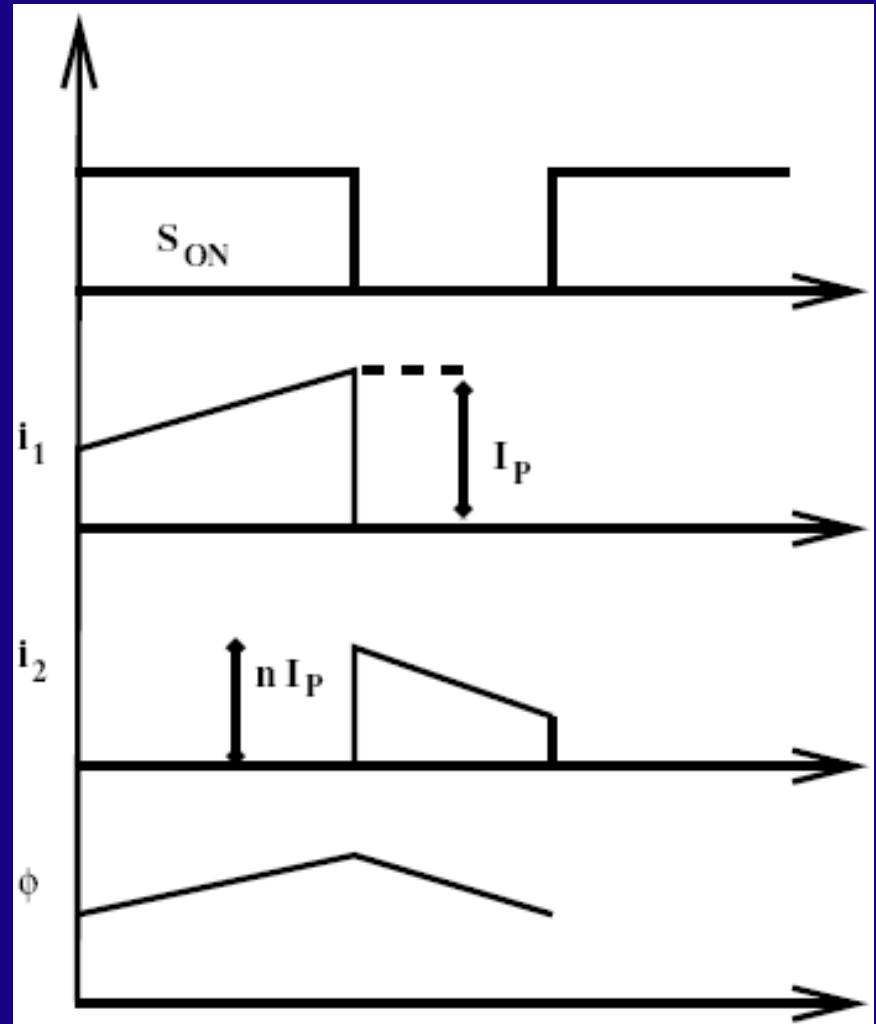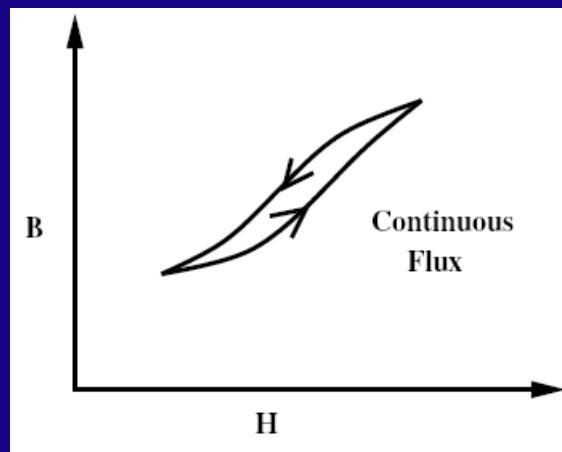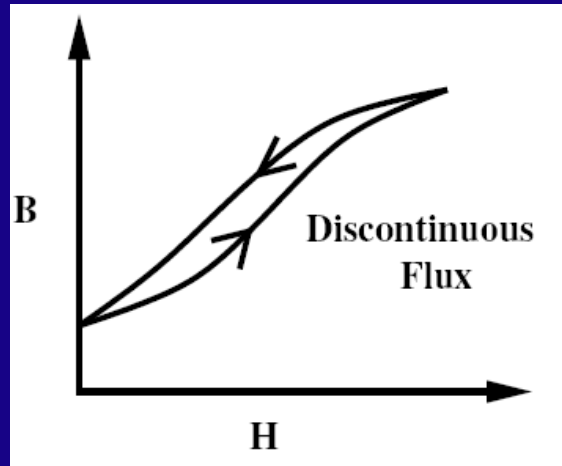\Rightarrow ' ϕ ' is continuous (unidirectional ' ϕ ')



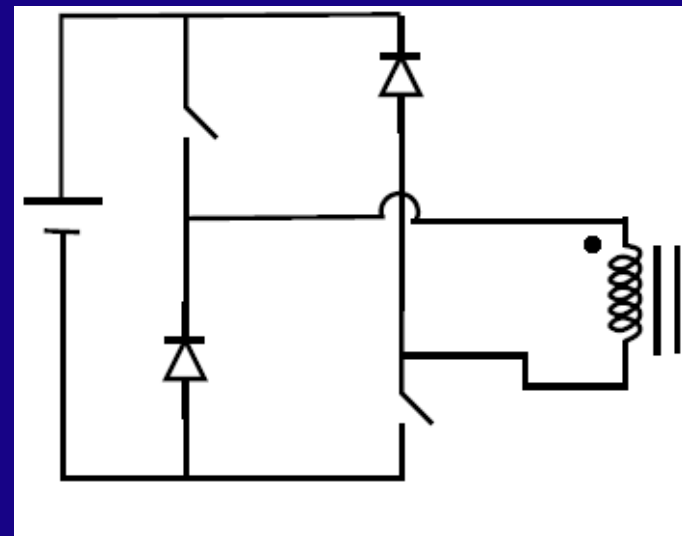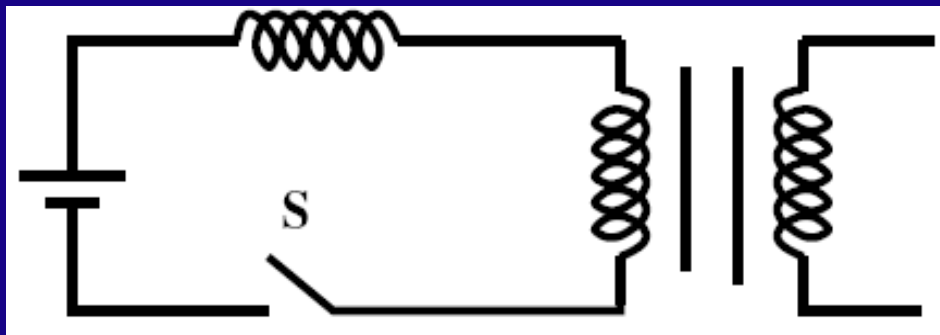- ⇒ Generally operated in discontinuous mode because if accidentally $D \uparrow$, core may saturate ⇒ 'S' may fail
- ⇒ Airgap is provided in the airgap
- ⇒ Not tightly coupled ⇒ Leakage flux



⇒ Flux will follow the above path only
if there is Volt.Sec./Turn balance



$$\uparrow \text{ in } d\phi = \downarrow \text{ in } d\phi$$

$$\uparrow \text{ in } d\phi = \frac{V_{DC}}{N_1} DT$$

$$\downarrow \text{ in } d\phi = \frac{V_0}{N_2} (1 - D)T$$

$$\therefore \frac{V_0}{N_2} (1 - D)T = \frac{V_{DC}}{N_1} DT$$
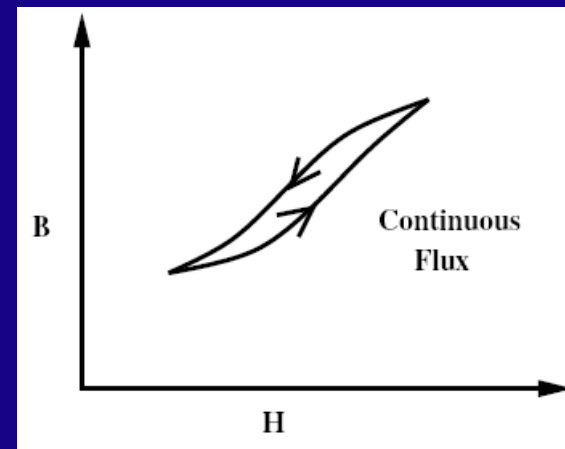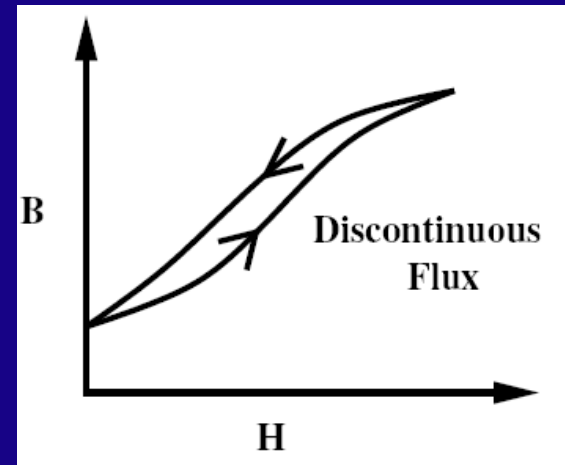
$$\therefore V_0 = V_{DC} \left(\frac{N_2}{N_1} \right) \left(\frac{D}{1 - D} \right)$$



⇒ $|V_0|$ & $|V_{DC}|$ can be significantly different

⇒ $D_{MAX} = 0.5$


⇒ Choose $\frac{N_2}{N_1}$ suitably

⇒ Primary 'L' is a very important parameter

$$I_P = \frac{V_{DC}}{L_1} DT$$

$$\therefore P_{in} = V_{DC} \left[\frac{1}{2} I_P \frac{DT}{T} \right] \approx P_0$$

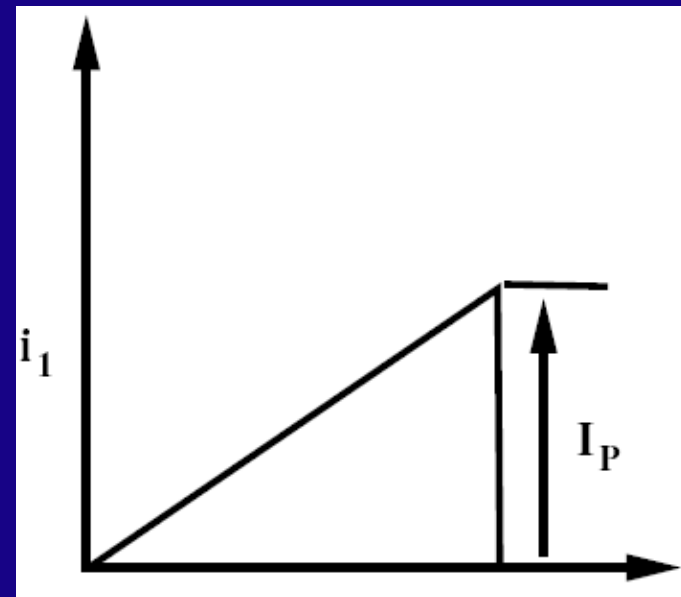
$$\therefore I_P = \frac{2P_{in}}{DV_{DC}} \approx \frac{2P_0}{DV_{DC}}$$



Advantage :

- 1) o/p can be significantly different.
- 2) Multiple o/p's are possible.
- 3) Isolation.

⇒ Closed loop is a must

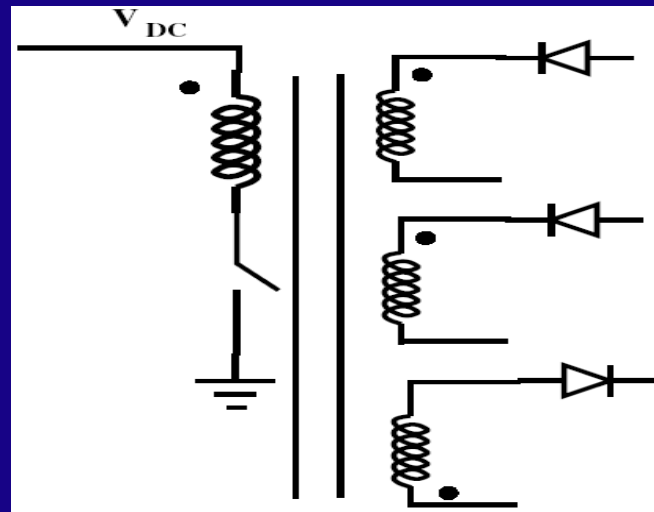

Various configuration :

