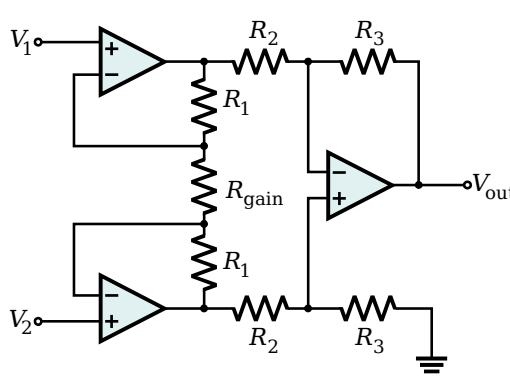


Assignment-8	EE204 - Analog Circuits	11 th Apr 2018
Submission Deadline-17.00 20 th Apr, 2018.	Submission Protocol: Drop hardcopy in the EE office	Comment: None

1.	Design an astable multi-vibrator using OPAMP for a period of 1 μ S and 25% duty cycle. It has unequal period for ON and OFF time.
2.	Derive the input impedance equations for all the GICs shown in Figs. 15.6(a)-(c) of the shared document "GIC and FDNR".
3.	It is required to derive a signal $V_o = 0.1\sin(4\pi 10^3 t + \pi/3)$ from an input signal $V_i = 0.01\sin(2\pi 10^3 t + \pi/2)$. Design an OPAMP based circuit for the same.
4.	The depletion capacitance of a diode under reverse bias voltage V follows the relation: $C = \alpha V^{-n}$. Find out the expression for α and n for an ideal diode. Design an LC or RC oscillator using the diode and find out the frequency of oscillation as a function of bias. Design the circuit in such a fashion that the bias can be controlled independently.
5.	Design an OPAMP based circuit to implement the following second order generalized differential function: $y = a \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + c$
6.	Find the output of the following instrumentation amplifier: 
7.	Design the following filters: 