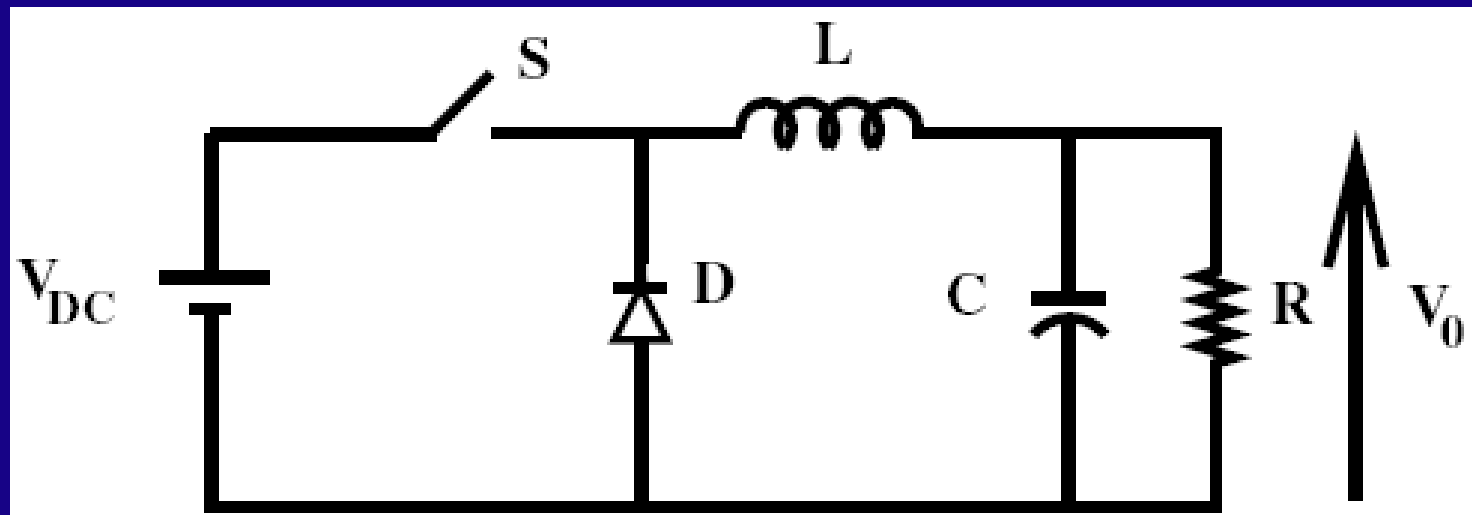


Buck converter :

$L \rightarrow$ Filter inductor.

$C \rightarrow$ Filter capacitor.


' V_0 ' is assumed to remain constant.



'S' is switched at a very high frequency.

S – ON for DT

– OFF for $(1-D)T$

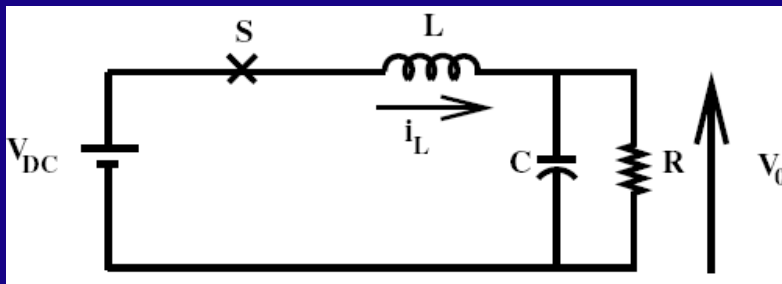


$$V_L = V_{DC} - V_0 \quad 0 < t < DT$$

= Constant t

$i_L \uparrow$ Linearly

$$i_L = C \frac{dV_0}{dt} + \frac{V_0}{R}$$

$$V_D = -V_{DC}$$

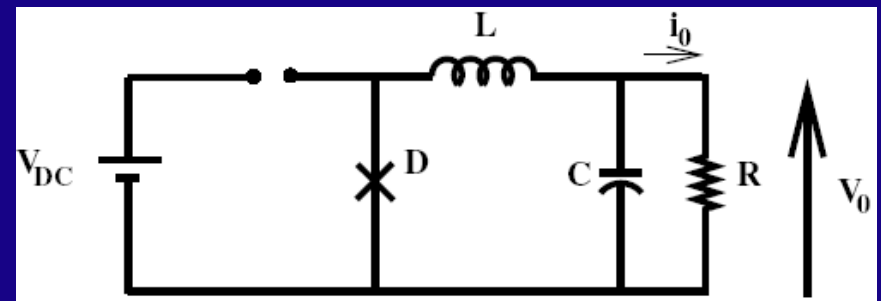


$$V_L = -V_0 \quad (1-D)T < t < T$$

$i_L \downarrow$ Linearly

$$i_L = C \frac{dV_0}{dt} + \frac{V_0}{R}$$

$$V_S = V_{DC}$$

Assume i_L is continuous.

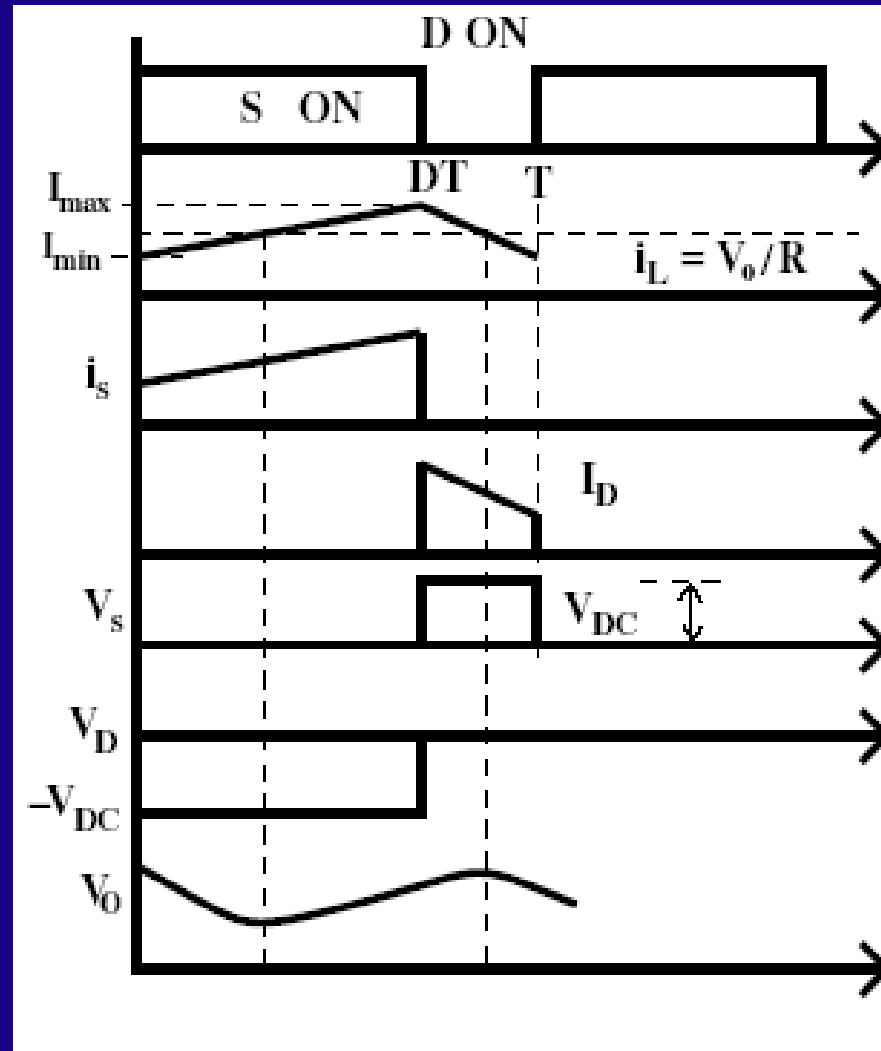

Neglect losses

Input power = Output power.

$$\begin{aligned} V_{DC} I_s &= V_o I_o \\ &= D V_{DC} I_o \end{aligned}$$

$$\therefore I_s = D I_o$$

Avg. source current < Avg. load current.

⇒ Similar to step-down transformer.

Source current waveform jumps from peak to zero.

⇒ peak value of $i_s > I_s$

⇒ L-C filter at the input side.

Expression for current ripple in i_L :


Assume that V_0 is constant (neglect the voltage ripple)

$$\frac{di_L}{dt} = \frac{V_{DC} - V_0}{L}$$

$$= \frac{V_{DC} - DV_{DC}}{L}$$

$$= I_{min} + \frac{V_{DC}}{L}(1-D)t$$
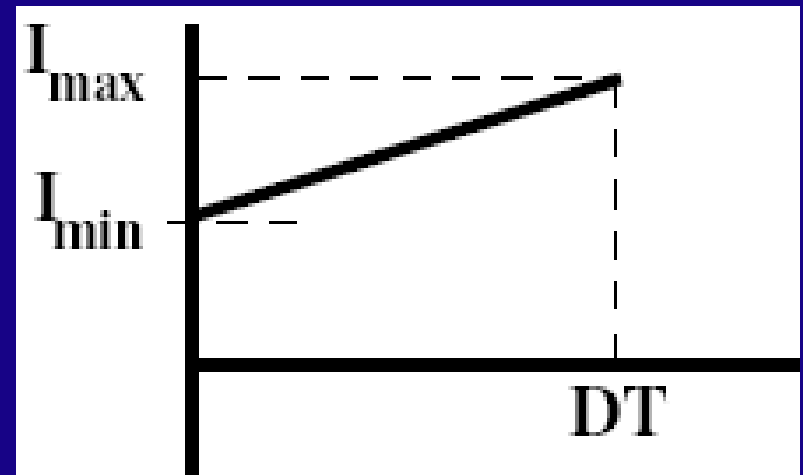
$$I_{max} = I_{min} + \frac{V_{DC}}{L}(1-D)DT$$



For $DT < t < T$


$$\frac{di_L}{dt} = \frac{-V_0}{L} = \frac{-DV_{DC}}{L}$$

$$\therefore i_L = I_{\max} - \frac{DV_{DC}}{L}(t - DT)$$

$$i_L = I_{\min} \text{ at } t = T$$

$$\therefore \Delta i_L = I_{\max} - I_{\min} = \frac{V_{DC}}{L}(1 - D)DT$$

$$\Delta i_L|_{\max} \text{ when } D = 0.5 = \underline{\underline{\frac{V_{DC}T}{4L}}}$$

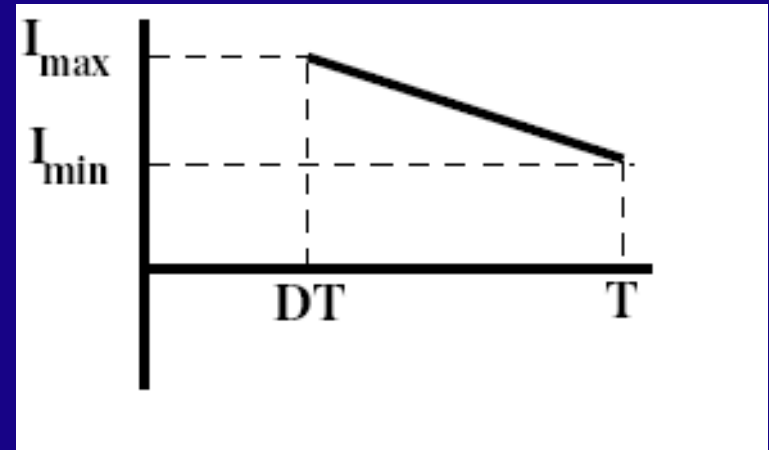

Capacitor voltage ripple :


for $0 < t < DT$

$$i_c = \frac{-\Delta i_L}{2} + \Delta i_L \frac{t}{DT}$$

for $DT < t < T$

$$i_c = \frac{-\Delta i_L}{2} - \Delta i_L \frac{t - DT}{T - DT}$$
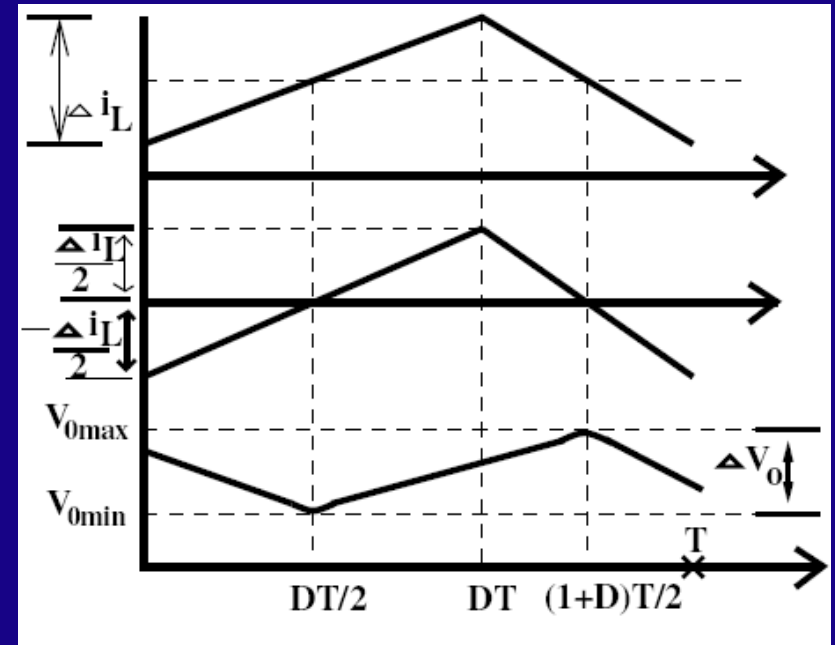
$$\begin{aligned} \Delta V_0 &= V_{0\max} - V_{0\min} = \frac{1}{C} \int_{DT/2}^{(1+D)T/2} i_c dt \\ &= \frac{1}{C} \Delta i_L \frac{T}{8} \end{aligned}$$



$$\therefore \Delta V_0 = \frac{V_{DC}}{8LC} (1-D)DT^2$$

for constant L, C & T , $\frac{\Delta V_0}{V_{DC}}$ is maximum

for $D = \underline{\underline{0.5}}$

Discontinuous Conduction:

Inductor current ' i_L ' and NOT I_0 .


$$I_0 = \frac{V_0}{R}.$$

Now i_L is continuous if

$$\frac{V_0}{R} \geq \frac{\Delta i_L}{2}$$

$$\frac{D V_{DC}}{R} \geq \frac{V_{DC}}{2L} (1-D) DT$$
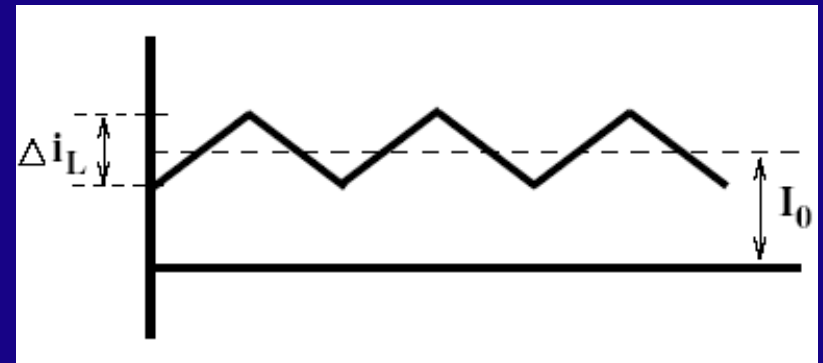
$$\therefore R \leq \frac{2L}{(1-D)T} = R_{CR}$$



If load $R > R_{CR}$,



i_L is DISCONTINUOUS.

$\Rightarrow i_L = 0$ for finite time.

i_s starts from zero.

If i_L is continuous, $V_0 = D V_{DC}$

\Rightarrow Independent of I_0

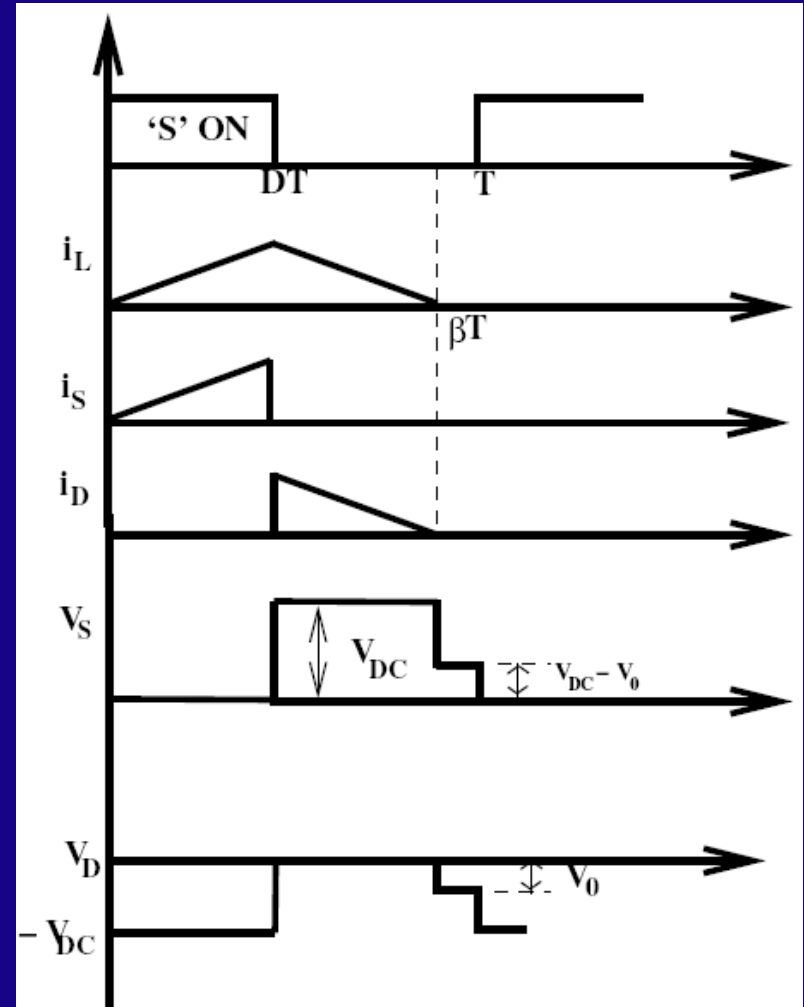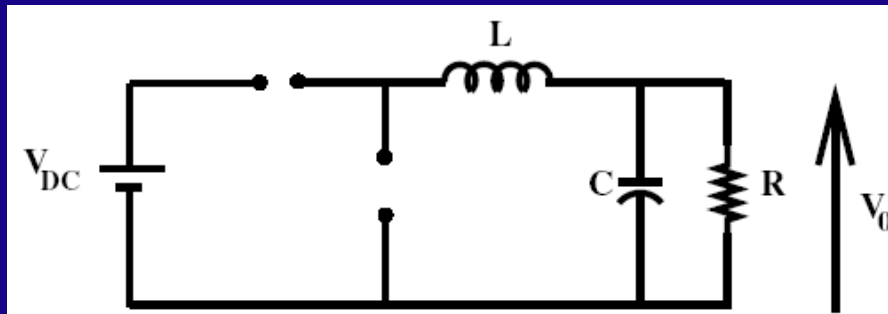

Circuit Equation:

For $0 < t < DT$

$$\frac{di_L}{dt} = \frac{V_{DC} - V_0}{L} \quad \therefore i_L = \frac{V_{DC} - V_0}{L} t.$$

For $DT < t < \beta T$

$$\frac{di_L}{dt} = \frac{-V_0}{L} \quad \therefore i_L = \frac{V_{DC} - V_0}{L} DT - \frac{V_0}{L} (t - DT) \quad \text{initially at } t=DT \text{ } i_L =$$

For $\beta T < t < T$ $i_L = 0.$

at $t = \beta T$, $i_L = 0.$

$$\frac{V_{DC} - V_0}{L} DT = \frac{V_0}{L} (\beta T - DT)$$

$$\therefore V_0 = \frac{D V_{DC}}{\beta}, \quad \beta < 1$$


\Rightarrow V_0 is higher than $D V_{DC}$ IF i_L is discontinuous.

Boost Converter

All components are ideal.

V_0 & V_{DC} are constant and ripple free.


Close S : for DT

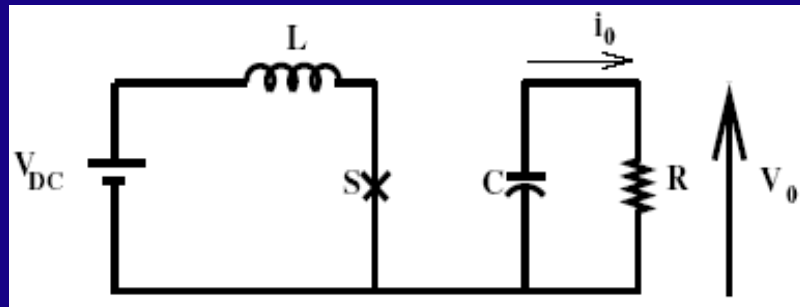


$$V_L = V_{DC}$$

$\therefore i_L \uparrow$ linearly.
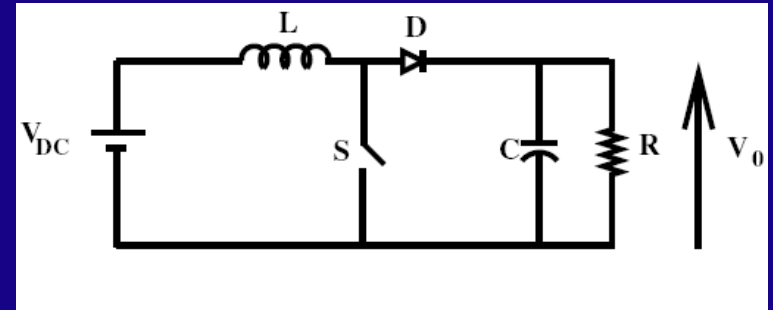
$$i_0 = -C \frac{dV_0}{dt} = \frac{V_0}{R}$$



Open S

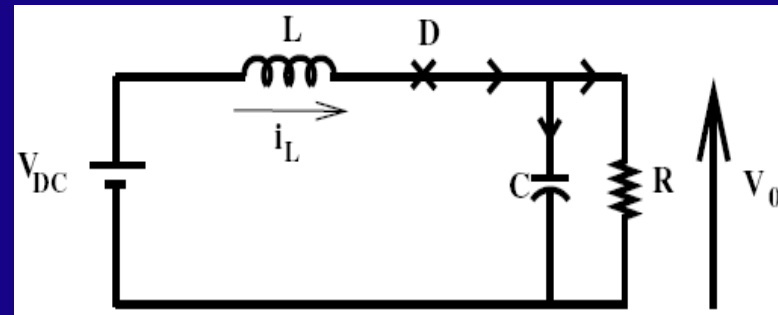

$$V_L = V_{DC} - V_0$$

$$C \frac{dV_C}{dt} + \frac{V_0}{R} = i_L$$

Capacitor supplies power to the load.

$$V_s = 0$$

$$V_D = -V_0$$


avg. voltage across 'L' = 0.

$$V_0 = \frac{V_{DC}}{(1-D)}$$

System is loss-less.

$$V_{DC} I_s = V_0 I_0$$

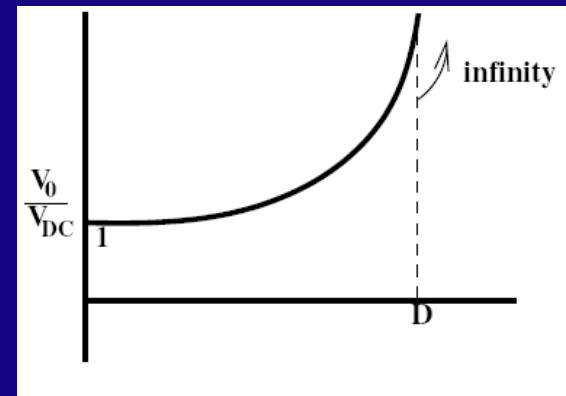
$$\therefore I_s = \frac{V_0}{V_{DC}} * I_0 = \frac{I_0}{(1-D)}$$



Effect of 'r':


$$V_{DC} = r i_L + L \frac{di_L}{dt} \quad || \quad 0 < t < DT$$
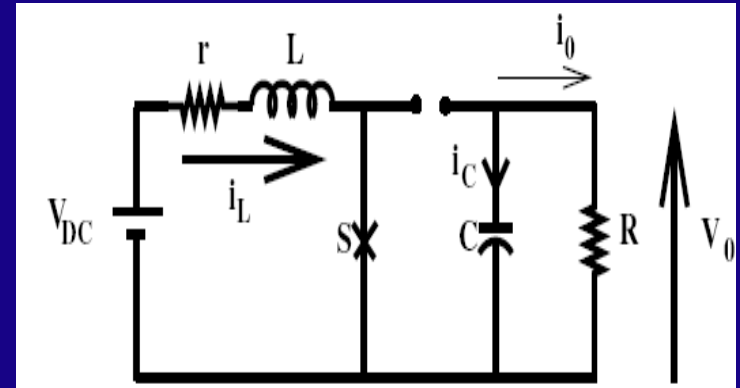
$$C \frac{dv_0}{dt} + \frac{v_0}{R} = 0$$



$$V_{DC} = r i_L + L \frac{di_L}{dt} + v_0 \quad || \quad DT < t < T$$
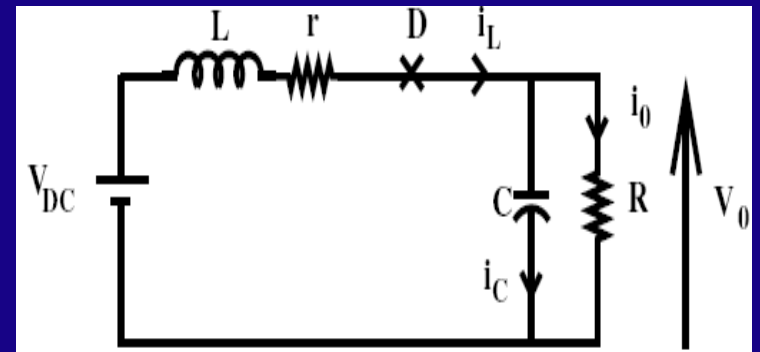
$$C \frac{dv_0}{dt} + \frac{v_0}{R} = i_L$$



Let the avg. values of v_0 & i_L be V_0 & I_L respectively.

$$V_{DC} = rI_L + L \left(\frac{di_L}{dt} \right)_{av} + \frac{1}{T} \int_{DT}^T v_0 dt.$$

$$C \left(\frac{dv_0}{dt} \right)_{av} + \frac{V_0}{R} = \frac{1}{T} \int_{\alpha T}^T i_L dt$$

Average values of $\frac{dv_0}{dt}$ & $\frac{di_L}{dt}$ are zero at steady state.

Also, variation of v_0 and i_L is assumed to be linear.

\Rightarrow avg. values of v_0 & i_L during (DT, T) are equal to avg. values of them varying on the whole cycle.

$$V_{DC} = rI_L + (1-D)V_0 \rightarrow (1)$$

$$\frac{V_0}{R} = (1-D) I_L \rightarrow (2)$$

multiply (1) by (1-D)

$$V_{DC} (1-D) = rI_L (1-D) + (1-D)^2 V_0$$

using (2)

$$V_{DC} (1-D) = r \frac{V_0}{R} + (1-D)^2 V_0$$

$$\therefore V_0 = \frac{V_{DC} (1-D)}{\frac{r}{R} + (1-D)^2} \rightarrow (3)$$

$$I_L = \frac{V_0}{R(1-D)} = \frac{I_0}{(1-D)} = \frac{V_{DC}}{r + (1-D)^2 R}$$

$$\text{If } r \rightarrow 0, V_0 = \frac{V_{DC}}{(1-D)}$$

$$\therefore I_L = \frac{V_0}{R(1-D)}$$

$$= \frac{I_0}{(1-D)}$$

$$= \frac{V_{DC}}{(1-D)^2 R}$$

$$D = 0, V_0 = \frac{V_{DC}}{r + R} * R$$

\Rightarrow As $D \uparrow$, $V_0 \uparrow$.

From (3), $V_0 = 0$! when $D = 1$

($V_0 \rightarrow \infty$ at $D = 1$ when $r = 0$)


Let $D = D_{\max}$ at $V_0 = V_{\max}$

$$\frac{dV_0}{dD} = 0. \quad D = 1 - \sqrt{\frac{r}{R}}$$

$$\therefore V_{0(\max)} = \frac{V_{DC}}{2} \sqrt{\frac{R}{r}}$$

⇒ Depends on $\frac{R}{r}$ ratio.

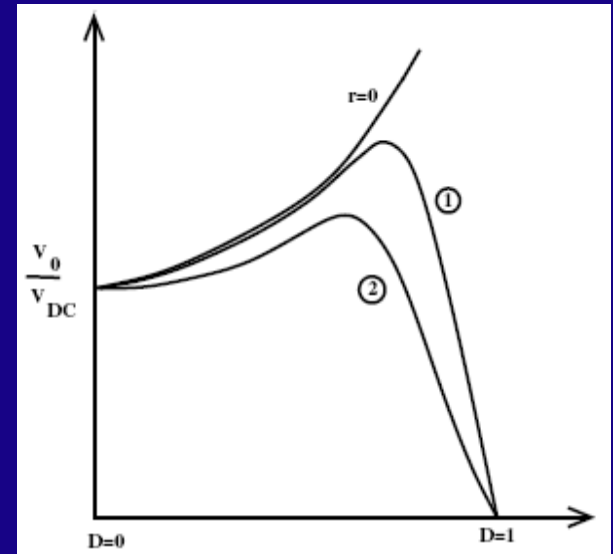$\frac{R}{r}$ for curve 1 > $\frac{R}{r}$ for curve 2



avg. value of $I_L = \frac{V_{DC}}{R + r}$ for $D = 0$

avg. value of $I_L \uparrow$ with D

$= \frac{V_{DC}}{r}$ when $D = 1$