

## Review

Each phase conducts for  $240^\circ$  (  $120^\circ$  in each  $1/2$  a cycle)

⇒ At a time only two devices are ON.

⇒ One phase is open circuited.

It does not supply power.

⇒ There are 6 pulses/cycle.

⇒ Hence the name Six Pulse Converter.

⇒ There are 6 pairs & each pair conducts for  $60^\circ$ .

⇒ At any given time 1 upper device & one lower device(not of the same leg) conduct.

⇒ Peak value of  $V_0 = \sqrt{3}V_m = \sqrt{2}(\sqrt{3}V)$

Where  $V_m$  = peak of phase voltage


$V$  = RMS Value of line-line voltage

$$\therefore \text{Avg. } V_0 = \frac{6}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{6}+\alpha+\frac{\pi}{3}} V_{ab} d(\omega t)$$

$$= \frac{6}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{6}+\alpha+\frac{\pi}{3}} \sqrt{3} V_m \sin(\omega t + 30^\circ) d(\omega t)$$

$$= \frac{3\sqrt{3}}{\pi} V_m \cos \alpha = 2.54 V \cos \alpha$$

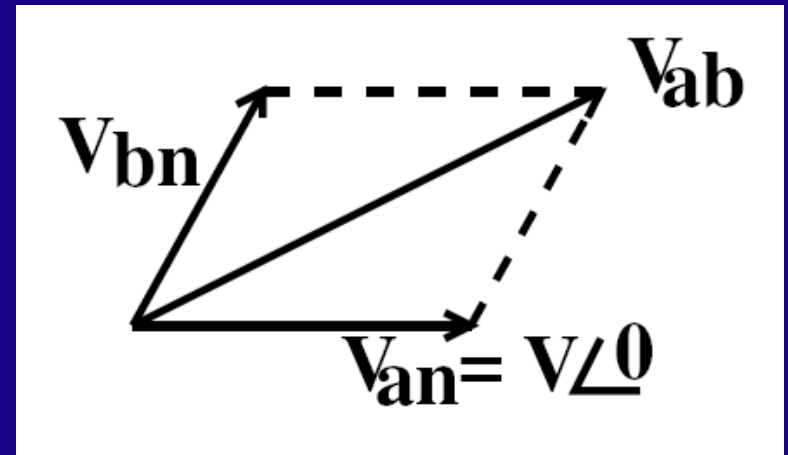
$$= 2 \left[ \frac{3\sqrt{3}}{2\pi} V_m \cos \alpha \right]$$



$\Rightarrow V_0 = 2[\text{o/p 'V' of 3-phase half wave controlled rectifier}]$

value of source current =  $\left[ \frac{1}{\pi} \times I_0 \times \frac{2\pi}{3} \right]^{\frac{1}{2}} = \sqrt{\frac{2}{3}} I_0$

$\therefore$  Equivalent circuit

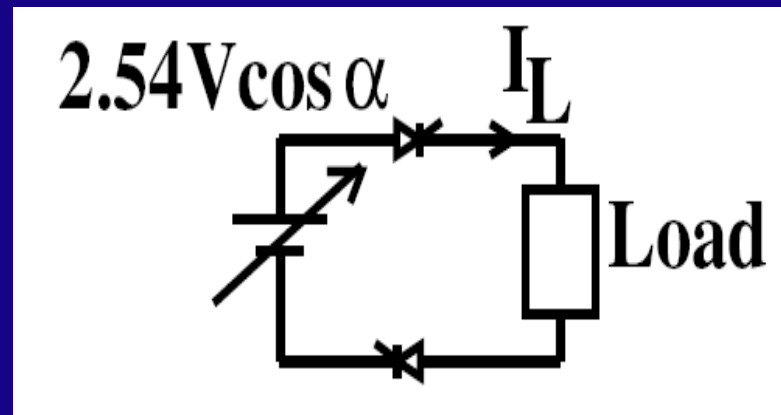

$$\alpha = 30^\circ$$

At  $\omega t = 60^\circ$  (w.r.t +ve zero crossing of phase A voltage).  $T_1$  is Triggered.


$\Rightarrow$  Prior to this  $T_5$  was conducting, in the lower half  $T_6$  is conducting.

At  $\omega t = 60^\circ$ ,

$$V_0 = V_{an} - V_{bn}$$

$$V_{an} = \sin 60^\circ = \frac{\sqrt{3}}{2}, V_{bn} = \sin 300^\circ = \frac{-\sqrt{3}}{2}$$

$$\therefore V_0 = \sqrt{3}$$

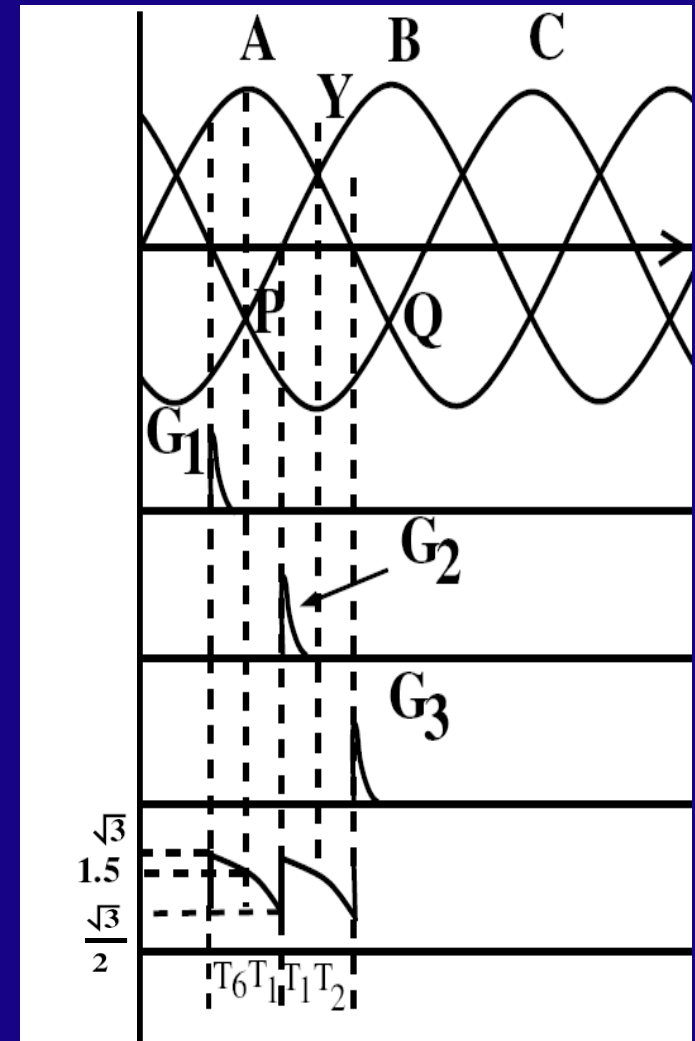


At  $\omega t = 60^\circ$ ,  $V_0 = V_{cn} - V_{bn}$  ( $\because T_6$  is conducting)

$$V_{cn} = \sin 180^\circ = 0, \quad V_{bn} = \sin 300^\circ = \frac{-\sqrt{3}}{2}$$

$$\therefore V_0 = \frac{\sqrt{3}}{2}$$

$$\therefore \text{At } \omega t = 60^\circ, \quad V_0 = \frac{\sqrt{3}}{2}$$

$$= 60^\circ, \quad V_0 = \sqrt{3}$$

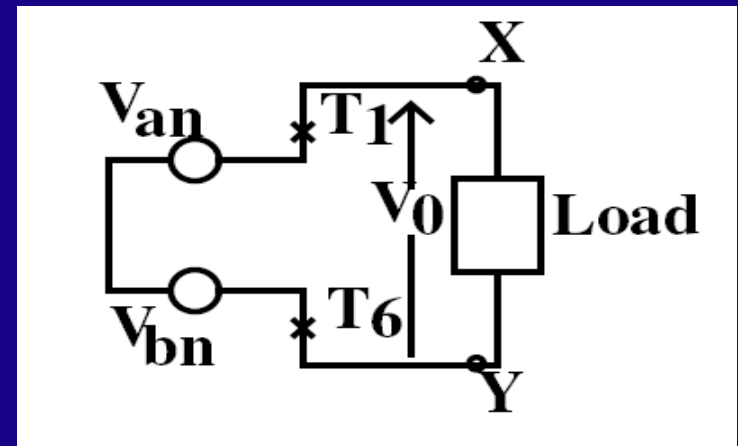

$$\text{At } \omega t = 90^\circ, \quad V_{an} = 1, \quad V_{bn} = \sin 330^\circ = \frac{-1}{2} \therefore V_0 = \frac{3}{2} = 1.5$$



$$\text{At } \omega t = 120^-, V_{an} = \frac{\sqrt{3}}{2}, V_{bn} = 0 \therefore V_0 = \frac{\sqrt{3}}{2}$$

$$\text{At } \omega t = 120^+, T_2 \text{ is Triggered. } \therefore V_0 = V_{an} - V_{cn}$$

$$V_{cn} = \sin 240^\circ = -\frac{\sqrt{3}}{2}, V_{an} = \frac{\sqrt{3}}{2} \therefore V_0 = \sqrt{3}$$

Observation :

Peak value of  $V_0 = \sqrt{3}V_m$  = Peak of line-line voltage

$$\alpha = 60^\circ$$

Just prior to triggering  $T_1$ ,  
 $T_5$  was conducting & from  
 lower half  $T_6$  is conducting.

$$V_0 = V_{cn} - V_{bn}$$


$$V_{cn} = \sin 210^\circ = -\frac{1}{2},$$

$$V_{bn} = \sin 330^\circ = -\frac{1}{2} \therefore V_0 = 0$$

When  $T_1$  is triggered  $\alpha = 60^\circ$

$$V_0 = V_{an} - V_{bn}, V_{an} = 1,$$
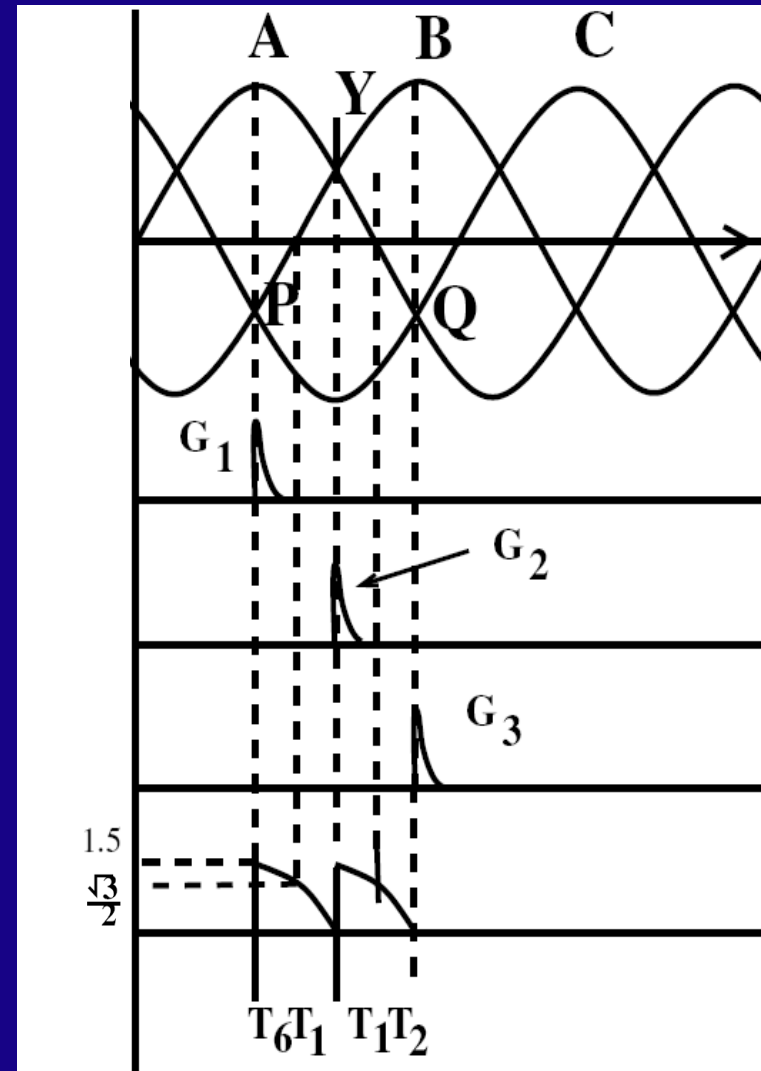
$$V_{bn} = \sin 330^\circ = -\frac{1}{2} \therefore V_0 = 1.5$$





$$\text{At } \omega t = 120, V_{an} = \sin 120^\circ = \frac{\sqrt{3}}{2}, V_{bn} = \sin 360^\circ = 0, \therefore V_0 = \frac{\sqrt{3}}{2}$$

$$\text{At } \omega t = 150^-, V_{an} = \frac{1}{2}, V_{bn} = \sin 30^\circ = \frac{1}{2} \therefore V_0 = 0$$

$$\text{At } \omega t = 150^+, T_2 \text{ is triggered, } V_0 = V_{an} - V_{cn}$$

$$V_{an} = \frac{1}{2}, V_{cn} = \sin 270^\circ = -1 \therefore V_0 = 1.5$$

Observation :

Peak value of  $V_0 = 1.5$

Min value of  $V_0 = 0$

$$\alpha = 90^\circ (\omega t = 120)$$

When  $T_1$  is triggered

$$V_{an} \propto \sin 120 = \sqrt{3}/2$$

$T_6$  is conducting in the lower half

$$V_{bn} \propto \sin 360 = 0$$


$$\therefore V_0 = \sqrt{3}/2$$

at  $\omega t = 150$

$$V_{an} \propto \sin 150 = 1/2$$

$$V_{bn} \propto \sin 30 = 1/2$$

$$\therefore V_0 = V_{an} - V_{bn} = 0$$

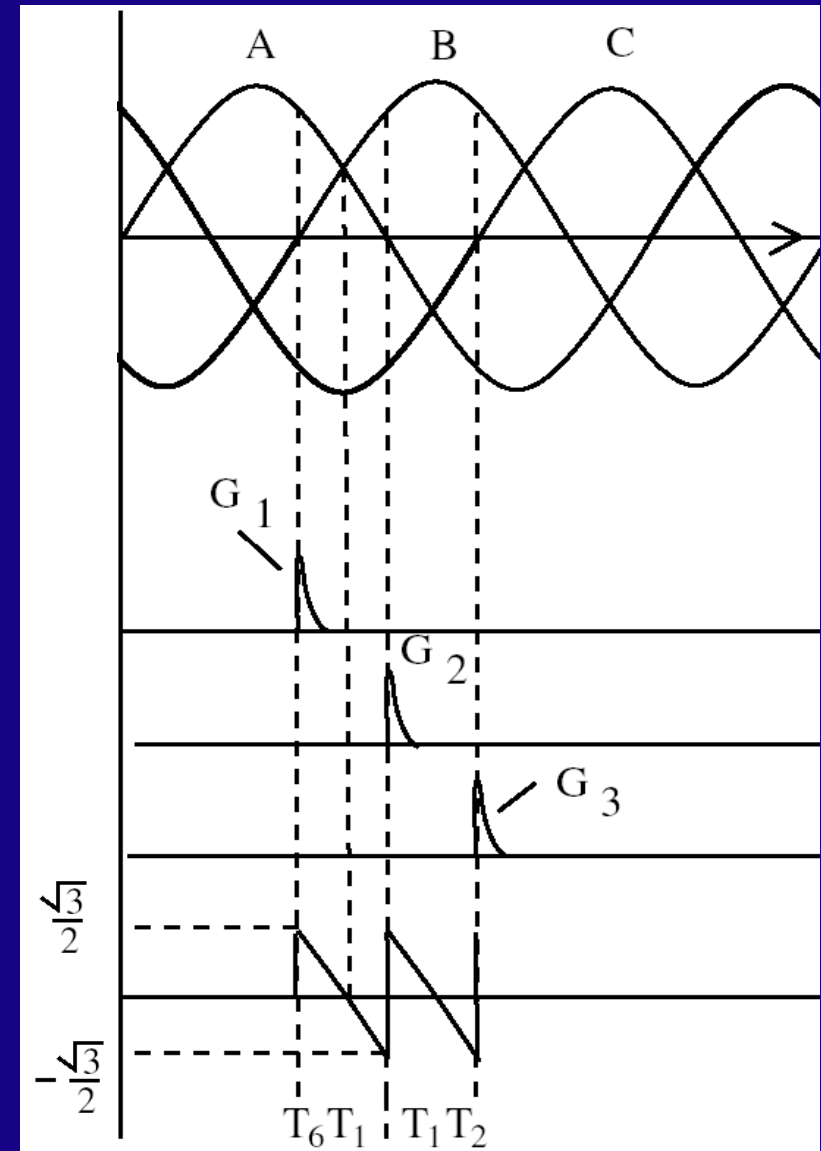

at  $\omega t = 180^-$

$$V_{an} = 0$$

$$V_{bn} \propto \sin 60^\circ = \sqrt{3}/2$$

$$\therefore V_0 = -\sqrt{3}/2$$

at  $\omega t = 180^+$   $T_2$  is triggered

$$V_0 = V_{an} - V_{cn}$$

$$V_{cn} \propto \sin 300^\circ = -\sqrt{3}/2$$

$$\therefore V_0 = \sqrt{3}/2$$

$\therefore \text{Av. } V_0 = 0$  (Provided  $i_L$  is continuous)

$$\alpha = 120^\circ (\omega t = 150)$$

When  $T_1$  is triggered

$$V_{an} \propto \sin 150 = 1/2$$

$T_6$  is conducting in the lower half

$$V_{bn} \propto \sin 30 = 1/2$$


$$\therefore V_0 = 0$$

$$\text{at } \omega t = 180$$

$$V_{an} = 0$$

$$V_{bn} \propto \sin 60 = \sqrt{3}/2$$

$$\therefore V_0 = -\sqrt{3}/2$$

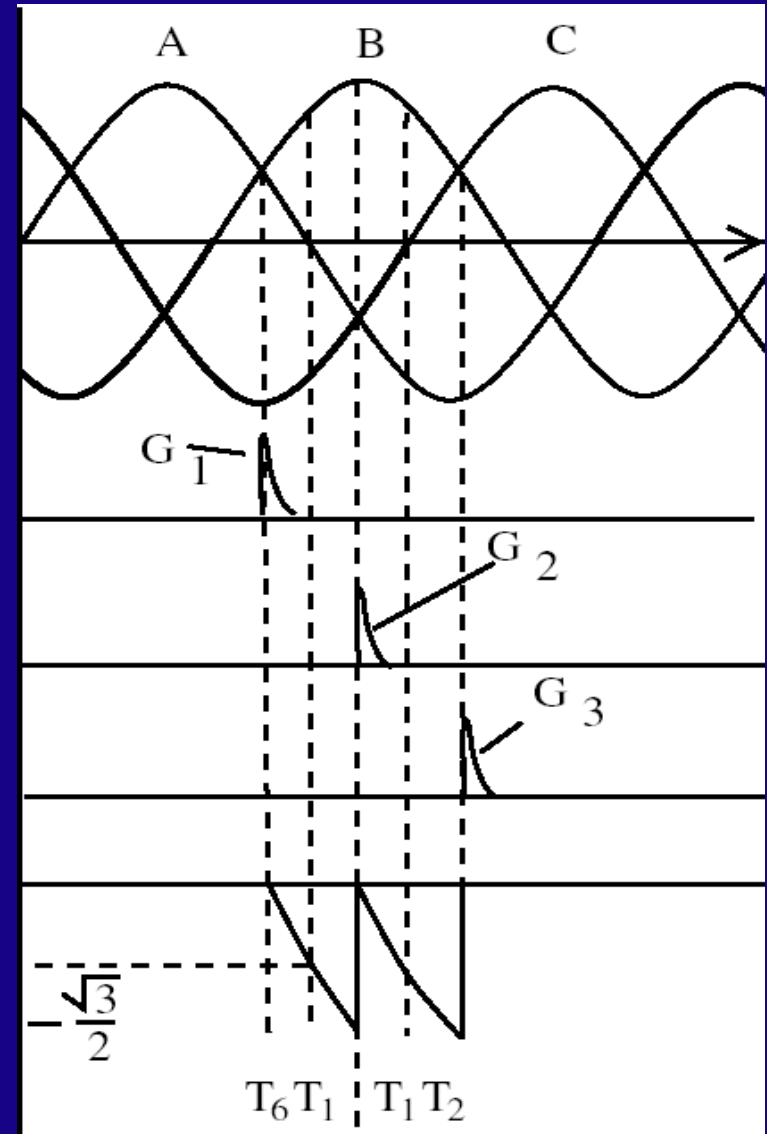

at  $\omega t = 210^\circ$

$$V_{an} \propto \sin 210 = -1/2$$

$$V_{bn} \propto \sin 90 = 1$$

$$\therefore V_0 = -1.5$$

at  $\omega t = 210^\circ$ ,  $T_2$  is Triggered

$$V_0 = V_{an} - V_{cn}$$

$$V_{an} \propto \sin 210 = -1/2$$

$$V_{cn} \propto \sin 330 = -1/2$$

$$\therefore V_0 = 0$$

Observation:  $V_0$  is either 0 or – ve

What is  $\alpha_{\max}$  to start the bridge?  
 $\Rightarrow$  ' $\alpha_{\max}$ ' For single phase bridge?  
can it be  $90^\circ$ ?

' $\alpha$ ' should be  $\approx 150 - 160^\circ$

Depends on ' $r$ ' and ' $L$ ' in dc side



If  $\approx 90^\circ$  :

instantaneous value of  $V_0 = V_m$

If ' $r$ ' & ' $L_a$ ' are very small

$i_{\text{peak}}$  will be large

$\Rightarrow$  May damage the bridge

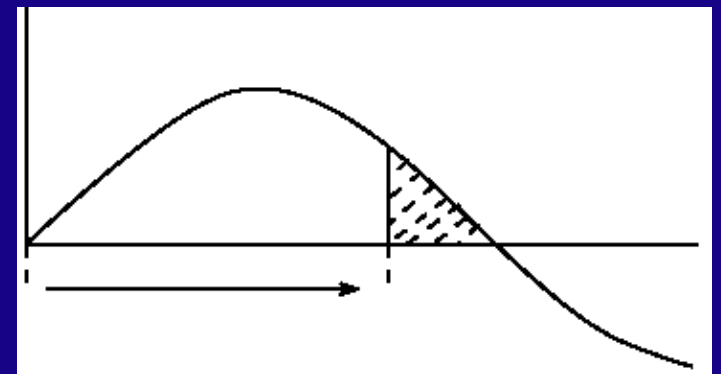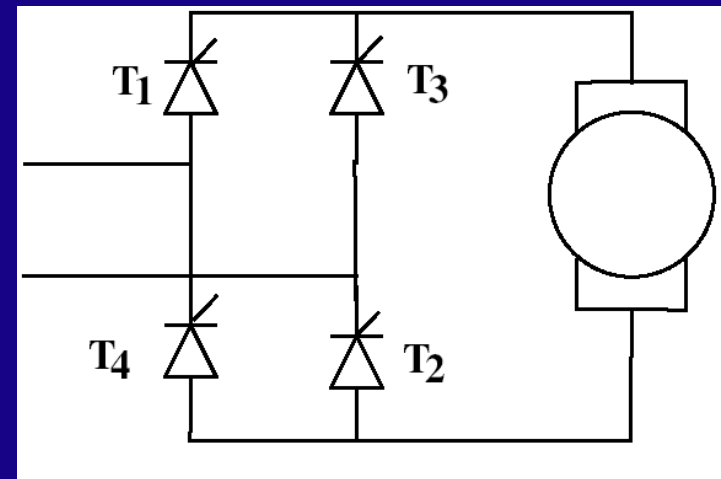



In 3 phase :

If  $\alpha > 120^\circ$ , no current can be established

Because instantaneous value of  $V_0$  is  
either 0 or – ve

$$\alpha_{\max} < 120^\circ$$

So that a + ve 'V' appears across 'L' &  
'i' starts flowing.

If Load = R

$i_L$  is continuous for  $0 < \alpha < 60^\circ$

What is the triggering pulse pattern :

Single phase bridge requires series of pulses for R – L – E load


In 3 phase : At any time two SCRs should be conducting

⇒ Change over from one device to another device doesnot takes place at same instant in both halves

⇒ To start the bridge or if  $i_L$  has becomes zero , to establish 'I' again

2 SCRs should be triggered simultaneously


Duration of each pair =  $60^\circ$

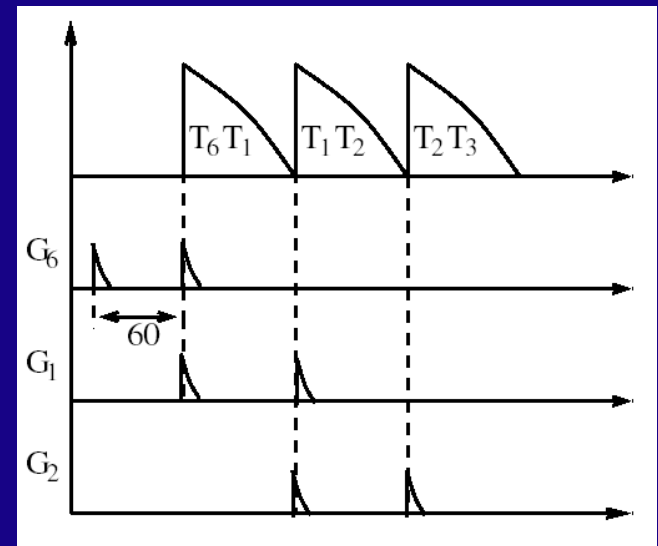

⇒ If load is highly inductive  $i_{\text{device}} > i_{\text{latch}}$

When  $i_g = 0$

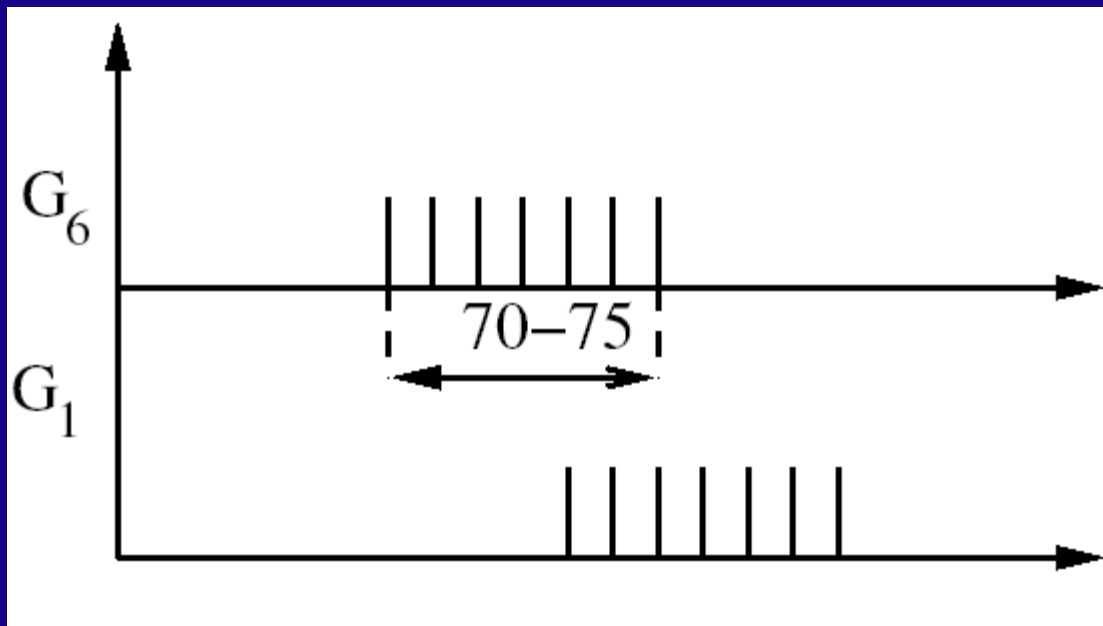⇒ Have large no. of pulses  
of width  $70 - 75^\circ$





Effect of source L :  
During change any two  
phases are short circuited

$$V_{an} - V_{bn} = 2L_s \frac{di_s}{dt}$$

Reference for  $\alpha$  is the point  
of natural commutation
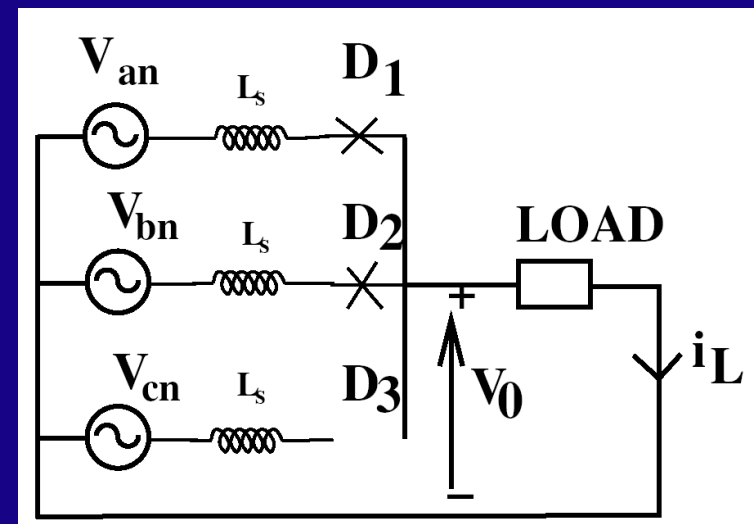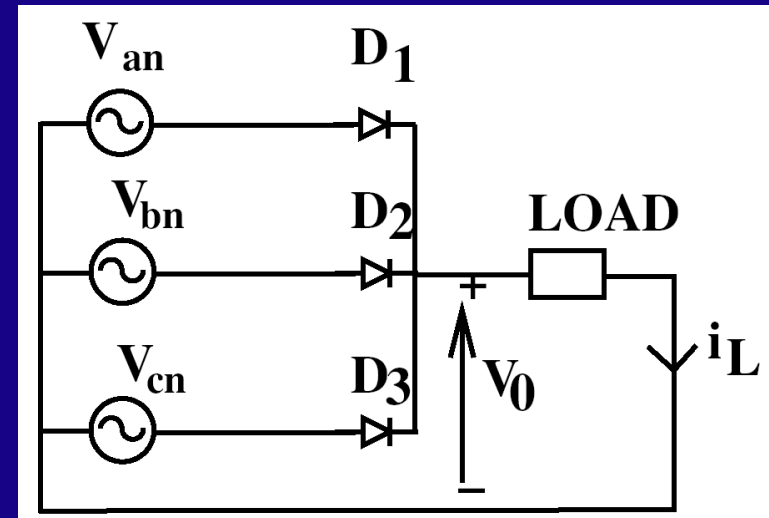
$$\therefore V_o = V_{an} - L_s \frac{di_s}{dt}$$



$$\begin{aligned}
 V_o &= V_{an} - L_s \frac{di_s}{dt} \\
 &= V_{an} - \left\{ \frac{V_{an} - V_{bn}}{2} \right\} \\
 &= \frac{V_{an} + V_{bn}}{2}
 \end{aligned}$$

