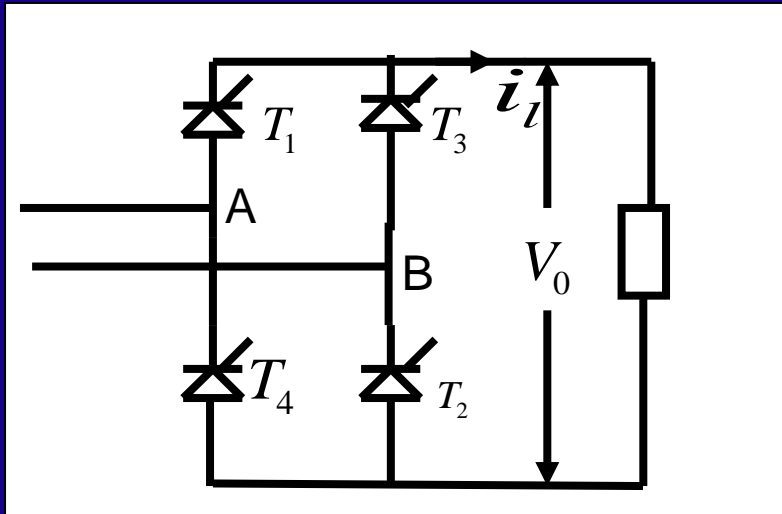



FULL CONTROLLED BRIDGE (Two Quadrant Converter)



➡ LOAD CURRENT IS CONSTANT & RIPPLE FREE

➡ IN THE +VE HALF T_1T_2 ARE F.B. & -VE HALF T_3T_4 ARE F.B.

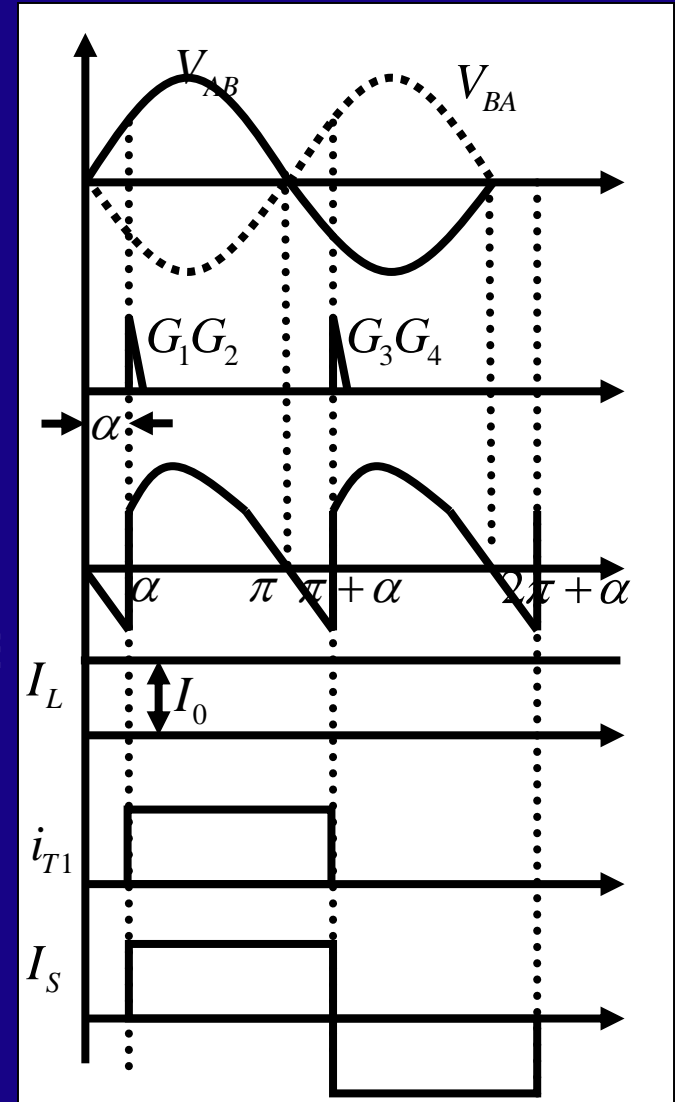T_1T_2 CONTINUE TO CONDUCT TILL T_3T_4 ARE TRIGGERED
($\because I_0$ IS CONTINUOUS)



α to $(\pi + \alpha)$

$$V_0 = V_i = V_m \sin \omega t$$

$$i_s = I_L$$

at $\omega t = \pi + \alpha$ T_3 & T_4 ARE TRIGGERED

POT. OF A < POT. OF C

WHEN T_3 STARTS CONDUCTING

$$V_K = POT. C$$

\Rightarrow -VE 'V' APPEARS ACROSS T_1



\Rightarrow TURNS OFF

\Rightarrow SIMILARLY T_2 TURNS OFF IN THE LOWER ARM

$$i_s = i_L$$

γ for each device is π rads

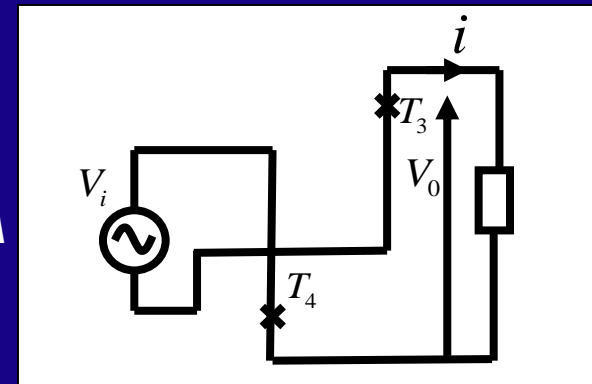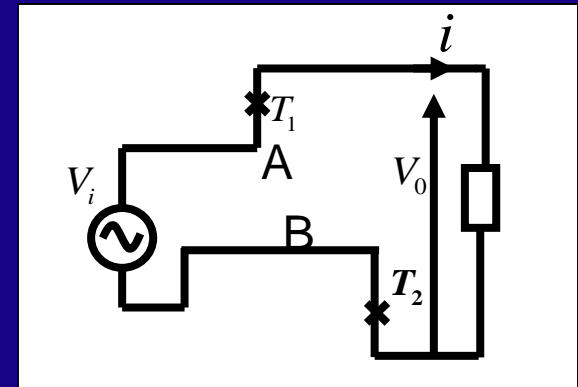There are 2 pulses per cycle \rightarrow Two pulse converter



$$V_0 = \frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d\omega t = \frac{2V_m}{\pi} \cos \alpha$$

$\Rightarrow V_0$ +ve For $0 < \alpha < \pi/2$

-ve For $\pi/2 < \alpha < \pi$



$\Rightarrow I_L$ is unidirectional

\Rightarrow 2 quadrant converter


$\Rightarrow 0 < \alpha < \pi/2$: 1st quadrant operation

Input Power = +ve \rightarrow Converter

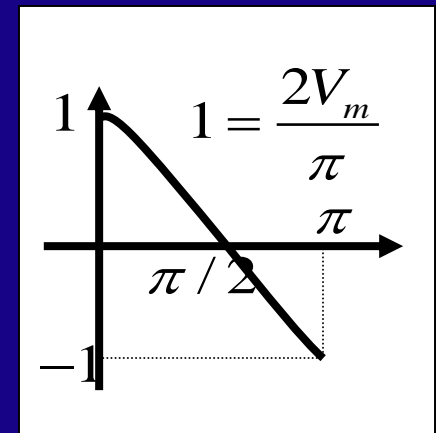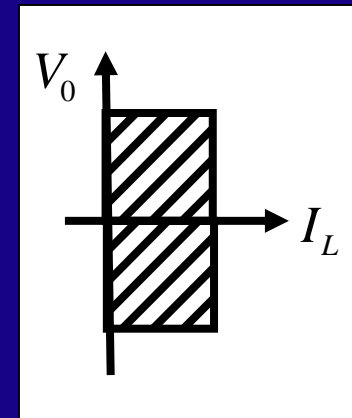$\Rightarrow \pi/2 < \alpha < \pi$: 4th quadrant operation



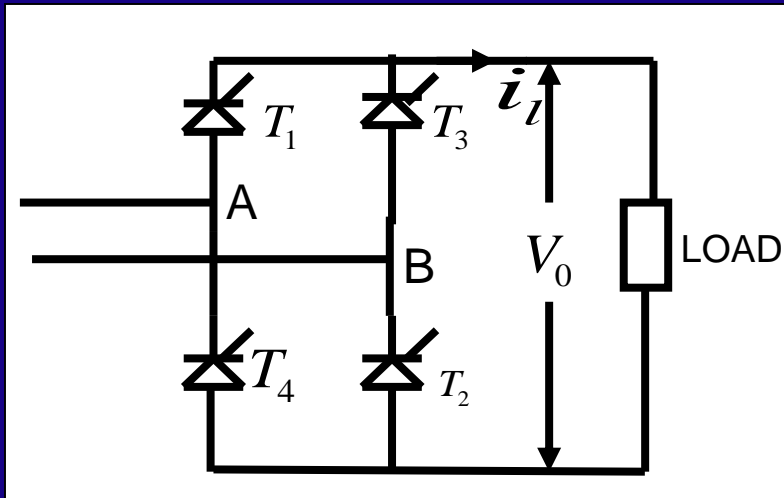FULL CONTROLLED BRIDGE ($\alpha > 90^\circ$)




$T_1 T_2$ are triggered in the +ve half

At steady State

Assume I_L is continuous (constant and ripple free)

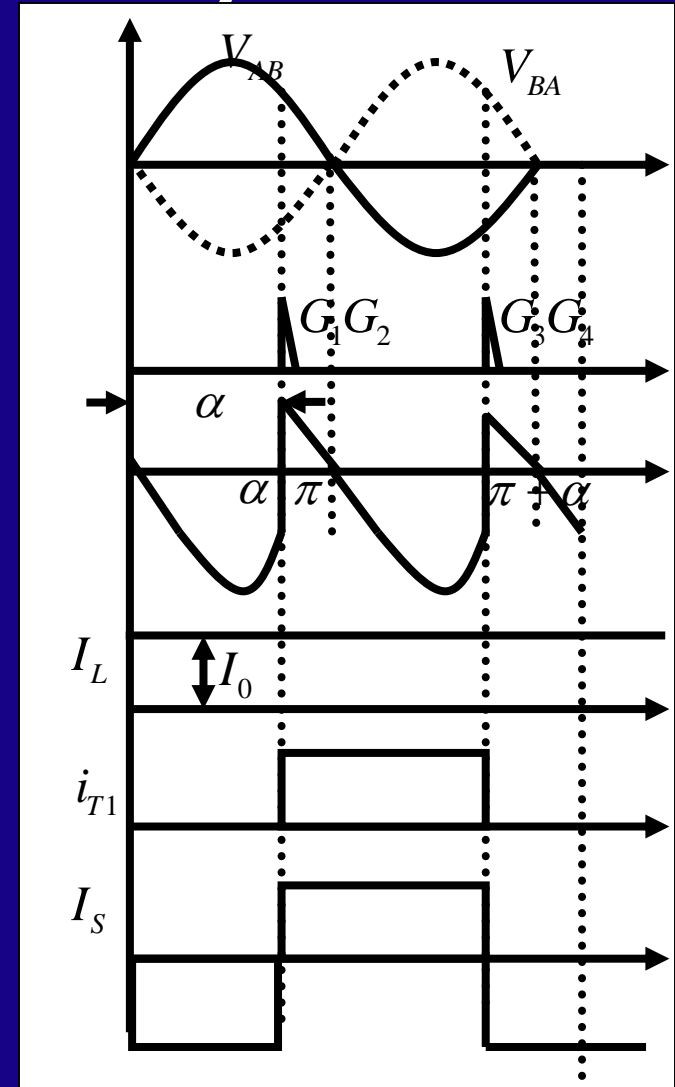$T_3 T_4$ will conduct till $T_1 T_2$ are triggered in the +ve half



In $0 < \omega t < \pi$

Pot. of Pt. B < Pot. of Pt. A

$$\therefore V_0 = V_{BA} \text{ (-ve)}$$



At $\omega t = \alpha^+$ (Immediately after T_1 and T_2 are triggered)

$\Rightarrow T_1 T_2$ are ON & $T_3 T_4$ OFF

(Assumed to be instantaneous turn ON and OFF)

$V_0 = V_{AB} \rightarrow +ve$ till $\alpha < \omega t < \pi$

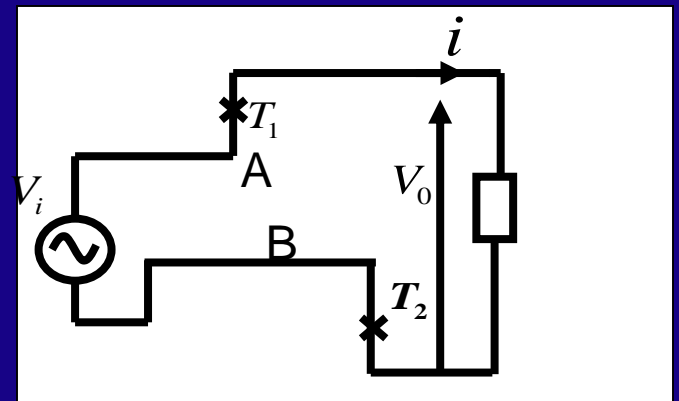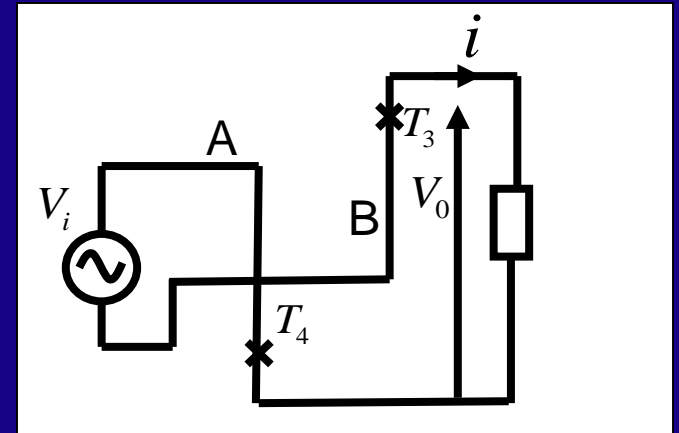$\rightarrow -ve$ for $\pi < \omega t < \alpha + \pi$



Input Power = -ve \rightarrow Inversion

$$\theta_1 = \alpha$$


$$\cos \theta_1 = \cos(-\alpha) \text{ (lagging)}$$

$$I_{rms} \text{ of } I_{s1} = \frac{2\sqrt{2}}{\pi} I_0$$

$$\text{RMS value of } I_s = I_0$$

$$P.F. = \frac{2\sqrt{2}}{\pi} \cos \alpha = \frac{V_{s1} I_{s1} \cos \alpha}{V_{rms} I_{rms}} = \frac{2\sqrt{2}}{\pi} \cos \alpha$$

\rightarrow lagging

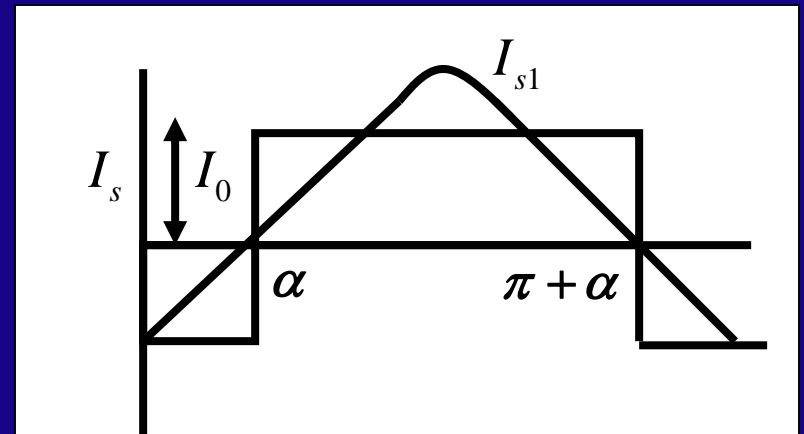

What sort of a load ?

Assuming that ' I_L ' is continuous

$$\Rightarrow \text{Avg. } V_0 = \frac{2V_m}{\pi} \cos \alpha \text{ is valid}$$

if ' I_L ' is discontinuous $V_0 \neq \frac{2V_m}{\pi} \cos \alpha$

\Rightarrow Avg. value of V_0 is determined

by integrating the o/p ' V_0 '

[output V_0 now dependent on load]

Avg. $V_0 \rightarrow -ve$

$I_L = \text{always } +ve \text{ (can not reverse)}$

\therefore SCR`s are unidirectional

$$\text{Avg. Power I/P} = V_{o(\text{avg})} I_{L(\text{avg})}$$

For Load = R

I/P Power = always +ve

Consumes power → dissipates as heat

For Load = L

For steady state $(L \frac{di}{dt})_{\text{avg}} = 0$

If $(L \frac{di}{dt})_{\text{avg}} > 0 \rightarrow \frac{di}{dt}$ is ↑

(recall Full wave diode rectifier feeding pure 'L' load, 'i' goes on ↑ till)

$(L \frac{di}{dt})_{\text{avg}}$ can never be -ve

\Rightarrow if load is passive $= V_{o(avg)} I_{L(avg)} \geq 0$

\Rightarrow If the load is R-L-E

Either a battery or a DC- motor


\Rightarrow Power can be fed back to the source

Both can supply or absorb power.

For DC-motor: If power i/p is +ve \Rightarrow motor

if power i/p is -ve \Rightarrow generator

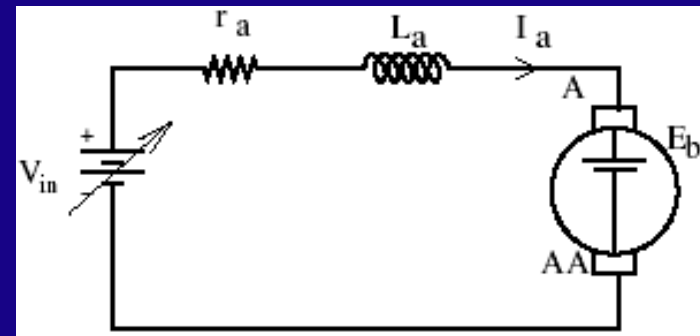For the m/c : To operate as a generator ' I_a ' should leave terminal 'A' (It enters 'A' during motoring)



If $|E_b| > |V_{in}|$

\Rightarrow ' I_a ' leaves 'A' terminal

For the Converter fed DC machine :

'I' can not reverse but 'V' can reverse.

$T_e \rightarrow -ve \rightarrow$ either ' ϕ ' or ' I_a ' should reverse

Consider DC M/C :-

Developed Torque $T_e = K\phi I_a$

$$\frac{d\omega}{dt} = \left(\frac{T_e - T_L}{J} \right), T_L \text{ is load torque.}$$

⇒ Assume that motor has attained a steady state and running at ω .

⇒ Want to stop the motor

Case1: Switch off the supply to the motor

$$T_e = 0$$

⇒ $-\frac{d\omega}{dt}$ depends on mechanical time constant

$$T_m = \frac{J}{B}$$

Stored energy is dissipated as heat

⇒ How to $\uparrow -\frac{d\omega}{dt}$

⇒ Make T_e -ve

$$\frac{d\omega}{dt} = -\frac{(T_e + T_L)}{J}$$

⇒ Faster deceleration

⇒ $T_e \rightarrow -ve$

Sign Convention:

+ve for motoring

-ve for Generating

⇒ Energy is fed back to the source

⇒ Regenerative braking

For I_a reversal:

Interchange armature terminals

\Rightarrow i/p to the bridge is -ve

\Rightarrow Motor current has reversed

\Rightarrow m/c is operating like a generator


\Rightarrow No mechanical i/p

\Rightarrow speed & $E_b \downarrow$

\Rightarrow In order to maintain constant I_a

$\downarrow V_{in}$

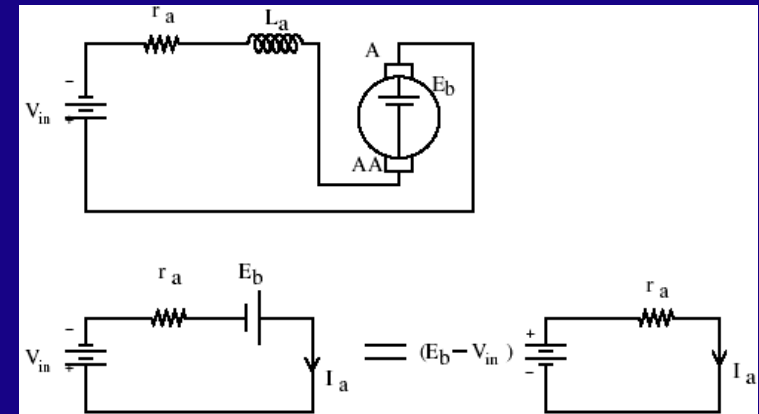$\Rightarrow \downarrow \alpha$ towards 90°



Discontinuous Conduction : R-L-E Load

Case I :

'i' is finite

When $T_1 T_2$ are triggered

T_3 & T_4 were conducting


Instantaneous V_0 is -ve (\because is V_{BA})

$\rightarrow T_1$ & T_2 are triggered at ' α '

$V_i < E \therefore \frac{di}{dt}$ is -ve

\rightarrow 'i' becomes zero before $\omega t = \sin^{-1}\left(\frac{E}{V_m}\right)$

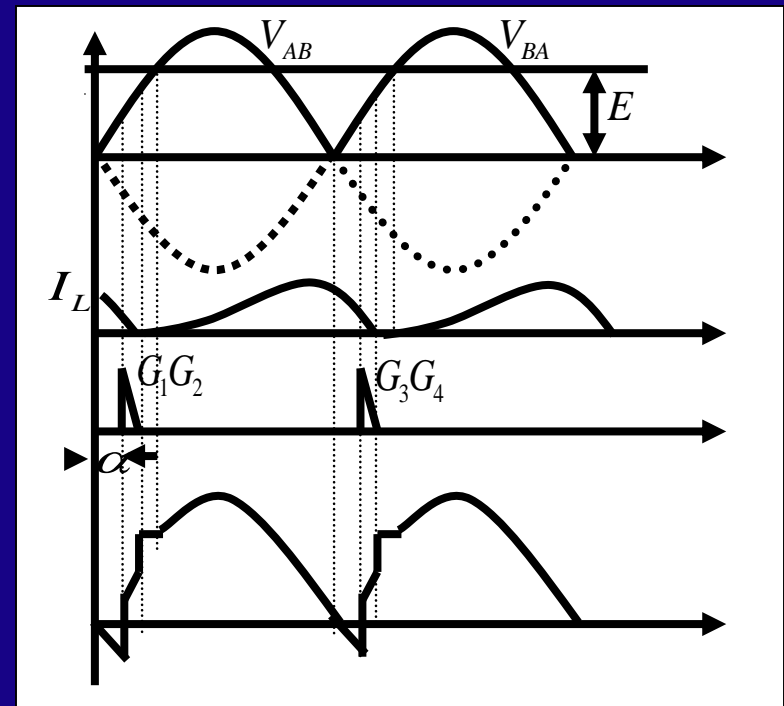\rightarrow Till 'i' is present, $V_0 = V_i$



From the instant $i=0$ till $\omega t = \sin^{-1}\left(\frac{E}{V_m}\right)$

$$V_0 = E$$

Beyond this instant SCR's are F.B

→ If gate pulse is present it starts conducting from this instant

Case II :

$$\alpha > \sin^{-1}\left(\frac{E}{V_m}\right)$$

$$I_L = 0 \quad 0 < \omega t < \sin^{-1}\left(\frac{E}{V_m}\right)$$

Prior to triggering $T_1 T_2$,

$T_3 T_4$ were conducting


till $I_L = 0$,

$V_i = V_{AB}$ (-ve in the +ve half)

From this instant to α , $V_o = E$

At ' α ', T_1 & T_2 are conducting,

$$V_o = V_m \sin \alpha > E$$

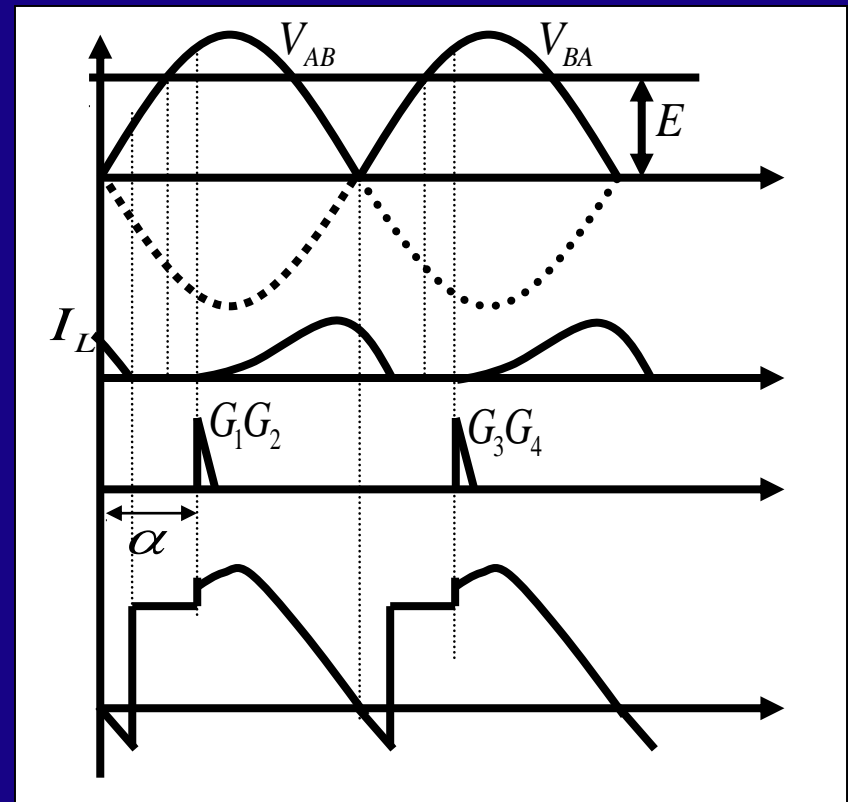

Case I:

$\alpha > 90^\circ$

Can I_L be continuous ?

\Rightarrow If I_L is continuous

$$V_0 = \left(\frac{L di}{dt} \right)_{av} = -ve$$

\Rightarrow Not possible



\Rightarrow If $\alpha = 110^\circ$

T_1 T_2 will turn off ($\because i_L = 0$)

at $180 + 70 = 250^\circ$

$\Rightarrow I_L$ is just continuous at $\alpha = 90^\circ$
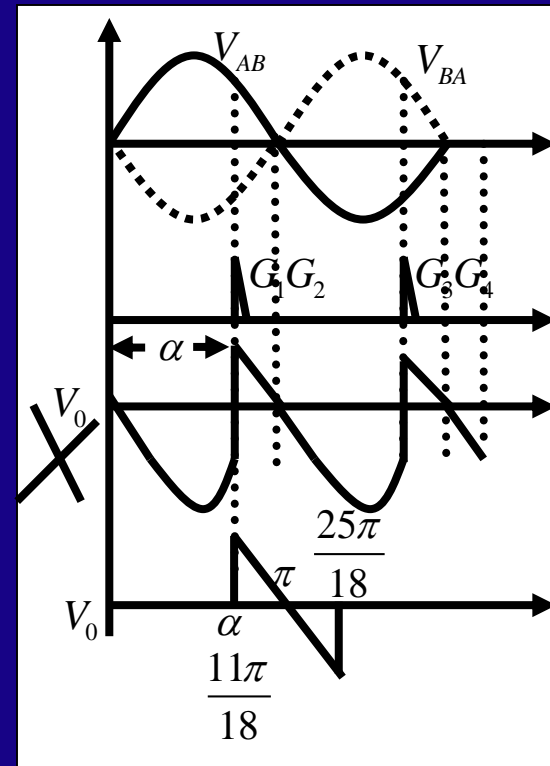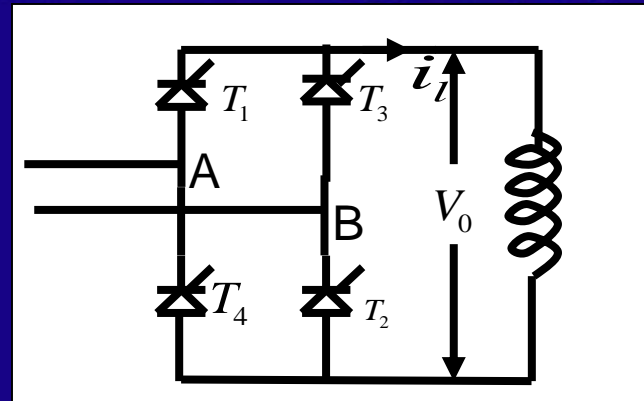
$$Av \ V_0 = \frac{2V_m}{\pi} \cos \alpha = 0$$



$$\alpha < 90^\circ$$

I will be continuous till

$$Av \ V_0 = +ve$$

$$\Rightarrow \left(L \frac{di}{dt} \right)_{av} = +ve$$

No steady state

I goes on \uparrow till.....

