

# Switched Capacitor Circuits

Wadhwani Electronics Lab

Department of Electrical Engineering  
Indian Institute of Technology Bombay

February 20, 2018



This lab consists of four modules:

- ▶ RC Integrator
- ▶ Switch Capacitor Integrator
- ▶ A Fourth Order Butterworth RC Filter
- ▶ A Fourth Order Butterworth Switched Capacitor Filter

The first two modules shows a comparison between an RC-integrator circuit and a switched capacitor integrator showing the nuances of implementing a resistor without using a resistor. The latter two modules are essentially the application perspective of the switched capacitors and how similar (or different) it is compared to a regular RC topology that we traditionally opt for.



Connect the circuit as shown in the fig.(1):

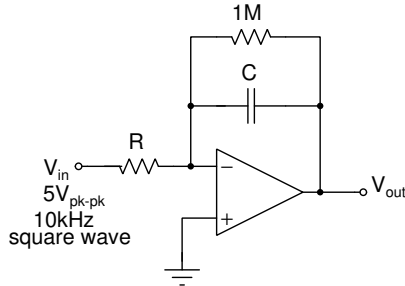


Figure 1: An RC Integrator

Connect a discrete resistor  $R$  and capacitor  $C$  obtained in Q5 and Q6 of Design Exercise.




- ▶ Observe the output of TTL source of AFG. Is it unipolar or bipolar? What are the minimum and maximum magnitude?
- ▶ Observe the relationship between the amplitude, frequency and phase settings of Channel-1 Output and TTL Output. Discuss your observation with your TA.
- ▶ The switches  $S_1$  and  $S_2$  are connected to the two control signals obtained from Channel-1 and TTL output of the AFG.
- ▶ In switch capacitor circuits there should be no overlapping of the two phase clocks (Fig.(2)). This can simply be obtained by exploiting AFG's Channel-1 and TTL relationship, rather than designing a different circuitry altogether.
- ▶ Generate two non-overlapping signals at a frequency of 10kHz with a voltage of 0 to 3.6V as shown below and show it to your TA



**Question:** Can we use a simple inverter to obtain non-overlapping clocks? What might be the problems one could face while using an inverter?

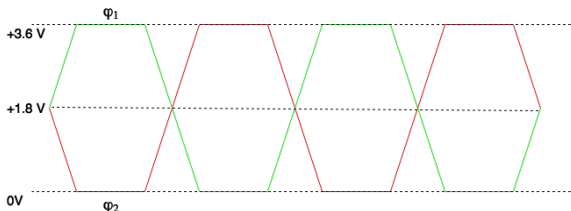**Question:** Suggest an alternative method to obtain non-overlapping clock using Op-Amps.



Connect the circuit as shown in the fig.(3), use switch from IC CD4066 (operating at supply voltage of  $V_{DD} = +5V$  and  $V_{SS} = 0V$ ) :

- ▶ Use the values of  $C_1$  and  $C_2$  as calculated in design exercise.
- ▶ Apply a 0 to 5V square wave signal at 10 Hz at the input.
- ▶ Vary the frequency from 10 Hz to 2 kHz and note the change in the output waveform.
- ▶ How can you explain the discrepancy between the obtained wave and RC integrator output?
- ▶ What change would you need to make to this circuit to obtain an output similar to the discrete RC integrator?



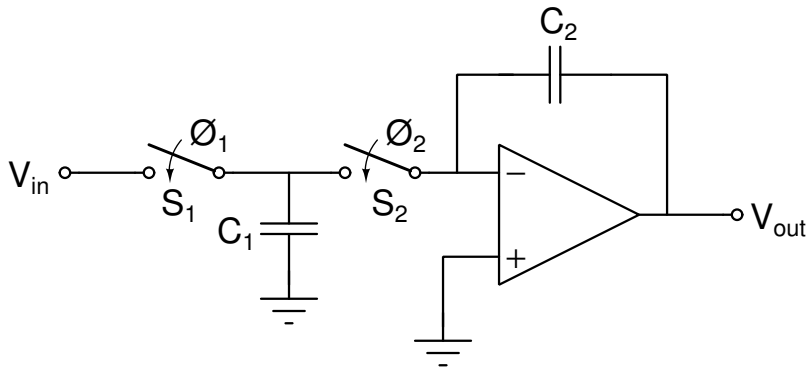


Figure 3: Switched Capacitor Based Integrator



Connect the circuit as shown Fig.(4) with the values of resistors  $R_{1A,B}$ ,  $R_{2A,B}$ ,  $R_{3A,B}$  and  $R_{4A,B}$  as calculated in design exercise and answer the following:

- ▶ Vary the input signal frequency from 1Hz to 10 kHz and note the Magnitude and Phase of the output.
- ▶ What is the measured DC gain of the circuit?
- ▶ How much is the measured 3-dB frequency of the filter?
- ▶ Refer to the block diagram of the IC in the datasheet, and comment on the functionality of the circuit.
- ▶ Draw the simplified circuit for the low pass configuration? How can you explain that the circuit is a 4<sup>th</sup> order circuit?
- ▶ Refer to the datasheet and answer what all types of filters can be implemented using IC LMF100CCN?





Objective  
An RC Integrator  
Switched Capacitor based Integrator  
**4<sup>th</sup> Order Butterworth Switched Cap Low Pass Filter**  
4<sup>th</sup> Order Butterworth RC Low Pass filter

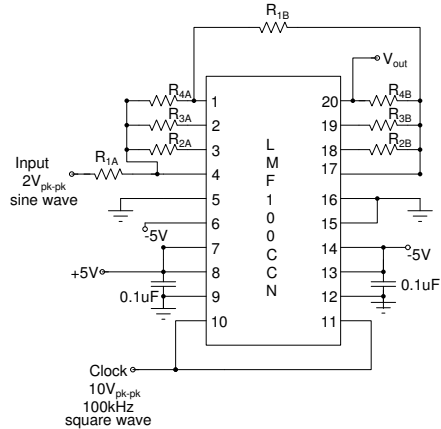


Figure 4: 4<sup>th</sup> order Butterworth switched capacitor Low pass filter



Connect the circuit as shown Fig.(5) and answer the following:

- ▶ Vary the input signal frequency from 1Hz to 10 kHz and note the Magnitude and Phase of the output.
- ▶ What is the measured DC gain of the circuit?
- ▶ How much is the measured 3-dB frequency of the filter?
- ▶ Based on the circuit diagram explain how does the circuit implement a 4<sup>th</sup> order filter?
- ▶ Plot the magnitude of the RC filter and the Switched-Capacitor filter overlaid in the same plot.
- ▶ Plot the phase of the RC filter and the Switched-Capacitor filter overlaid in the same plot.
- ▶ What are the roll-off (in dB/dec) and phase after the filter corner frequency? Explain your observation.



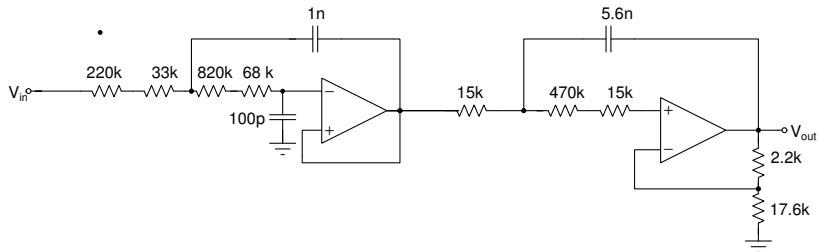


Figure 5: 4<sup>th</sup> order Butterworth RC low pass filter

