

## Review :

1) V.S.I with device conduction period =  $180^\circ$   
is known as "square wave inverter"

⇒ 6 step/cycle in line current

6 step/cycle in phase voltage

load is Y connected



$$V_{ab} = \frac{2\sqrt{3}}{\pi} V_{dc} \left\{ \sin \omega t - \frac{1}{5} \sin 5\omega t - \frac{1}{7} \sin 7\omega t - \dots \right\}$$
$$= (6N \pm 1) \text{ harmonics}$$

$$V_{AN} = \frac{2}{\pi} V_{dc} \left[ \sin \omega t + \frac{1}{5} \sin 5\omega t + \frac{1}{7} \sin 7\omega t \right]$$

$V_{AO}$ ,  $V_{BO}$ ,  $V_{CO}$  have triple harmonics

○ Isolated neutral, all triple harmonics = 0

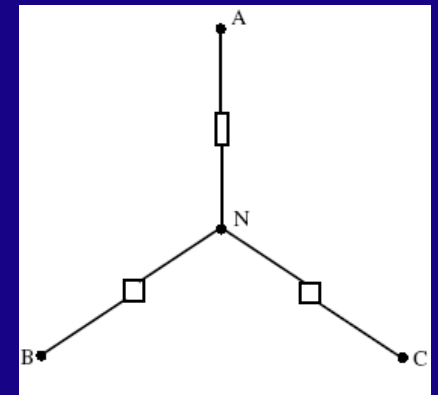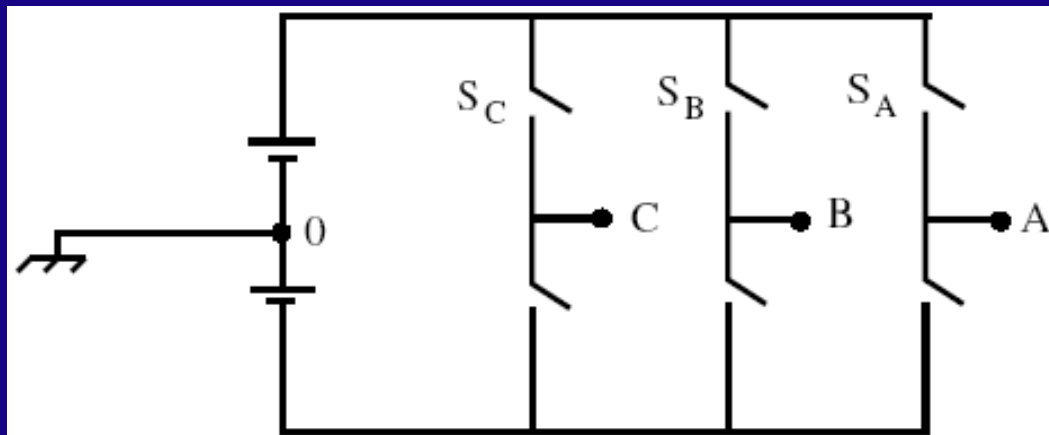$\therefore V_{N0} \rightarrow$  Will have triplen harmonics



- ⇒ Frequency of the Fundamental itself is changing
- ⇒ Frequency of the Pre-dominant Harmonic will also change
- ⇒ Difficult to design a filter
- ⇒ Frequency of the fundamental can be varied by varying the duration of half a cycle

**How to vary the magnitude?**

Magnitude of phase voltage &  
line voltage  $\propto 'V_{dc}'$

In V.V.V.F. sources, magnitude  
of 'V' should vary 'F'

⇒ Vary input 'V'



⇒ In DC to AC converter

there is a AC to DC converter

→  $V_{dc} \propto \cos\alpha$

→ As to  $\downarrow V_{dc} \propto \uparrow$  towards  $90^\circ$

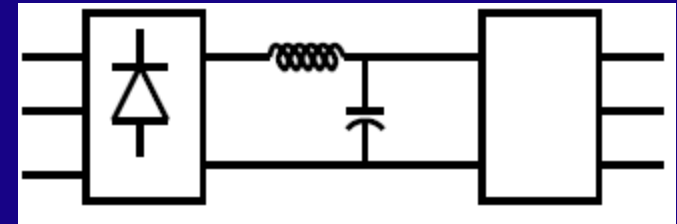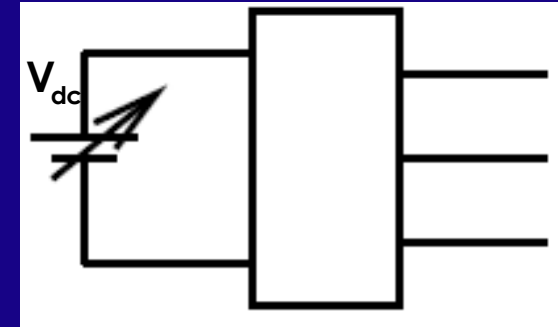→ P.F.  $\downarrow$  also  $\phi_1 \uparrow$



$\Rightarrow \phi_1$  is maximum for  $\alpha=0 \Rightarrow$  uncontrolled rectification

$\Rightarrow$  Source line I has  $(6N \pm 1)$  harmonics

$\Rightarrow$  'F' of fundamental=50Hz

$\Rightarrow$  Requires filter at the input

---

Now  $V_{out} \propto V_{dc}$  if device is ON for  $180^\circ$

$\Rightarrow$  Instead keep  $V_{dc}$  constant

(Corresponding to  $\alpha=0 \Rightarrow$  diode bridge)

& control conduction period of each device

⇒ Use P.W.M

1) Switching frequency  $F_s$  is a function of load.  
(as Power Rating  $\uparrow$ ,  $F_s \downarrow$ )

2) Distortion in the current waveform  $\uparrow$  as  $F_s \downarrow$ .

⇒ PWM strategy must aim at  $\downarrow$  this distortion.

⇒ It can be shown that it is leakage reactance that limits the current due to harmonic voltage.



⇒ As the 'F' of harmonic 'V'  $\uparrow$ ,  $|x| \uparrow$   
&  $\therefore I \downarrow$ .

⇒ Harmonic I produces torque pulsations  
in addition to  $I^2R$  loss.

⇒ Q 'F' of harmonic I is high, speed  
pulsations ; 0

How to choose the no. of pulses/cycle?

Sub-harmonics = 0 if pulse number is an integer.

PWM waveform should have  $\frac{1}{2}$  wave

symmetry (no even harmonics)

∴ Pulse number is an odd integer



**3- $\phi$  symmetry must also be attained.**

**(Only then will every component be balanced)**

**$\Rightarrow$  In addition,  $\frac{1}{4}$  wave symmetry results  
in low distortion.**

**In sinusoidal PWM technique,**

**$F_c \Rightarrow$  Frequency of the carrier wave**

**$F_s = F_c \rightarrow$  multiple of frequency of  $F_{\text{Sine}}$   
for synchronization.**

**$\Rightarrow$  Odd multiples of  $F_c$  for  $\frac{1}{2}$  wave symmetry.**

⇒ Multiples of 3 for 3- $\phi$  symmetry.

∴  $\frac{F_c}{F_{\text{Sine}}}$  = should be ODD multiples of 3

for synchronization,  $\frac{1}{2}$  wave symmetry  
& 3- $\phi$  symmetry.


## 1) Sinusoidal PWM Technique:

3 sinusoids, displaced by  $120^\circ$ .

$$V_{an} = V_m \sin \omega_1 t,$$

$$V_{bn} = V_m \sin(\omega_1 t - 120^\circ) \text{ \&}$$
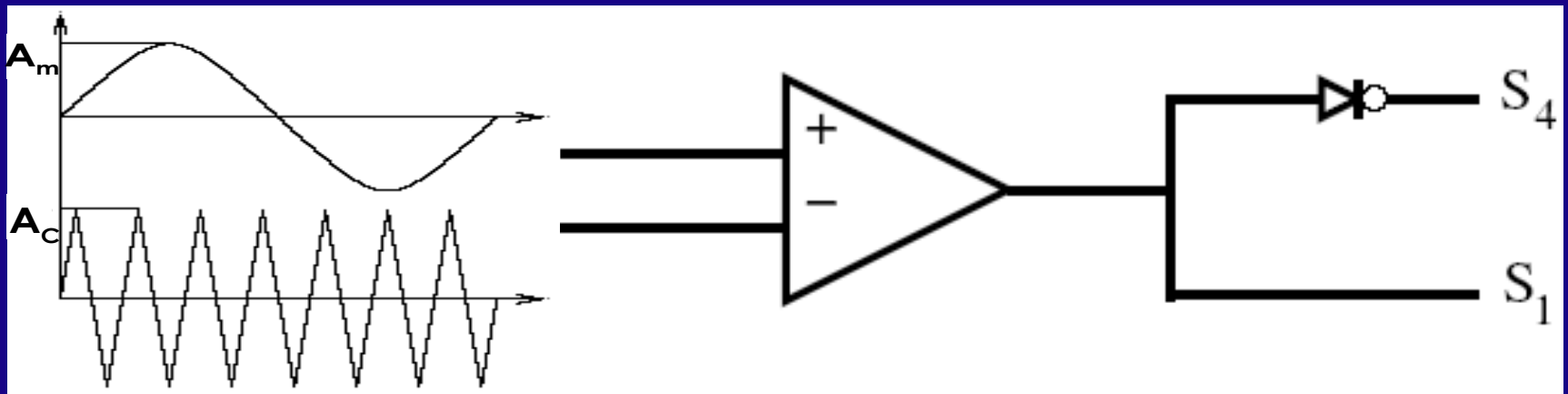
$$V_{cn} = V_m \sin(\omega_1 t + 120^\circ)$$




Both  $A_M$  and  $F$  of sine wave  
(modulating wave) are varying.

$F$  of sine wave =  $F$  of fundamental  
component o/p  $V$

$A_C$  &  $F_C \rightarrow$  constant

$$V_0 \propto m = \frac{A_M}{A_C}$$

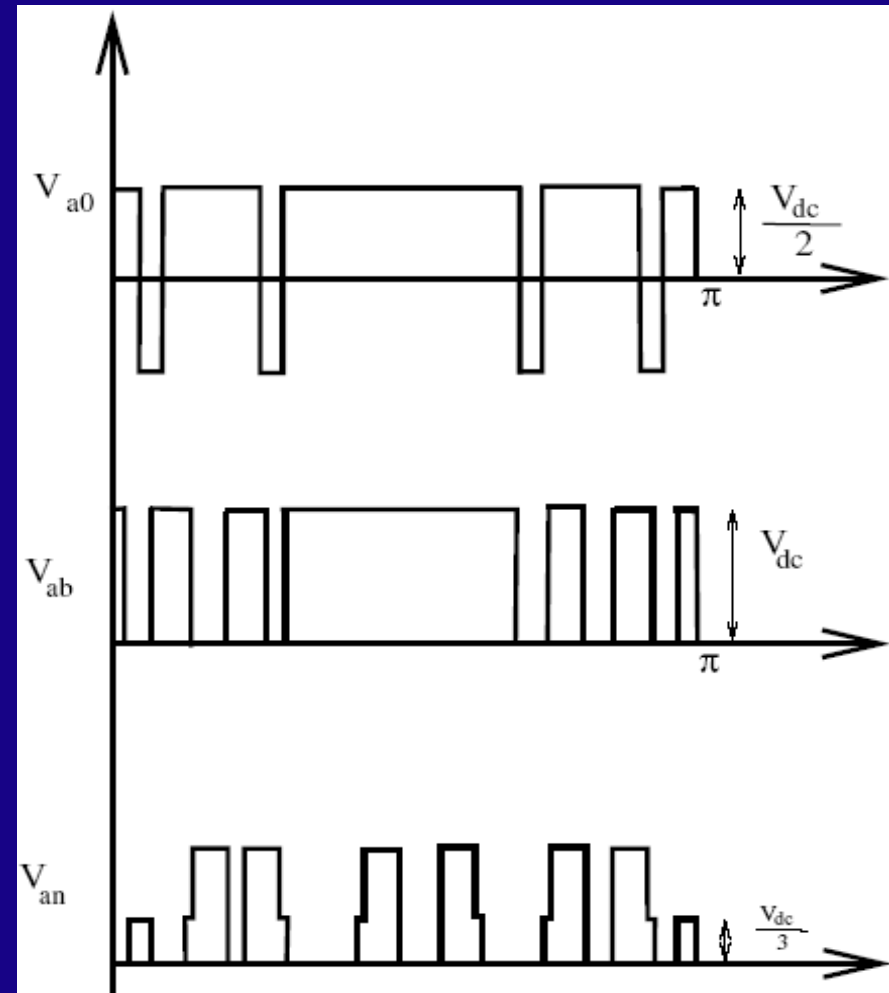All phase voltages are identical & out of phase by  $120^\circ$   
(no even harmonics)




Peak of fundamental component of

$$V_{a0} = \frac{V_{dc}}{2} * m$$
$$= \frac{V_{dc}}{2} \text{ when } m=1$$

Peak of fundamental for 180° conduction
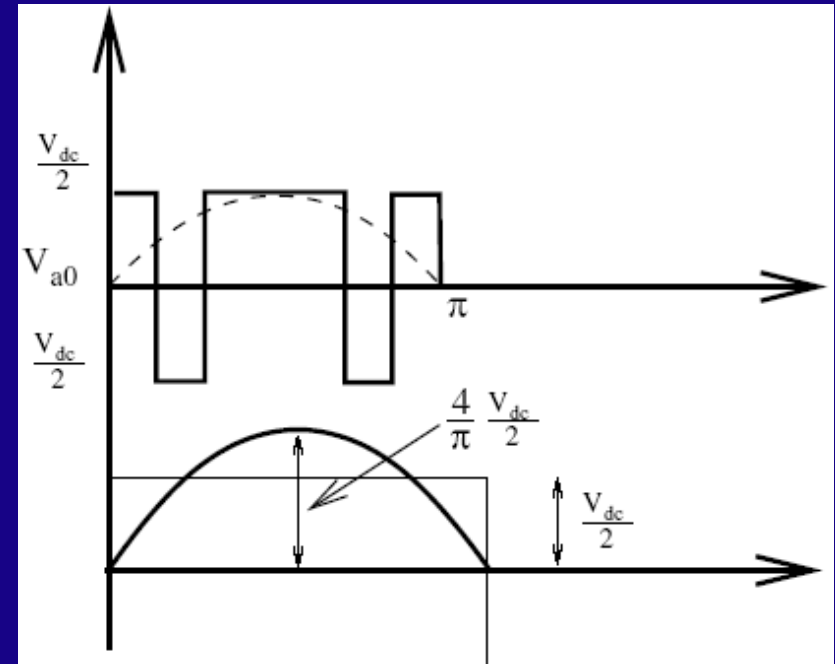
$$= \frac{4}{\pi} * \frac{V_{dc}}{2} = 1.27 \frac{V_{dc}}{2}$$





$$\therefore V_{ab(\text{PWM})} = \sqrt{3} \frac{V_{dc}}{2}$$

$$V_{ab1(\text{square})} = \frac{2\sqrt{3}}{\pi} V_{dc}$$

**Magnitude of  $n^{\text{th}}$  harmonic for  
fundamental frequency  $> F_{\text{rated}}$**

$$= \frac{1}{n} * \frac{2\sqrt{3}}{\pi} V_{dc}$$

⇒ Frequency spectrum :

$$\text{Let } F_N = \frac{F_C}{F_{\text{sine}}}$$

$$\therefore n = j F_N \pm k$$

where  $j = 1, 3, 5 \dots$  for  $k = 2, 4, 6 \dots$  and  
 $= 2, 4, 6 \dots$  for  $k = 1, 5, 7 \dots$

such that 'n' is not a multiple of 3

If  $F_N = 45$

'F' of harmonic =  $45 F_{\text{sine}} \pm 2 F_{\text{sine}}$

$45 F_{\text{sine}} \pm 4 F_{\text{sine}}$


...

---

$90 F_{\text{sine}} \pm F_{\text{sine}}$



$90 F_{\text{sine}} \pm 5 F_{\text{sine}}$

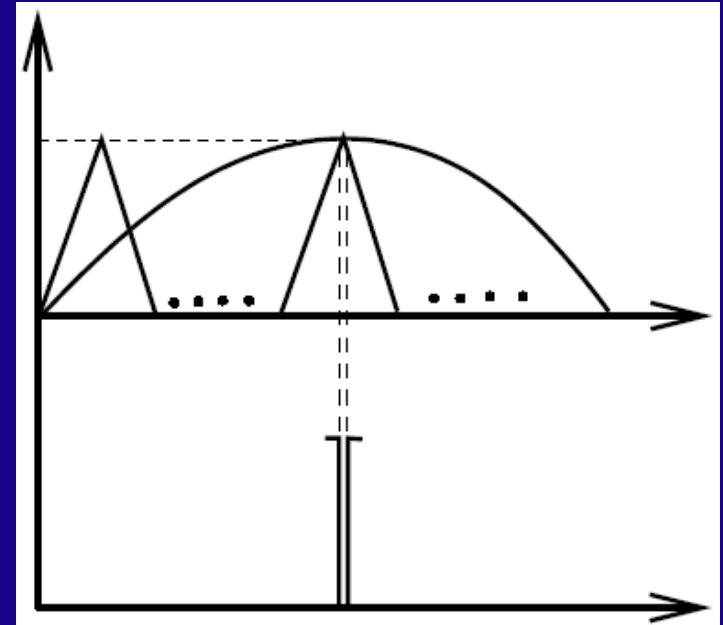As  $m \rightarrow 1$ , narrow pulses near the center



⇒ To complete switching operation of the devices, minimum notch and pulse width must be maintained.

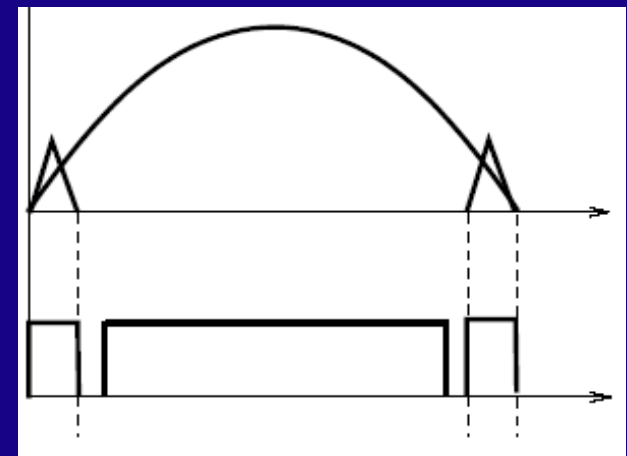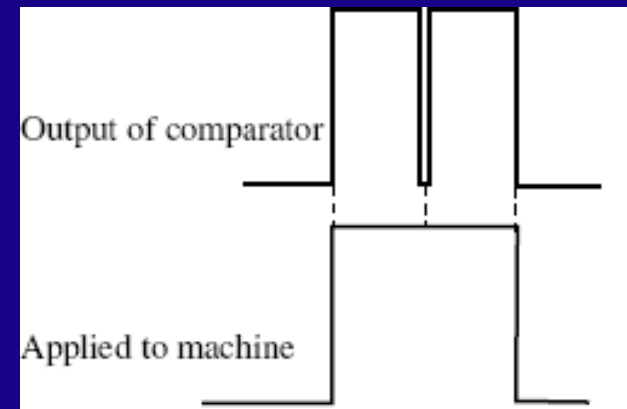- ⇒ These narrow pulses may be blocked.
- ⇒ Affects the machine performance
- ⇒ As  $m \uparrow$ , operation  $\Rightarrow$  6 step operation
- ⇒ harmonics will re-appear  
 $5^{\text{th}}$  &  $7^{\text{th}}$
- ⇒ This happens at  $F > 50$  Hz
- ⇒ Frequency of  $F_5 > 250$



- ⇒ Possible to design a filter or  
get filtered by machine leakage 'L'
- ⇒ 'F' of predominant harmonic till  
rated  $F ; F_c$
- ⇒ 'F' of predominant harmonic above the  
rated  $F = 5F_1$
- ⇒ May not have a choice !



- ⇒ Peak of fundamental = 78.55% of the peak of square wave ( $1/1.27$ )
- ⇒ Using sinusoidal P.W.M
  - Frequency of predominant harmonic  $\uparrow$
  - Distortion in I  $\downarrow$
  - Utilization of DC link voltage  $\downarrow$
  - $\Delta$  wave intersects only near the zero crossings as  $m \uparrow$  above 1

Is it possible to change the shape of the modulating waveform without  $\uparrow$  harmonic content &  $\uparrow$  DC link utilization?

$\Rightarrow$  Add 3<sup>rd</sup> harmonic component to the sinusoidal modulating wave.

$\Rightarrow$  Cannot appear in line-line voltage waveform

