


## FULL WAVE RECTIFICATION

IN HALF WAVE :


- APPLIED 'V' TO THE LOAD IS '0' OR '-VE' BEYOND  $\pi$
- RIPPLE IN THE OUTPUT 'V' INCREASES
- USE FULL WAVE RECTIFICATION

## USING CENTRE TAPPED TRANSFORMER

POPULAR IN POWER SUPPLIES

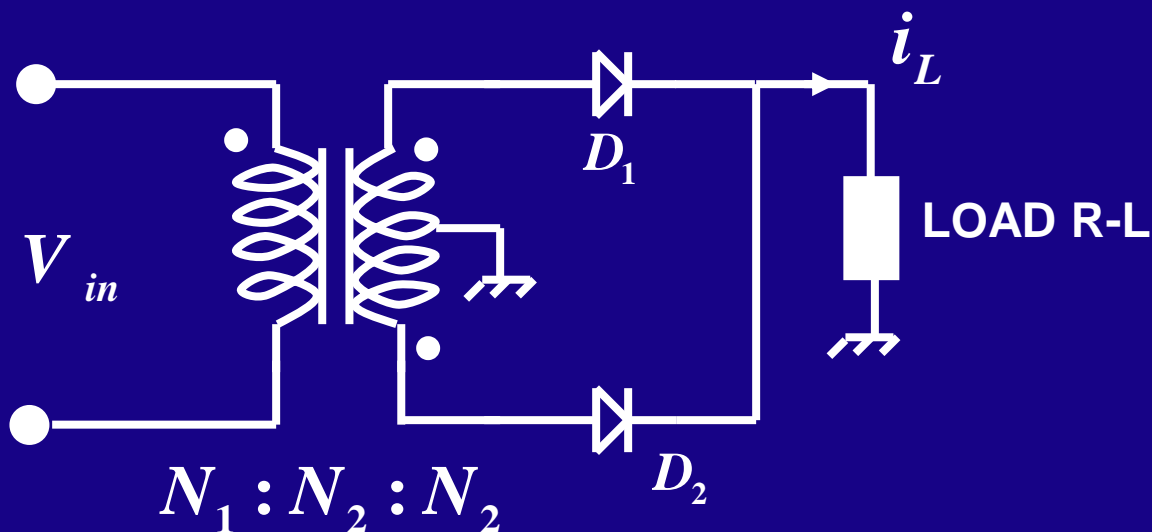

In the +ve HALF  $D_1$  Conducts

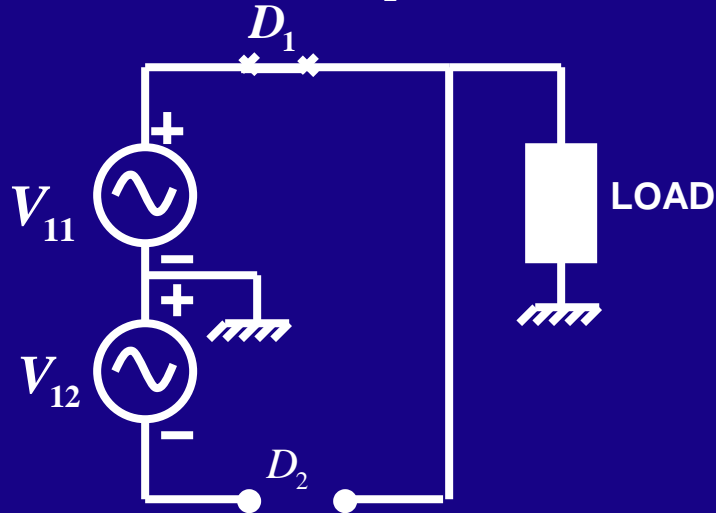


$$V_{D2} = -(V_{11} + V_{12})$$


$$V_{D2(\max)} = -2V_{11(\max)}$$

$$V_{11} = \left( \frac{N_2}{N_1} \right) V_{in}$$

AV. O / P  $V = \frac{2V_m}{\pi}$

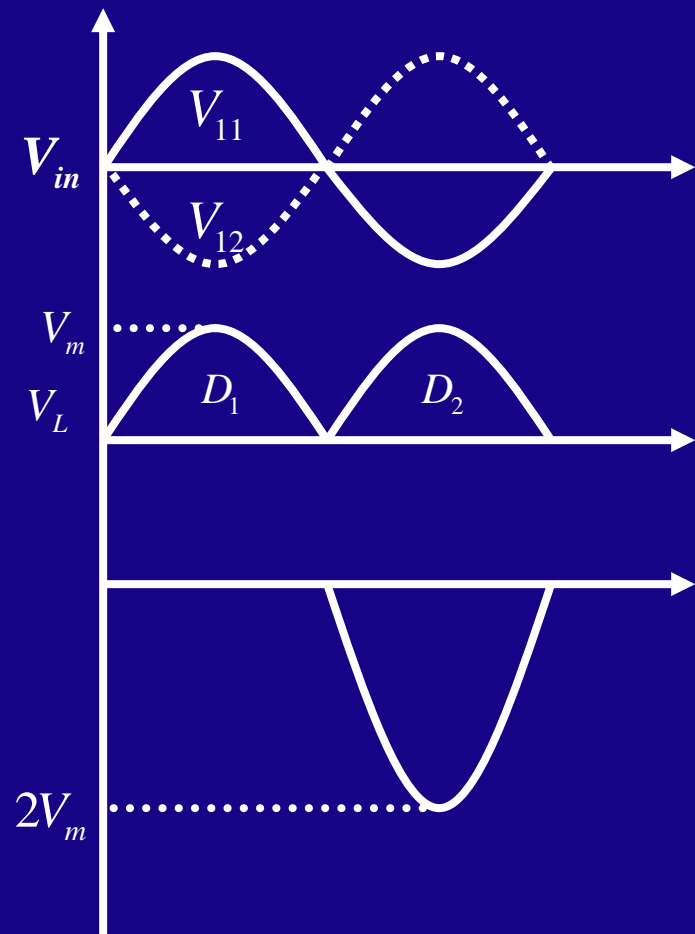
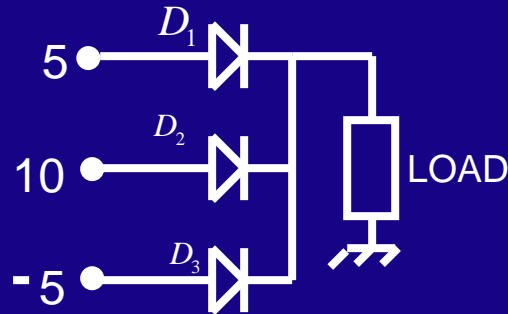
## CONSIDER: A COMMON CATHOD CONFIGURATION




ONLY  $D_2$  CAN CONDUCT



DIODE WHOSE ANODE POTENTIAL IS HIGHEST WILL CONDUCT

## A COMMON ANODE CONFIGURATION

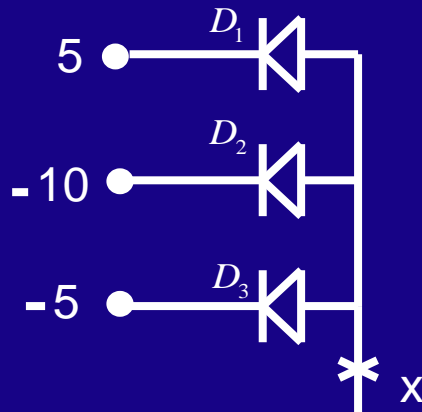

POTENTIAL OF x CAN BE -10V




ONLY  $D_2$  CAN CONDUCT



DIODE WHOSE CATHOD POTENTIAL IS MINIMUM WILL CONDUCT

## SINGLE PHASE BRIDGE

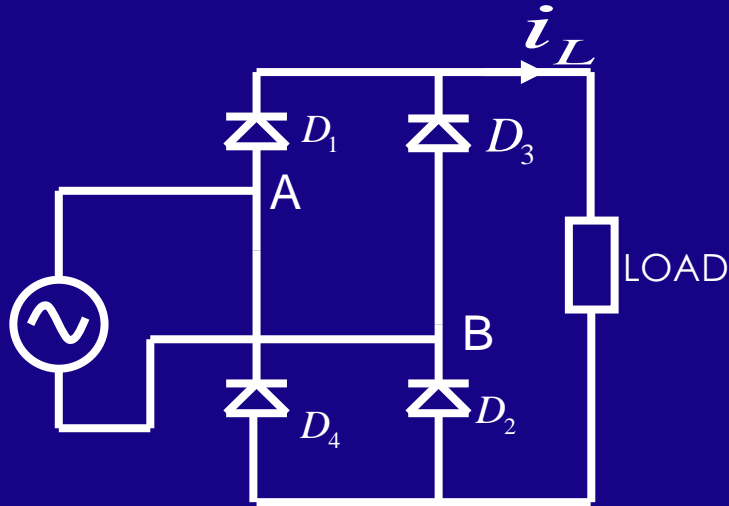


$D_1 D_3$  → COMMON CATHOD CONFIGURATION  
 $D_2 D_4$  → COMMON ANODE CONFIGURATION

IN +VE HALF

POT. OF A > POT. B

$D_1$  WILL CONDUCT IN THE UPPER HALF

$D_2$  WILL CONDUCT IN THE LOWER HALF

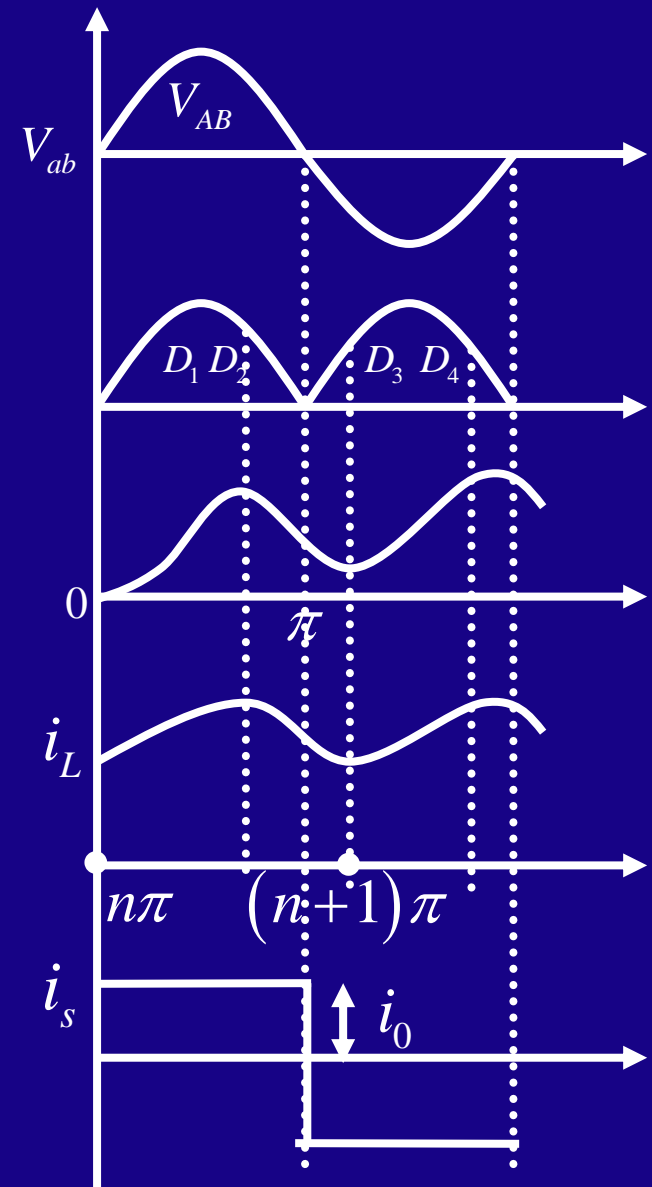


## EQUIVALENT CIRCUIT

$$V_m \sin \omega t = Ri + L \frac{di}{dt}$$

$$i = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) + \sin \phi e^{-t/\tau} \right]$$

$$i = i_{\max} \quad \pi/2 < \omega t < \pi$$
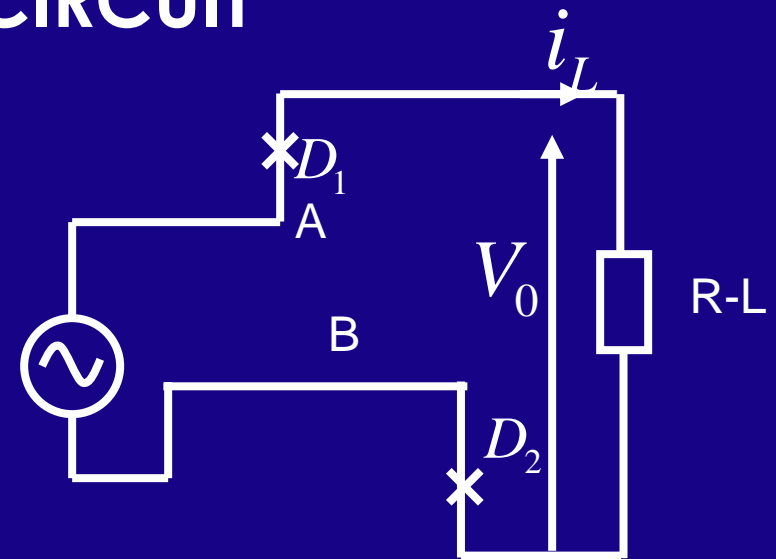
$$v_i = Ri_{\max} \quad \because L \frac{di_{\max}}{dt} = 0$$



At  $\omega t = \pi^+$ ,  $D_3$  &  $D_4$  starts conducting.

+ve  $V$  is applied to the load.

At steady state if load is highly  $L$   $i_0$  becomes almost constant.

Whenever Diode conducts source  $I = \text{Load } I$

⇒ For analysis assume that  $i_L$  is constant & ripple free.

⇒ Source  $I$  is square wave

⇒ Odd function

⇒ Fourier series will have all odd component

Peak of 1<sup>st</sup> or Fundamental component =  $\frac{4I_0}{\pi} = b_1$

Displacement Angle  $\theta_1 \angle_{V_i}^{b_1} = 0$

Displacement Factor =  $\cos \theta_1 = 1$

Input power factor :

$$\text{P.F.} = \frac{\text{Mean i/p power}}{\text{R.M.S. Input VA}}$$



⇒ only fundamental component of i/p  $I$  contributes to mean i/p power.

⇒ other components contribute to heat ( $I^2 R$  loss)

$$P.F. = \frac{V_1 I_1 \cos \theta_1}{V_{rms} I_{rms}}$$

⇒ supply is a pure sinusoid.

$$\Rightarrow V_1 = V_{rms}$$

⇒ Source  $I$  is a square waveform.

⇒ 3<sup>rd</sup>, 5<sup>th</sup>, 7<sup>th</sup> Harmonics

$$I_{rms} = I_0 \quad I_1 = \frac{4I_0}{\sqrt{2\pi}} \quad \cos \theta = 0.9 \text{ lag}$$

⇒ Decides the VA requirement

$$T.H.D. = \frac{\text{Ripple}}{\text{Fundamental}} = \frac{(I_{rms}^2 - I_1^2)^{1/2}}{I_1} \approx 49\%$$

## LOAD IS PURE $L$ : -

In the +ve Half  $L \frac{di}{dt} = V$

$i = i_{\max}$  at  $\omega t = \pi$  ,

At  $\omega t = \pi^+$


+ve  $V$  is again applied to the Load

$i \uparrow$  continuously

$\Rightarrow$  No steady state


$\Rightarrow V$  across  $L = +ve$

$\Rightarrow \frac{di}{dt}$  is +ve

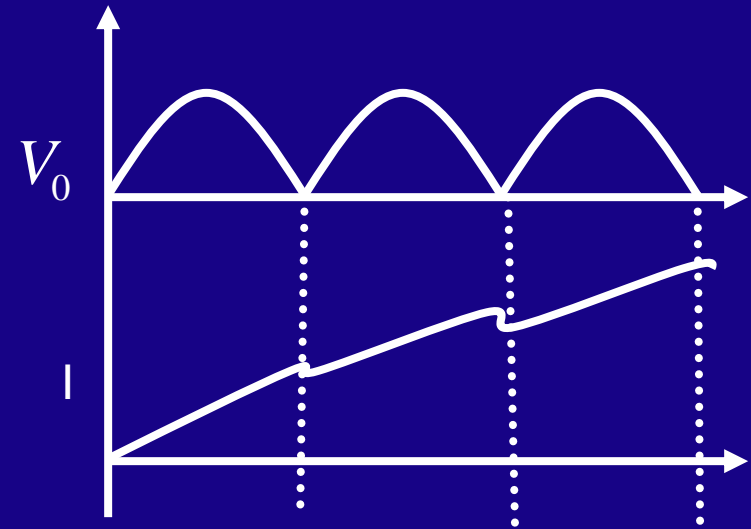




## CONTROLLED RECTIFICATION

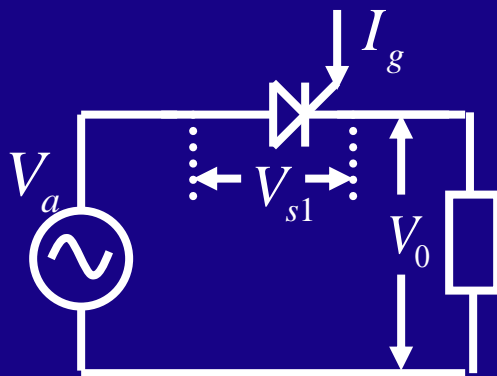

SCR (THYRISTOR) IS USED

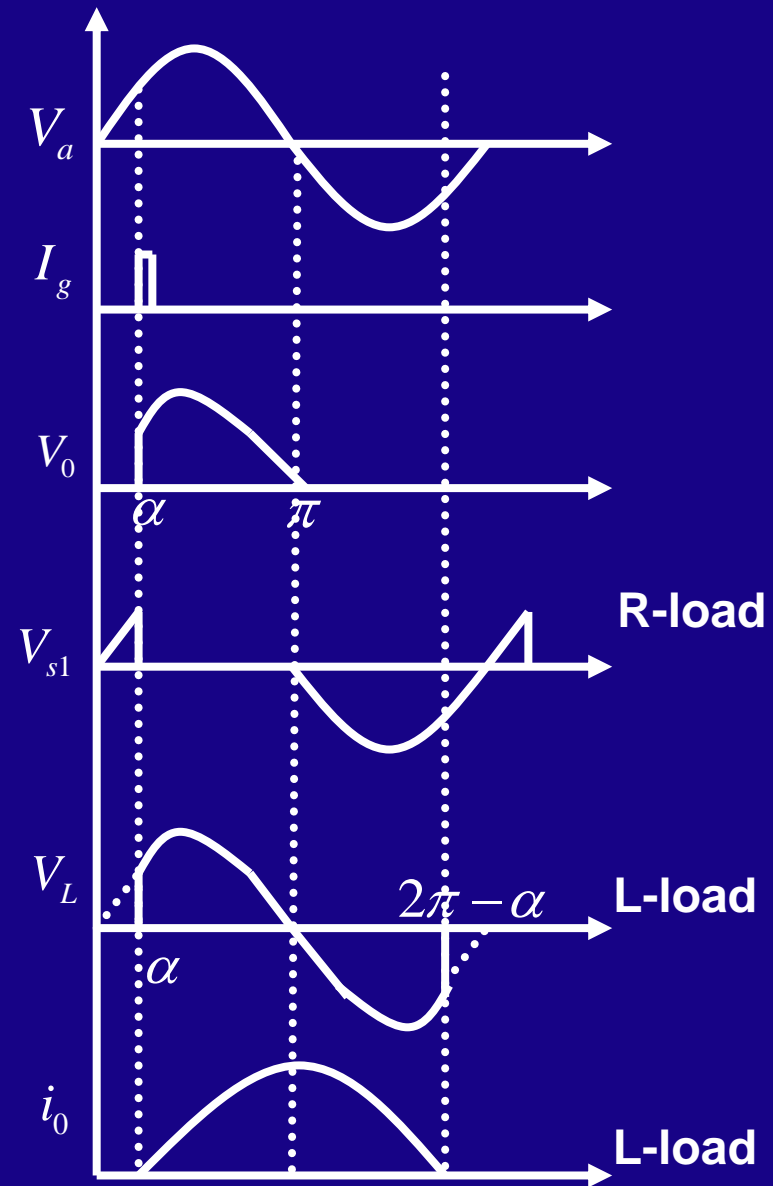- ➔ CAN BE TURNED 'ON' BY APPLYING GATE SIGNAL WHEN IT IS F.B.
- ➔ OPERATION IS ALMOST THE SAME AS THAT OF 'D' CIRCUIT
- ➔ IF LOAD  $I$  IS CONTINUOUS,  $\alpha_{\min} = 0$  & IS INDEPENDENT OF TYPE OF LOAD



## HALF CONTROLLED BRIDGE

ASSUMING:  $\dot{i}_l$  CONST. AND RIPPLE FREE

POSSIBLE IF 'L' IS HIGH


ASSUME 'L' ON SOURCE SIDE IS = 0

SCR TURNS OFF IMMEDIATELY WHEN


-VE VOLTAGE IS APPLIED ACROSS IT



AT  $\omega T = \alpha$   $T_1$  IS TURNED ON

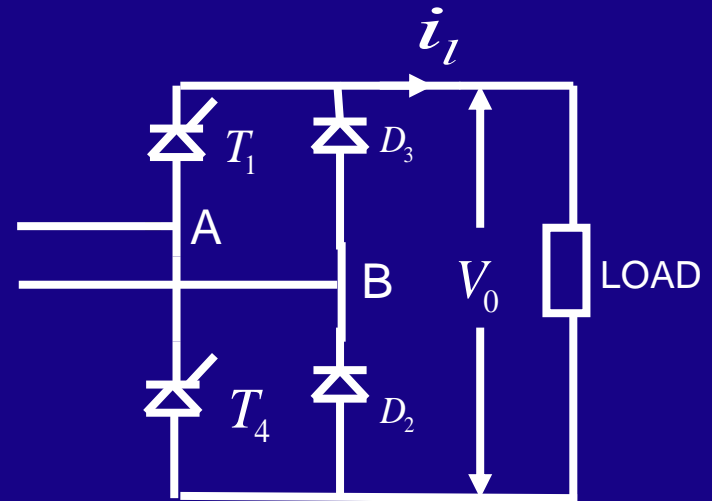AT  $\omega T = \pi + \alpha$   $T_4$  IS TURNED ON



FROM  $\alpha$  to  $\pi$

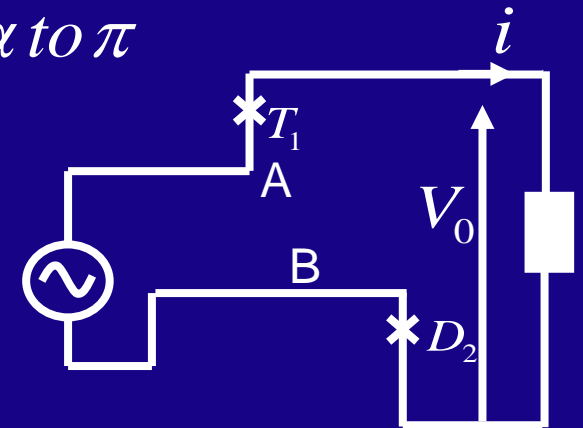

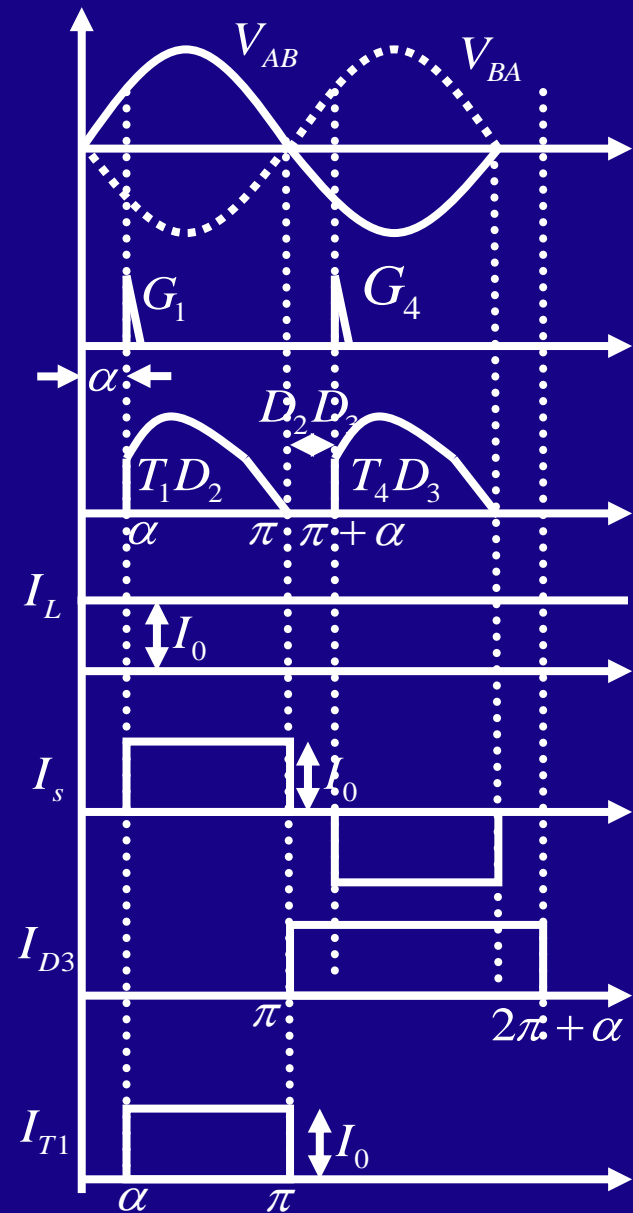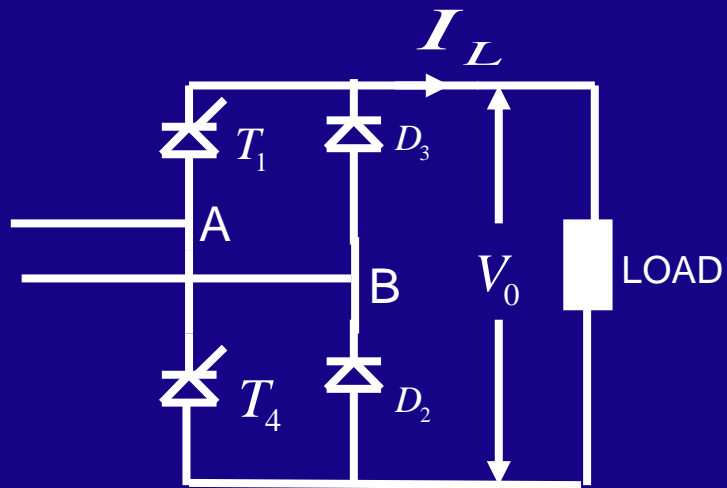

At  $\omega t = \pi^+$

Potential (Pot.) of B > Pot. of A

**Upper half:- Common cathode configuration**

$\Rightarrow$  Diode  $D_3$  starts conducting

$\Rightarrow$  Cathode Pot. of  $T_1$  = Pot. of B

$\Rightarrow$  -ve V across  $T_1$

$\Rightarrow T_1$  Turns off

$\Rightarrow$  Line Commutation



## Lower Arm:

$\Rightarrow T_4$  is F.B.

$\Rightarrow$  Gate signal is applied only at  $\pi + \alpha$

$\Rightarrow$  From  $\pi$  to  $\pi + \alpha$   $T_4$  is O.C.

$\Rightarrow D_2$  continues to conduct

$\Rightarrow$  Load is free wheeling through  $D_2 - D_3$


$V_0 = 0$  Source  $I = 0$

$\Rightarrow$  Continues till  $\pi + \alpha$  while  $T_4$  is Triggered

$\Rightarrow \because$  It is F.B. & gate signal present

$T_4$  starts conducting

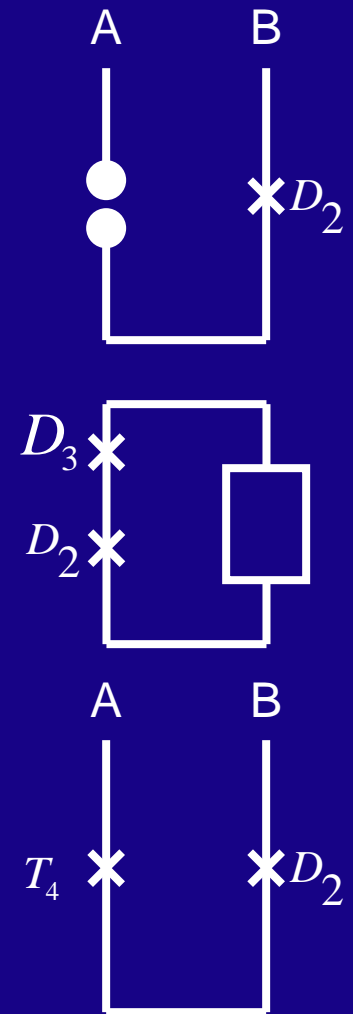$\Rightarrow$  Applied -ve 'V' across  $D_2 \Rightarrow D_2$  turns off



⇒ From  $\pi + \alpha$  to  $2\pi$

⇒ Operation is similar to that of  $\alpha$  to  $\pi$

Only direction of  $I_s$  has reversed

⇒ From  $2\pi$  to  $2\pi + \alpha$

⇒ Operation is similar to that of  $\pi$  to  $\pi + \alpha$


⇒  $T_4$  &  $D_2$  form common anode config.

⇒  $D_2$  starts conducting

⇒ Applies -ve 'V' across  $T_4$

$T_4$  turns off

⇒ Upper half :  $T_1$  is not triggered

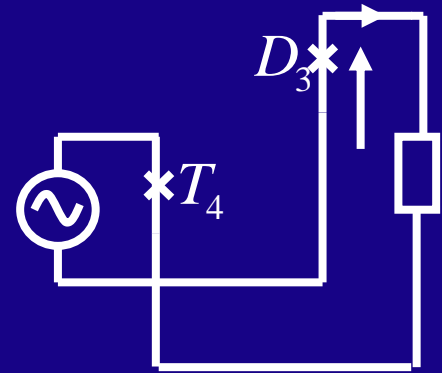



$$V_{av} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$\Rightarrow V_{av}$  is always +ve

$\Rightarrow$  Load  $I$  is always unidirectional


$\Rightarrow$  Single Quadrant Converter  $1 = \frac{2V_m}{\pi}$

$$\text{Displacement Factor} = \cos \left( -\frac{\alpha}{2} \right)$$

Lagging : RMS value of the fundamental component source  $I_s$

$$I_s = \frac{2\sqrt{2}}{\pi} I_a \cos \left( \frac{\alpha}{2} \right)$$
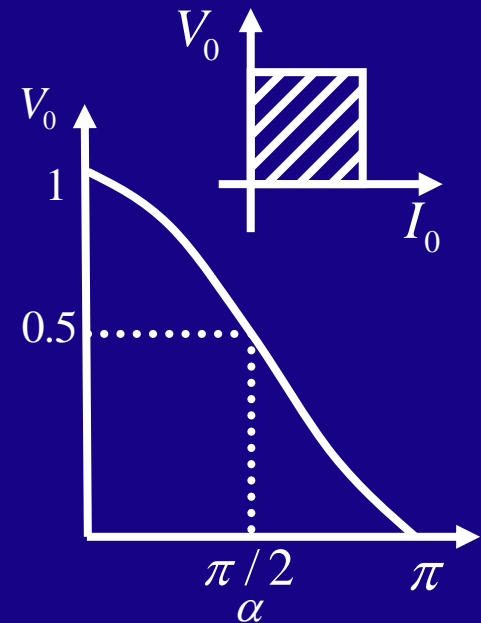
$$P.F = \frac{\sqrt{2}(1 - \cos \alpha)}{[\pi(\pi - \alpha)]^{1/2}}$$



Observation:

$\Rightarrow$  If  $\alpha \neq 0$   $\gamma$  for  $T \neq \gamma$  for  $D$

$\Rightarrow$  Av. Current rating of  $T <$  Av. Current rating of  $D$

**Case II:** Operation  $\alpha$  to  $\pi$  is same

$$V_0 = V_{in}$$

From  $\pi$  to  $\pi + \alpha$


Lower arm common Anode config.

$D_4$  starts conducting

In Upper half  $T_3$  F.B.

$\Rightarrow$  No triggering pulse ( Gets only at  $\pi + \alpha$  )

Till then it can not conduct

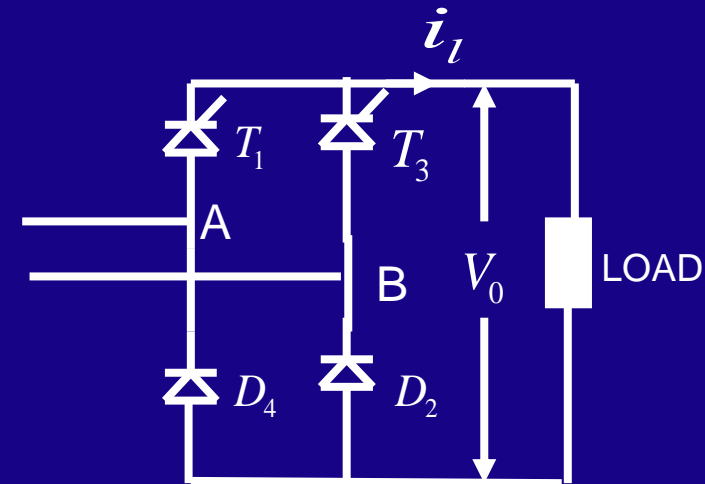

$\Rightarrow I_L$  freewheels through  $T_1$  &  $D_4$

$$I_s = 0, V_0 = 0$$


$\Rightarrow$  At  $\pi + \alpha$ :  $T_3$  is triggered

$\Rightarrow$  Starts conducting

$\Rightarrow$  Applies -ve 'V' across  $T_1$

$\Rightarrow$  Turns off

$$V_0 = V_{in}$$

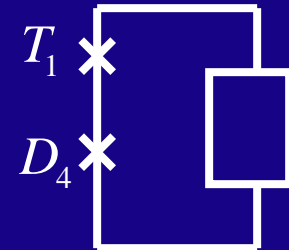

From  $2\pi$  to  $2\pi + \alpha$  (or 0 to  $\alpha$ )

Pot. of A > Pot. of B

$\Rightarrow D_2$  starts conducting  
(C.A. config.)



$\Rightarrow D_4$  turns off

$\Rightarrow T_1$  starts conducting  
only at  $2\pi + \alpha$  (or  $\alpha$ )


$\gamma$  for  $T = \gamma$  for  $D$

Av.  $I$  of  $T$  = Av.  $I$  of  $D$

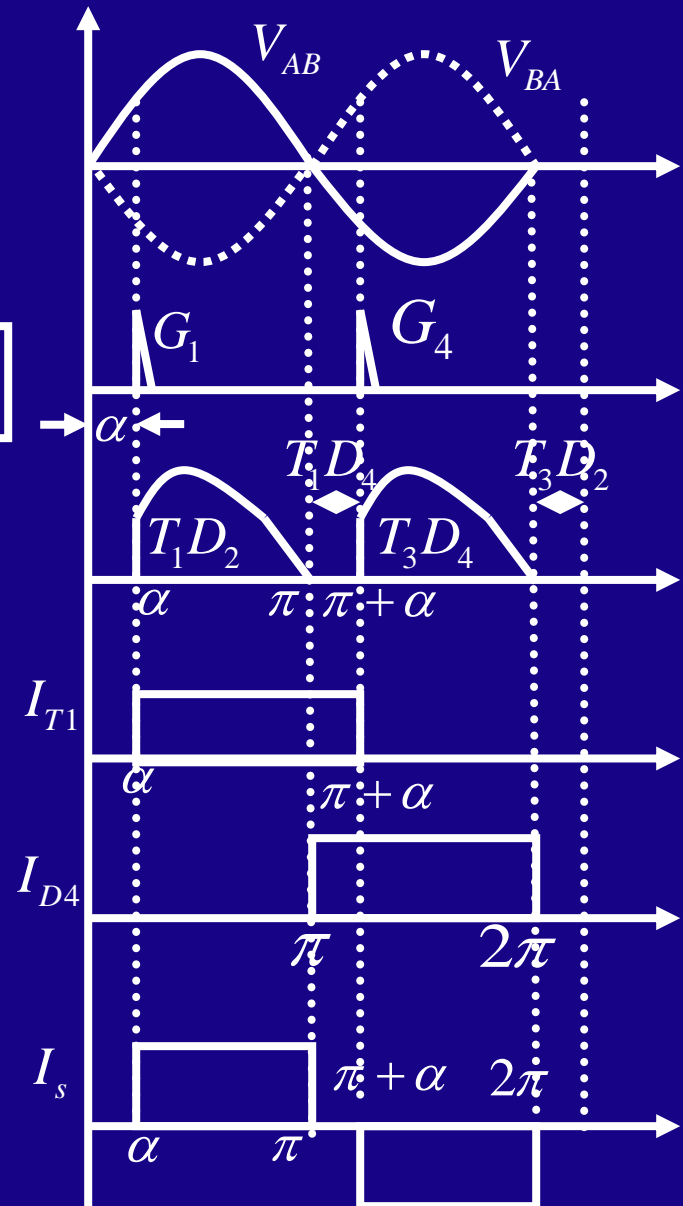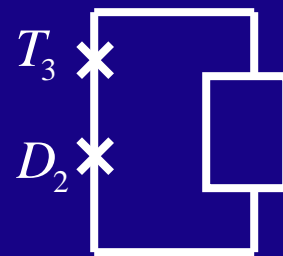
$$V_0 = \frac{V_m}{\pi} (1 + \cos \alpha)$$



## CASE I

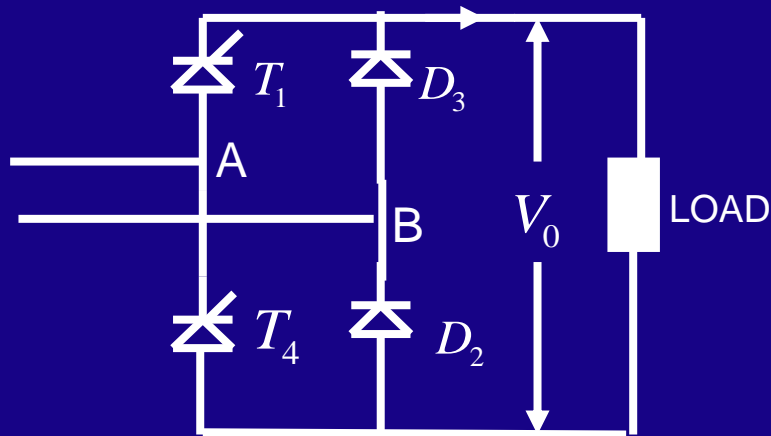

## CASE II

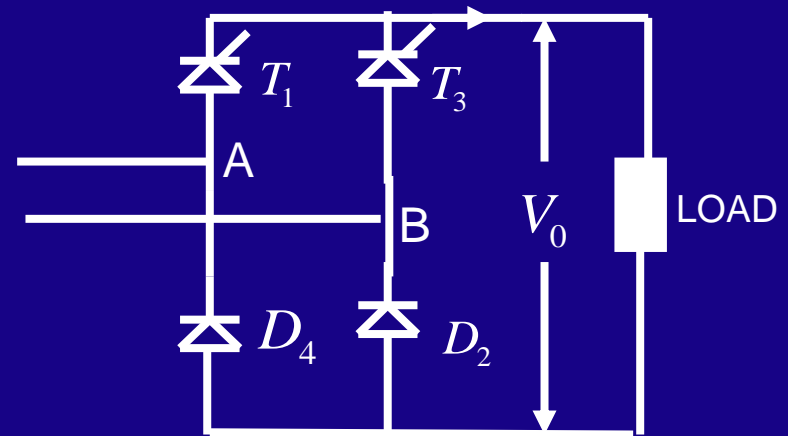

➡ DEVICE SHOULD ATTAIN THE FORWARD BLOCKING CAPABILITY BEFORE IT IS F.B.

- OTHERWISE IT WILL NOT TURN OFF

➡ COMMUTATION FAILURE

### IN CASE I

AT  $\omega T = \pi^+$ ,  $T_1$  IS TURNED OFF

BECAUSE DIODE STARTS CONDUCTING



## → CASE II

→  $T_1$  CONTINUES TO CONDUCT TILL  $T_3$  IS TRIGGERED

$T_3$  CAN BE TURNED OFF ONLY BY TURNING ON  $T_1$

→ IF  $\alpha \rightarrow \pi$

→ BEFORE  $\omega t = \pi^+ \rightarrow T_3$  GETS FORWARD BAISED

→  $T_3$  SHOULD ATTAIN ITS F.B.  
CAPABILITY BEFORE  $\omega t = \pi^+$

→ REQUIRES FINITE TIME

→ IF AVAILABLE TIME < THE ABOVE TIME

$T_3$  CONTINUOUS TO CONDUCT

→  $\frac{1}{2}$  WAVE EFFECT

