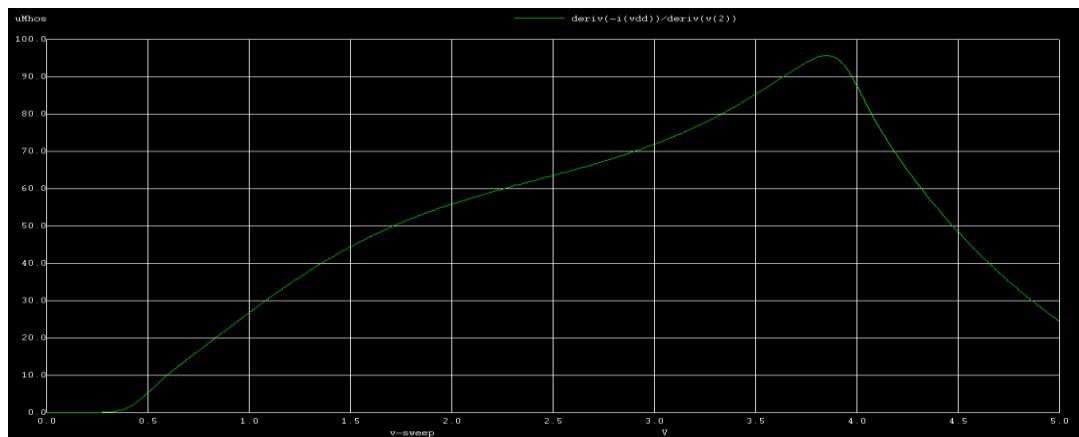


1.

a),b)


```
1 .include NMOS.txt
2 M1 3 2 0 0 CMOSN W=1u
3 R1 2 1 470
4 VDD 3 0 DC 5v
5 VIN 1 0 DC 0v
6 .dc VIN 0 5 0.01
7 .control
8 run
9 plot -i(VDD)
10 plot deriv(-i(VDD))/deriv(v(2))
11 .endc
12 .end
```



The peak transconductance (g_m) for the MOSFET at $V_{DS} = 5$ V was found to be $95.66 \mu\text{S}$ and corresponding V_{GS} was 3.85V .


c)
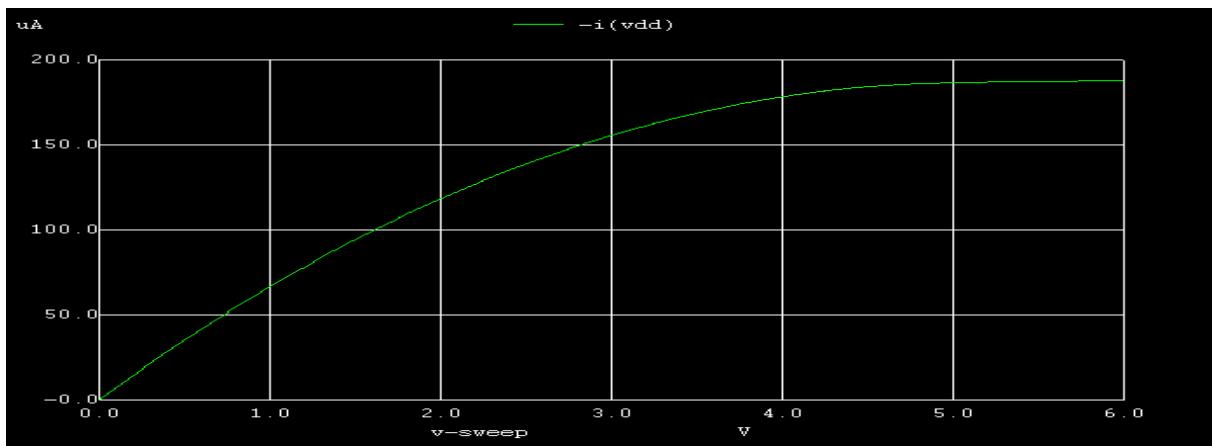
```
1 .include NMOS.txt
2 M1 3 2 0 0 CMOSN W=1u
3 VDD 3 0 DC 0v
4 VGS 2 0 DC 3.85v
5 .dc VDD 0 6 0.01
6 .control
7 run
8 plot -i(VDD)
9 .endc
10 .end
11
12
```




Output impedance is 0.2282 Mohm (reciprocal of slope from saturation region).


d)

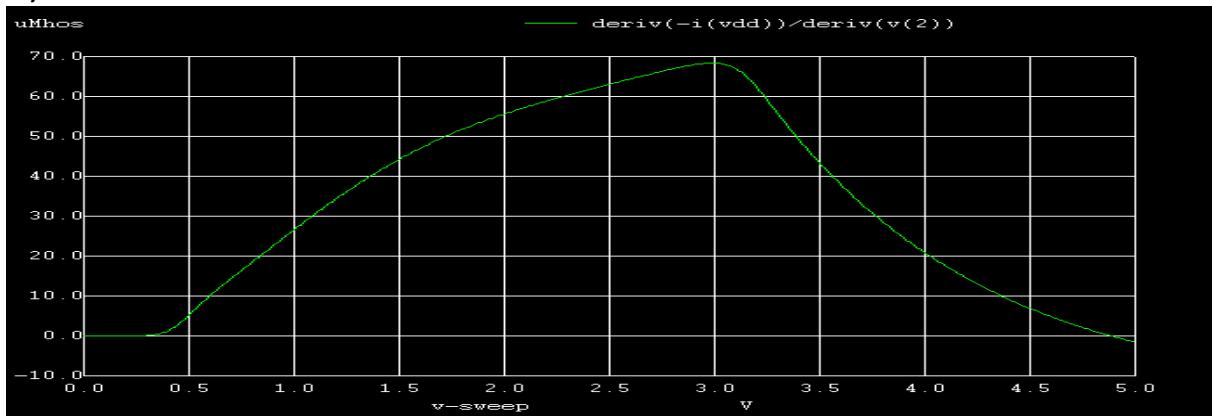

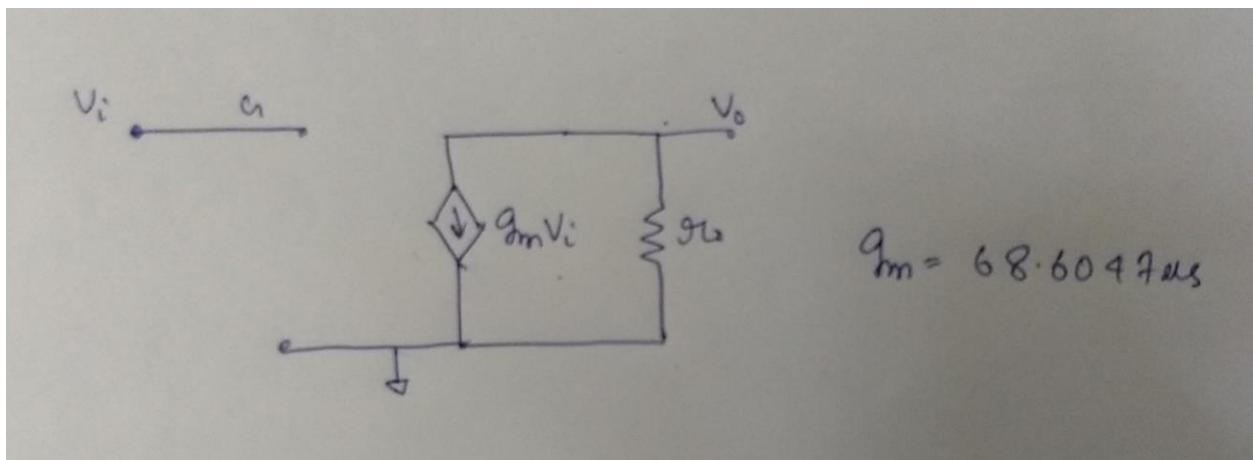Peak transconductance (g_m) for the MOSFET at $V_{DS} = 3$ V is $68.6047 \mu\text{S}$ ($V_{GS}=3\text{V}$)



e)

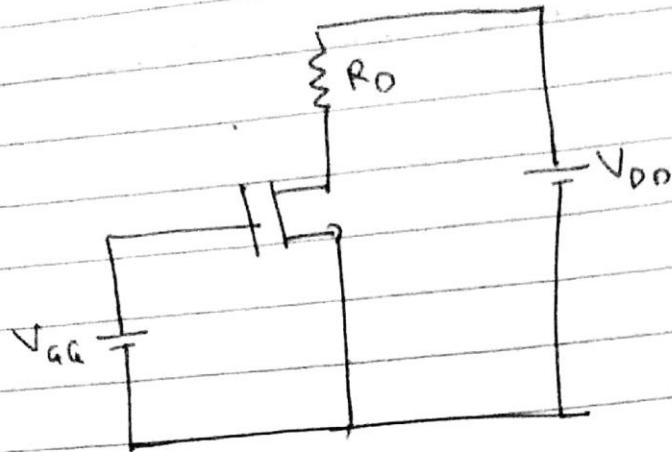

From Spice simulation


$$g_m = 95.66 \text{ } \mu\Omega^{-1}$$

$$r_o = 0.22826 \text{ M}\Omega$$

$$I_D = 0.186 \text{ mA}$$

$$V_{GS} = 3.85 \text{ V}$$

Small signal equivalent ckt

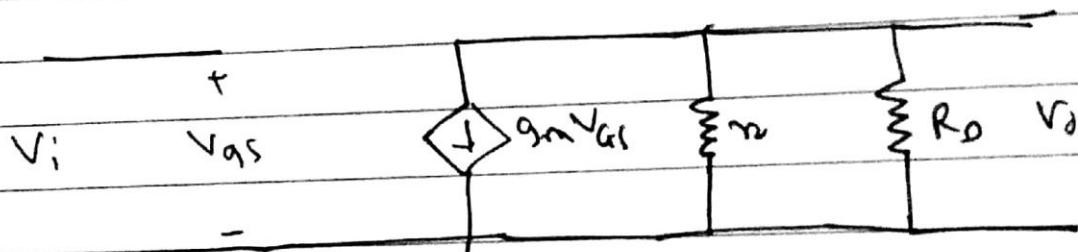

Designed gain = $A_V = 2$

$$g_m (r_o || R_D) = 2$$

$$95.66 \text{ } \mu\Omega^{-1} (r_o || R_D) \text{ M}\Omega = 2$$

$$(r_o || R_D) = 0.021$$

$$r_o R_D = 0.021 r_o + 0.021 R_D$$

$$(r_o - 0.021) R_D = 0.021 r_o$$

$$R_D = \frac{0.021 r_o}{r_o - 0.021}$$

$$R_D = 0.0231 \text{ M}\Omega$$

Output impedance


$$\text{with } R_D = (r_o || R_D) = 0.021 \text{ M}\Omega$$

$$\text{without } R_D = r_o = 0.2282 \text{ M}\Omega$$

$$V_{GS} = V_{DS} = 3.85 \text{ V}$$

$$\begin{aligned} V_{DS} &= V_{DS} + I_D R_D \\ &= 5 + 0.186 \times \text{MAX } 0.0231 \text{ M}\Omega \end{aligned}$$

$$V_{DD} = 5.8 \text{ V}$$

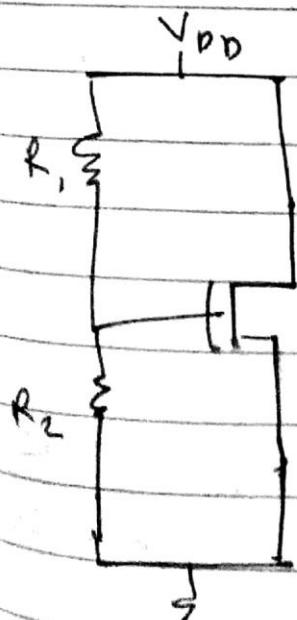


For gain = 2 $V_{DS} = V_{DD} = 5 \text{ V}$

$$V_{GS} = 3.85$$

$$\frac{R_2}{R_1 + R_2} \times \frac{V_{DD}}{V_{GS}} = 3.85$$

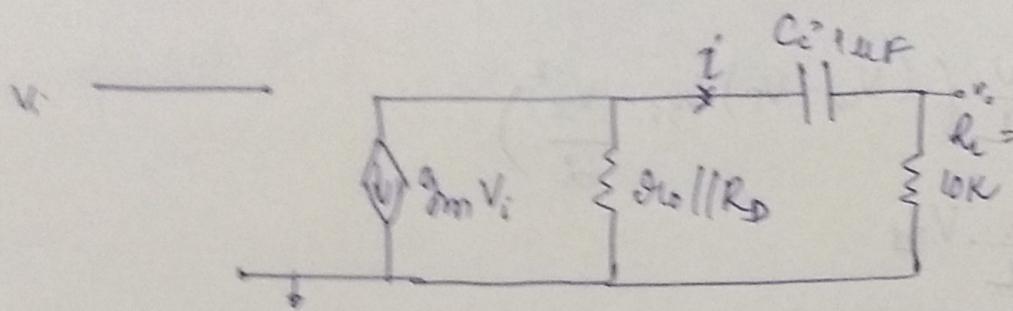Let $R_2 = 10 \text{ k}\Omega$ $R_1 = 2.987 \text{ k}\Omega$



$$g_o || R_D = 0.0231 \text{ M}\Omega \parallel 0.22826 \text{ M}\Omega \\ = 0.020977 \text{ M}\Omega$$

$$i = - g_m V_i \frac{g_o || R_D}{g_o || R_D + \frac{1}{C_C s} + R_L}$$

$$= - g_m V_i \frac{(g_o || R_D) C_L s}{1 + (g_o || R_D + R_L) C_L s}$$

$$V_o = i R_L$$

$$A_V = - \frac{g_m R_L (g_o || R_D) C_L s}{1 + (g_o || R_D + R_L) C_L s}$$

$$= - \frac{95.66 \times 10^{-6} \times 0.020977 \times 10^6 \times 10^{-6} s \times 10K}{1 + (30.977 \times 10^3) 10^{-6} s}$$

$$= - \frac{2.067 \times 10^{-2}}{1 + 0.030977 s}$$

$A_V @ 1 \text{ MHz},$

$$|A_V| = \frac{2.067 \times 10^{-2} \times 2\pi \times 10^6}{\sqrt{1 + (0.030977 \times 10^6 \times 2\pi)^2}}$$

$$\approx \frac{2.067 \times 10^{-2}}{3.0977 \times 10^{-2}}$$

$$\approx 0.667269$$

$A_v @ 1 \text{ mHz}$

$$|A_v| = \frac{2.067 \times 10^{-2} \times 2\pi \times 10^{-3}}{\sqrt{1 + (0.030977 \times 10^{-3} \times 2\pi)^2}}$$
$$\approx 1.2987 \times 10^{-4}$$


Q.No. 2

A

when $V_{BS} \neq 0$ then

Small signal equivalent circuit is given below at current
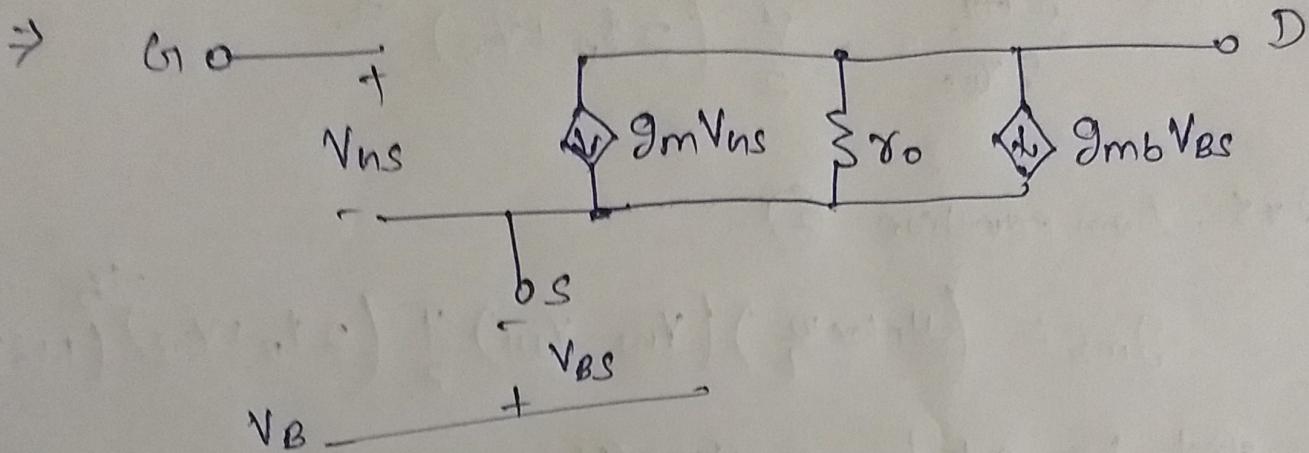
$$I_{DS} = \frac{1}{2} \mu n \lambda \times \frac{W}{L} (V_{DS} - V_{TH})^2 (1 + dV_{BS}) \quad \text{--- (1)}$$



$$\Rightarrow \text{where } r_o = \left(\frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \frac{1}{\frac{1}{2} \mu n \lambda \times \frac{W}{L} (V_{DS} - V_{TH})^2} \parallel$$

$r_o \approx \frac{1}{d I_D}$

and $g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS}=\text{constant}}$

(transconductance)
$$g_m = \mu n \lambda \times \frac{W}{L} (V_{GS} - V_{TH}) (1 + dV_{DS}) \quad \text{(from equation (1))}$$

and $g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \mu n \lambda \times \frac{W}{L} (V_{GS} - V_{TH}) \left(-\frac{\partial V_{TH}}{\partial V_{BS}} \right) (1 + dV_{DS})$

\Rightarrow Also given $V_{TH} = V_{TO} + \gamma \left(\int 2\phi_B + V_{SB} - \int 2\phi_B \right)$ --- (2)

$$\text{then } \frac{\partial V_{TH}}{\partial V_{SB}} = \frac{\gamma}{2} (2\phi_B + V_{SB})^{-\gamma/2}$$

We can write $\frac{\partial V_{TH}}{\partial V_{SB}} = - \frac{\partial V_{TH}}{\partial V_{BS}} \neq$

Hence $\frac{\partial V_{TH}}{\partial V_{BS}} = - \frac{\gamma}{2} (2\phi_B + V_{SB})^{-\gamma/2}$

thus, from equation ②

$$g_{mb} = (\mu n \cos \frac{\omega}{2})(V_{BS} - V_{TH}) \frac{\gamma}{2} (2\phi_B + V_{SB})^{-\gamma/2} (1 + \alpha V_{DS})$$


~~and also from equation ④~~

and from equation of $g_m = \mu n \cos \frac{\omega}{2} (V_{BS} - V_{TH})(1 + \alpha V_{DS})$

Hence

$$g_{mb} = \boxed{g_m \cdot \frac{\gamma}{2 \sqrt{2\phi_B + V_{SB}}}}$$

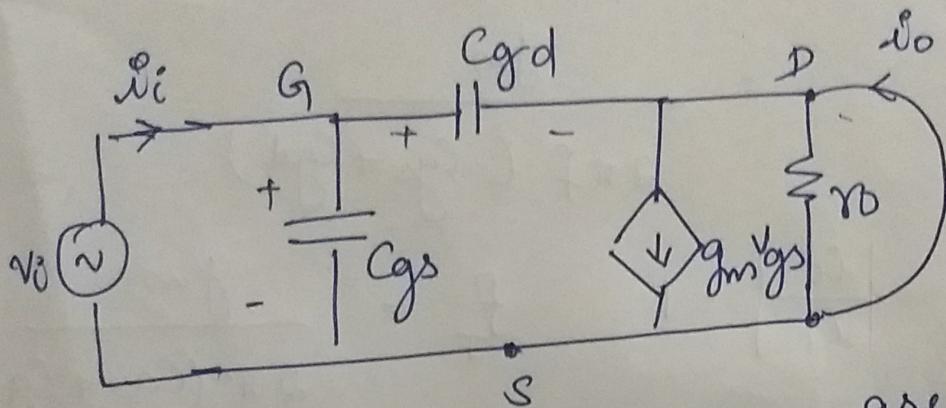3. The small signal equivalent model of MOSFET when o/p terminal is shorted to ground is shown below



Since drain and source are shorted

$$v_{gd} = v_{gs} = v_o$$

\therefore The input current

$$i_i = j\omega(C_{gs} + C_{gd})v_{gs}$$

The output current

$$i_o = g_m v_{gs} - j\omega C_{gd} v_{gs}$$

The short circuit current gain

$$\frac{i_o}{i_i} = \frac{g_m - j\omega C_{gd}}{j\omega(C_{gs} + C_{gd})}$$

Since C_{gd} is very small

$$\approx \frac{g_m}{j\omega(C_{gs} + C_{gd})}$$

$$\left| \frac{d_o}{d_i} \right| = \frac{g_m}{w(C_{gs} + C_{gd})}$$

$$= \frac{g_m}{2\pi f(C_{gs} + C_{gd})}$$

When $\left| \frac{d_o}{d_i} \right| = 1$ $f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$

when $C_{gs} = 1nF$ & $C_{gd} = 0$

$$f_{T1} = \frac{g_m}{2\pi C_{gs}} = \frac{g_m \times 6 \text{ Hz}}{2\pi} = 15.2247 \text{ kHz}$$



when $C_{gs} = 1nF$ & $C_{gd} = 0.2nF$

$$f_{T2} = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = \frac{g_m}{2 \cdot 4\pi} \text{ GHz}$$

$$= 12.6873 \text{ kHz}$$

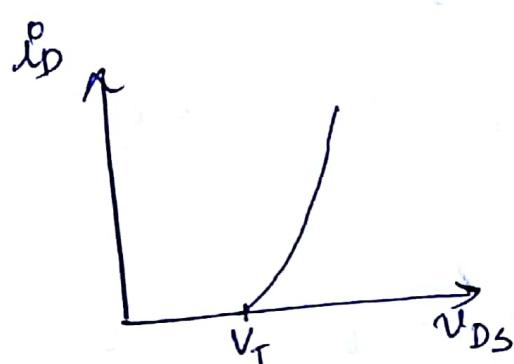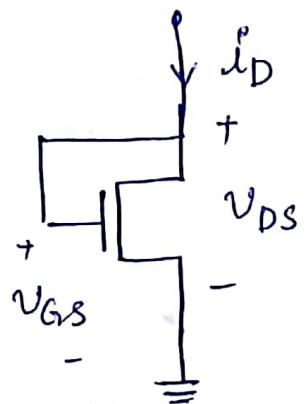Q.4)


When the MOSFET has the gate connected to the drain, it acts like a diode with characteristics similar to a pn junction diode



$$\begin{aligned}
 V_{GS} &= V_{DS}, \text{ MOSFET is in saturation} \\
 i_D &= \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 \\
 &= \frac{\mu_n C_{ox} W}{2L} (V_{DS} - V_T)^2 \\
 &= \frac{\beta}{2} (V_{DS} - V_T)^2 \\
 V_{DS} &= V_{GS} = V_T + \sqrt{\frac{2i_D}{\beta}}
 \end{aligned}$$

where $\beta = \mu_n C_{ox} \frac{W}{L}$.

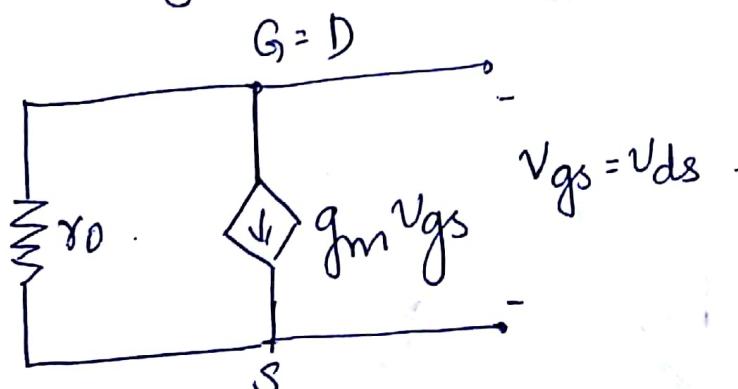The small signal equivalent circuit model (excluding capacitor) & bulk and source are at same potential




The output resistance

$$\begin{aligned}
 R_{out} &= \frac{1}{gm} \parallel R_D \\
 &\approx \frac{1}{gm}
 \end{aligned}$$

1. How to synthesize a voltage source with the given assumption a current source is available

Assume a current source is available

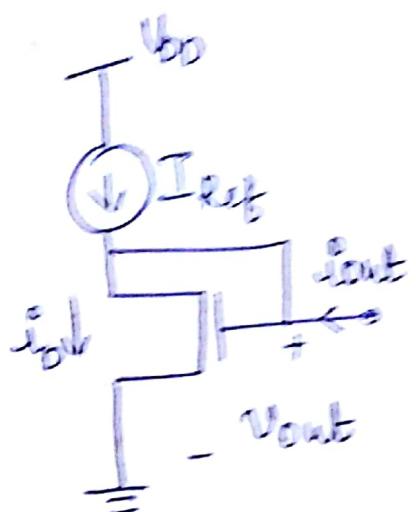

$V_{GS} = V_{DS}$ take a value needed to mark the current.

$$i_D = i_{out} + I_{ref} = \frac{R}{2} (V_{out} - V_T)^2$$


$$\therefore V_{out} = V_T + \sqrt{\frac{I_{ref} + i_{out}}{R/2}}$$

where $R = \mu n \frac{L}{w_L}$


V_{out} is a function of I_{ref} as w_L .

$I_{ref} \uparrow \Rightarrow V_{out} \uparrow$

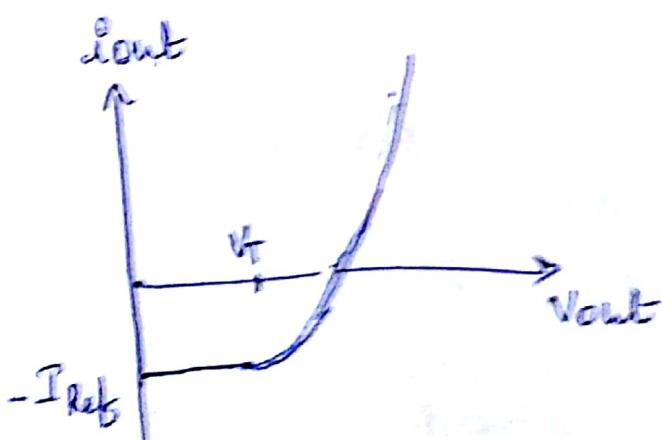
$w_L \uparrow \Rightarrow V_{out} \downarrow$



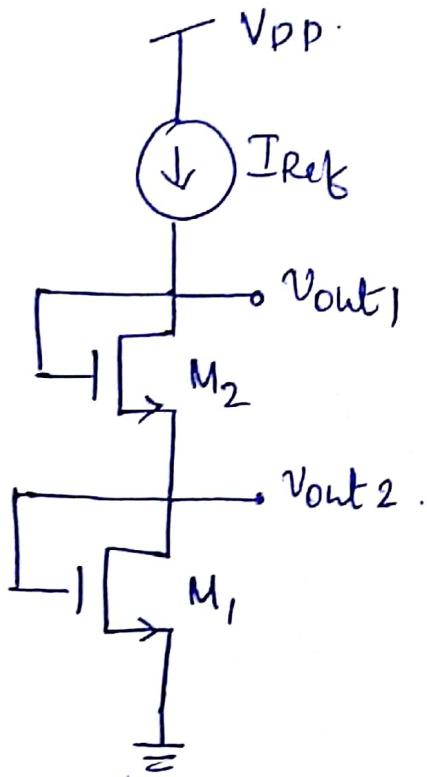2. Voltage divider network using diode connected MOSFET (active resistor)




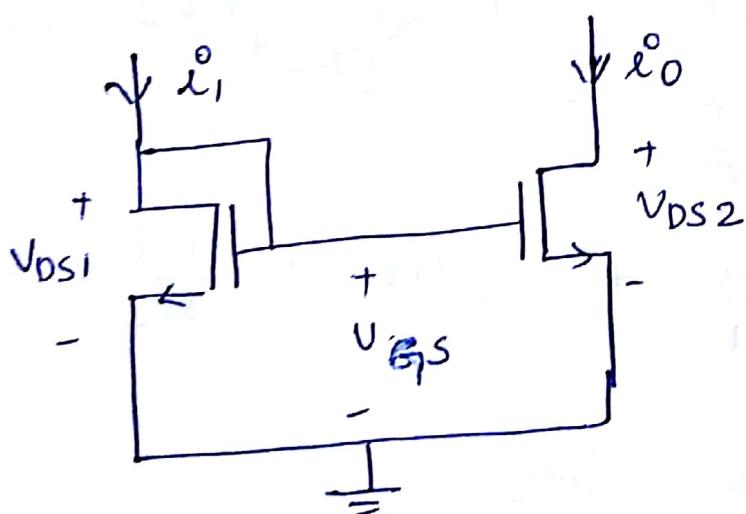3. The MOS diode is used as a component of a current mirror



$$\frac{i_2^o}{i_1^o} = \frac{\beta_2}{\beta_1} \frac{(V_{GS} - V_{T1})^2}{(V_{GS} - V_{T2})^2} \cdot \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

5. nmos inverter with active pmos load

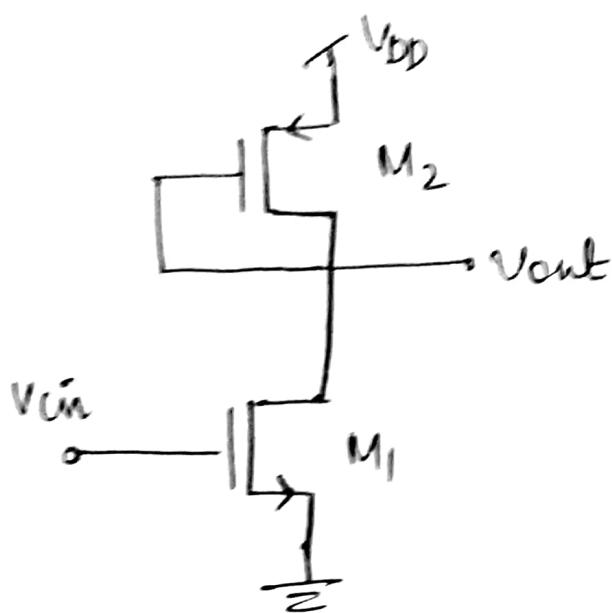

$$\frac{V_{out}}{V_{in}} \approx -\frac{g_{m_1}}{g_{m_2}}$$

$$R_{out} \approx \frac{1}{g_{m_2}}$$

Q5.

For calculating Cgd..

Ngspice code:

*Compute unity current gain frequency

.include tsmc.txt

M1 2 1 0 0 CMOSN W=1u

RD 2 6 10k

VDD 6 5 DC 10v

VGG 1 0 DC 4.5V

V0 5 0 AC 0.01

*defining the run-time control functions

.AC DEC 20 1 1000Gig


.control

run

plot 20*log10(V(2))

.endc

.en

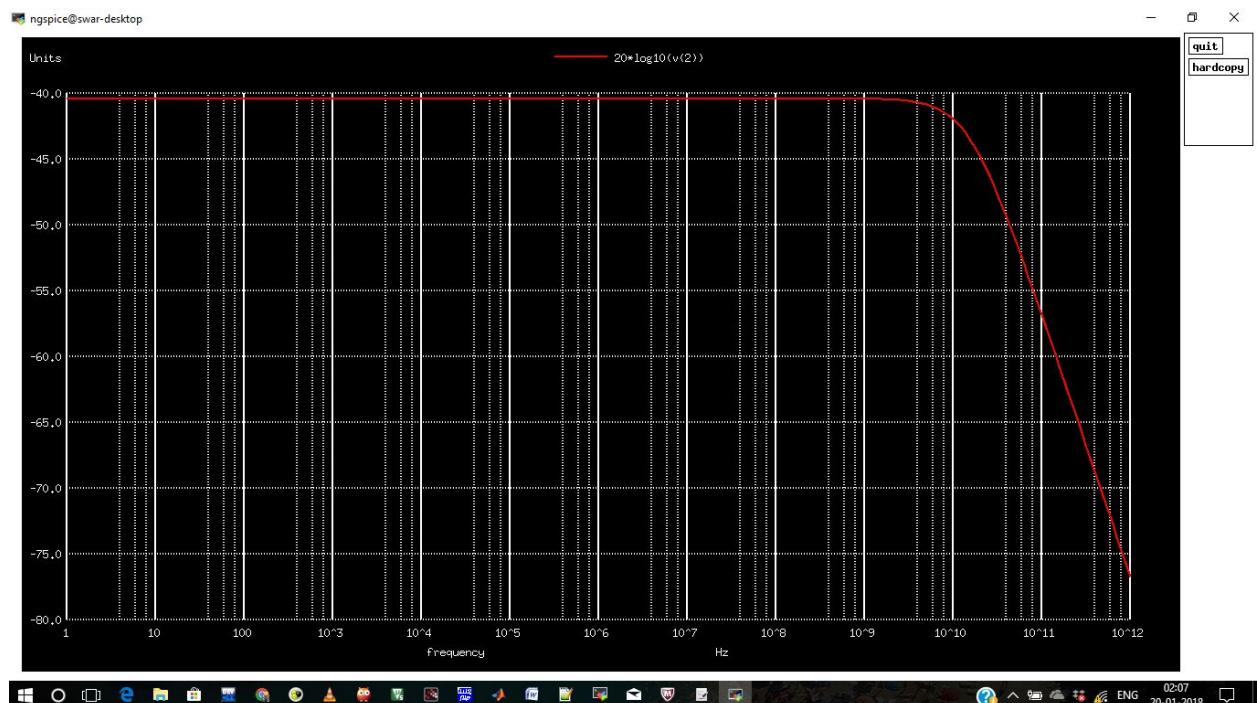

$$f_T = \frac{1}{2\pi C_{gd} * R_d}$$

Here, f_T corresponds to the point where amplitude is 3dB below the highest.

From Figure above $f_T = 15.7 \text{ GHz}$

Putting $R_D = 10k\Omega$ we get $C_{gd} = 0.001\text{pF}$

For Calculating Cgs ..

*Compute unity current gain frequency

.include tsmc.txt

M1 2 1 0 0 CMOSN W=1u

RD 2 6 40k

VDD 6 0 DC 40v

VGG 1 3 DC 3.8V

*Vin 3 0 AC 0.01 sin(0 0.1 0.5Gig)

Vin 3 0 AC 0.01

C0 2 4 1

R0 4 5 0

V0 5 0 0

*defining the run-time control functions

.AC DEC 20 10Meg 1Gig

*.tran 0.005m 0.4m


.control

run

plot (log10(I(V0))-log10(I(Vin)))

.endc

.end

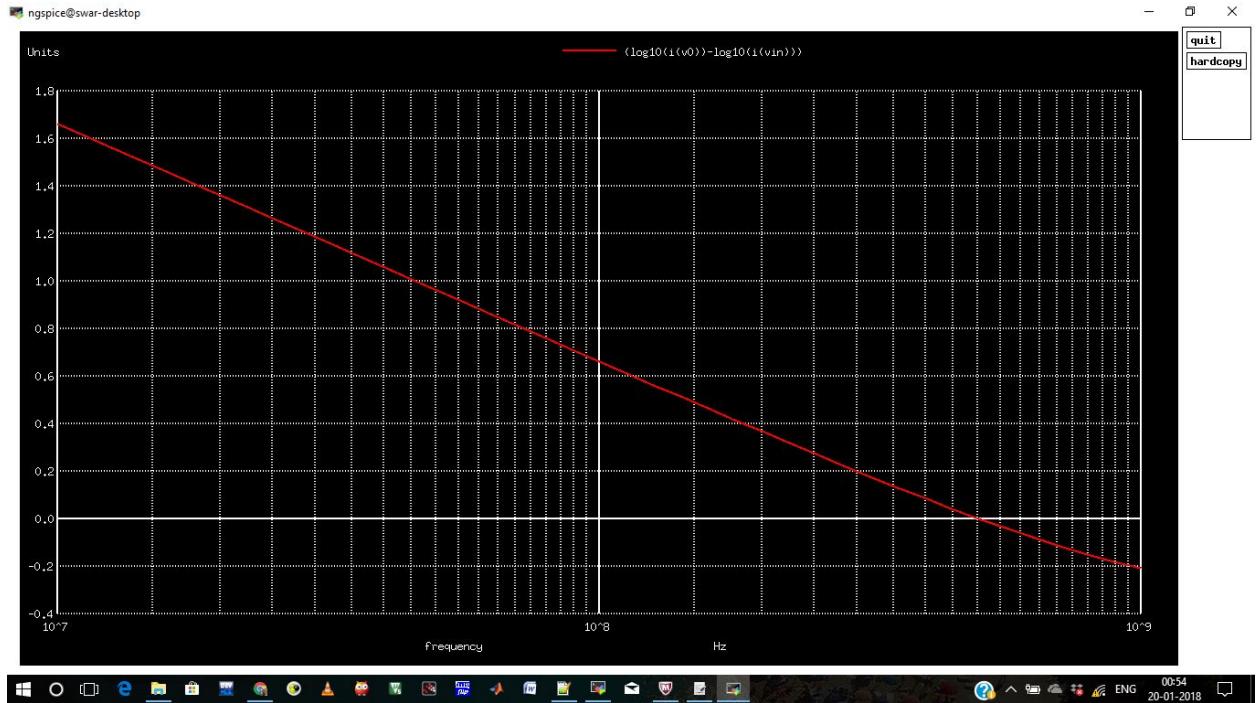

$$f_T = \frac{g_m}{2\pi(C_{gs}+C_{gd})}$$

Here, f_T corresponds to the point where current gain is unity.

From Figure above $f_T = 0.49 \text{ GHz}$

Putting $g_m = 95.66 \mu\text{S}$ we get $C_{gs} = 0.031 \text{ pF} - C_{gd} = 0.030 \text{ pF}$