

DC – DC Power Conversion

Switched mode power supplies / Choppers.


→ High power → D.C. motor speed control

Calcutta metro : 750V DC

Bombay – Igatpuri : 1500V

Power supplies : In computers, any electronic equipments.

Consider Linear regulated power supply

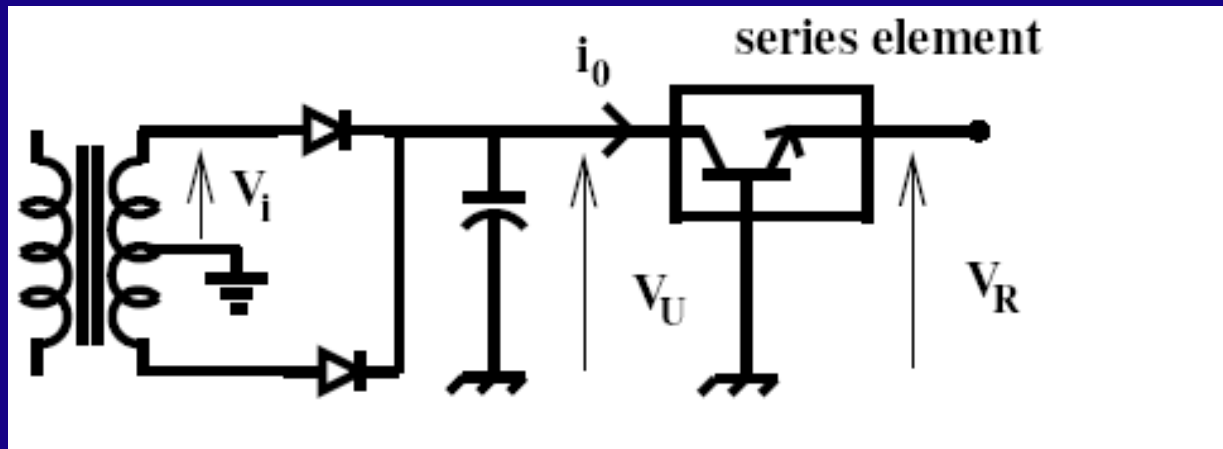


Cathode pot. of diode = V_u

\therefore 'D' is off $V_{\text{anode}} < V_u$

When 'D' is ON, $V_i = V_u$

$$i_s = C \frac{dV_u}{dt} + i_0$$

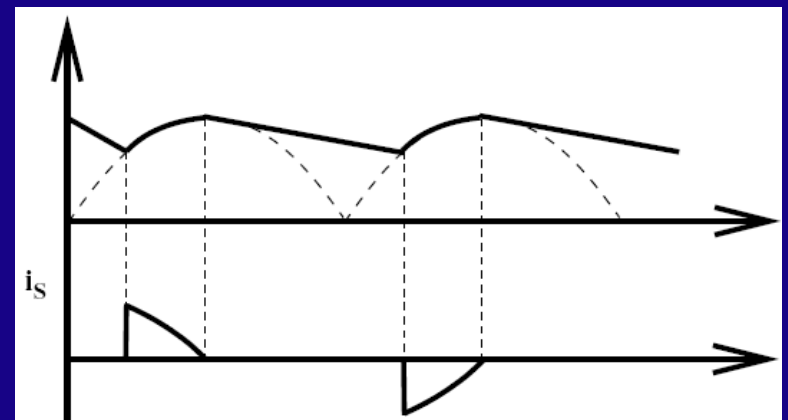

In order to get regulated power supply,
use series regulator.

$$V_{SR} = V_U - V_R$$

As $V_U \uparrow$, $V_{SR} \uparrow$


\Rightarrow 7805 Regulator

$$V_{U(\min)} = 7.5V$$

$$V_{U(\max)} = 35V$$

$$V_R = 5V$$

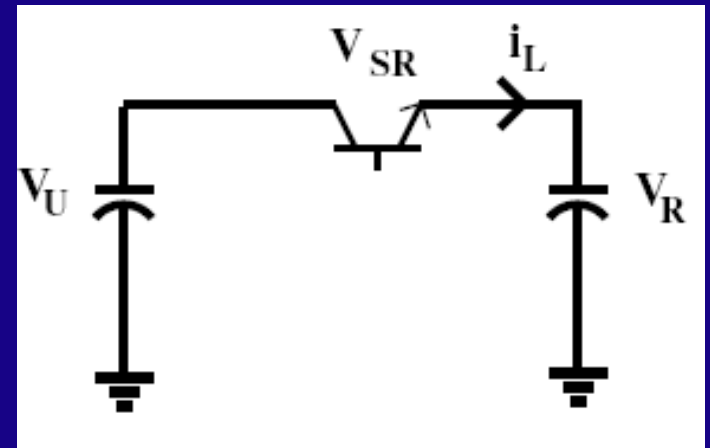Power loss in the device = $V_{SR} * i_L$



Disadvantages :

- η is low.
 - 50Hz Transformer.
 - Heat sink requirement \uparrow
 - Large size of C
 - Source I is peaky, Harmonic content is high.
- Bulky

S.M.P.S. : – Frequency of operation is high $\approx 100\text{KHz}$

\Rightarrow Magnetics are operated at this frequency.

\Rightarrow Broadly classified into 2 groups.

a) Without Transformer

b) With Transformer



Operation is not at 50Hz

$$VA = (4.44F\phi N) * I$$

As $F \uparrow$, $N \downarrow$, core loss \uparrow

\Rightarrow Use ferrite core – Brittle, B_{av} is around 0.2 - 0.25 T


\Rightarrow Amorphous Alloy - B_{av} is of the order 1-1.1 T

Buck converter :

$L_F \rightarrow$ Filter inductor.

$C_F \rightarrow$ Filter capacitor.


' V_0 ' is assumed to remain constant.

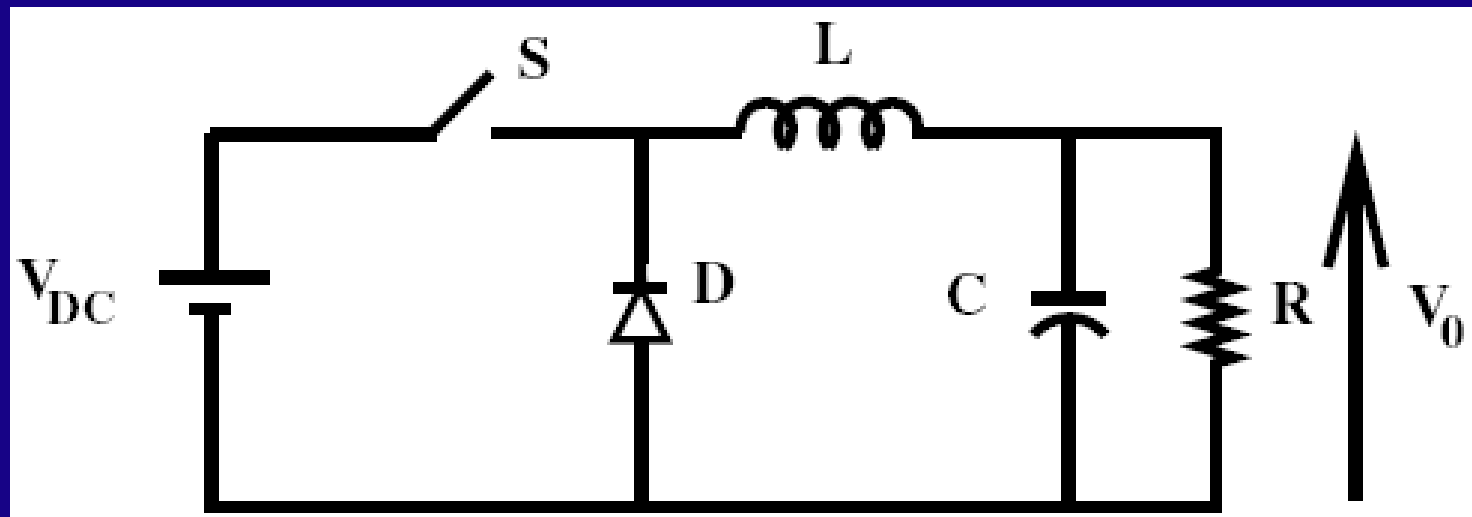

'S' is switched at a very high frequency.

S – ON for DT

– OFF for $(1-D)T$

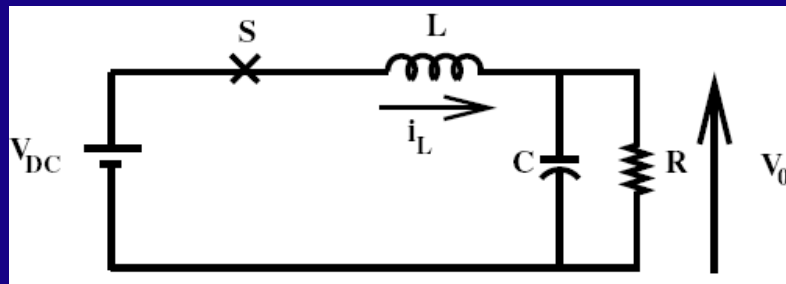


$$V_L = V_{DC} - V_0 \quad 0 < t < DT$$

= Constant

$i_L \uparrow$ Linearly

$$i_L = C \frac{dV_0}{dt} + \frac{V_0}{R}$$

$$V_D = -V_{DC}$$

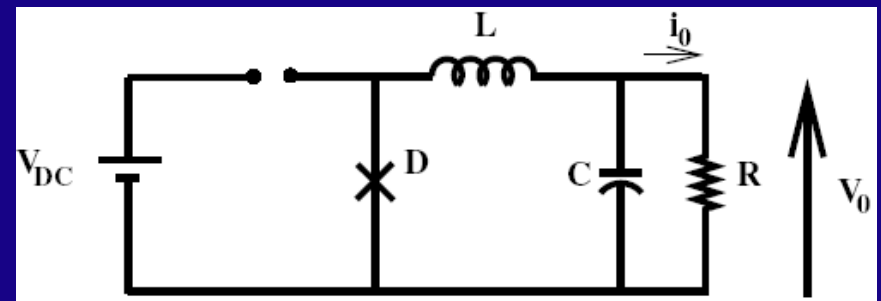

$$V_L = -V_0 \quad (1-D)T < t < T$$

$i_L \downarrow$ Linearly

$$i_L = C \frac{dV_0}{dt} + \frac{V_0}{R}$$

$$V_S = V_{DC}$$

Av. 'V' across L = 0

$$(V_{DC} - V_0)DT = (V_0)(1-D)T$$

$$V_0 = DV_{DC}$$

$$(i_L)_{av} = C \left(\frac{dV_0}{dt} \right)_{av} + \frac{(V_0)_{av}}{R}$$

**'V₀' is assumed to be constant
(variation over the cycle = 0)**

At steady state $V_0|_{t=0} = V_0|_T$

$$\therefore \left. \frac{dV_0}{dt} \right|_{av} = \underline{0} \quad \therefore \frac{V_0}{R} = I_L$$