



$$v_o = A v_x$$

$$v_o = -v_{in} \frac{R_2}{R_1} \left[\frac{1}{1 - \frac{1}{A} (1 + R_2/R_1)} \right]$$

We will consider one non-ideality at a time and understand the meaning of an ideal OPAMP.

Case I. v_o vs v_x graph. The OPAMP is driven by a finite voltage $\pm V_{DD}$ and gain A is finite. $|v_x| \leq \frac{V_{DD}}{A}$ for linearity.

$$v_o = A v_x = -v_{in} \frac{R_2}{R_1} \left[\frac{1}{1 - \frac{1}{A} (1 + R_2/R_1)} \right] \quad \text{--- Eq. 1}$$

$$\Rightarrow |v_x| = \left| -\frac{v_{in}}{A} \frac{R_2}{R_1} \left[\frac{1}{1 - \frac{1}{A} (1 + R_2/R_1)} \right] \right| \leq \frac{V_{DD}}{A}$$

$$\Rightarrow |v_{in}| \leq \frac{V_{DD} R_1}{R_2} \left[1 - \frac{1}{A} \left(1 + \frac{R_2}{R_1} \right) \right]$$

Condition I for ideality $A \rightarrow \infty$.

$$|v_{in}| \leq V_{DD} R_1 / R_2$$

What happens if $|v_{in}| > V_{DD} R_1 / R_2$, i.e. $|v_{in}| = a V_{DD} R_1 / R_2$ $a > 1$

Eqn. (1) suggests that

$$|v_o| = \left| a V_{DD} \left[\frac{1}{1 - \frac{1}{A} (1 + R_2/R_1)} \right] \right|$$

But, $A \rightarrow \infty$ from condition I; so

$$|v_o| = a V_{DD} > V_{DD}$$

But we started with the assumption that $+V_{DD}$ is finite and maximum available voltage.

Condition II for ideality, $V_{DD} \rightarrow \infty$

Case II

So far we have assumed that the signal is all DC in the circuit. Let us bring in a non-ideality that the amplifiers are usually a single pole amplifier.

$$A = \frac{A_0}{1 + s/\omega_0}, \quad \text{where } \omega_0 \text{ is the corner frequency}$$

A_0 is the low frequency gain.

$$V_o = -V_{in} \frac{R_2}{R_1} \left[\frac{1}{1 - \frac{1}{A} \left(1 + \frac{R_2}{R_1}\right)} \right]$$

$$= -V_{in} \frac{R_2}{R_1} \left[\frac{1}{1 - \frac{1 + s/\omega_0}{A_0} \left(1 + \frac{R_2}{R_1}\right)} \right]$$

$$V_o(s) = -V_{in}(s) \frac{R_2}{R_1} \frac{A_0}{A_0 - (1 + s/\omega_0)(1 + R_2/R_1)}$$

$$= -V_{in}(s) \frac{R_2}{R_1} \frac{A_0}{\left[A_0 - (1 + R_2/R_1) \right] - \frac{s}{\omega_0} (1 + R_2/R_1)}$$

$$= -V_{in}(s) \frac{R_2}{R_1} \frac{A_0 \omega_0}{\left(\frac{A_0}{1 + R_2/R_1} - 1 \right) - s} \quad \text{--- Eqn (2)}$$

$$= V_{in}(s) \frac{R_2}{R_1} \frac{s - \left(\frac{A_0}{1 + R_2/R_1} - 1 \right) \omega_0}{s - \left(\frac{A_0}{1 + R_2/R_1} - 1 \right) \omega_0}$$

Please note it may appear that we can now take limit $A_0 \rightarrow \infty$ and $V_o(s) = -V_{in}(s)(R_2/R_1)$ but s (frequency) can be very large also, hence such operation is mathematically wrong.

Independent of the form of $V_{in}(s)$, the output will always have a time dependent signal

$$V_o(t) = V_o'(t) + K_1 e^{\left(\frac{A_0}{1 + R_2/R_1} - 1 \right) \omega_0 t}$$

This can make the signal grow out of bound. So we need to make sure pole remains on the left half plane i.e.

$$\omega_0 \left(\frac{A_0}{1 + R_2/R_1} - 1 \right) < 0$$

$$\Rightarrow A_0 < \left(1 + R_2/R_1 \right)$$

But we also need $A_0 \rightarrow \infty$. Hence this condition can't be met with finite s . However, if we start with the assumption that $s \rightarrow 0$ [DC condition only] then Eqn (2) will boil down to $V_o(s) = -\frac{R_2}{R_1} V_{in}(s)$ when $A_0 \rightarrow \infty$

However there is always noise in the ckt which will have all sorts of frequency components.


Condition III The OPAMP is noiseless and no time varying signal is present.

Equivalently speaking, $A = A_0 / (1 + s/\omega_0) \approx A_0$
i.e. $\omega_0 \rightarrow \infty$ in comparison $s (= j\omega)$. So the operating frequency is always small w.r.t the bandwidth of OPAMP.


Condition IV $\omega_0 \rightarrow \infty$, OPAMP has infinite bandwidth.

Case - III

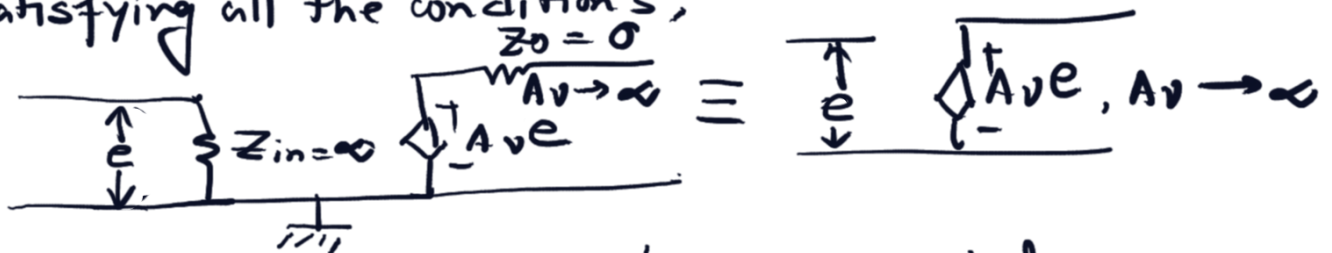So, what is the equivalent ckt of an ideal opAMP satisfying all the conditions,



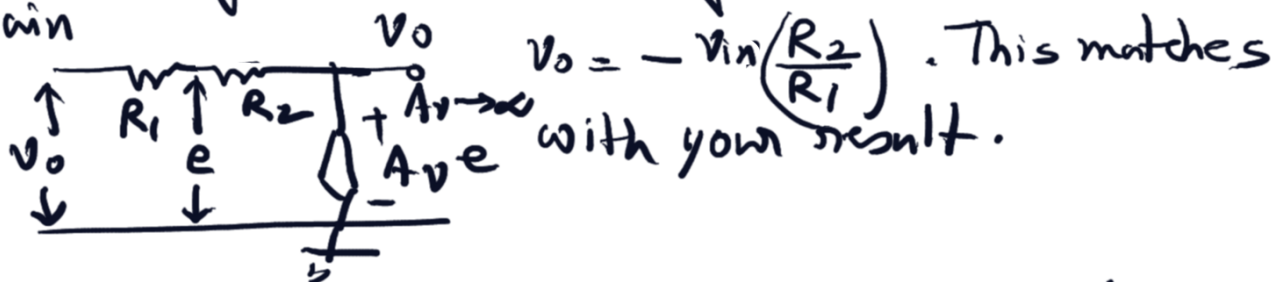As long as the OPAMP can be approximated as an ideal voltage controlled voltage source only with infinite gain



[Please note I have not considered input and output bias currents, resistances and capacitances elsewhere. In the ideal condition they have all been assumed to be zero.]