
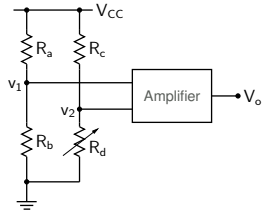


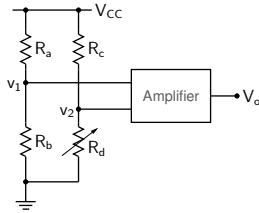
Common-mode and differential-mode voltages





Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

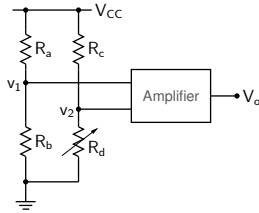
$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .



Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

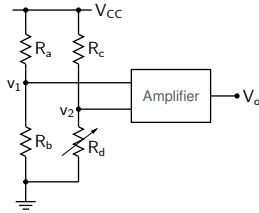The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.




Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

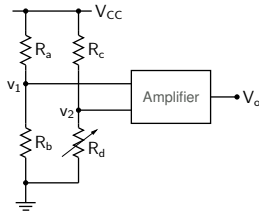Assuming that the amplifier has a large input resistance,




Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,
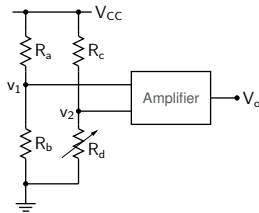
$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC}.$$



Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .


The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,

$$v_1 = \frac{R}{R+R} V_{CC} = \frac{1}{2} V_{CC}.$$

$$v_2 = \frac{(R + \Delta R)}{R + (R + \Delta R)} V_{CC} = \frac{1}{2} \frac{1+x}{1+x/2} V_{CC} \approx \frac{1}{2} (1+x) (1-x/2) V_{CC} = \frac{1}{2} (1+x/2) V_{CC},$$

where $x = \Delta R/R$.

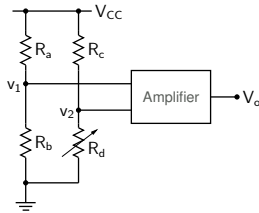

Consider a bridge circuit for sensing temperature, pressure, etc., with $R_a = R_b = R_c = R$.

$R_d = R + \Delta R$ varies with the quantity to be measured. Typically, ΔR is a small fraction of R .

The bridge converts ΔR to a signal voltage which can then be suitably amplified and used for display or control.

Assuming that the amplifier has a large input resistance,

$$v_1 = \frac{R}{R + R} V_{CC} = \frac{1}{2} V_{CC} .$$

$$v_2 = \frac{(R + \Delta R)}{R + (R + \Delta R)} V_{CC} = \frac{1}{2} \frac{1 + x}{1 + x/2} V_{CC} \approx \frac{1}{2} (1 + x) (1 - x/2) V_{CC} = \frac{1}{2} (1 + x/2) V_{CC} ,$$


where $x = \Delta R/R$.

For example, with $V_{CC} = 15 \text{ V}$, $R = 1 \text{ k}$, $\Delta R = 0.01 \text{ k}$,

$$v_1 = 7.5 \text{ V} ,$$


$$v_2 = 7.5 + 0.0375 \text{ V} .$$

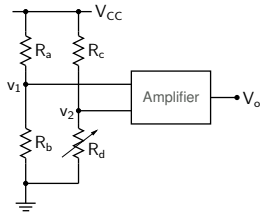Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

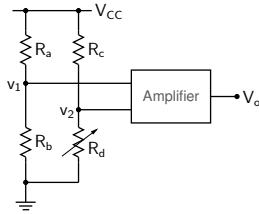
Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

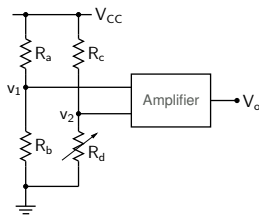Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$


The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

Definitions:

Given v_1 and v_2 ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$
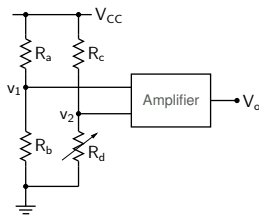
$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

Definitions:


Given v_1 and v_2 ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$

$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

v_1 and v_2 can be rewritten as,
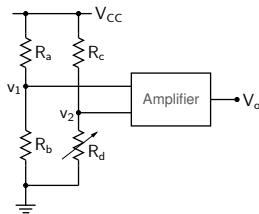
$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

Definitions:

Given v_1 and v_2 ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$


$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$

v_1 and v_2 can be rewritten as,

$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$

In the above example, $v_c \approx 7.5 \text{ V}$, $v_d = 37.5 \text{ mV}$.

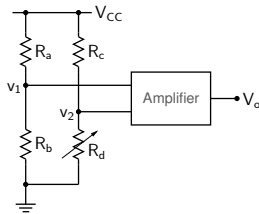Common-mode and differential-mode voltages



$$v_1 = 7.5 \text{ V}, \quad v_2 = 7.5 + 0.0375 \text{ V}.$$

The amplifier should only amplify $v_2 - v_1 = 0.0375 \text{ V}$ (since that is the signal arising from ΔR).

Definitions:

Given v_1 and v_2 ,

$$v_c = \frac{1}{2} (v_1 + v_2) = \text{common-mode voltage},$$

$$v_d = (v_2 - v_1) = \text{differential-mode voltage}.$$


v_1 and v_2 can be rewritten as,

$$v_1 = v_c - v_d/2, \quad v_2 = v_c + v_d/2.$$


In the above example, $v_c \approx 7.5 \text{ V}$, $v_d = 37.5 \text{ mV}$.

Note that the common-mode voltage is quite large compared to the differential-mode voltage.

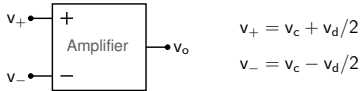This is a common situation in transducer circuits.



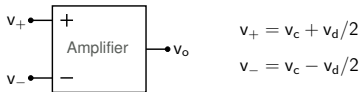An ideal amplifier would only amplify the difference $(v_+ - v_-)$, giving $v_o = A_d (v_+ - v_-) = A_d v_d$, where A_d is called the “differential gain” or simply the gain (A_V).



An ideal amplifier would only amplify the difference ($v_+ - v_-$), giving


$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where A_d is called the “differential gain” or simply the gain (A_V).

In practice, the output can also have a common-mode component:

$$v_o = A_d v_d + A_c v_c,$$

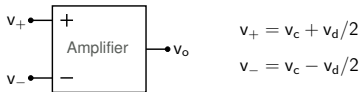where A_c is called the “common-mode gain”.



An ideal amplifier would only amplify the difference ($v_+ - v_-$), giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where A_d is called the “differential gain” or simply the gain (A_V).

In practice, the output can also have a common-mode component:


$$v_o = A_d v_d + A_c v_c,$$

where A_c is called the “common-mode gain”.

The ability of an amplifier to *reject* the common-mode signal is given by the

Common-Mode Rejection Ratio (CMRR):

$$\text{CMRR} = \frac{A_d}{A_c}$$

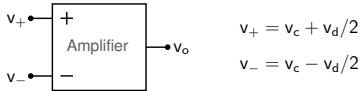

An ideal amplifier would only amplify the difference $(v_+ - v_-)$, giving

$$v_o = A_d (v_+ - v_-) = A_d v_d,$$

where A_d is called the “differential gain” or simply the gain (A_V).

In practice, the output can also have a common-mode component:

$$v_o = A_d v_d + A_c v_c,$$

where A_c is called the “common-mode gain”.


The ability of an amplifier to *reject* the common-mode signal is given by the

Common-Mode Rejection Ratio (CMRR):


$$\text{CMRR} = \frac{A_d}{A_c}$$

For the 741 op-amp, the CMRR is 90 dB ($\simeq 30,000$), which may be considered to be infinite in many applications. In such cases, mismatch between circuit components will determine the overall common-mode rejection performance of the circuit.

Op-amp circuits (linear region)

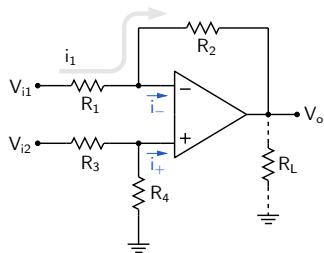


Op-amp circuits (linear region)

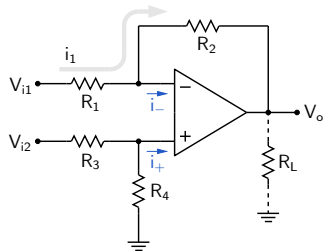

Method 1:

Large input resistance of op-amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Op-amp circuits (linear region)

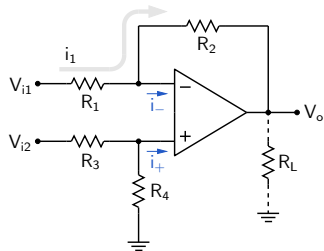


Method 1:

Large input resistance of op-amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.

Op-amp circuits (linear region)

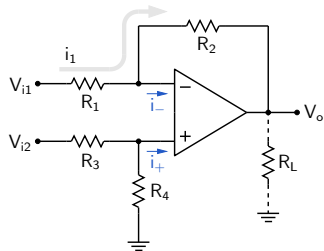


Method 1:

Large input resistance of op-amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.

$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$.

Op-amp circuits (linear region)

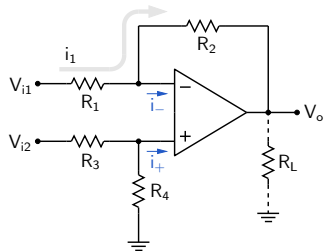

Method 1:

Large input resistance of op-amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.


Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.

$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$.

Substituting for V_+ and selecting $\frac{R_4}{R_3} = \frac{R_2}{R_1}$, we get (show this)

$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}).$$

Op-amp circuits (linear region)

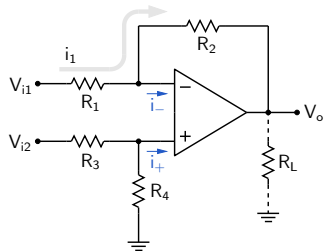

Method 1:

Large input resistance of op-amp $\rightarrow i_+ = 0$, $V_+ = \frac{R_4}{R_3 + R_4} V_{i2}$.

Since $V_+ - V_- \approx 0$, $i_1 = \frac{1}{R_1} (V_{i1} - V_-) \approx \frac{1}{R_1} (V_{i1} - V_+)$.




$i_- \approx 0 \rightarrow V_o = V_- - i_1 R_2 \approx V_+ - \frac{R_2}{R_1} (V_{i1} - V_+)$.

Substituting for V_+ and selecting $\frac{R_4}{R_3} = \frac{R_2}{R_1}$, we get (show this)

$$V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}).$$

The circuit is a "difference amplifier."




Difference amplifier

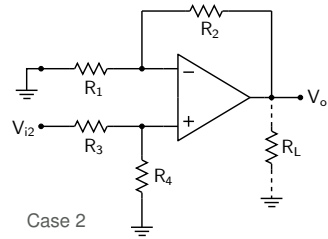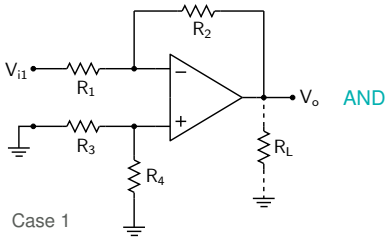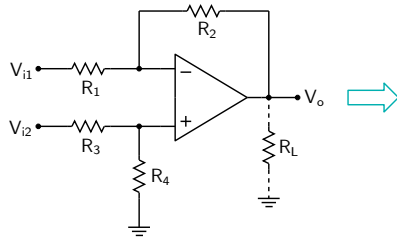

Method 2:

Since the op-amp is operating in the linear region, we can use superposition:

Difference amplifier

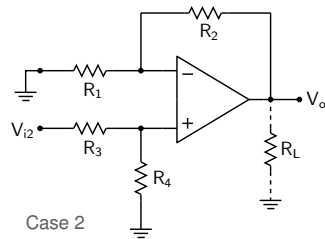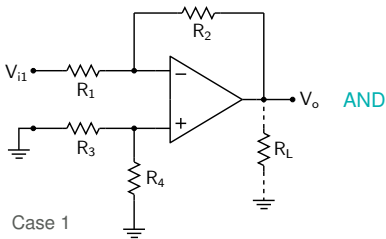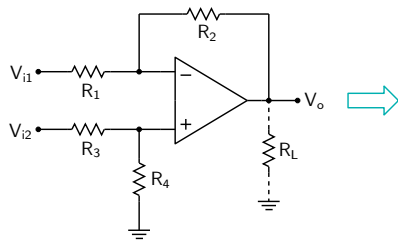


Method 2:

Since the op-amp is operating in the linear region, we can use superposition:

Case 1: Inverting amplifier (note that $V_+ = 0\text{ V}$).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$

Difference amplifier

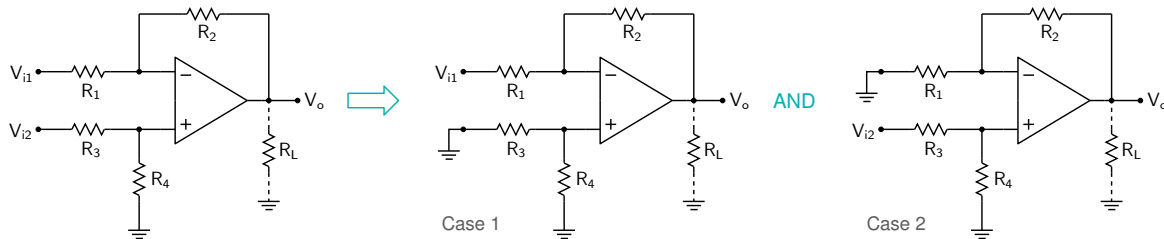

Method 2:

Since the op-amp is operating in the linear region, we can use superposition:


Case 1: Inverting amplifier (note that $V_+ = 0\text{ V}$).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$

Case 2: Non-inverting amplifier, with $V_i = \frac{R_4}{R_3 + R_4} V_{i2}$.

$$\rightarrow V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2}.$$

Difference amplifier

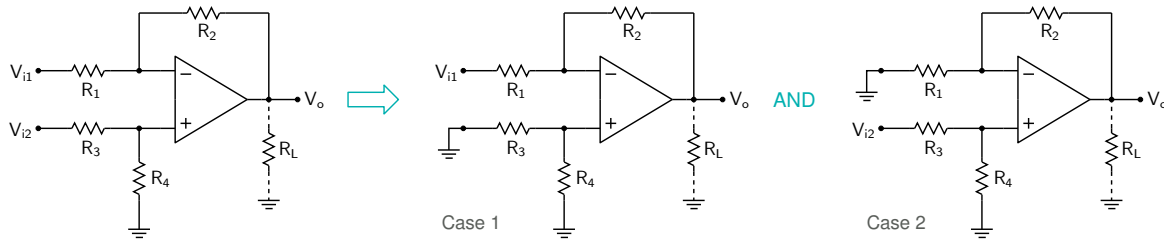

Method 2:

Since the op-amp is operating in the linear region, we can use superposition:

Case 1: Inverting amplifier (note that $V_+ = 0$ V).

$$\rightarrow V_{o1} = -\frac{R_2}{R_1} V_{i1}.$$


Case 2: Non-inverting amplifier, with $V_i = \frac{R_4}{R_3 + R_4} V_{i2}$.

$$\rightarrow V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2}.$$


The net result is,

$$V_o = V_{o1} + V_{o2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1} = \frac{R_2}{R_1} (V_{i2} - V_{i1}), \text{ if } \frac{R_4}{R_3} = \frac{R_2}{R_1}.$$

Difference amplifier

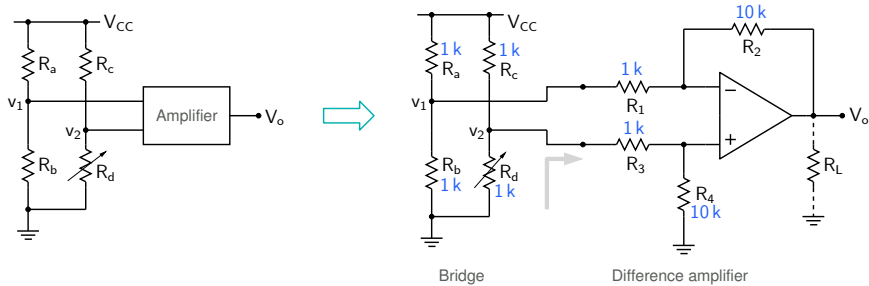


Difference amplifier

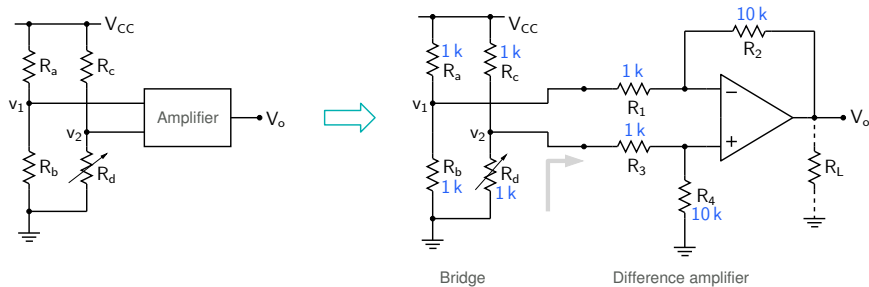

The resistance seen from v_2 is $(R_3 + R_4)$ which is small enough to cause v_2 to change.
This is not desirable.

Difference amplifier

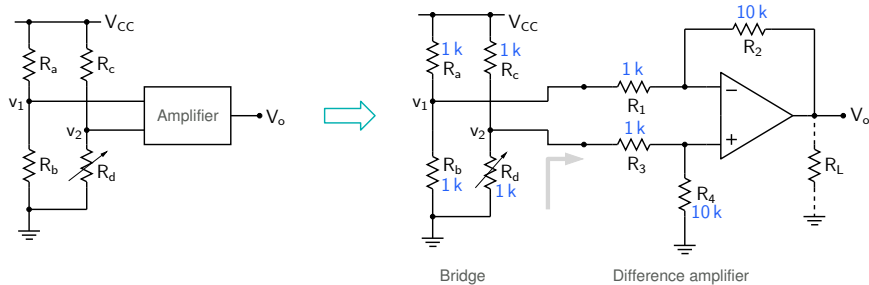


The resistance seen from v_2 is $(R_3 + R_4)$ which is small enough to cause v_2 to change.

This is not desirable.

→ need to improve the input resistance of the difference amplifier.

Difference amplifier

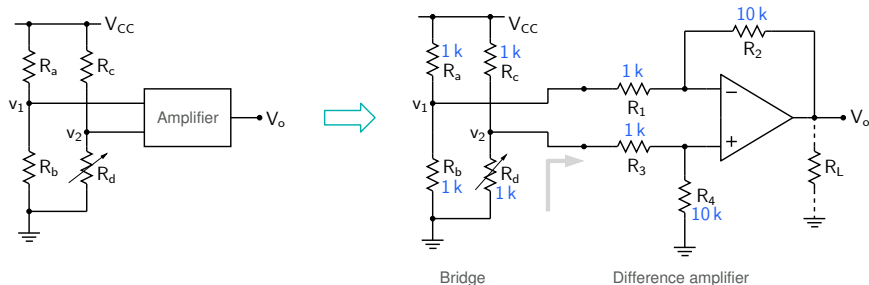


The resistance seen from v_2 is $(R_3 + R_4)$ which is small enough to cause v_2 to change.

This is not desirable.


→ need to improve the input resistance of the difference amplifier.

We will discuss an improved difference amplifier later. Before we do that, let us discuss another problem with the above difference amplifier which can be important for some applications (next slide).

Difference amplifier

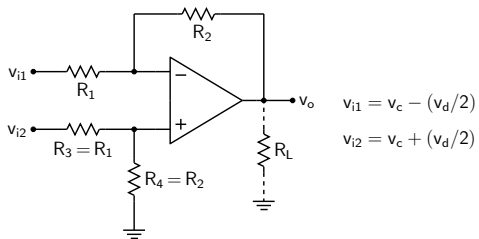


Difference amplifier

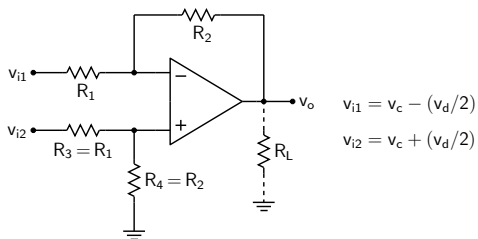

Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.

The output voltage depends only on the differential-mode signal $(v_{i2} - v_{i1})$,
i.e., A_c (common-mode gain) = 0.

Difference amplifier

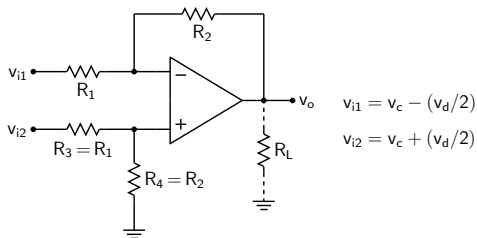


Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.

The output voltage depends only on the differential-mode signal $(v_{i2} - v_{i1})$,
i.e., A_c (common-mode gain) = 0.

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

Difference amplifier

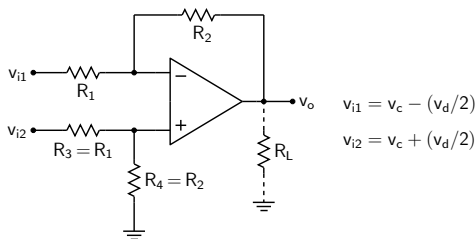


Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.

The output voltage depends only on the differential-mode signal $(v_{i2} - v_{i1})$,
i.e., A_c (common-mode gain) = 0.

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

$$\begin{aligned} v_o &= \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} = \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\ &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this}) \end{aligned}$$

Difference amplifier

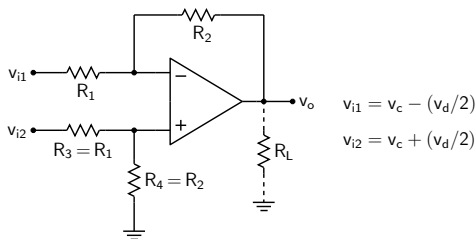

Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.


The output voltage depends only on the differential-mode signal $(v_{i2} - v_{i1})$,
i.e., A_c (common-mode gain) = 0.

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

$$\begin{aligned}
 v_o &= \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} = \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1} \right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\
 &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this})
 \end{aligned}$$

$$|A_c| = \frac{\Delta R}{R_1 + R_2} \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}.$$

Difference amplifier

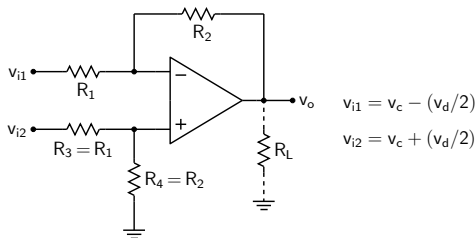

Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow V_o = \frac{R_2}{R_1} (v_{i2} - v_{i1})$.


The output voltage depends only on the differential-mode signal $(v_{i2} - v_{i1})$,
i.e., A_c (common-mode gain) = 0.

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

$$\begin{aligned}
 v_o &= \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) v_{i2} - \frac{R_2}{R_1} v_{i1} = \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1}\right) v_{i2} - \frac{R_2}{R_1} v_{i1} \\
 &\simeq \frac{R_2}{R_1} (v_d - x v_c), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this})
 \end{aligned}$$


$|A_c| = \frac{\Delta R}{R_1 + R_2} \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}$. However, since v_c can be large compared to v_d , the effect of A_c cannot be ignored.

Difference amplifier

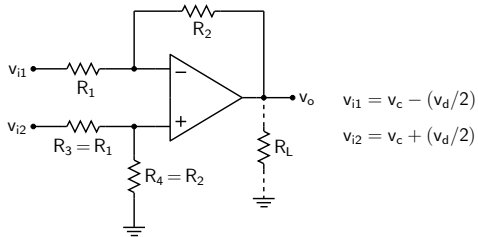

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$


Difference amplifier

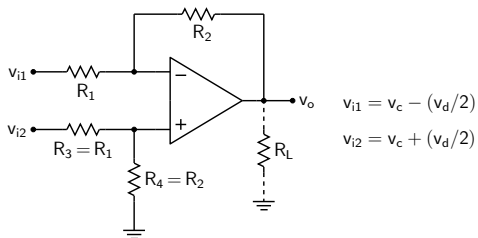

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

Difference amplifier

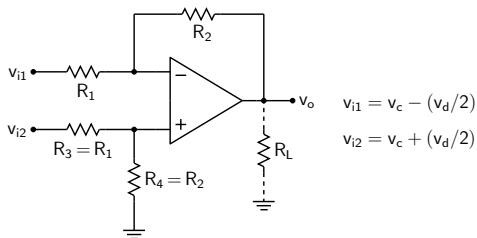


$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

With $R_1 = 1 \text{ k}$, $R_2 = 10 \text{ k}$, $x = \frac{0.01 \text{ k}}{11 \text{ k}} = 0.00091 \rightarrow |A_c| = 0.00091 \frac{10 \text{ k}}{1 \text{ k}} = 0.0091$, $|A_d| = \frac{10 \text{ k}}{1 \text{ k}} = 10$.

$$|v_o^c| = |A_c v_c| = 0.0091 \times 7.5 = 0.068 \text{ V}.$$

Difference amplifier

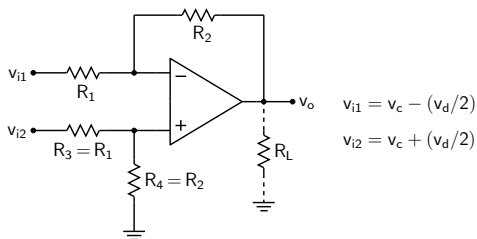

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$


In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

$$\text{With } R_1 = 1 \text{ k}, R_2 = 10 \text{ k}, x = \frac{0.01 \text{ k}}{11 \text{ k}} = 0.00091 \rightarrow |A_c| = 0.00091 \frac{10 \text{ k}}{1 \text{ k}} = 0.0091, |A_d| = \frac{10 \text{ k}}{1 \text{ k}} = 10.$$

$$|v_o^c| = |A_c v_c| = 0.0091 \times 7.5 = 0.068 \text{ V}.$$

$$|v_o^d| = |A_d v_d| = 10 \times 0.0375 = 0.375 \text{ V}.$$

Difference amplifier

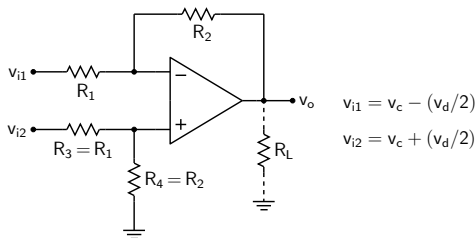

$$|A_c| = x \frac{R_2}{R_1}, |A_d| = \frac{R_2}{R_1}, \text{ where } x = \frac{\Delta R}{R_1 + R_2}.$$

In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

$$\text{With } R_1 = 1 \text{ k}, R_2 = 10 \text{ k}, x = \frac{0.01 \text{ k}}{11 \text{ k}} = 0.00091 \rightarrow |A_c| = 0.00091 \frac{10 \text{ k}}{1 \text{ k}} = 0.0091, |A_d| = \frac{10 \text{ k}}{1 \text{ k}} = 10.$$

$$|v_o^c| = |A_c v_c| = 0.0091 \times 7.5 = 0.068 \text{ V}.$$


$$|v_o^d| = |A_d v_d| = 10 \times 0.0375 = 0.375 \text{ V}.$$

The (spurious) common-mode contribution is substantial.

If we measure v_o , we will conclude that $v_d = \frac{v_o}{A_d}$, but in reality, it would be different.


→ need a circuit which will drastically reduce the common-mode component at the output.

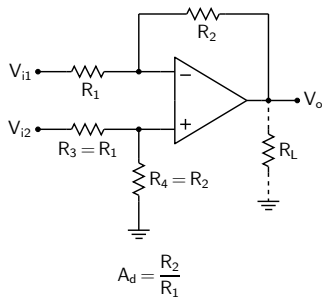Difference amplifier: resistance mismatch



$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

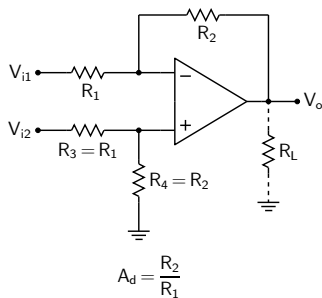Difference amplifier: resistance mismatch




$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$A_c = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1}$$

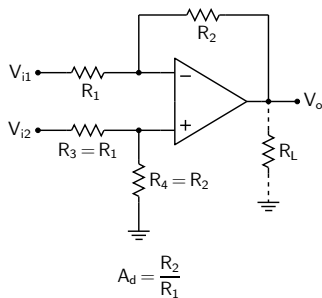Difference amplifier: resistance mismatch




$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

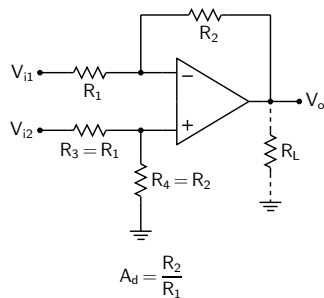Difference amplifier: resistance mismatch




$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with $R_1 = R_1^0(1 + x_1)$, etc. 1 % resistor $\rightarrow x = 0.01$.

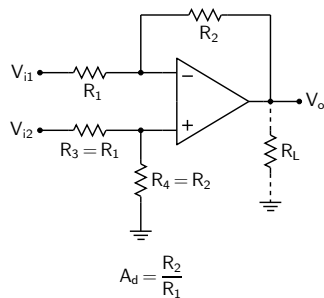Difference amplifier: resistance mismatch




$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with $R_1 = R_1^0(1 + x_1)$, etc. 1 % resistor $\rightarrow x = 0.01$.
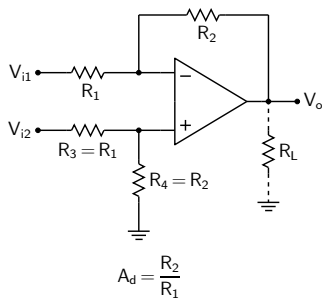
$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$



$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$


$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with $R_1 = R_1^0(1 + x_1)$, etc. 1% resistor $\rightarrow x = 0.01$.

$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$

Using $(1 + u_1)(1 + u_2) \approx 1 + u_1 + u_2$ if $|u_1| \ll 1$, $|u_2| \ll 1$,

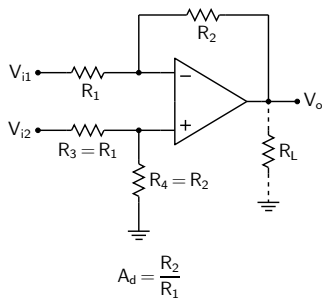

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$


$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with $R_1 = R_1^0(1 + x_1)$, etc. 1% resistor $\rightarrow x = 0.01$.

$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$

Using $(1 + u_1)(1 + u_2) \approx 1 + u_1 + u_2$ if $|u_1| \ll 1, |u_2| \ll 1$,

and $\frac{1}{1 + u} \approx 1 - u$ if $|u| \ll 1$,

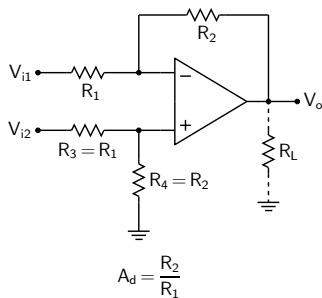

$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

$$\text{Let } V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}.$$

$$\begin{aligned} A_c &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1} \\ &= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right) \end{aligned}$$

Assume ideal op-amp with $R_1 = R_1^0(1 + x_1)$, etc. 1 % resistor $\rightarrow x = 0.01$.


$$\rightarrow A_c = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0(1 + x_2)}{R_1^0(1 + x_1)} \times \frac{R_3^0(1 + x_3)}{R_4^0(1 + x_4)}\right).$$

Using $(1 + u_1)(1 + u_2) \approx 1 + u_1 + u_2$ if $|u_1| \ll 1$, $|u_2| \ll 1$,

and $\frac{1}{1 + u} \approx 1 - u$ if $|u| \ll 1$,


$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

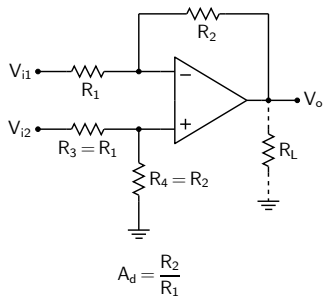Difference amplifier: resistance mismatch



$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

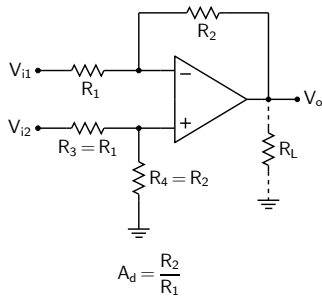
Difference amplifier: resistance mismatch



$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

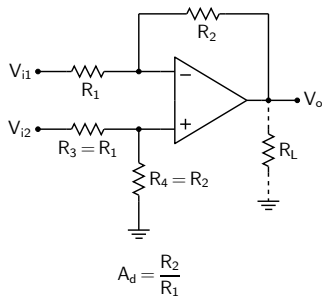Difference amplifier: resistance mismatch




$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) \quad R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$

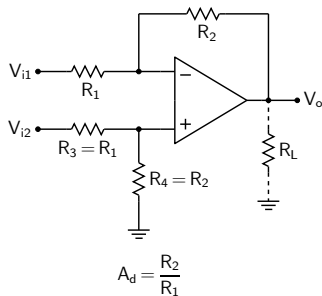Difference amplifier: resistance mismatch




$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) \quad R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$

$$A_c = \frac{1}{2} (x_1 - x_2 - x_3 + x_4)$$

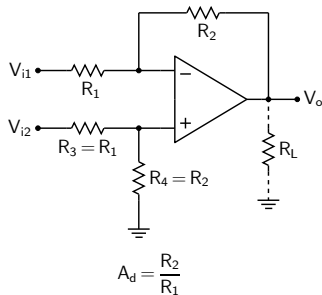Difference amplifier: resistance mismatch




$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$
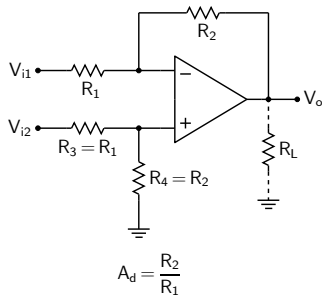
$$\begin{aligned} A_c &= \frac{1}{2} (x_1 - x_2 - x_3 + x_4) \\ &= \frac{1}{2} 4x = 2x \text{ (worst case)} \end{aligned}$$



$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$


$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$

$$(1) R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$

$$\begin{aligned}
 A_c &= \frac{1}{2} (x_1 - x_2 - x_3 + x_4) \\
 &= \frac{1}{2} 4x = 2x \text{ (worst case)}
 \end{aligned}$$

$$(2) R_1^0 \ll R_2^0 \text{ (i.e., } R_3^0 \ll R_4^0)$$

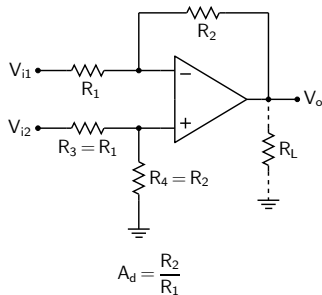Difference amplifier: resistance mismatch



$$A_c = \frac{R_4}{R_3 + R_4} (x_1 - x_2 - x_3 + x_4).$$

$$\frac{R_4}{R_3 + R_4} \approx \frac{R_4^0}{R_3^0 + R_4^0}.$$


$$(1) \ R_1^0 = R_2^0 \text{ (i.e., } R_3^0 = R_4^0)$$

$$\begin{aligned} A_c &= \frac{1}{2} (x_1 - x_2 - x_3 + x_4) \\ &= \frac{1}{2} 4x = 2x \text{ (worst case)} \end{aligned}$$


$$(2) \ R_1^0 \ll R_2^0 \text{ (i.e., } R_3^0 \ll R_4^0)$$

$$A_c = \frac{(R_4^0/R_3^0)}{1 + (R_4^0/R_3^0)} (x_1 - x_2 - x_3 + x_4) \approx 4x \text{ (worst case)}$$

Improved difference amplifier

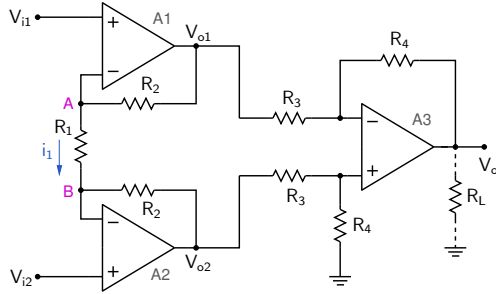


Improved difference amplifier

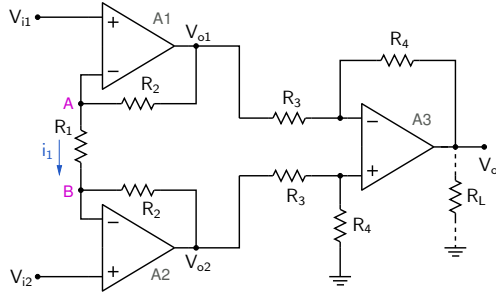

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$


Improved difference amplifier

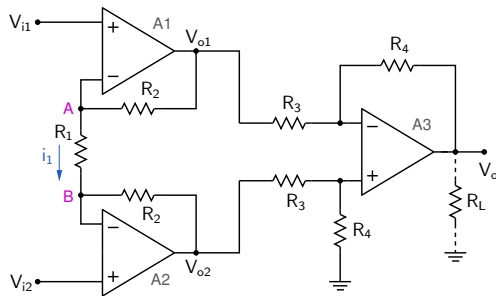

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .


Improved difference amplifier

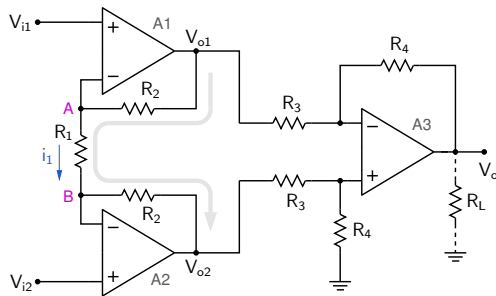

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

Improved difference amplifier

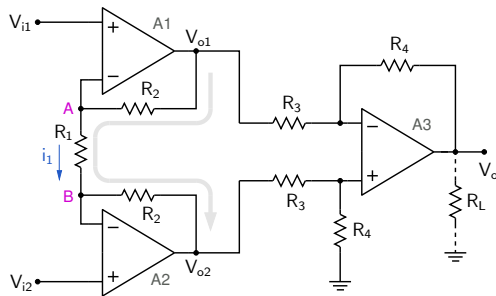


$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2}) (R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1} \right).$$

Improved difference amplifier

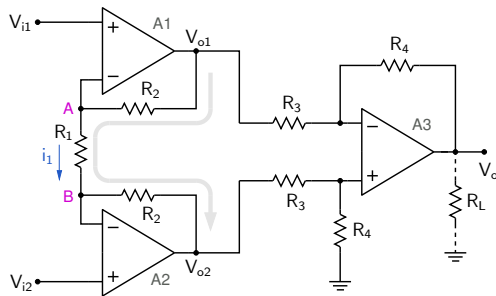


$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$

Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2}) (R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1} \right).$$

$$\text{Finally, } V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (V_{i2} - V_{i1}).$$

Improved difference amplifier

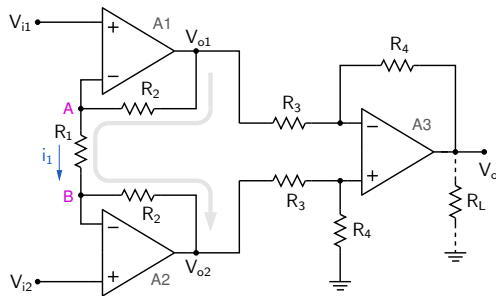

$$V_+ \approx V_- \rightarrow V_A = V_{i1}, V_B = V_{i2}, \rightarrow i_1 = \frac{1}{R_1} (V_{i1} - V_{i2}).$$


Large input resistance of A1 and A2 \Rightarrow the current through the two resistors marked R_2 is also equal to i_1 .

$$V_{o1} - V_{o2} = i_1(R_1 + 2R_2) = \frac{1}{R_1} (V_{i1} - V_{i2}) (R_1 + 2R_2) = (V_{i1} - V_{i2}) \left(1 + \frac{2R_2}{R_1}\right).$$


$$\text{Finally, } V_o = \frac{R_4}{R_3} (V_{o2} - V_{o1}) = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right) (V_{i2} - V_{i1}).$$

This circuit is known as the “instrumentation amplifier.”

Instrumentation amplifier

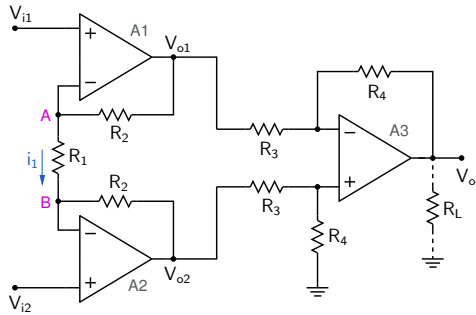


Instrumentation amplifier

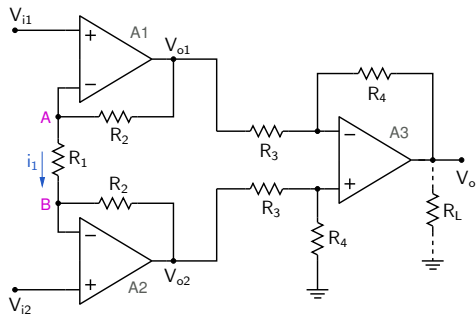


The input resistance seen from V_{i1} or V_{i2} is large (since an op-amp has a large input resistance).

Instrumentation amplifier

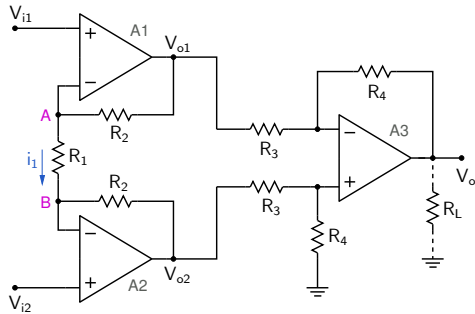


The input resistance seen from V_{i1} or V_{i2} is large (since an op-amp has a large input resistance).
→ the amplifier will not “load” the preceding stage, a desirable feature.

Instrumentation amplifier

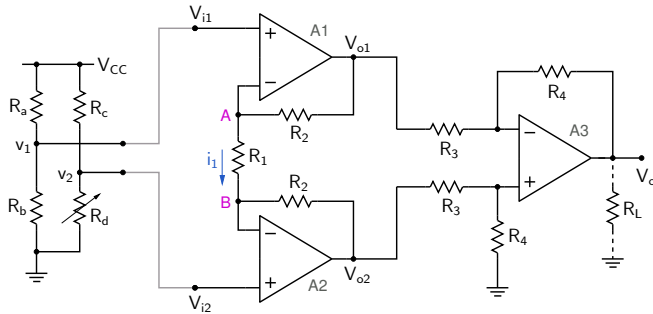

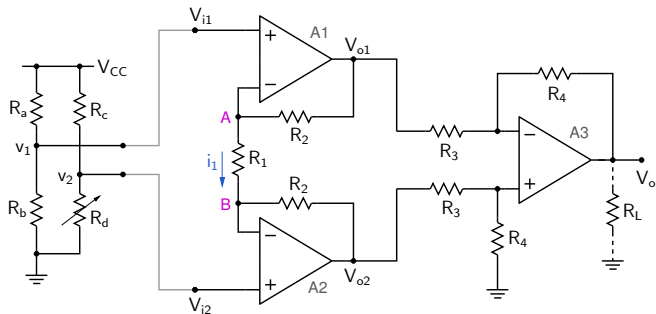The input resistance seen from V_{i1} or V_{i2} is large (since an op-amp has a large input resistance).
→ the amplifier will not “load” the preceding stage, a desirable feature.




The input resistance seen from V_{i1} or V_{i2} is large (since an op-amp has a large input resistance).

→ the amplifier will not “load” the preceding stage, a desirable feature.

As a result, the voltages v_1 and v_2 in the bridge circuit will remain essentially the same when the bridge circuit is connected to the instrumentation amplifier.

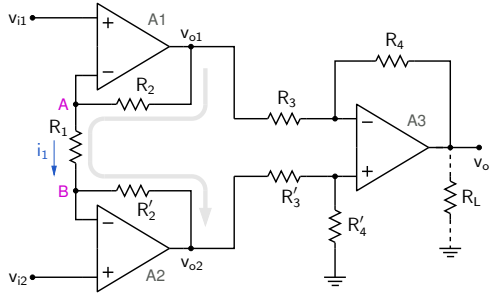
Instrumentation amplifier: common-mode rejection



$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$

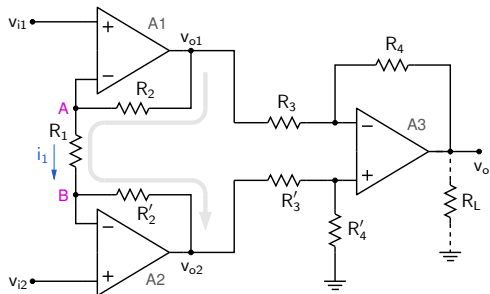Instrumentation amplifier: common-mode rejection




$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$

Note that v_{o1} serves as v_{i1} for the difference amplifier, and v_{o2} as v_{i2} . Let us find the differential-mode and common-mode components associated with v_{o1} and v_{o2} .
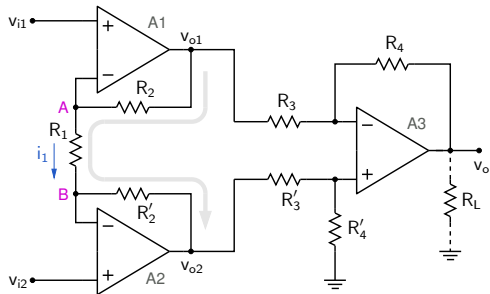
$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$




$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$

Note that v_{o1} serves as v_{i1} for the difference amplifier, and v_{o2} as v_{i2} . Let us find the differential-mode and common-mode components associated with v_{o1} and v_{o2} .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$
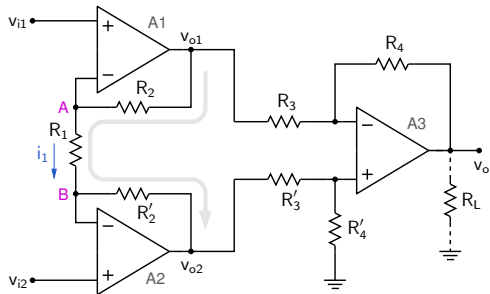
$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[\left(v_c + \frac{v_d}{2} \right) - \left(v_c - \frac{v_d}{2} \right) \right] = \left(1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$



$$v_{i1} = v_c - (v_d/2)$$


$$v_{i2} = v_c + (v_d/2)$$

Note that v_{o1} serves as v_{i1} for the difference amplifier, and v_{o2} as v_{i2} . Let us find the differential-mode and common-mode components associated with v_{o1} and v_{o2} .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$

$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[\left(v_c + \frac{v_d}{2} \right) - \left(v_c - \frac{v_d}{2} \right) \right] = \left(1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$
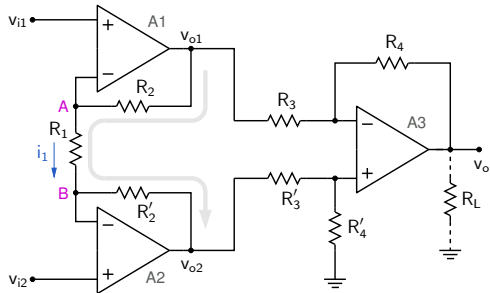
$$v'_{ic} = \frac{1}{2} \left[\left(v_c - \frac{v_d}{2} \right) + i_1 R_2 + \left(v_c + \frac{v_d}{2} \right) - i_1 R'_2 \right] \approx v_c.$$



$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$


Note that v_{o1} serves as v_{i1} for the difference amplifier, and v_{o2} as v_{i2} . Let us find the differential-mode and common-mode components associated with v_{o1} and v_{o2} .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$

$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[\left(v_c + \frac{v_d}{2} \right) - \left(v_c - \frac{v_d}{2} \right) \right] = \left(1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$

$$v'_{ic} = \frac{1}{2} \left[\left(v_c - \frac{v_d}{2} \right) + i_1 R_2 + \left(v_c + \frac{v_d}{2} \right) - i_1 R'_2 \right] \approx v_c.$$

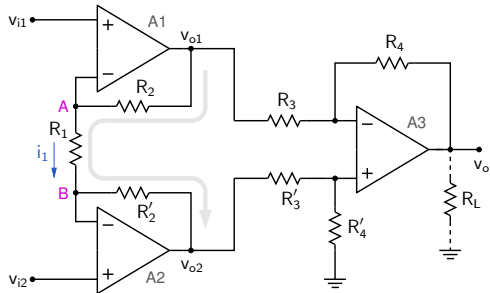→ v_d has got amplified but not v_c → overall improvement in CMRR.



$$v_{i1} = v_c - (v_d/2)$$

$$v_{i2} = v_c + (v_d/2)$$

Note that v_{o1} serves as v_{i1} for the difference amplifier, and v_{o2} as v_{i2} . Let us find the differential-mode and common-mode components associated with v_{o1} and v_{o2} .

$$v'_{id} = v_{o2} - v_{o1}, \quad v'_{ic} = \frac{1}{2} (v_{o1} + v_{o2})$$

$$v'_{id} = (R_2 + R'_2 + R_1) \frac{1}{R_1} \left[\left(v_c + \frac{v_d}{2} \right) - \left(v_c - \frac{v_d}{2} \right) \right] = \left(1 + \frac{R_2 + R'_2}{R_1} \right) v_d.$$

$$v'_{ic} = \frac{1}{2} \left[\left(v_c - \frac{v_d}{2} \right) + i_1 R_2 + \left(v_c + \frac{v_d}{2} \right) - i_1 R'_2 \right] \approx v_c.$$

→ v_d has got amplified but not v_c → overall improvement in CMRR.


(Note that resistor mismatch in the second stage needs to be considered, but it will have a limited effect.)

Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

Current-to-voltage conversion


Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

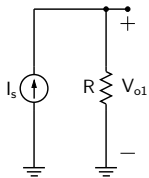Current-to-voltage conversion can be achieved by simply passing the current through a resistor: $V_{o1} = I_s R$.




Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.

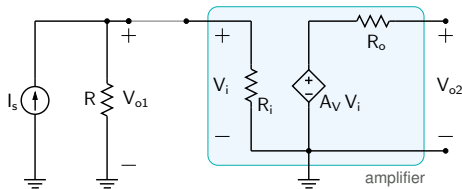Current-to-voltage conversion can be achieved by simply passing the current through a resistor: $V_{o1} = I_s R$.




However, this simple approach will not work if the next stage in the circuit (such as an amplifier) has a finite R_i , since it will modify V_{o1} to $V_{o1} = I_s (R_i \parallel R)$, which is not desirable.


Current-to-voltage conversion

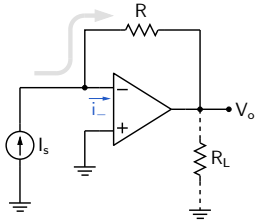

Current-to-voltage conversion

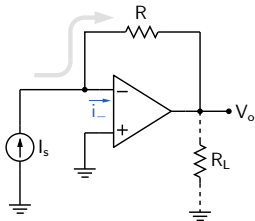

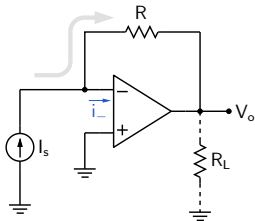
$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$



$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

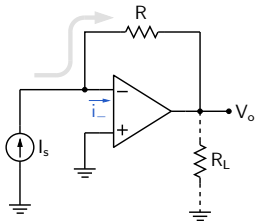
The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.



$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.


Example: a photocurrent detector.

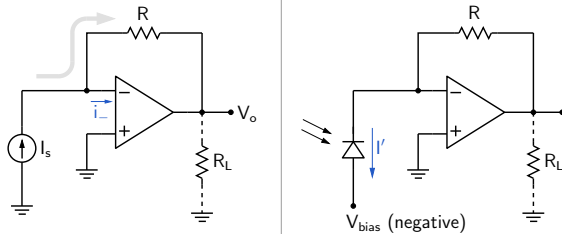

$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.

Example: a photocurrent detector.

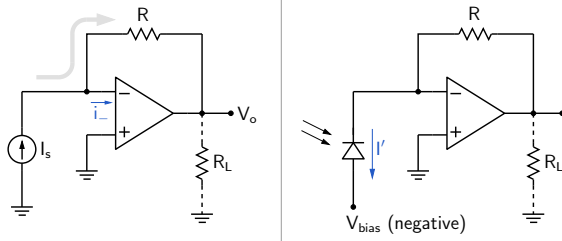


$$V_- \approx V_+, \text{ and } i_- \approx 0 \Rightarrow V_o = V_- - I_s R = -I_s R.$$

The output voltage is proportional to the source current, *irrespective* of the value of R_L , i.e., irrespective of the next stage.


Example: a photocurrent detector.

$$V_o = I' R. \text{ (Note: The diode is under a reverse bias, with } V_n = 0 \text{ V and } V_p = V_{bias}.)$$

Op-amp circuits (linear region)

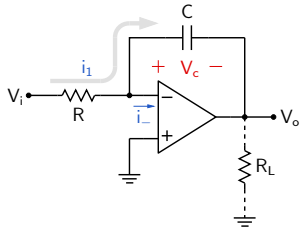


Op-amp circuits (linear region)

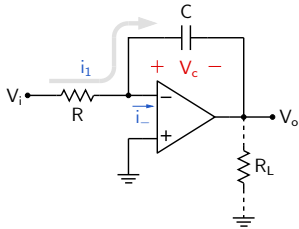

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Op-amp circuits (linear region)

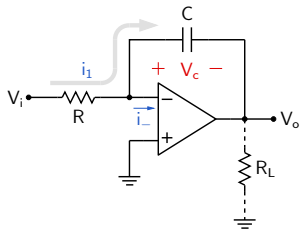


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i/R.$$

Since $i_- \approx 0$, the current through the capacitor is i_1 .

$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

Op-amp circuits (linear region)

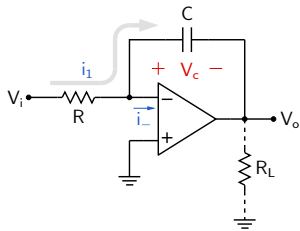


$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Since $i_- \approx 0$, the current through the capacitor is i_1 .

$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

$$V_c = V_- - V_o = 0 - V_o = -V_o \rightarrow C \left(-\frac{dV_o}{dt} \right) = \frac{V_i}{R}$$

Op-amp circuits (linear region)

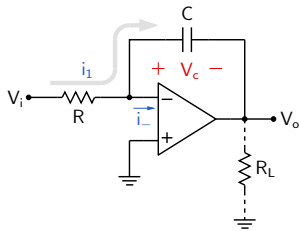

$$V_- \approx V_+ = 0 \text{ V} \rightarrow i_1 = V_i / R.$$

Since $i_- \approx 0$, the current through the capacitor is i_1 .



$$\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_i}{R}.$$

$$V_c = V_- - V_o = 0 - V_o = -V_o \rightarrow C \left(-\frac{dV_o}{dt} \right) = \frac{V_i}{R}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

The circuit works as an integrator.



Integrator

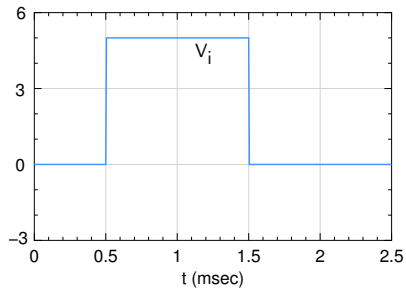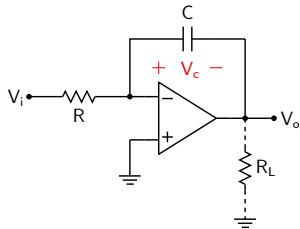

Given: $R = 10 \text{ k}$, $C = 0.2 \mu\text{F}$.

If $V_o = 0 \text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5 \text{ msec}$, $t_1 = 1.5 \text{ msec}$).

Integrator

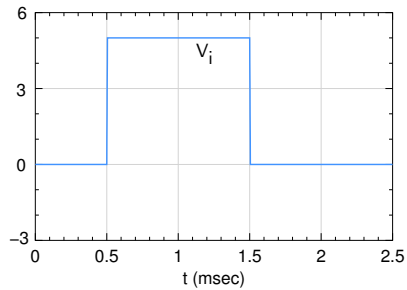
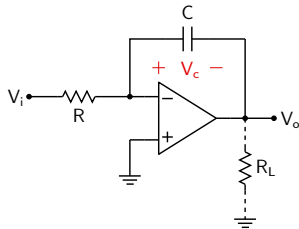


Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.

If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

Integrator

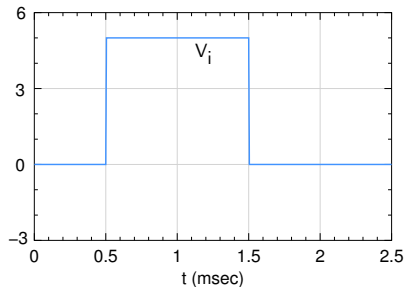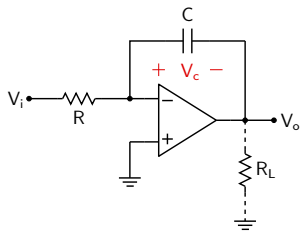



Given: $R = 10 \text{ k}$, $C = 0.2 \mu\text{F}$.

If $V_o = 0 \text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5 \text{ msec}$, $t_1 = 1.5 \text{ msec}$).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2 \text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0 \text{ V}$$

Integrator

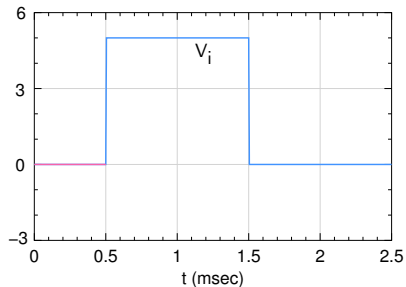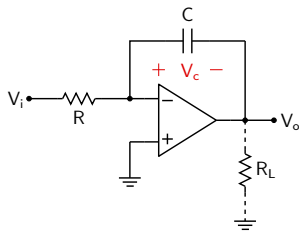



Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.

If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$

Integrator

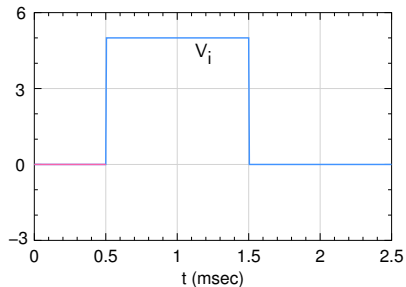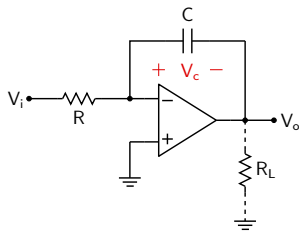

Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.



If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$

$$* \text{ For } t_0 < t < t_1, V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow \text{a straight line with a negative slope}$$

Integrator

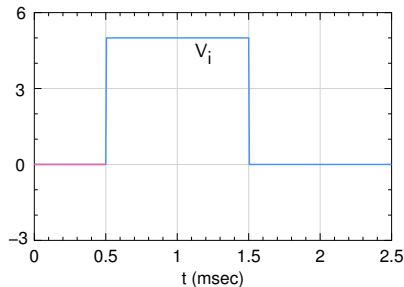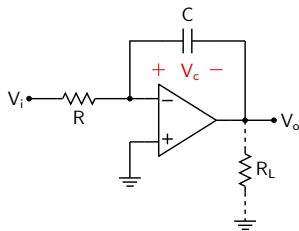

Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.

If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).



$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

* For $t < t_0$, $V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$

* For $t_0 < t < t_1$, $V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow$ a straight line with a negative slope

At $t = t_1$, $V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$

Integrator

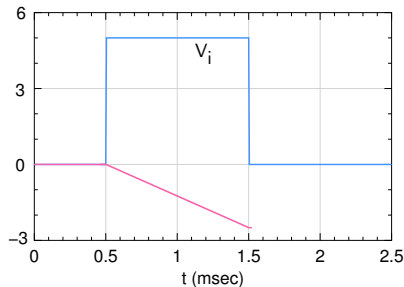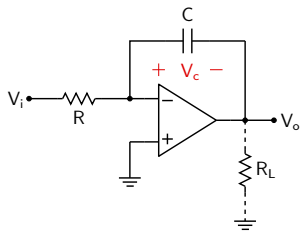

Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.

If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).



$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

* For $t < t_0$, $V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$

* For $t_0 < t < t_1$, $V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow$ a straight line with a negative slope

At $t = t_1$, $V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$

Integrator

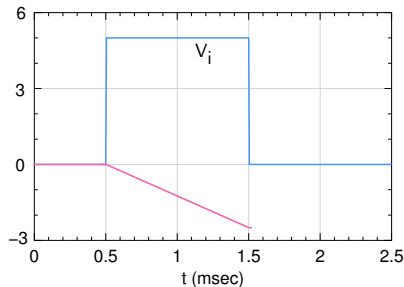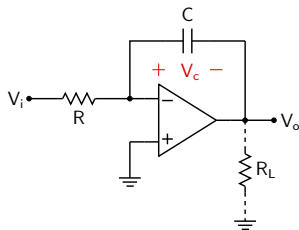

Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.

If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).



$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

* For $t < t_0$, $V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$

* For $t_0 < t < t_1$, $V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow$ a straight line with a negative slope

$$\text{At } t = t_1, V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$$

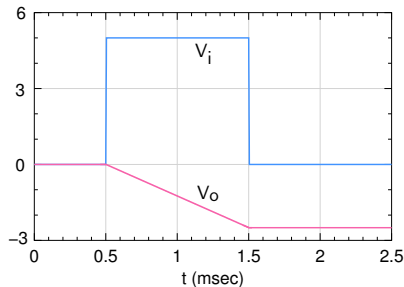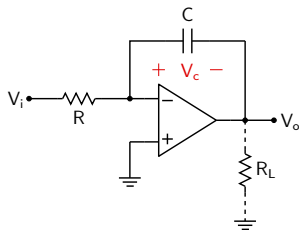* For $t > t_1$, $V_o(t)$ remains constant since $V_i = 0\text{ V}$.



Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.

If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).



$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

* For $t < t_0$, $V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$

* For $t_0 < t < t_1$, $V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow$ a straight line with a negative slope

At $t = t_1$, $V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$

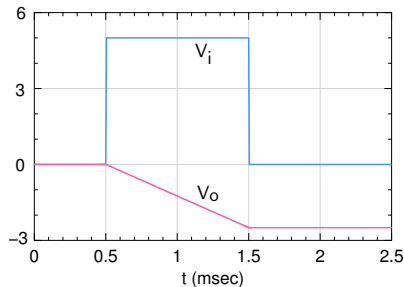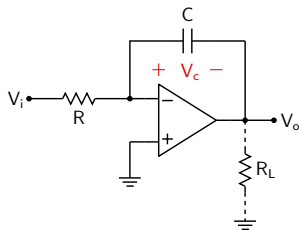* For $t > t_1$, $V_o(t)$ remains constant since $V_i = 0\text{ V}.$



Given: $R = 10\text{ k}$, $C = 0.2\text{ }\mu\text{F}$.

If $V_o = 0\text{ V}$ at $t = 0$, find $V_o(t)$ (Let $t_0 = 0.5\text{ msec}$, $t_1 = 1.5\text{ msec}$).

$$V_o = -\frac{1}{RC} \int V_i dt, \quad \tau \equiv RC = 2\text{ msec}.$$

$$* \text{ For } t < t_0, V_o(t) - V_o(0) = -\frac{1}{\tau} \int_0^t 0 dt' = 0 \rightarrow V_o(t) = V_o(0) = 0\text{ V}$$



$$* \text{ For } t_0 < t < t_1, V_o(t) - V_o(t_0) = -\frac{1}{\tau} \int_{t_0}^t 5 dt' = -\frac{1}{\tau} 5(t - t_0) \rightarrow \text{a straight line with a negative slope}$$

$$\text{At } t = t_1, V(t_1) - V(t_0) = -\frac{1}{2\text{ msec}} 5\text{ V} \times 1\text{ msec} = -2.5\text{ V} \rightarrow V_o(t_1) = -2.5\text{ V}.$$



$$* \text{ For } t > t_1, V_o(t) \text{ remains constant since } V_i = 0\text{ V}.$$

SEQUEL file: ee101_integrator_1.sqproj



Integrator

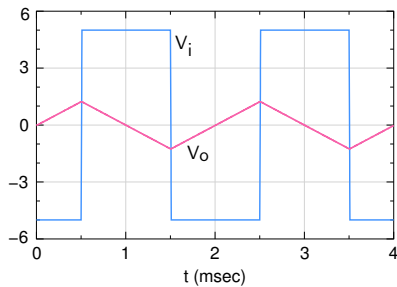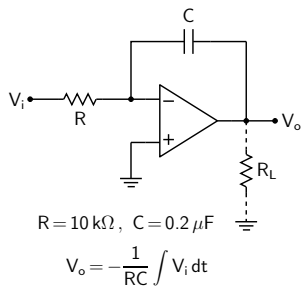

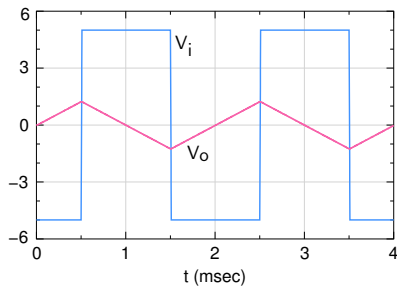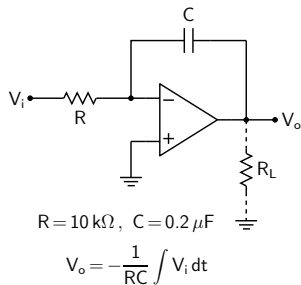- * An integrator can be used to convert a square wave to a triangle wave.



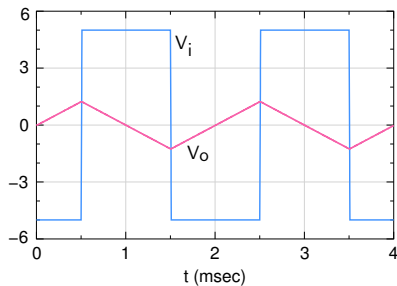
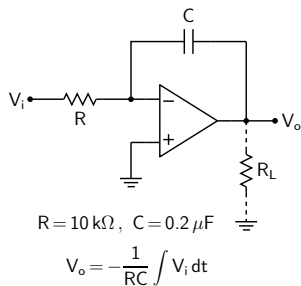
- * An integrator can be used to convert a square wave to a triangle wave.
- * In practice, the circuit needs a small modification, as discussed in the following.







- * An integrator can be used to convert a square wave to a triangle wave.
- * In practice, the circuit needs a small modification, as discussed in the following.

SEQUEL file: ee101_integrator_2.sqproj





Practical op-amps: Offset voltage

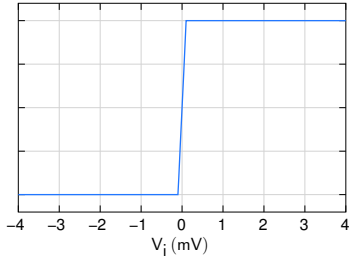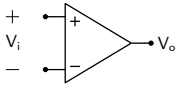

Practical op-amps: Offset voltage

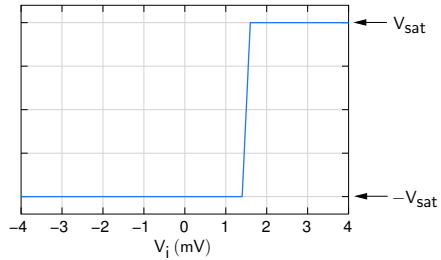
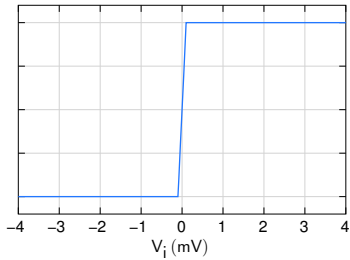
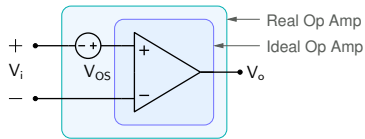
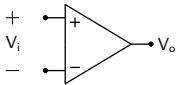


Practical op-amps: Offset voltage

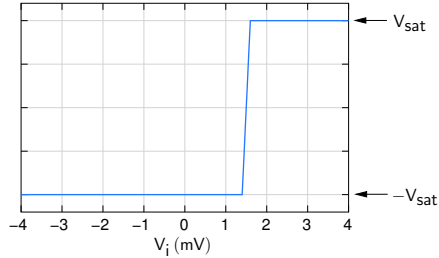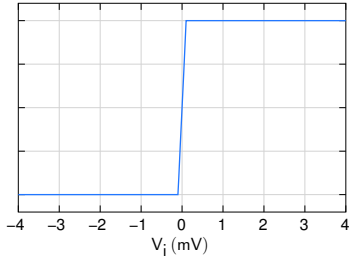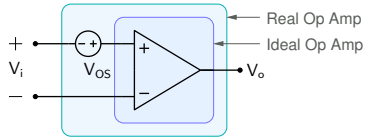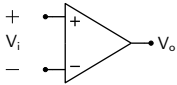

For the real op-amp, $V_o = A_V((V_+ + V_{os}) - V_-)$.





Practical op-amps: Offset voltage

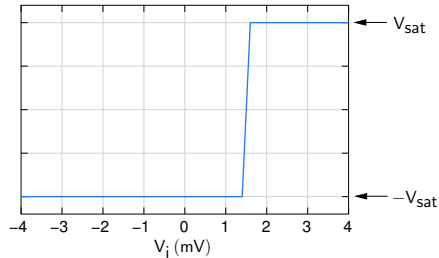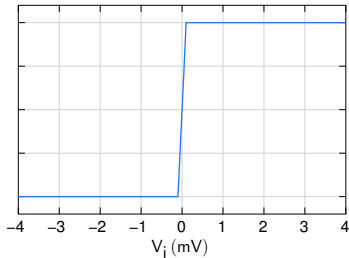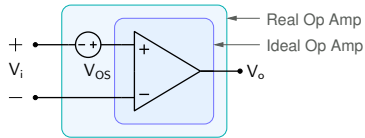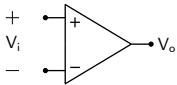

For the real op-amp, $V_o = A_V((V_+ + V_{OS}) - V_-)$.

For $V_o = 0$ V, $V_+ + V_{OS} - V_- = 0 \rightarrow V_i = V_+ - V_- = -V_{OS}$.

Practical op-amps: Offset voltage

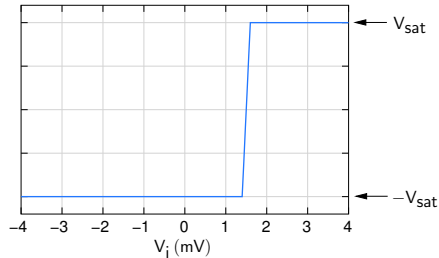
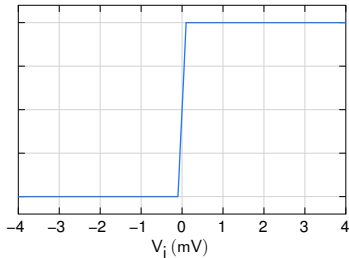
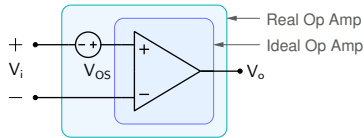
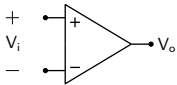


For the real op-amp, $V_o = A_V((V_+ + V_{OS}) - V_-)$.

For $V_o = 0$ V, $V_+ + V_{OS} - V_- = 0 \rightarrow V_i = V_+ - V_- = -V_{OS}$.

V_o versus V_i curve gets shifted (Note: V_{OS} is negative in the above example).

Practical op-amps: Offset voltage

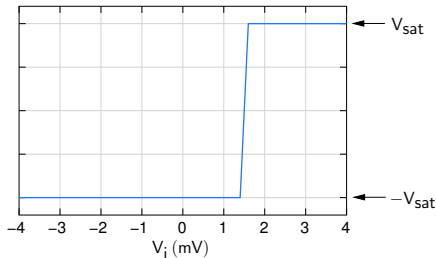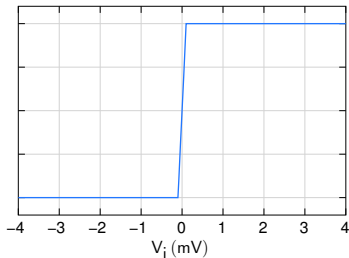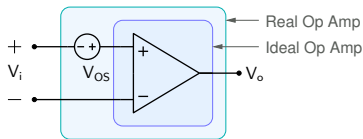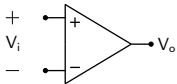


For the real op-amp, $V_o = A_V((V_+ + V_{OS}) - V_-)$.

For $V_o = 0$ V, $V_+ + V_{OS} - V_- = 0 \rightarrow V_i = V_+ - V_- = -V_{OS}$.


V_o versus V_i curve gets shifted (Note: V_{OS} is negative in the above example).

741: $-6 \text{ mV} < V_{OS} < 6 \text{ mV}$, OP-77: $-50 \mu\text{V} < V_{OS} < 50 \mu\text{V}$.

Effect of V_{OS} : inverting amplifier

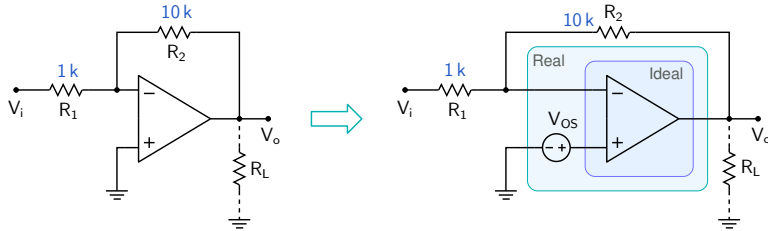


Effect of V_{OS} : inverting amplifier

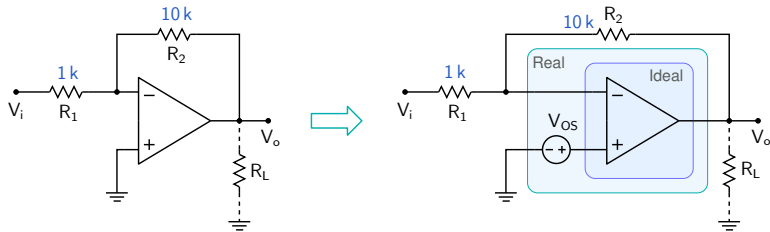

By superposition, $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1}\right).$


Effect of V_{OS} : inverting amplifier

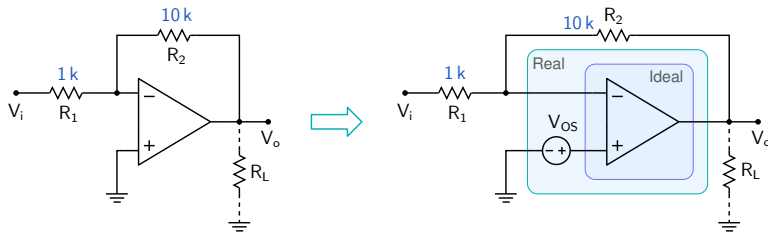

By superposition, $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1}\right)$.

For $V_{OS} = 2\text{ mV}$, the contribution from V_{OS} to V_o is 22 mV ,

Effect of V_{OS} : inverting amplifier

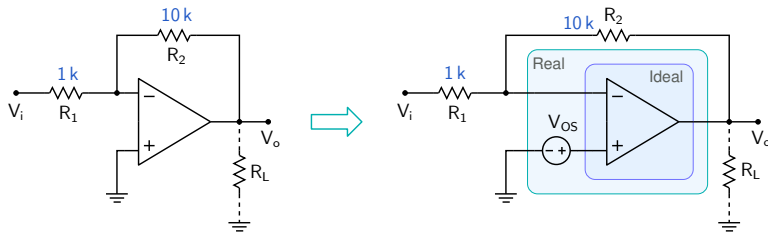



By superposition, $V_o = -\frac{R_2}{R_1} V_i + V_{OS} \left(1 + \frac{R_2}{R_1}\right)$.

For $V_{OS} = 2\text{ mV}$, the contribution from V_{OS} to V_o is 22 mV ,

i.e., a DC shift of 22 mV .


Effect of V_{OS} : integrator

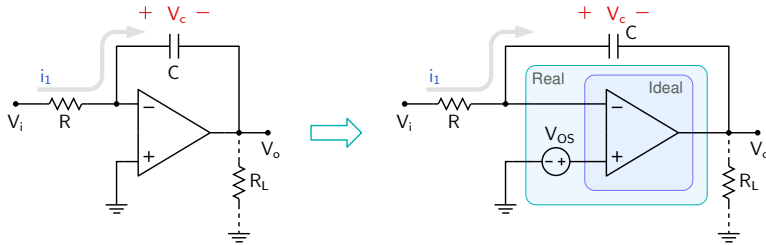

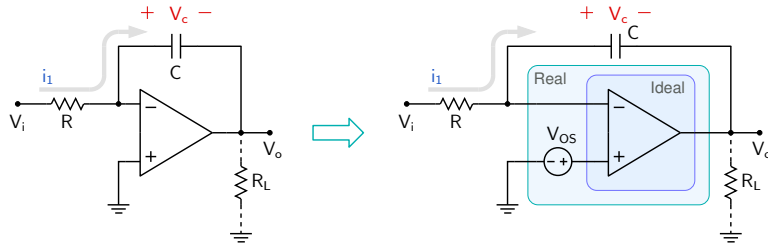

$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$


Effect of V_{OS} : integrator

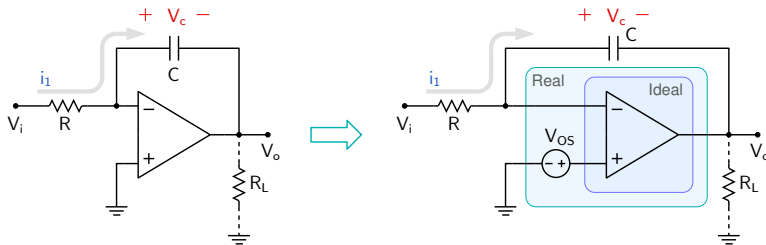

$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$

$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$

Effect of V_{OS} : integrator

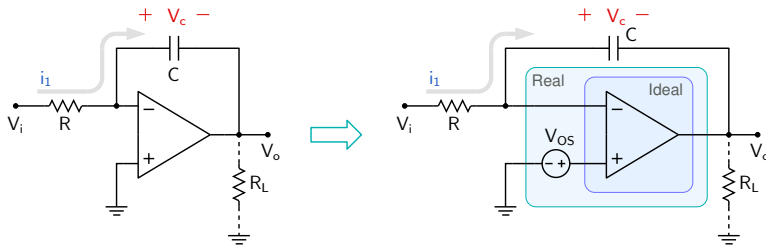


$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$

$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$

Even with $V_i = 0$ V, V_c will keep rising or falling (depending on the sign of V_{OS}).

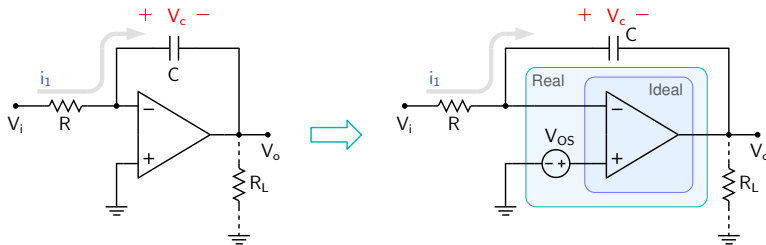Eventually, the Op Amp will be driven into saturation.



$$V_- \approx V_+ = V_{OS} \rightarrow i_1 = \frac{1}{R}(V_i - V_{OS}) = C \frac{dV_c}{dt}.$$



$$\text{i.e., } V_c = \frac{1}{RC} \int (V_i - V_{OS}) dt.$$


Even with $V_i = 0$ V, V_c will keep rising or falling (depending on the sign of V_{OS}).

Eventually, the Op Amp will be driven into saturation.


→ need to address this issue!

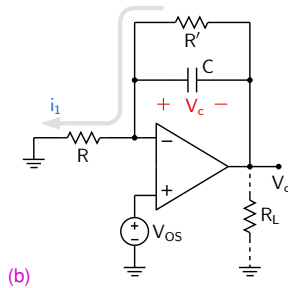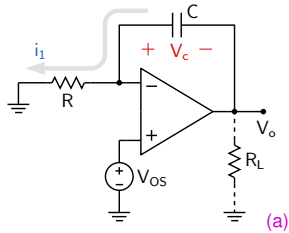Effect of V_{OS} : integrator with $V_i = 0$



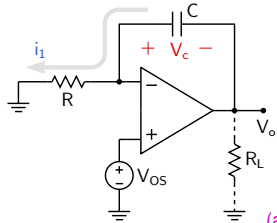


(a)

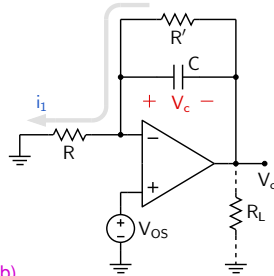


(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$
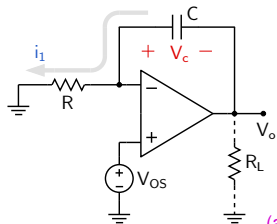
$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$



(a)

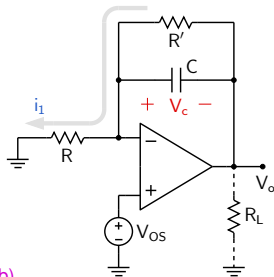


(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$


$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

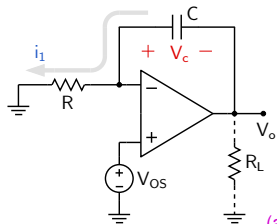(b) There is a DC path for the current.

$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$



(a)

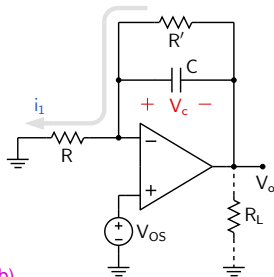

(b)


$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$

$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

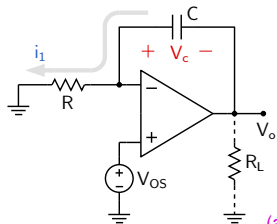
(b) There is a DC path for the current.

$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

R' should be small enough to have a negligible effect on V_o .



(a)

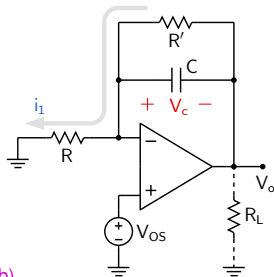

(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$


$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

(b) There is a DC path for the current.


$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

R' should be small enough to have a negligible effect on V_o .

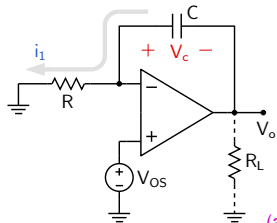However, R' must be large enough to ensure that the circuit still functions as an integrator.



(a)

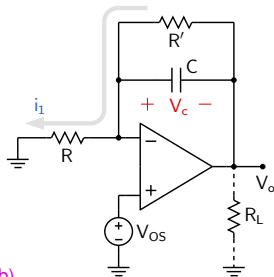

(b)

$$(a) \quad i_1 = \frac{V_{OS}}{R} = -C \frac{dV_c}{dt}$$

$$V_c = -\frac{1}{RC} \int V_{OS} dt \rightarrow \text{op-amp saturates.}$$

(b) There is a DC path for the current.


$$\rightarrow V_o = \left(1 + \frac{R'}{R}\right) V_{OS}.$$

R' should be small enough to have a negligible effect on V_o .

However, R' must be large enough to ensure that the circuit still functions as an integrator.


$\rightarrow R' \gg 1/\omega C$ at the frequency of interest.

Op-amp 741: offset null

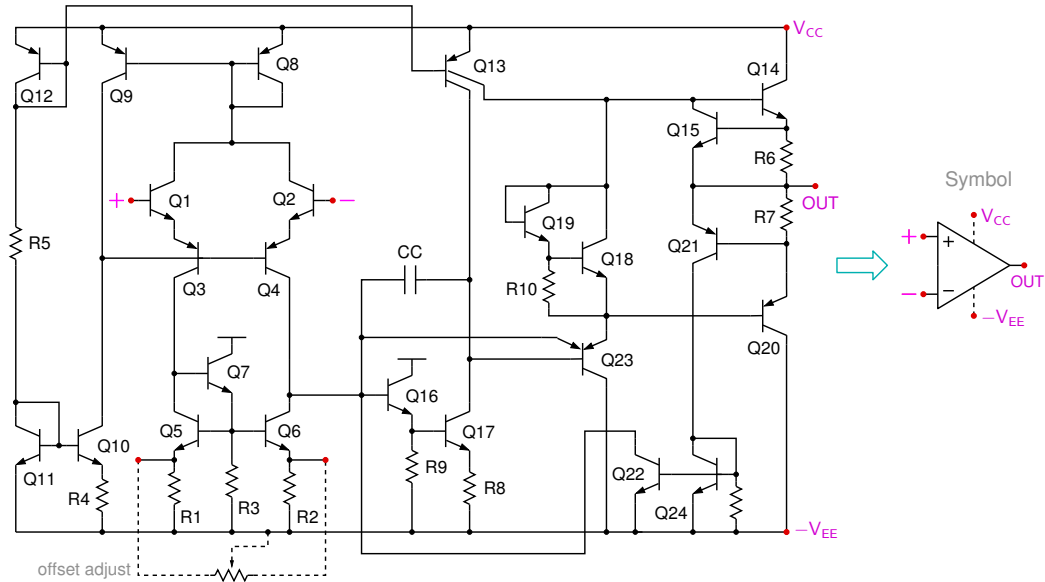



Input bias currents

741

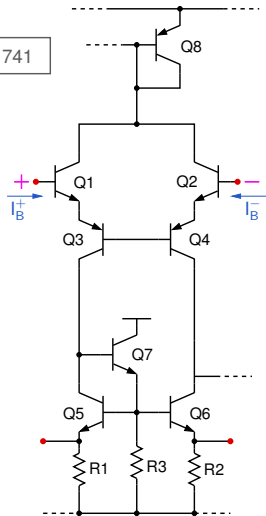



Input bias currents

741

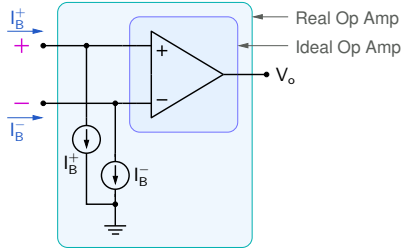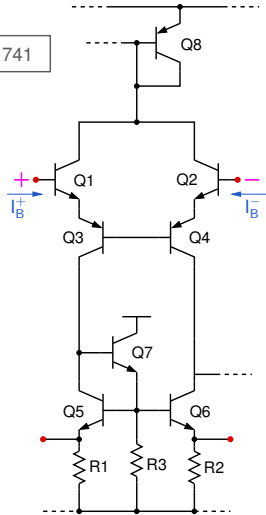

Input bias currents

741

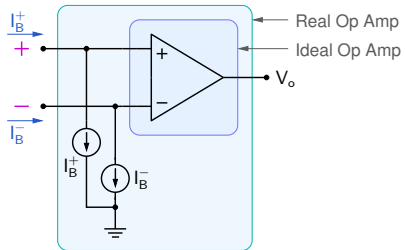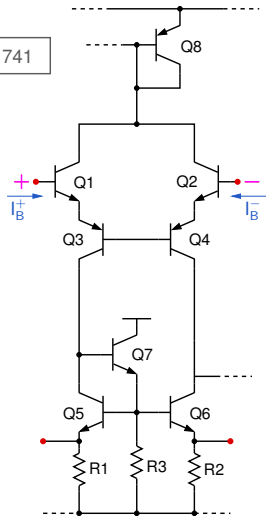



I_B^+ and I_B^- are generally not equal.

$|I_B^+ - I_B^-|$: "offset current" (I_{OS})

$(I_B^+ + I_B^-)/2$: "bias current" (I_B)

Input bias currents

741

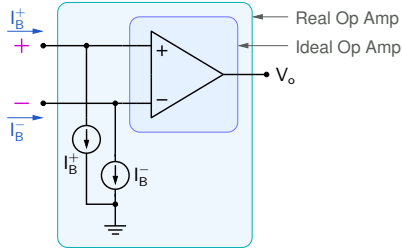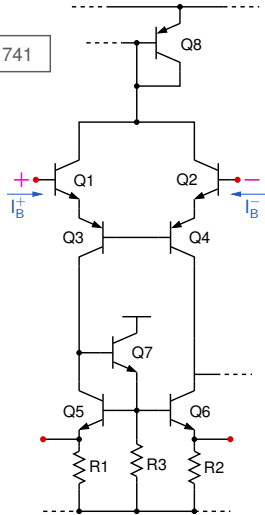


Typical values


Op-Amp	I_B	I_{OS}	V_{OS}	Type
741	80 nA	20 nA	1 mV	BJT input
OP77	1.2 nA	0.3 nA	$10 \mu V$	BJT input
411	50 pA	25 pA	0.8 mV	FET input

I_B^+ and I_B^- are generally not equal.
 $|I_B^+ - I_B^-|$: "offset current" (I_{OS})
 $(I_B^+ + I_B^-)/2$: "bias current" (I_B)

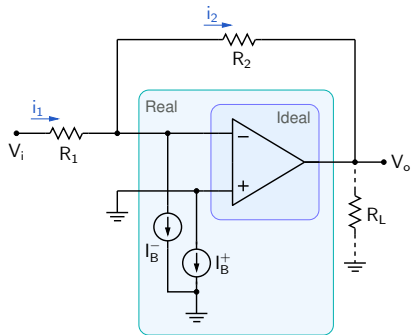Effect of bias currents: inverting amplifier




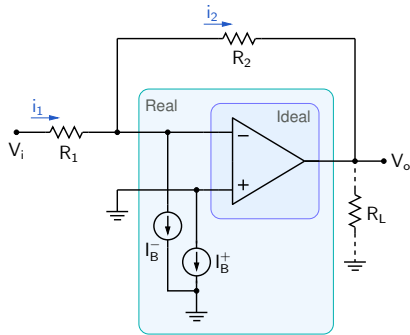Effect of bias currents: inverting amplifier



Assume that the op-amp is ideal in other respects (including $V_{OS} = 0\text{ V}$).

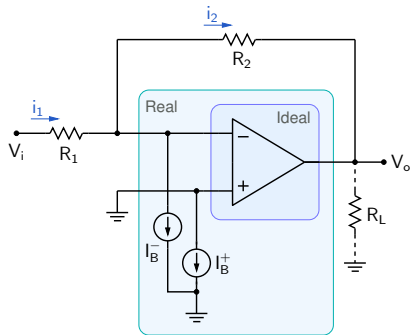
Effect of bias currents: inverting amplifier



Assume that the op-amp is ideal in other respects (including $V_{OS} = 0\text{ V}$).

$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i / R_1.$$

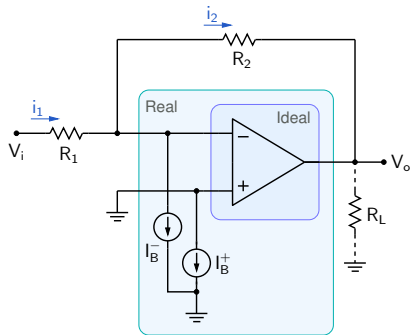Effect of bias currents: inverting amplifier




Assume that the op-amp is ideal in other respects (including $V_{OS} = 0\text{ V}$).

$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i / R_1.$$

$$i_2 = i_1 - I_B^- \rightarrow V_o = V_- - i_2 R_2 = 0 - \left(\frac{V_i}{R_1} - I_B^- \right) R_2 = -\frac{R_2}{R_1} V_i + I_B^- R_2,$$

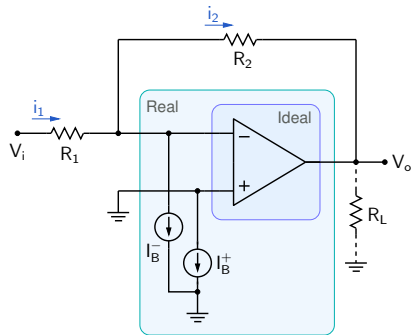Effect of bias currents: inverting amplifier



Assume that the op-amp is ideal in other respects (including $V_{OS} = 0\text{ V}$).


$$V_- \approx V_+ = 0\text{ V} \rightarrow i_1 = V_i / R_1.$$

$$i_2 = i_1 - I_B^- \rightarrow V_o = V_- - i_2 R_2 = 0 - \left(\frac{V_i}{R_1} - I_B^- \right) R_2 = -\frac{R_2}{R_1} V_i + I_B^- R_2,$$


i.e., the bias current causes a DC shift in V_o .

$$\text{For } I_B^- = 80\text{ nA}, R_2 = 10\text{ k}, \Delta V_o = 0.8\text{ mV}.$$

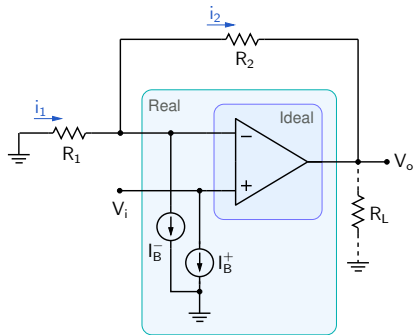Effect of bias currents: non-inverting amplifier




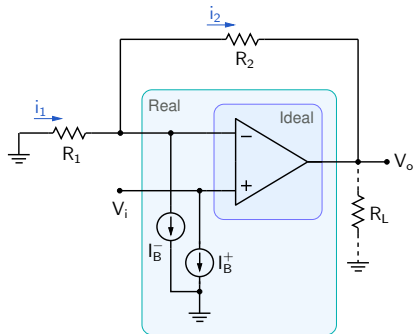Effect of bias currents: non-inverting amplifier



Assume that the op-amp is ideal in other respects (including $V_{OS} = 0$ V).

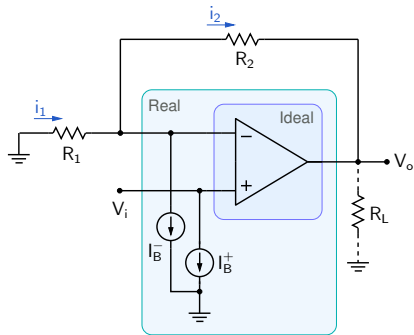
Effect of bias currents: non-inverting amplifier



Assume that the op-amp is ideal in other respects (including $V_{OS} = 0$ V).

$$V_- \approx V_+ = V_i \rightarrow i_1 = \frac{0 - V_i}{R_1} = -\frac{V_i}{R_1}.$$

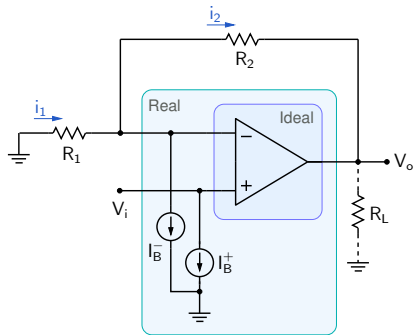Effect of bias currents: non-inverting amplifier




Assume that the op-amp is ideal in other respects (including $V_{OS} = 0$ V).

$$V_- \approx V_+ = V_i \rightarrow i_1 = \frac{0 - V_i}{R_1} = -\frac{V_i}{R_1}.$$

$$i_2 = i_1 - I_B^- = -\frac{V_i}{R_1} - I_B^-.$$

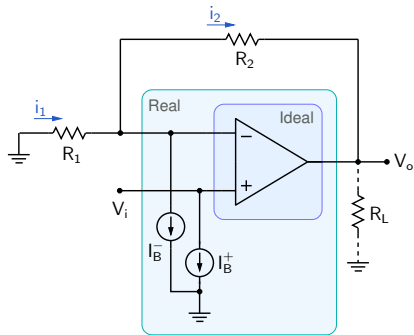Effect of bias currents: non-inverting amplifier



Assume that the op-amp is ideal in other respects (including $V_{OS} = 0$ V).


$$V_- \approx V_+ = V_i \rightarrow i_1 = \frac{0 - V_i}{R_1} = -\frac{V_i}{R_1}.$$

$$i_2 = i_1 - I_B^- = -\frac{V_i}{R_1} - I_B^-.$$


$$V_o = V_- - i_2 R_2 = V_i - \left(-\frac{V_i}{R_1} - I_B^- \right) R_2 = V_i \left(1 + \frac{R_2}{R_1} \right) + I_B^- R_2.$$

→ Again, a DC shift ΔV_o .

Effect of bias currents: integrator

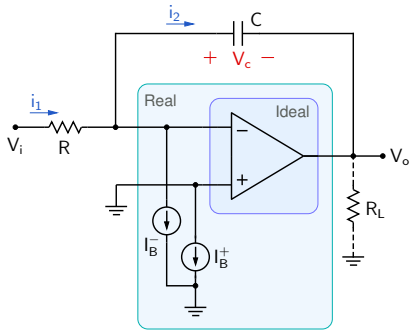


Effect of bias currents: integrator

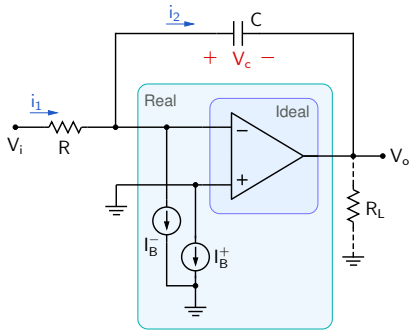

Even with $V_i = 0 \text{ V}$, $V_c = \frac{1}{C} \int -I_B^- dt$ will drive the op-amp into saturation.


Effect of bias currents: integrator

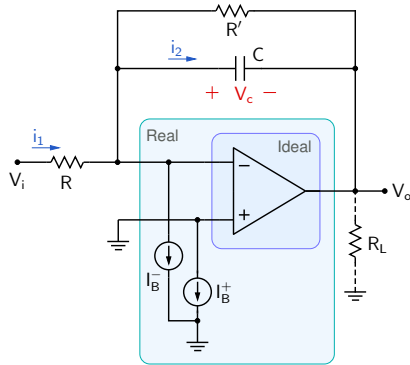

Even with $V_i = 0$ V, $V_c = \frac{1}{C} \int -I_B^- dt$ will drive the op-amp into saturation.

Connecting R' across C provides a DC path for the current, and results in a DC shift $\Delta V_o = I_B^- R'$ at the output.

Effect of bias currents: integrator

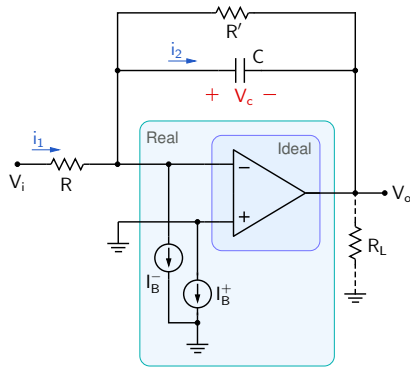


Even with $V_i = 0$ V, $V_c = \frac{1}{C} \int -I_B^- dt$ will drive the op-amp into saturation.

Connecting R' across C provides a DC path for the current, and results in a DC shift $\Delta V_o = I_B^- R'$ at the output.


As we have discussed earlier, R' should be small enough to have a negligible effect on V_o .



However, R' must be large enough to ensure that the circuit still functions as an integrator.

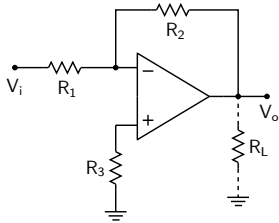Effect of bias currents: inverting amplifier




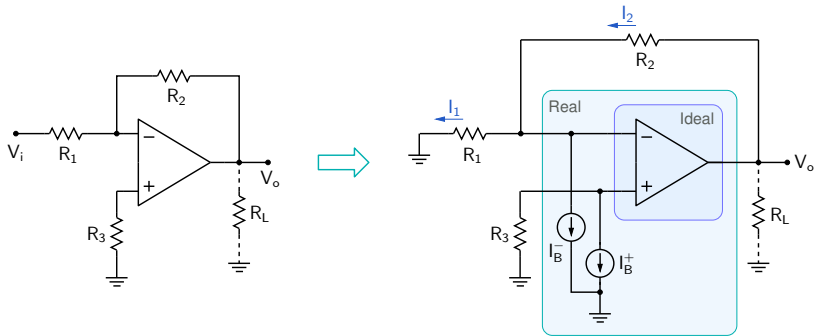Effect of bias currents: inverting amplifier



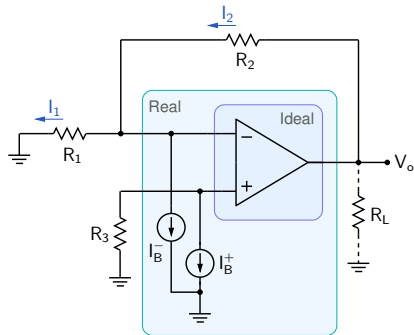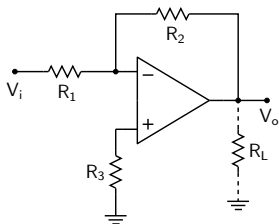

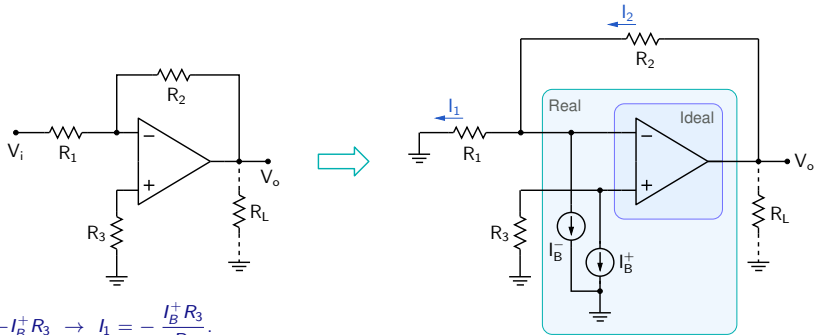
$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$



$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

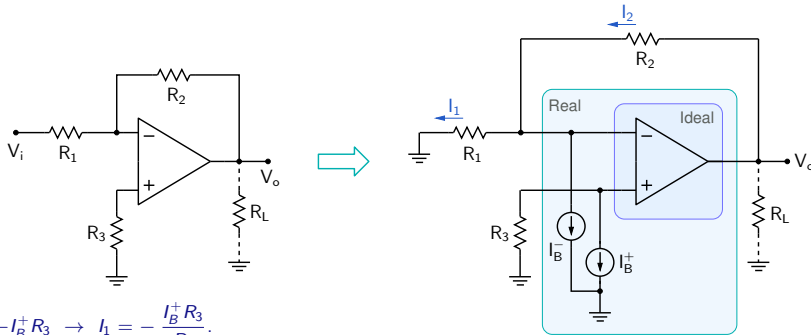
$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left(-\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left(1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$



$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left(-\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left(1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$
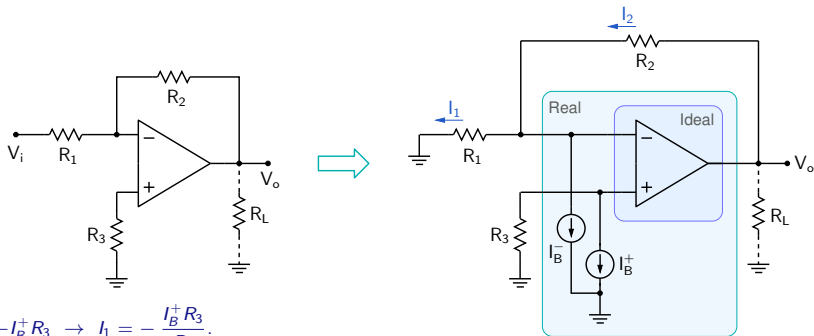
$$\text{Using } I_B = \frac{I_B^+ + I_B^-}{2}, I_{OS} = I_B^+ - I_B^-, \text{ i.e., } I_B^+ = I_B + \frac{I_{OS}}{2}, I_B^- = I_B - \frac{I_{OS}}{2}, \text{ we get}$$




$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left(-\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left(1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$

Using $I_B = \frac{I_B^+ + I_B^-}{2}$, $I_{OS} = I_B^+ - I_B^-$, i.e., $I_B^+ = I_B + \frac{I_{OS}}{2}$, $I_B^- = I_B - \frac{I_{OS}}{2}$, we get
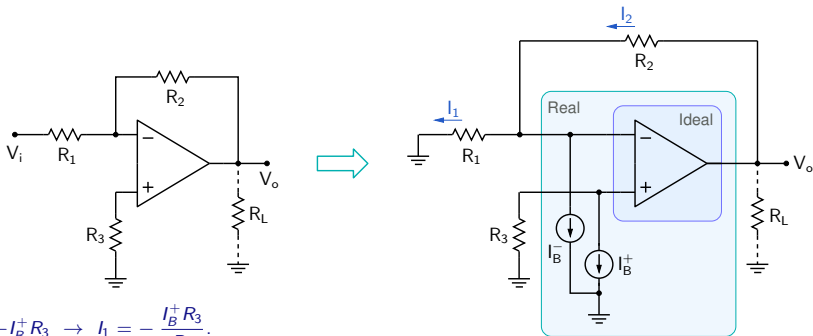
$$V_o = -R_3 \left(1 + \frac{R_2}{R_1} \right) \left(I_B + \frac{I_{OS}}{2} \right) + R_2 \left(I_B - \frac{I_{OS}}{2} \right) = \left(1 + \frac{R_2}{R_1} \right) \left\{ [(R_1 \parallel R_2) - R_3] I_B - [(R_1 \parallel R_2) + R_3] \frac{I_{OS}}{2} \right\}$$



$$V_- \approx V_+ = -I_B^+ R_3 \rightarrow I_1 = -\frac{I_B^+ R_3}{R_1}.$$

$$V_o = V_- + I_2 R_2 = -I_B^+ R_3 + R_2 \left(-\frac{I_B^+ R_3}{R_1} + I_B^- \right) = -\left(1 + \frac{R_2}{R_1} \right) I_B^+ R_3 + I_B^- R_2.$$

Using $I_B = \frac{I_B^+ + I_B^-}{2}$, $I_{OS} = I_B^+ - I_B^-$, i.e., $I_B^+ = I_B + \frac{I_{OS}}{2}$, $I_B^- = I_B - \frac{I_{OS}}{2}$, we get

$$V_o = -R_3 \left(1 + \frac{R_2}{R_1} \right) \left(I_B + \frac{I_{OS}}{2} \right) + R_2 \left(I_B - \frac{I_{OS}}{2} \right) = \left(1 + \frac{R_2}{R_1} \right) \left\{ [(R_1 \parallel R_2) - R_3] I_B - [(R_1 \parallel R_2) + R_3] \frac{I_{OS}}{2} \right\}$$

The first term can be made zero if we select $R_3 = R_1 \parallel R_2$.

$\rightarrow V_o = -R_2 I_{OS}$ (Compare with $V_o = R_2 I_B^-$ when R_3 is not connected.)

- * For the integrator, V_{OS} and I_B will lead to saturation unless a DC path (a resistor) is provided.

Should we worry about V_{OS} and I_B ?

- * For the integrator, V_{OS} and I_B will lead to saturation unless a DC path (a resistor) is provided.
- * In AC applications (e.g., audio), the DC shift arising due to V_{OS} or I_B is of no consequence since a coupling capacitor will block it anyway.

Should we worry about V_{OS} and I_B ?

- * For the integrator, V_{OS} and I_B will lead to saturation unless a DC path (a resistor) is provided.
- * In AC applications (e.g., audio), the DC shift arising due to V_{OS} or I_B is of no consequence since a coupling capacitor will block it anyway.
- * A DC shift is a matter of concern when the output is expected to be a DC (or slowly varying) quantity, e.g., a temperature sensor or a strain gauge circuit.