


Review :

1. Buck – Boost: $\frac{DV_{DC}}{1-D}$

$$\therefore I_0 = \frac{1-D}{D} I_s$$

2. Cuk' Converter: $\frac{DV_{DC}}{1-D}$

$$\therefore I_0 = \frac{1-D}{D} I_s$$


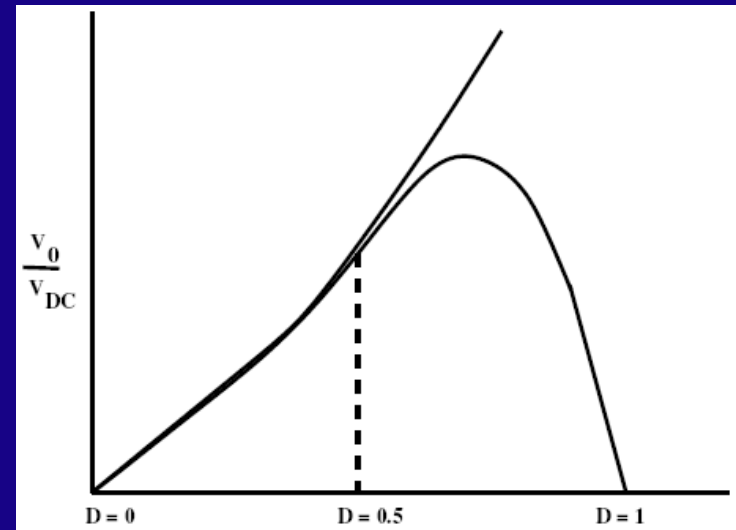




$$I_2 D T = I_s (1 - D) T$$



$$\text{Av. } I_2 = I_0$$

$$\therefore I_0 D T = I_s (1 - D) T$$

$$\Rightarrow I_0 = \frac{I_s (1 - D)}{D}$$

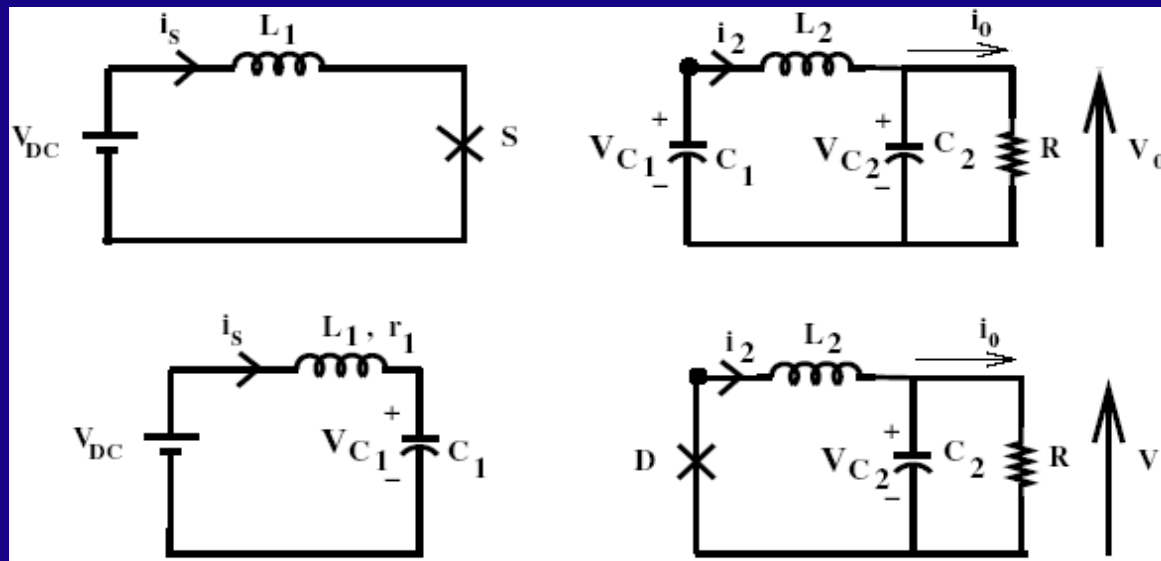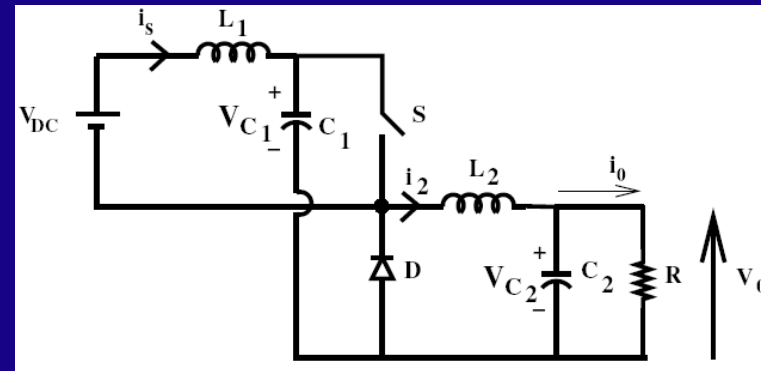

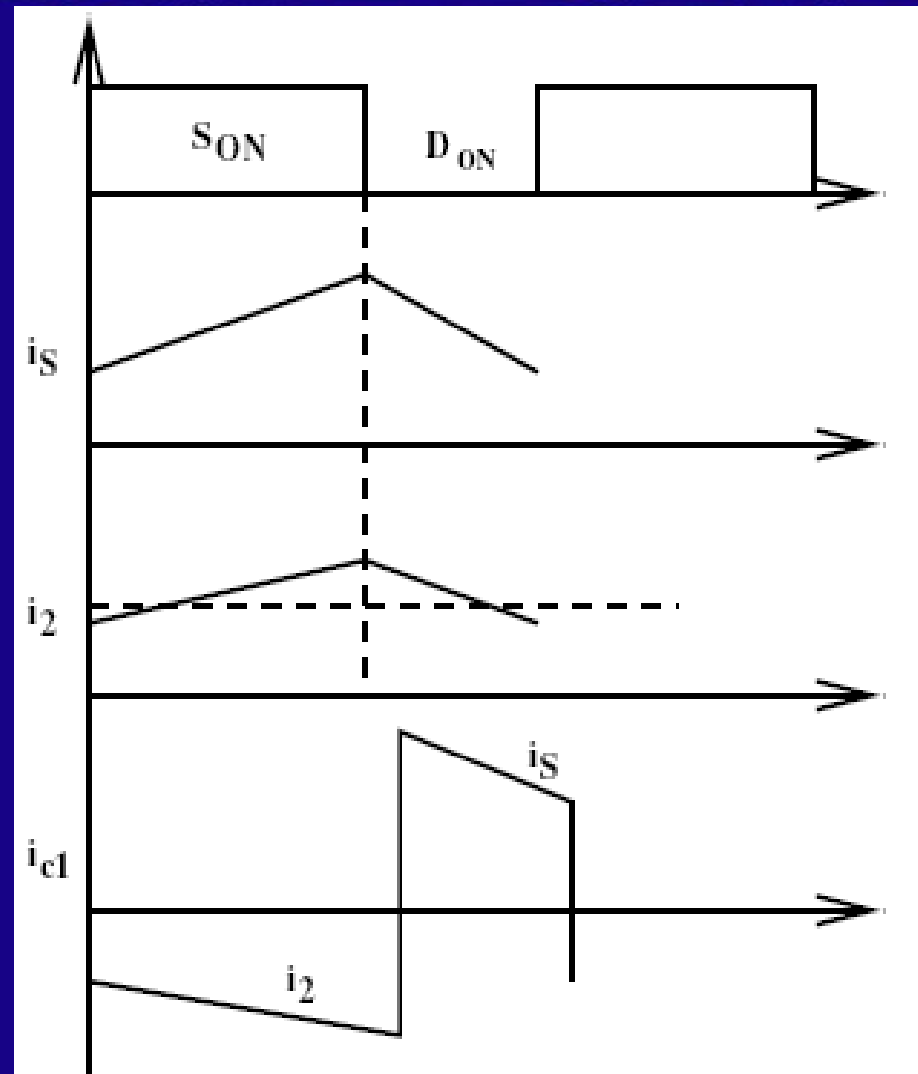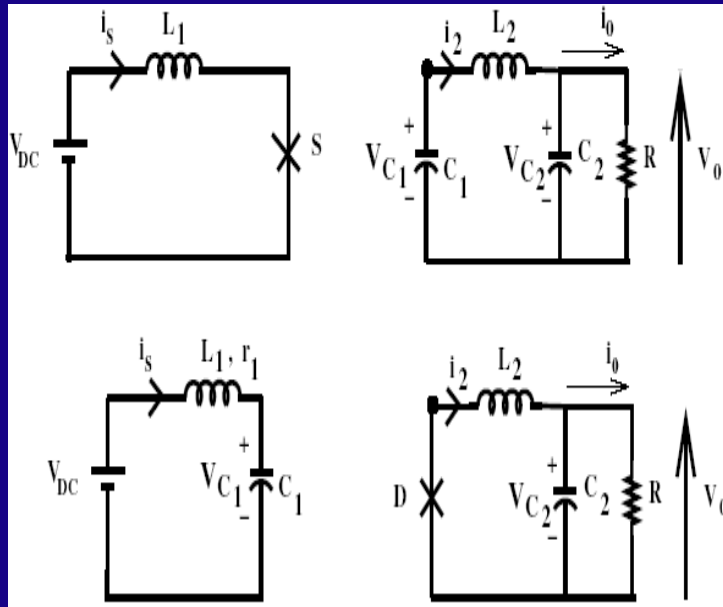

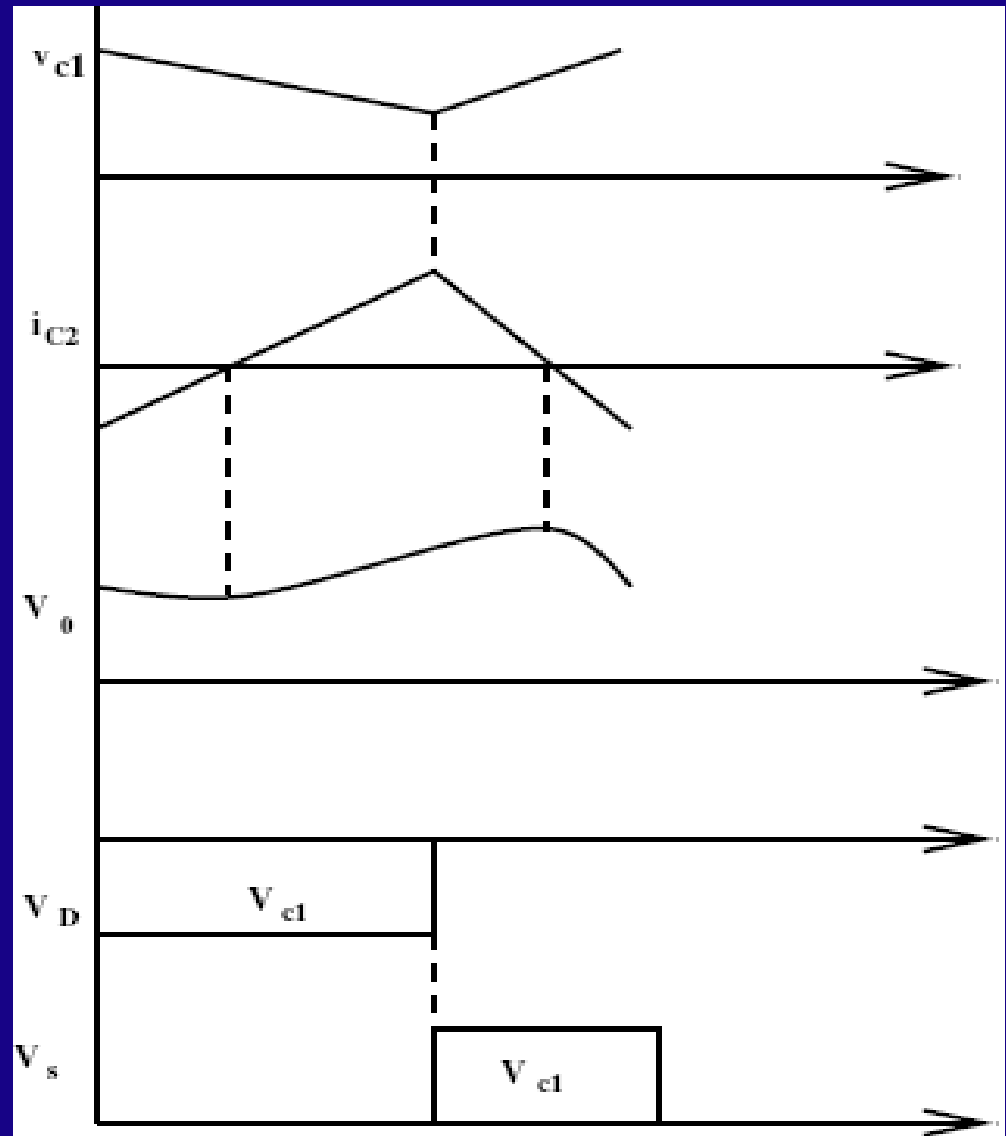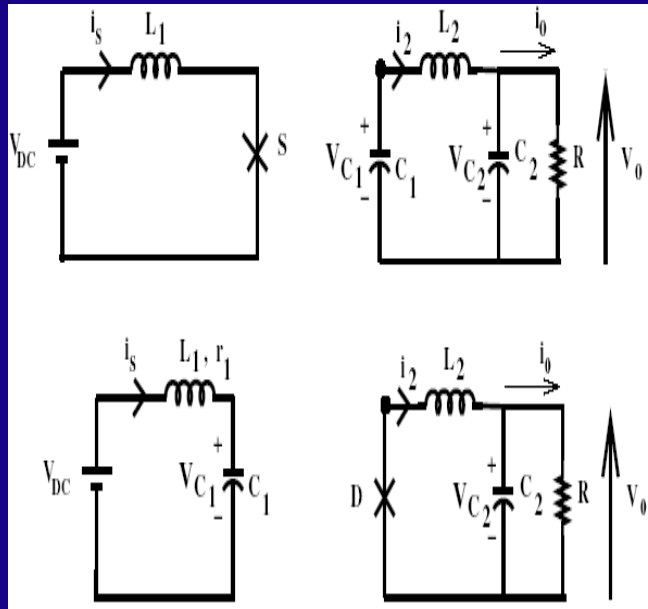

Problem 1:

$r_a \approx 0$, Total 'L' in circuit = 50 mH.

Switching frequency = 500 Hz and $d = 0.5$


Av. current drawn by the motor = 10A.

Assume that i_L is continuous.

Determine I_{\max} and I_{\min} .

Sol:

$$E_b = V_{DC} * D = 100V$$

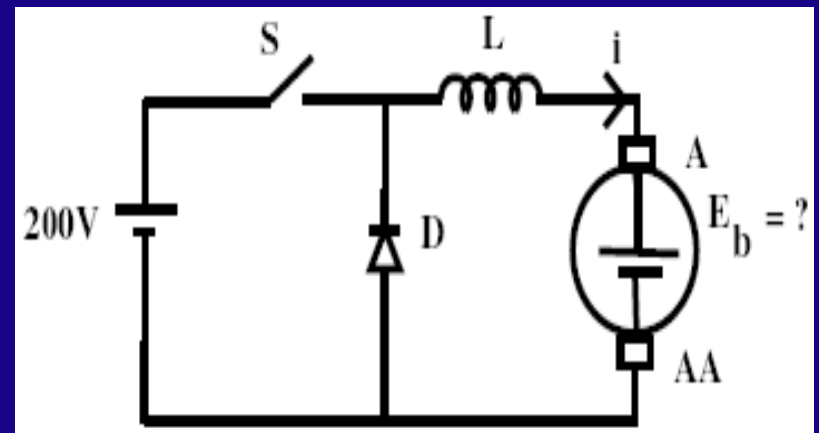

$$200 = L \left(\frac{di}{dt} \right)_I + E_b \quad 0 < t < DT \text{ ---(1)}$$

$$-E_b = L \left(\frac{di}{dt} \right)_D \quad DT < t < T \text{ ---(2)}$$

$$\left(\frac{di}{dt} \right)_I - \left(\frac{di}{dt} \right)_D = \frac{200}{L} = 4000 \text{ A/s}$$



$$\therefore L \frac{di}{dt} = 100$$

$$-L \frac{di}{dt} = 100$$

$$\therefore \left(\frac{di}{dt} \right)_I = - \left(\frac{di}{dt} \right)_D = 2000 \text{ A/s}$$

$$I_{\text{avg}} = 20 \text{ A}$$

$$\therefore I_{\text{min}} = 19\text{A} \text{ \& } I_{\text{max}} = 21\text{A}$$

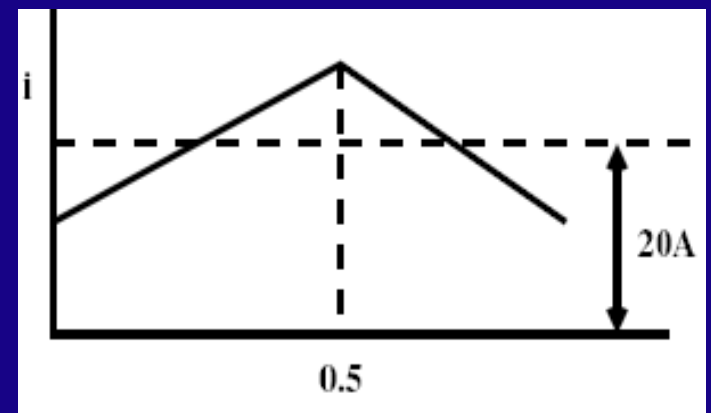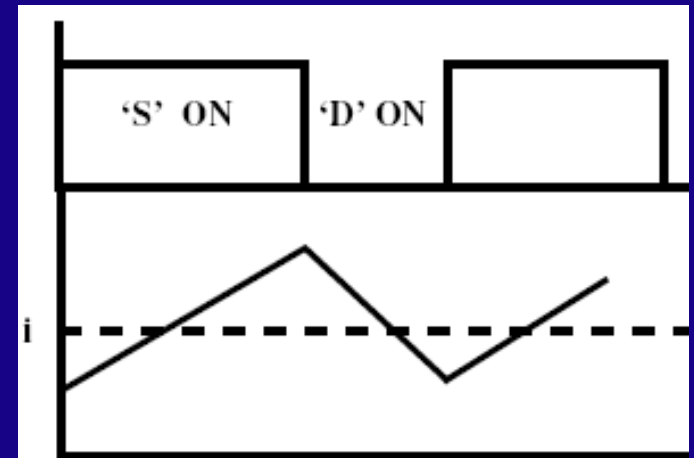

Problem 2 :

$$F_s = 20 \text{ kHz}, D = 0.5$$

Calculate power transferred from 100V source to 300V source.

Assume that the circuit has attained a steady state.

Sol:


When 'S' is ON

$$L \frac{di}{dt} = 100V \quad 0 < t < DT$$

$$L \frac{di}{dt} = -200V \text{ when 'S' is OFF and 'i' is finite.}$$

i_L is DISCONTINUOUS.
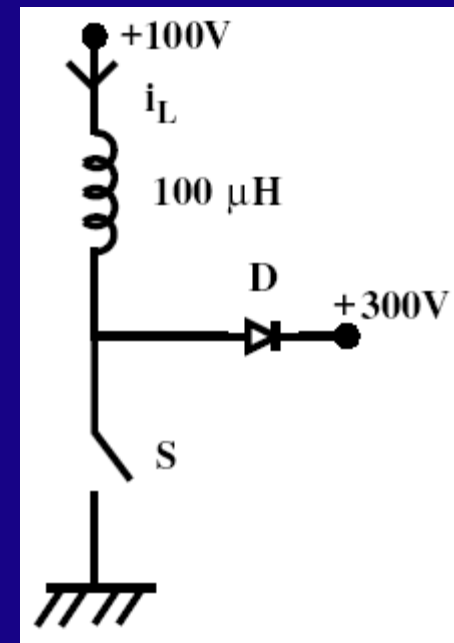
$$\therefore I_{\text{peak}} = \frac{100}{L} * 25 * 10^{-6} = 25A$$



Let ' β ' be the instant 'I' becomes zero.
'V' across it during this period = -200V



$$\therefore 25 = \frac{200}{L} * t_2$$

$$\therefore t_2 = 12.5 \mu\text{sec.}$$

Energy transferred to 300V source in one cycle
= the area shaded as shown in the fig.

$$= V * \frac{1}{2} * I_{\text{peak}} * t_2 = 0.047\text{J}$$

$$\therefore \text{Power transferred} \\ = 20 * 10^3 * E = 938\text{W}$$

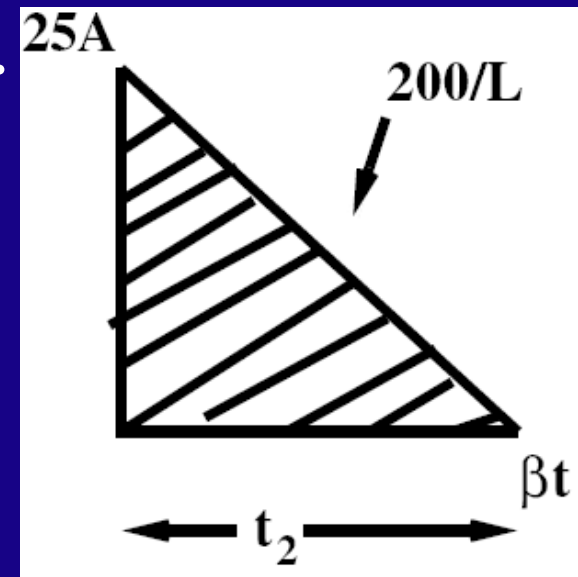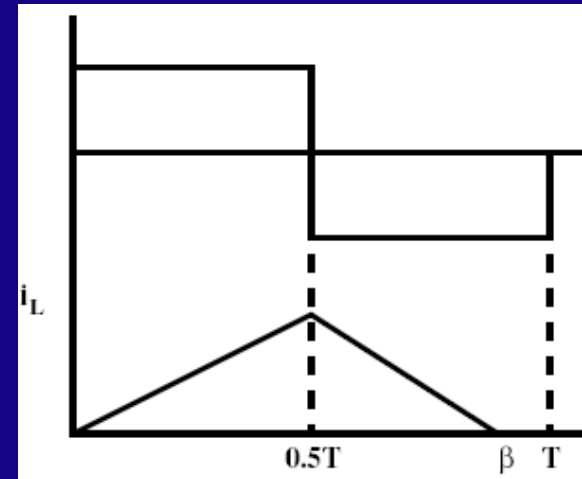

Problem 3.

Switching frequency = 10kHz

'i' is just continuous. $T_{ON} = ?$ & $i_p = ?$

Sol:


$$T = \frac{1}{10 * 10^3} = 100 \mu \text{ sec.}$$

$$\begin{aligned} \text{Peak 'i'} = i_p &= \frac{100}{100 * 10^{-6}} * DT \\ &= \frac{500}{100 * 10^{-6}} (T - DT) \end{aligned}$$

$$\therefore DT = 5(100 * 10^{-6} - DT)$$

$$\therefore DT = t_{ON} = 83.3 \mu \text{sec}$$


$$\therefore I_p = \frac{100 * 83.3 * 10^{-6}}{100 * 10^{-6}} = 83.3 \text{A}$$

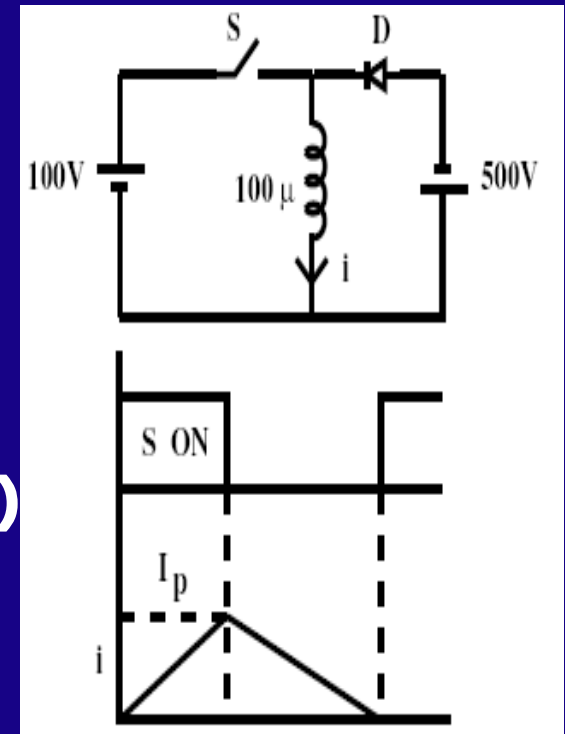

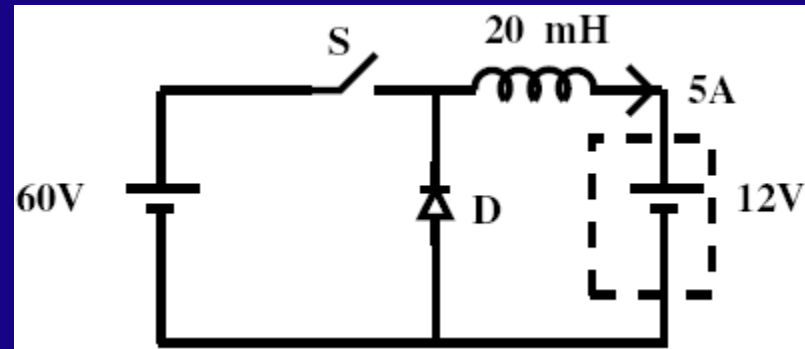Problem 4.

$$F_s = 1 \text{ kHz}, D = 0.2$$

$$L = 20 \text{ mH}, I_{av} = 5 \text{ A}$$



What is the peak to peak current ripple flowing through the load ?

Sol :

$$L \frac{di}{dt} = 60 - 12 = 48$$

$$DT = 0.2 \text{ msec}$$

$$\begin{aligned} \therefore di &= \frac{60 - 12}{20 * 10^{-3}} * 0.20 * 10^{-3} \\ &= 0.48 \text{ A} \end{aligned}$$

Problem5 :


Peak to peak ripple in current flowing through L_1 and L_2 is 1A & Peak to peak voltage ripple in V_{C1} is 10V and that in $V_{C2} = 1V$ and $F_s = 25\text{kHz}$. Neglect internal resistance of L_1 and L_2 .

Sol:

$$V_0 = V_{DC} \frac{D}{(1-D)}$$

$$\therefore D = 0.75$$

(i/p and o/p are current sources)

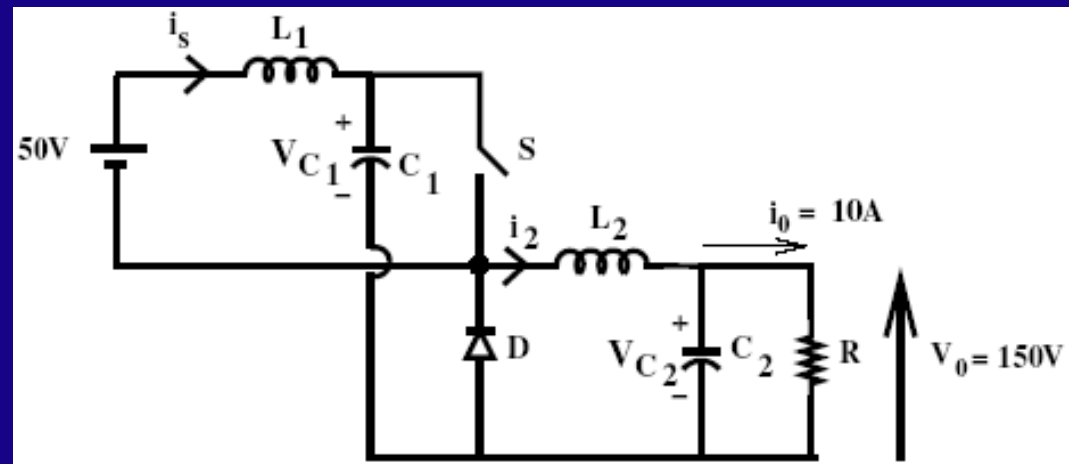

$$T = 40 \mu\text{sec}. \quad \therefore T_{\text{ON}} = 30 \mu\text{sec} \text{ and } T_{\text{OFF}} = 10 \mu\text{sec}.$$

$$\text{Avg. load current} = \text{Avg. current through } L_2 = 10\text{A}$$

$$V_{C1} = ?$$

$$\text{avg. } V_{L1} = 0$$

$$(V_{C1} - V_{DC}) = 50 * \frac{30}{10}$$


$$\therefore V_{C1} = 200\text{V}$$

C_1 is being charged by i_{L1} for $10 \mu\text{sec}$ (t_{OFF})
& discharged by current (i_{L2}) for $30 \mu\text{sec}$.

Neglect ripple.

$$I_{L1} * 10 = I_{L2} * 30 \text{ (where } I_{L2} = 10\text{A)}$$

$$\therefore I_{L1} = 30\text{A}$$

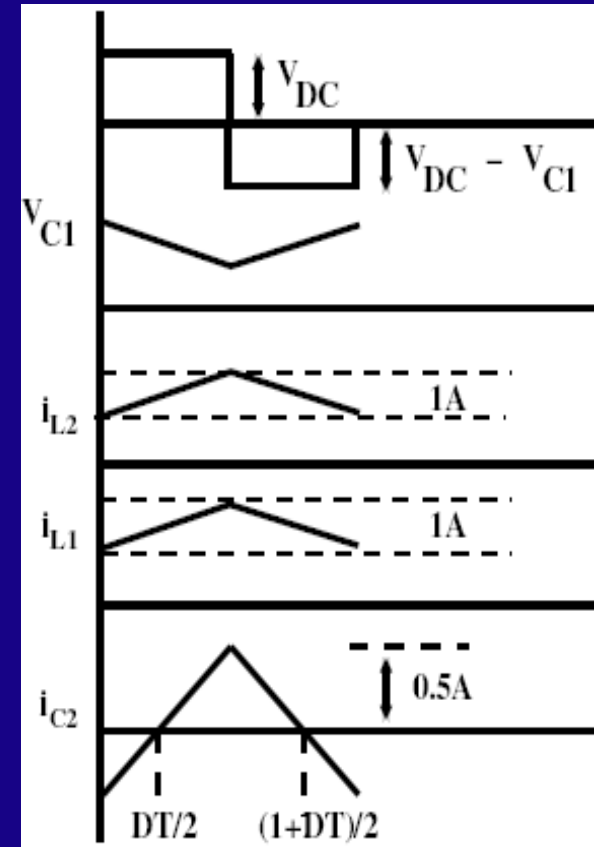

Ripple in $i_{L1} = 1\text{A}$

$$\therefore L \frac{di}{dt} = V_{DC} \Rightarrow \frac{50}{L_1} = \frac{1}{30 \mu\text{sec.}} \quad \therefore L_1 = 1.5 \text{ mH}$$

Similarly, ripple in $i_{L2} = 1\text{A}$.

$$\therefore \frac{V_{C1} - V_0}{L_2} = \frac{di}{dt}$$


$$dt = 30 \mu\text{sec}, V_{C1} = 200\text{V}, V_0 = 150\text{V}, di = 1\text{A}.$$

$$\therefore L_2 = 1.5 \text{ mH}.$$

$$C_1 = ? \text{ \& } C_2 = ?$$

C_2 charges when $i_{L2} > I_0$
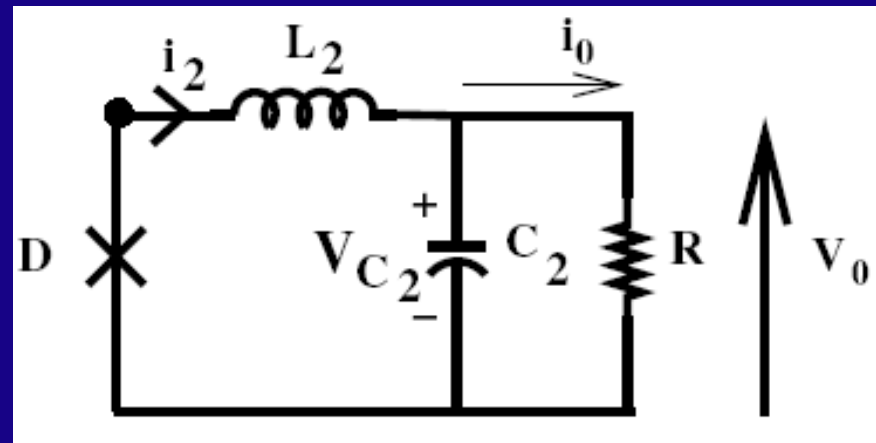
$$\text{i.e. from } \frac{DT}{2} \text{ to } \left(\frac{1+D}{2} \right) T$$



$$\therefore \Delta q_2 = \frac{1}{2} * 0.5 * 20 * 10^{-6} = 5 \mu C$$

$$\therefore C_2 = \frac{\Delta q}{\Delta V} = 5 \mu F$$

Similarly, C_1 is discharged by an average current of 10A for 30 μ sec.

$$\therefore \Delta V \text{ for } V_{C1} = 10V$$

$$\therefore C = \frac{10 * 30}{10 V} = 30 \mu F$$

