

## \* Boolean formulae.

$$1 \quad 0 + a = a, \quad 1 \cdot a = a \quad \text{Axiom}$$

$$1 + a = 1, \quad 0 \cdot a = 0$$

$$2 \quad a + \bar{a} = 1, \quad a \cdot \bar{a} = 0 \quad \text{Axiom}$$

$$3 \quad a(b+c) = ab + ac \quad \text{Axiom}$$

$$a+bc = (a+b)(a+c) \quad \text{Axiom}$$

$$4 \quad a \cdot a = a + a = a$$

$$5 \quad a + \bar{a}b = a + b$$

## 6 Consensus

## 7 De Morgan.


5/72

→ Shift - to - left

$$(1011 \rightarrow 0110)$$


= Multiplication by 2 (without MSB)

 \* Shift - to - right :- Division by 2 (without remainder)



- Number at B indicates number of places to shift

 - If  $B \geq 8$ ,  $Out = 00000000$ - Only  $B[2:0]$  are important.



- We could have another I/p 'Right', which decides whether shift left (when 0) and right (when 1)

Meth1 Build left shifter and right-shifter, use MUX to choose.

Meth2 Build only left shifter.

If you want to shift right, first reverse all digits

→ Comparator (better method)


Compare highest 4 bits ( $A_H$  &  $B_H$ ) and lowest 4 bits ( $A_L$  &  $B_L$ ) to obtain  $G_H, E_H, G_L, E_L$

Then compare  $A_{total}$  &  $B_{total}$

$$G_{total} = G_H + E_H \cdot G_L$$

• Cos


Cascade these comparators in binary tree

 

- In this method, more computation is required but delay is lower  
 $\text{Delay} \sim O(\log n)$   
 Meth 1  $\sim O(n)$
- No. of gates required for both methods  $\sim O(n)$
- It is difficult to position this tree on a circuit board.

\* Critical Path:-

 The path which takes longest time (determines delay)



- In adder, the 'carry' path is critical ( $C_0 \rightarrow C_1 \rightarrow \dots \rightarrow C_7$ )



## FASTER ADDER

\* For adder,

$$C_0 = (a \oplus b) C_1 + ab$$

$$S = (a \oplus b) \oplus C_1$$

$$\text{Write } C_0 = p C_1 + g$$

$$S = p \oplus C_1$$

$$\text{where } p = a \oplus b = \text{'propagate'}$$

$$g = a \cdot b = \text{'generate'}$$

6/2 •  $p = a \oplus b$  can be calculated in parallel for all 8-bits

• To make critical path (carry overs) faster,

$$C_1 = p_0 C_0 + g_0$$

$$C_2 = p_1 p_0 C_0 + p_1 g_0 + g_1$$

$$C_3 = \underbrace{p_2 p_1 p_0 C_0}_{\substack{\downarrow \\ C_0 \text{ was propagated} \\ \text{if } p_2 = p_1 = p_0 = 1}} + \underbrace{p_2 p_1 g_0 + p_2 g_1 + g_2}_{\substack{\downarrow \\ \text{Carry was 'generated'}}}$$

$$C_n = \underbrace{(p_{n-1} p_{n-2} \dots p_0)}_{\substack{O(\log n) \\ \text{product of } n \text{ literals}}} C_0 + \underbrace{[g_{n-1} + p_{n-1} g_{n-2} + p_{n-1} p_{n-2} g_{n-3} \dots]}_{\text{sum of } n \text{ terms}}$$

• 'Divide and conquer' gives ↓ delay, requires ↑ no. of gates.

$$\text{Delay} \sim O(\log n)$$

$$\star \text{ No. of gates} \sim O(n^3)$$

$$\text{" " " for one } C \sim O(n^2)$$



$$\text{Delay} \sim O\left(\frac{n}{k} \log k\right)$$

$$\text{No. of gates} \sim O\left(\frac{n}{k} k^3\right)$$

- To reduce no. of gates, ~~error~~ calculate only  $C_n$  carry fast using log method. Calculate remaining at leisure.

'Delay % Cost'


### MULTIPLIER.

$$\begin{array}{r} a_7 \dots a_0 \\ \times b_7 \dots b_0 \\ \hline \end{array}$$


$$= a_0 b_0 + 2(a_1 b_0 + a_0 b_1) + 2^2(a_2 b_0 + a_1 b_1 + a_0 b_2) \dots$$

\* No. of gates  $\sim O(n^2)$


### A] Array Multiplier

 

 
- The fastest possible time is  $O(\log n)$



8/2

  $a_7 a_6 a_5 a_4 \dots a_0$  $b_7 b_6 b_5 b_4 \dots b_0$  $P_{15} \dots P_0$ 


Use Full adders to achieve this:-

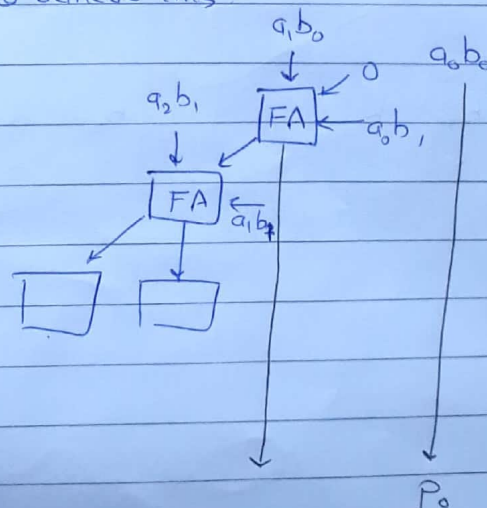



- Critical path of carry-over  $\sim O(n)$




eg  $3 \times 3$  multiplication

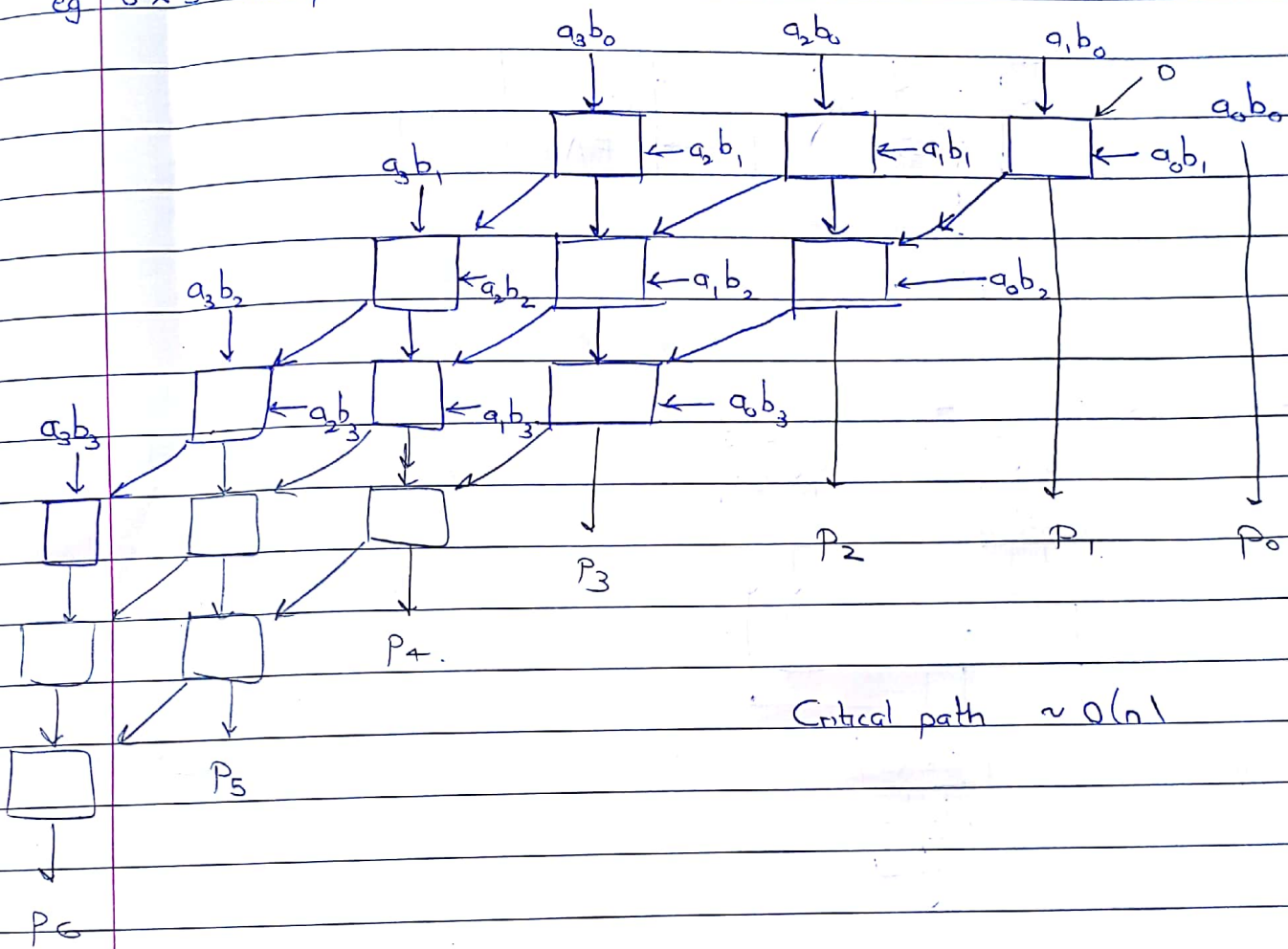

 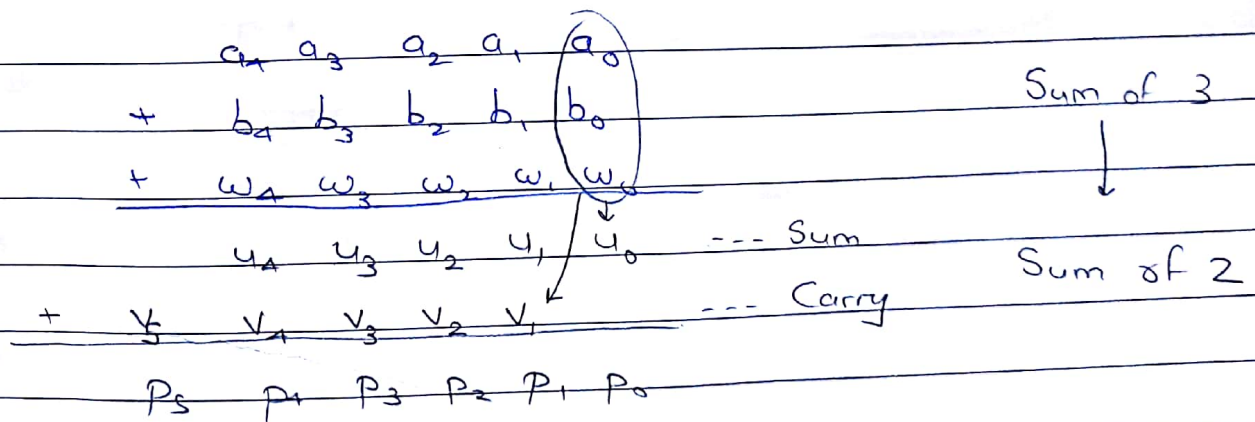
→ To improve the critical path length, better way to add:-  
'Carry Save Adder'



For more than 3 numbers,

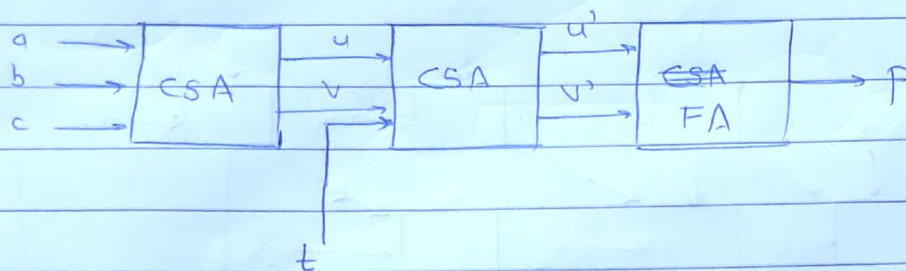

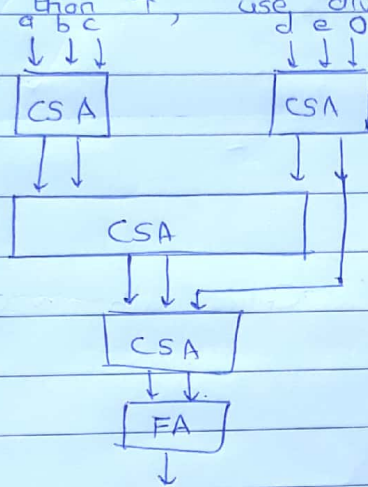- For more than 4, use divide and conquer.





# SEQUENTIAL CIRCUITS


- Have memory

Finite sets of I/p, O/p, state.


## I FINITE STATE MACHINE

'Mealy Machine'

set of possible states of system.

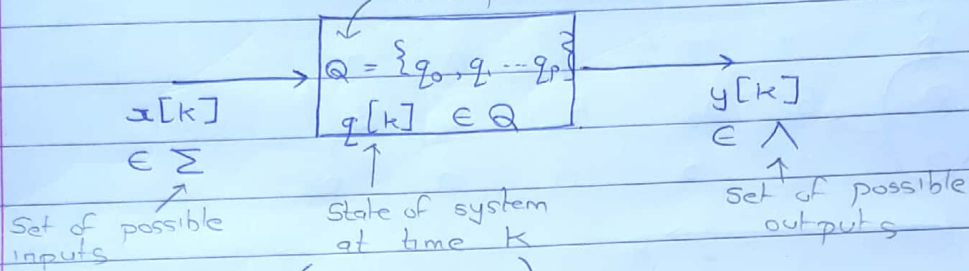

 1.  $y[k] = \lambda(x[k], q[k])$
2.  $q[k+1] = \delta(x[k], q[k])$   
= Define as 'next  $q[k]$ ' (next  $q$ )





eg Design a finite state machine.

$$x[k] \in \Sigma \equiv \{a, b\}$$

$$y[k] \in \Lambda \equiv \{y, n\}$$

$\exists$  such that  $y[k] = y$  if last three inputs are 'aba' or 'bab'  
n otherwise

 
 
eg-  $x[k]$       a   b   a   a   b   a   b   a   a  
                  ↓  
 $y[k]$       n   n   y   n   n   y   y   y   n



- The discrete time ' $k$ ' can be provided using edges of clock cycle
- The signal must have settled (be constant) at the times of sampling.


## II D FLIP FLOPS

- Clock :

  

- Changes in signal should occur before S interval
- The input value expected to be read must be held till after H interval
- $\Rightarrow$  Input must be stable in  $[S, H]$

eg Above example

 




- Say  $q[k+1] = nq[k]$

Take  $D$  = Delay of flip-flop

$m$  = Minimum delay in finite state machine (shortest path)

 $M$  = Maximum " " " " (for critical path)



$q$  value is updated at  $t = D$ .

- Then  $nq$  value is updated soonest at  $D+m$   
latest at  $D+M$

For  $t \in (D+m, D+M)$ ,  $nq$  may hold (possibly wrong) updated values

- Hence, for correct functioning of circuiting,
 

①	$D+m \geq H$
②	$D+M \leq T-S$


- It is easy to rectify, and if ② is not satisfied  
→ Increase  $T$ .

19/2

Write  $m+D \sim m$  and  $M+D \sim M \Rightarrow m \geq H$  and  $M \leq T-S$



 
- We cannot let  $x[k]$  change anywhere in the time period, as the consequential update of  $nq[k]$  might fall in  $[S, H]$  of flip flop
- Similarly, we cannot let  $y[k]$  change at any arbit time.





Ensure these intervals do not intersect with  $[S, H]$

   → What if clocks themselves are not synchronous?




For correct capture of  $P$ , we worry about  $[S, H]$  of  $CLK_C$

- 1  $m \geq H + \Delta$  ----- More difficult
- 2  $M \leq (T - S) + \Delta$  ----- Easier

• If  $\Delta$  is positive, and if we can ensure that  $m \geq H + \Delta$ , then we can choose a lower  $T$  for '2' 😊  
We can en
 
## II TRACEFILES FOR FINITE STATE MACHINES




just after


\*  $q$  is changing at positive edge of CLK.

Make  $X$  change at negative edge of CLK.

 Sample  $Y$  after a predecided delay after negative edge of CLK.



## III EQUIVALENCE OF FSMs

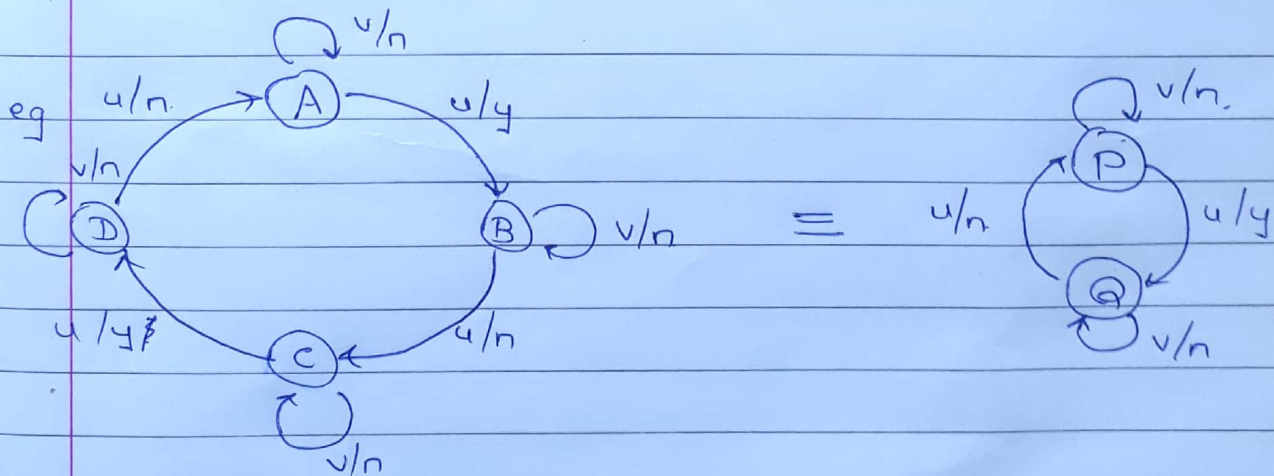

In LHS figure, A and C are not distinct states  
B and D.



- Two states A and B are distinct if the same input produces different output.

0-equivalent	1-equivalent	2-equivalent	
$\{A, B, C, D\}$	$\{A, C\} \{B, D\}$	$\{A, C\} \{B, D\}$	IF next I/p is 4
All are equivalent before input is given	After giving 1 input $x_0$ , if both give same output	After giving 1 new input to 1-equivalents, their next states are 1-equivalent	$A \rightarrow B$ and $C \rightarrow D$ But $\{B, D\}$ are 1- $\therefore \{A, C\}$ are 2-eg

----converged.

The equivalent classes will 'converge' in at most 'n' steps  
↳ No. of states

→ We can reduce the number of states by combining equivalent states. This reduces the size of chip and length of program