
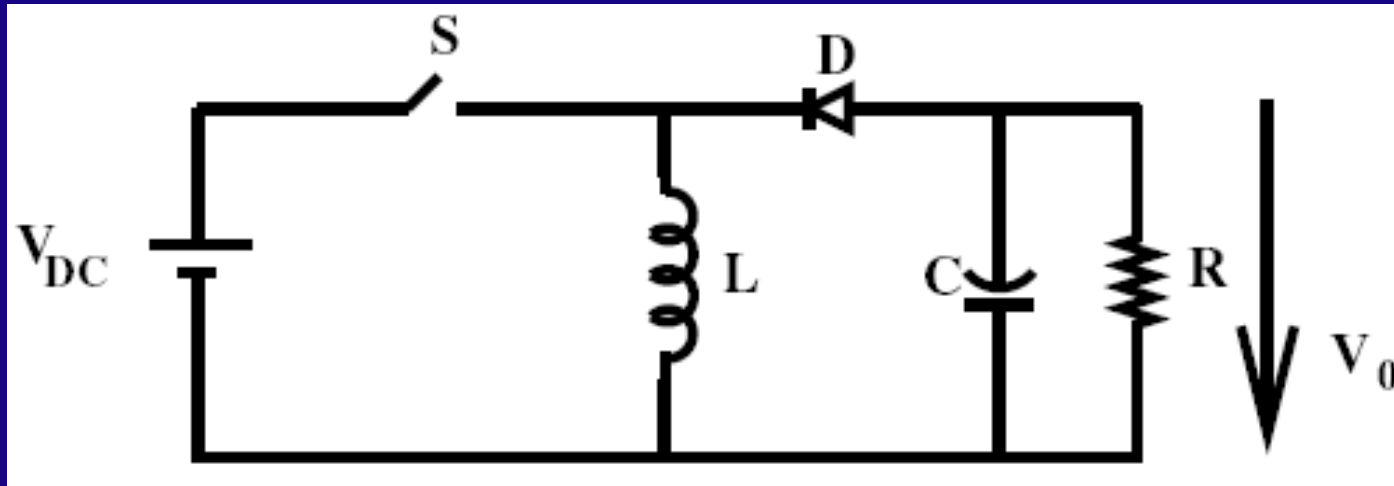


Buck – Boost :

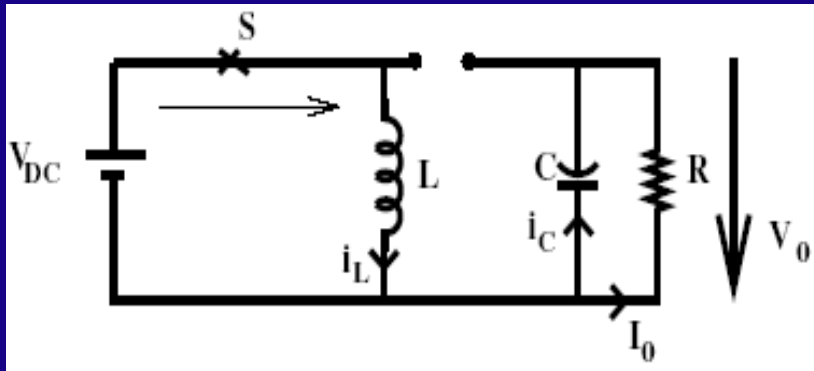

⇒ Can be regarded as cascade connection of Buck + Boost.

⇒ Hence the name Buck – Boost.




$$0 < t < DT$$

$$v_L = V_{DC}$$

$$r i_L + L \frac{di_L}{dt} = V_{DC}$$
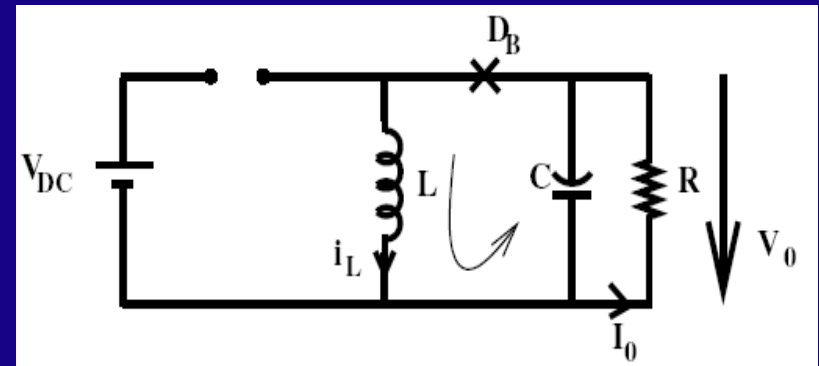
$$C \frac{dv_0}{dt} + \frac{v_0}{R} = 0$$



$$DT < t < T$$

$$v_L = -v_0$$

$$r i_L + L \frac{di_L}{dt} + v_0 = 0$$

$$i_L = C \frac{dv_0}{dt} + \frac{v_0}{R}$$

Av. values of v_0 & i_L are V_0 & I_L

$$rI_L + L \left(\frac{di_L}{dt} \right)_{av} + \frac{1}{T} \int_{DT}^T V_0 dt = DV_{DC}$$

$$C \left(\frac{dV_0}{dt} \right)_{av} + \frac{V_0}{R} = \frac{1}{T} \int_{DT}^T i_L dt$$

At steady state $\left(\frac{di_L}{dt} \right)_{av}$ & $\left(\frac{dv_0}{dt} \right)_{av} = 0$

$$rI_L + (1 - D)V_0 = DV_{DC}$$

$$\frac{V_0}{R} = I_L(1 - D)$$

$$r \frac{V_0}{R(1-D)} + (1-D)V_0 = DV_{DC}$$

$$\therefore V_0 = \frac{V_{DC}D(1-D)}{\frac{r}{R} + (1-D)^2} \text{-----} \rightarrow 1$$

$$I_L = \frac{V_{DC}D}{r + R(1-D)^2}$$

$$\text{if } r \rightarrow 0 \quad V_0 = V_{DC} \frac{D}{(1-D)} \text{-----} \rightarrow 2$$

$$I_L = V_{DC} \frac{D}{R(1-D)^2}$$

This can also be proved by equating Voltage across the inductor over the cycle = 0

$$V_{DC}DT = V_0(1-D)T$$

$$\therefore V_0 = V_{DC} \frac{D}{(1-D)}$$

$$\text{In eq.-2} \quad \left| \frac{V_0}{V_{DC}} \right| < 1 \quad \text{for } 0 < D < 0.5$$

$$\& \quad \left| \frac{V_0}{V_{DC}} \right| > 1 \quad \text{for } 0.5 < D < 1$$

$$V_0 \rightarrow \infty \text{ as } D \rightarrow 1$$

$\Rightarrow V_0$ is –ve W.R.T. reference point of V_{DC} .

\Rightarrow True in an ideal converter.

In non – ideal converter :


$\frac{V_0}{V_{DC}}$ reaches a peak and then reduces.



$V_0 = 0$ when $D = 1$

Using eq.1 $\left| \frac{dV_0}{dD} \right|_{=0}$




$$D_{max.} = 1 + \frac{r}{R} - \sqrt{\frac{r(1 + \frac{r}{R})}{R}}$$
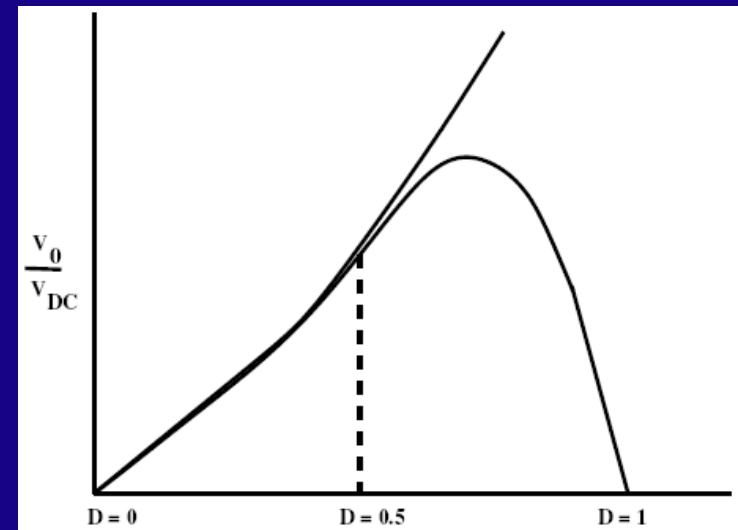
$$V_{0(max.)} = \frac{V_{DC}}{2} \left(\sqrt{1 + \frac{R}{r}} - 1 \right)$$



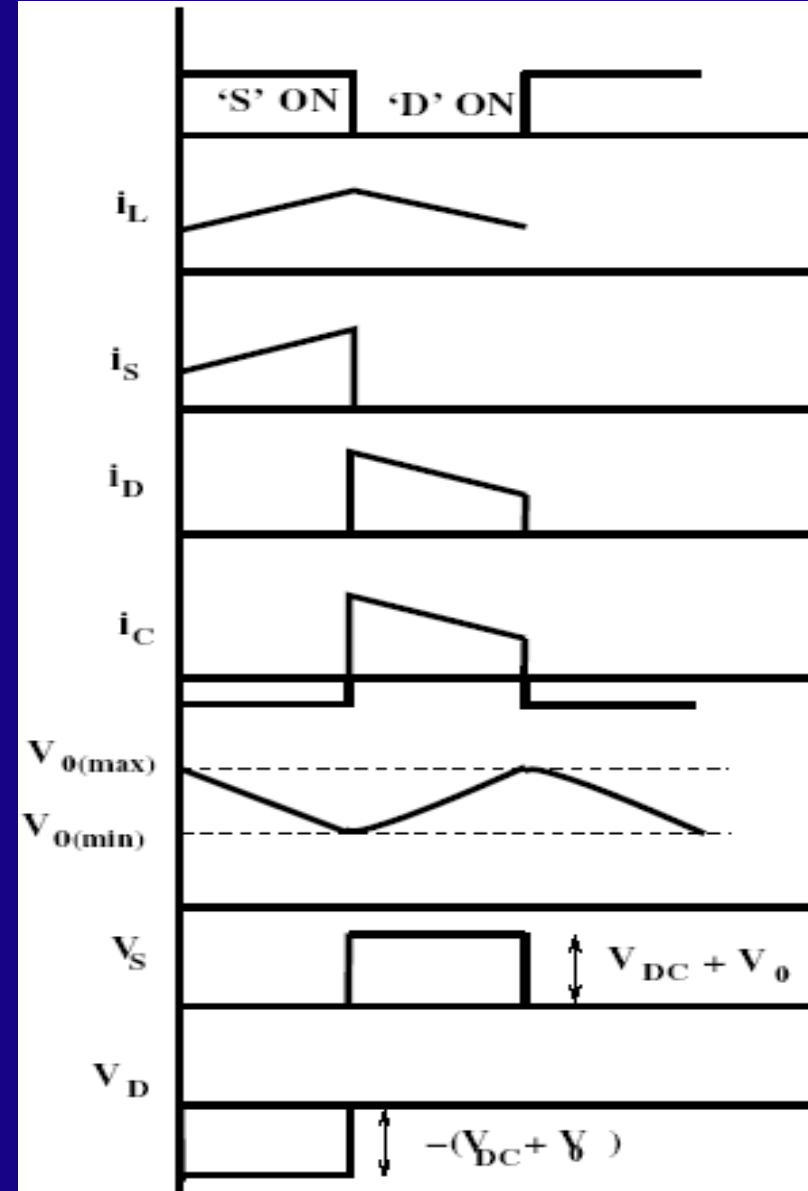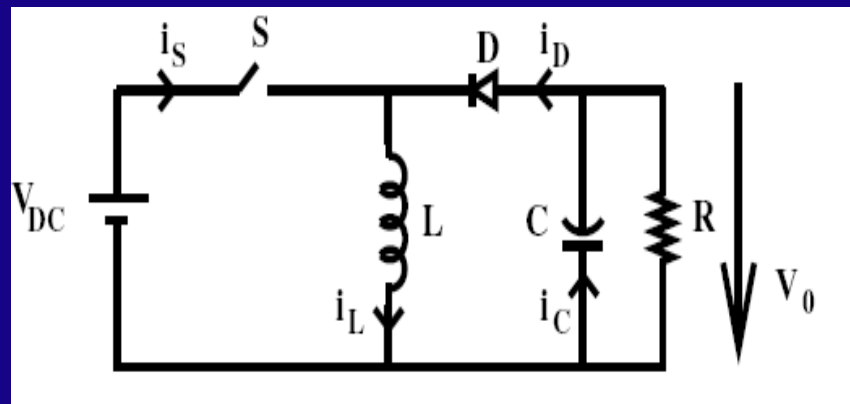



Cuk' Converter:

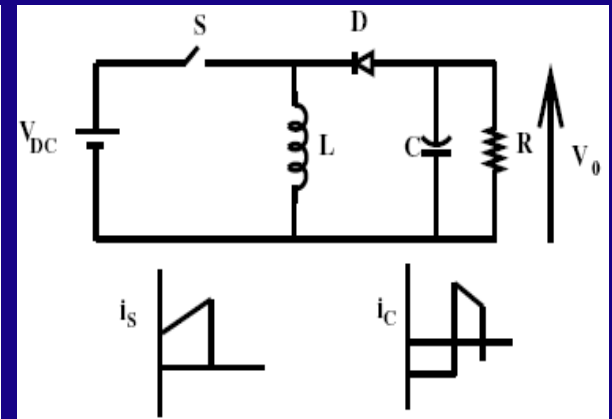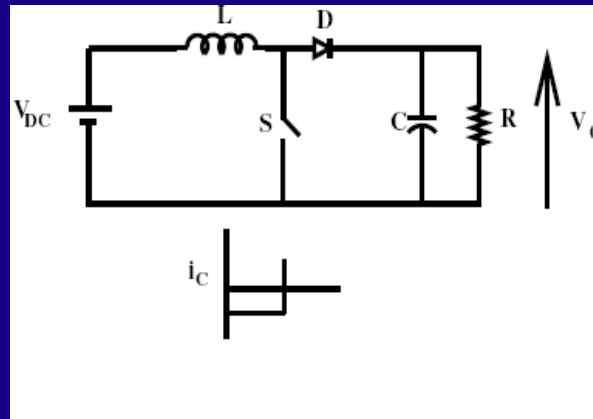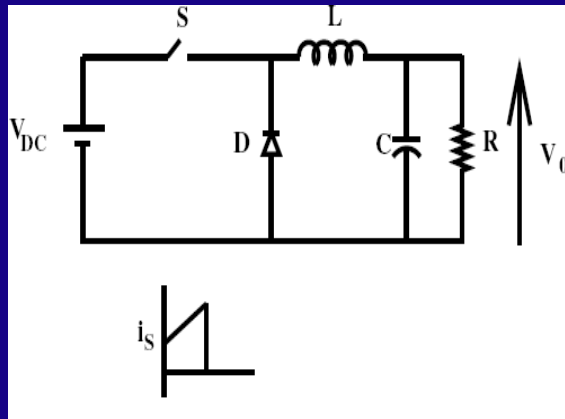


Load is current source.

Source is current source.

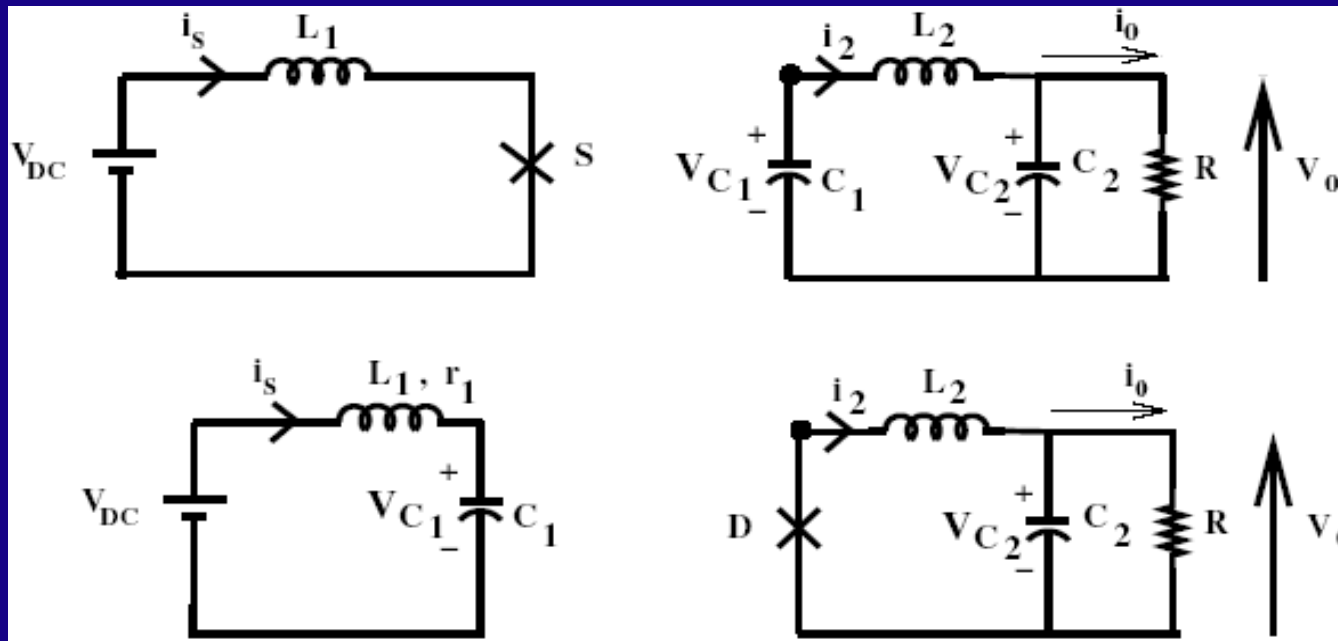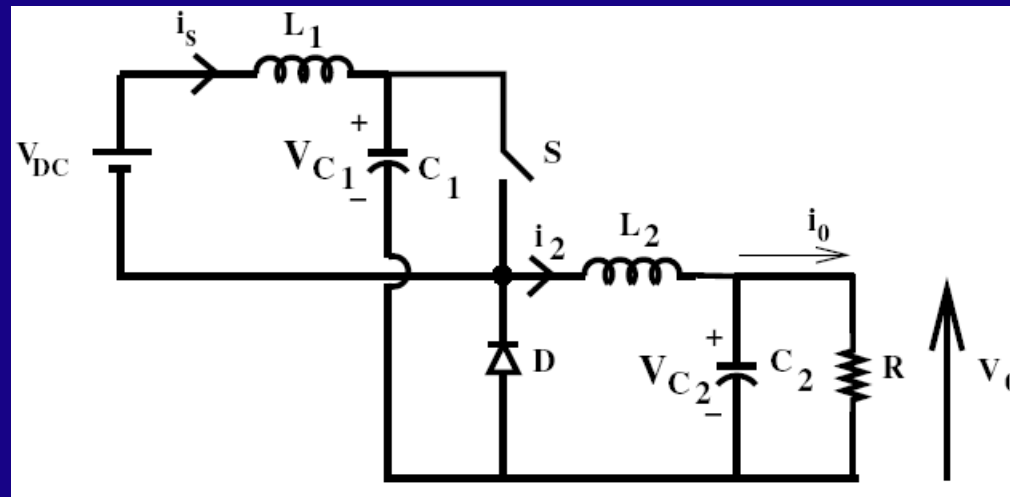
⇒ Current source both at input & source side are desirable.



'S' Closed

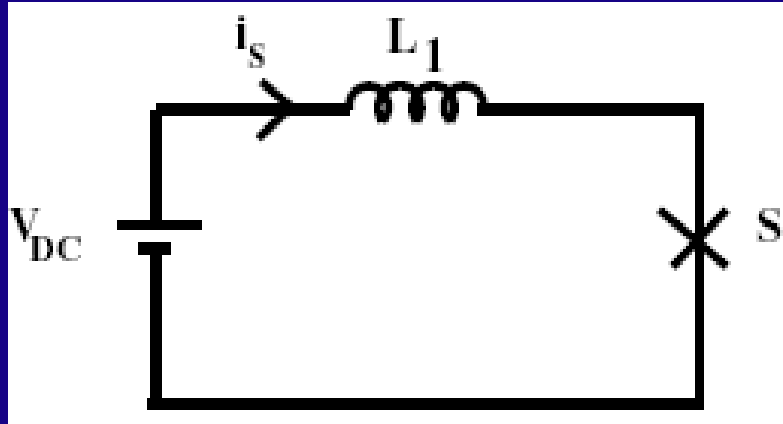
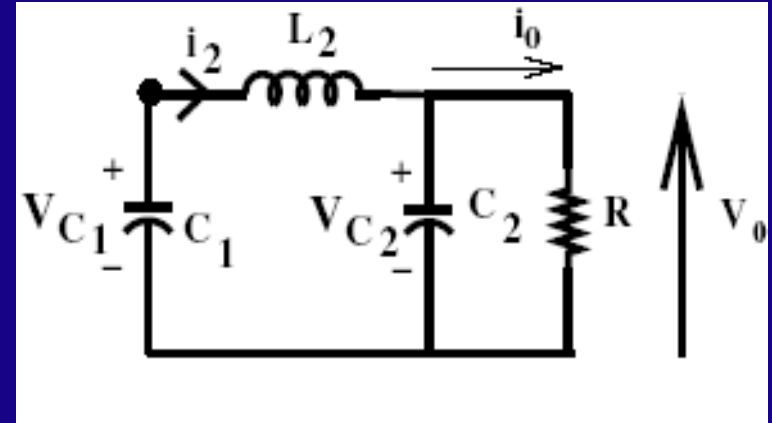
$$V_{DC} = L_1 \frac{di_s}{dt} + r_1 i_s$$




$$V_{C1} = L_2 \frac{di_2}{dt} + r_2 i_2 + v_0$$

$$i_2 = C \frac{dv_0}{dt} + \frac{v_0}{R}$$


$$C_1 \frac{dV_{C1}}{dt} = -i_2, \quad 0 < t < DT$$

'S' open:

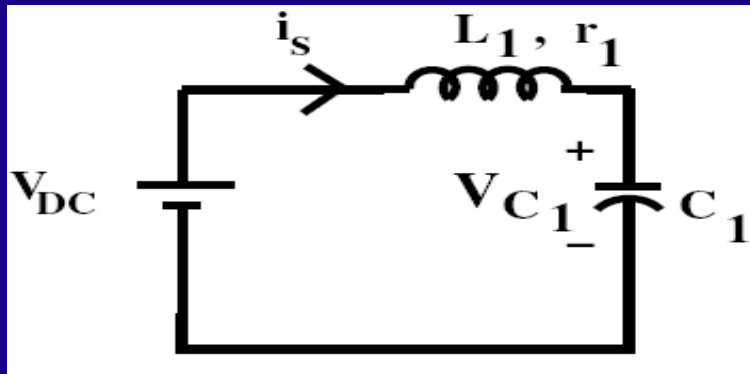

$$V_{DC} = r_1 i_s + L_1 \frac{di_s}{dt} + v_{C1}$$

$$C_1 \frac{dv_{c1}}{dt} = i_s$$

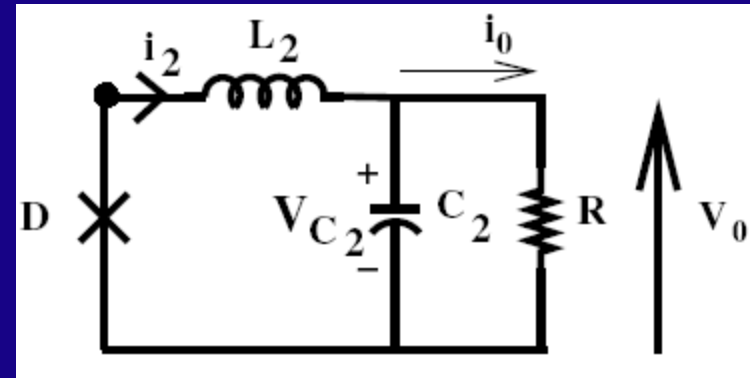

$$r_2 i_2 + L_2 \frac{di_2}{dt} + v_0 = 0$$

$$i_2 = C \frac{dv_0}{dt} + \frac{v_0}{R}$$

$$\int_0^{DT} V_{DC} dt = \int_0^{DT} r_1 i_s dt + \int_0^{DT} L_1 \frac{di_s}{dt} dt \quad 0 \leq t \leq DT$$

$$\int_{DT}^T V_{DC} dt = \int_{DT}^T r_1 i_s dt + \int_{DT}^T L_1 \frac{di_s}{dt} dt + \int_{DT}^T v_{C1} dt \quad DT \leq t \leq T$$

$$\therefore V_{DC} = r_1 I_s + L_1 \left(\frac{di_s}{dt} \right)_{av} + \frac{1}{T} \int_{DT}^T v_{C1} dt$$

$$\text{similarly, } r_2 I_2 + L_2 \left(\frac{di_2}{dt} \right)_{av} + V_0 = \frac{1}{T} \int_0^{DT} v_{C1} dt$$

$$I_2 = C \left(\frac{dv_0}{dt} \right)_{av} + \frac{V_0}{R}$$

$$C \left(\frac{dv_{C1}}{dt} \right)_{av} = \frac{1}{T} \int_0^{DT} (-i_2) dt + \frac{1}{T} \int_{DT}^T i_s dt$$

In steady state $\left(\frac{di_s}{dt}\right)_{av} = 0$, $\left(\frac{di_2}{dt}\right)_{av} = 0$

$$\left(\frac{dV_0}{dt}\right)_{av} = 0 \text{ \& } \left(\frac{dV_c}{dt}\right)_{av} = 0$$

Also neglecting ripple in V_{c1} , i_2 & i_s

$$V_{DC} = r_1 I_s + (1-D)V_{c1} \text{ ----- (1)}$$

$$r_2 I_2 + V_0 = DV_{c1} \text{ ----- (2)}$$

$$I_2 = \frac{V_0}{R} \text{ ----- (3)}$$

$$0 = -DI_2 + (1-D)I_s \text{ ----- (4)}$$

$$i_s = \frac{D}{(1-D)} I_2 \rightarrow \text{Av. load } I \quad \because \text{av. } I \text{ through } C = 0$$

$$r_2 \frac{V_0}{R} + V_0 = D V_{c1}$$

$$\therefore V_{c1} = \frac{V_0}{DR} (r_2 + R)$$

$$\begin{aligned} V_{DC} &= r_1 I_s + (1-D) \frac{I_2 R}{DR} (r_2 + R) \\ &= r_1 I_s + (1-D) I_s \frac{(1-D)}{D^2} (r_2 + R) \end{aligned}$$

$$\therefore I_s = \frac{V_{DC}}{r_1 + \left(\frac{1-D}{D} \right)^2 (r_2 + R)} \rightarrow \text{av. source } I \text{ in terms of } V_{DC} \text{ \& } D$$

$$V_0 = I_2 R = \left(\frac{1-D}{D} \right) R I_s = \left(\frac{1-D}{D} \right) R \frac{V_{DC}}{r_1 + \left(\frac{1-D}{D} \right)^2 (r_2 + R)}$$

$$\therefore V_0 = \frac{V_{DC}}{\frac{r_1}{R} \frac{D}{(1-D)} + \left(\frac{1-D}{D} \right) \left(\frac{R+r_2}{R} \right)} \rightarrow \text{av. } V_0 \text{ in terms of } V_{DC} \text{ \& } D$$

$$V_{c1} = \frac{V_0}{DR} (r_2 + R) = \frac{V_{DC}}{(1-D) + \frac{r_1}{(r_2 + R)} * \frac{D^2}{(1-D)}}$$

If r_1 & $r_2 = 0$

$$I_s = \frac{D}{(1-D)} I_2 = \left(\frac{D}{1-D} \right)^2 \frac{V_{DC}}{R}$$

$$V_{c1} = \frac{V_{DC}}{(1-D)} \quad V_0 = V_{DC} \frac{D}{(1-D)}$$

$$\text{'OR' } V_0 = \underline{\underline{DV_{c1}}}$$

$$V_{DC}DT = (V_{c1} - V_{DC})(1-D)T$$

$$\therefore V_{c1} = \frac{V_{DC}}{(1-D)}$$

$$\therefore V_0 = DV_{c1} \text{ (is buck converter with } V_{c1} \text{ as the input voltage)}$$

$$\therefore V_0 = \frac{DV_{DC}}{(1-D)}$$

⇒ Buck Boost converter.

⇒ Both I/P & O/P 'I' waveform are quite smooth.