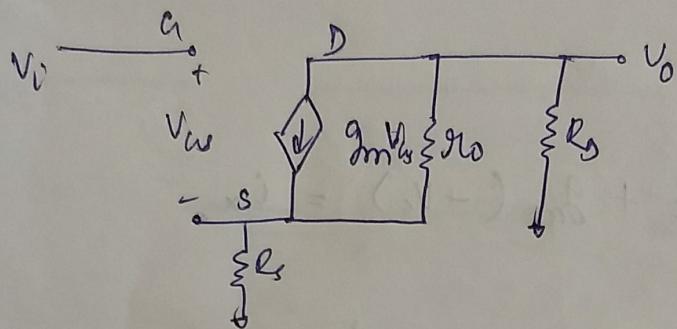


common source configuration




$$g_m(V_i - V_s) + \frac{(V_o - V_s)}{R_o} + \frac{V_o}{R_D} = 0$$

$$\frac{V_s}{R_S} = -\frac{V_o}{R_D} \Rightarrow V_s = -\frac{R_S}{R_D} V_o$$

$$g_m V_i + \left(\frac{R_S}{R_D} g_m + \left(1 + \frac{R_S}{R_D} \right) \frac{1}{R_o} + \frac{1}{R_D} \right) V_o = 0$$

$$\begin{aligned}
 \text{a) } A_v &= \frac{V_o}{V_i} = \frac{-g_m}{\frac{R_S}{R_D} g_m + \left(1 + \frac{R_S}{R_D} \right) \frac{1}{R_o} + \frac{1}{R_D}} \\
 &= \frac{-10^{-3}}{\frac{5 \times 10^3}{10 \times 10^3} \times 10^{-3} + \left(1 + \frac{5 \times 10^3}{10 \times 10^3} \right) \frac{1}{50 \times 10^3} + \frac{1}{10 \times 10^3}} \\
 &= \frac{-10^{-3}}{0.5 \times 10^{-3} + 0.03 \times 10^{-3} + 0.1 \times 10^{-3}} \\
 &= 1.587
 \end{aligned}$$

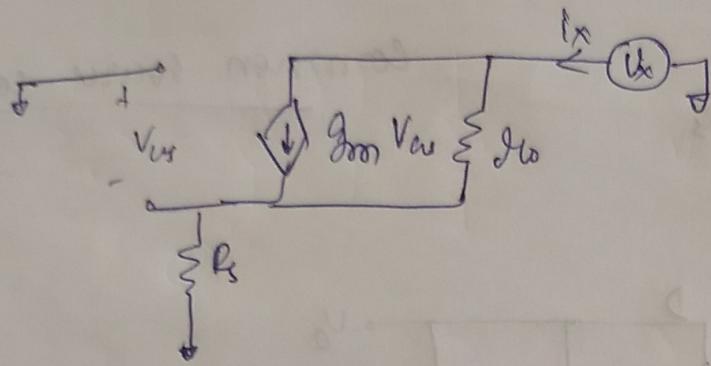b) To calculate o/p impedance (without R_D)



$$i_x = \frac{V_s}{R_s}, \quad \frac{V_x - V_s}{R_o} + g_m (-V_s) = i_x$$

$$\frac{V_x}{R_o} - \frac{i_x R_s}{R_o} - g_m i_x R_s = i_x$$



$$\frac{V_x}{R_o} = \left(\frac{R_s}{R_o} + g_m R_s + 1 \right) i_x$$

$$R_{out} = R_s + (1 + g_m R_s) R_o$$

including R_D

$$\begin{aligned} R'_{out} &= (R_s + (1 + g_m R_s) R_o) \parallel R_D \\ &= (5K + (1 + 1m \cdot 5K) 50K) \parallel 10K \\ &= 305K \parallel 10K \\ &= 9.6825K\Omega \end{aligned}$$

c) I/O impedance is infinity.

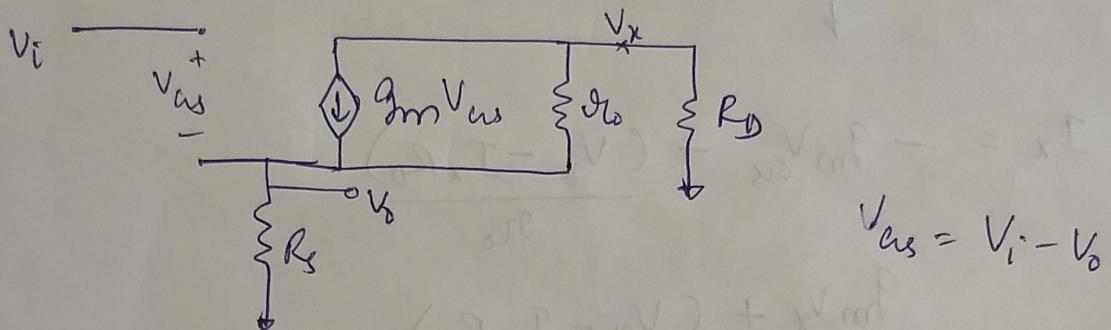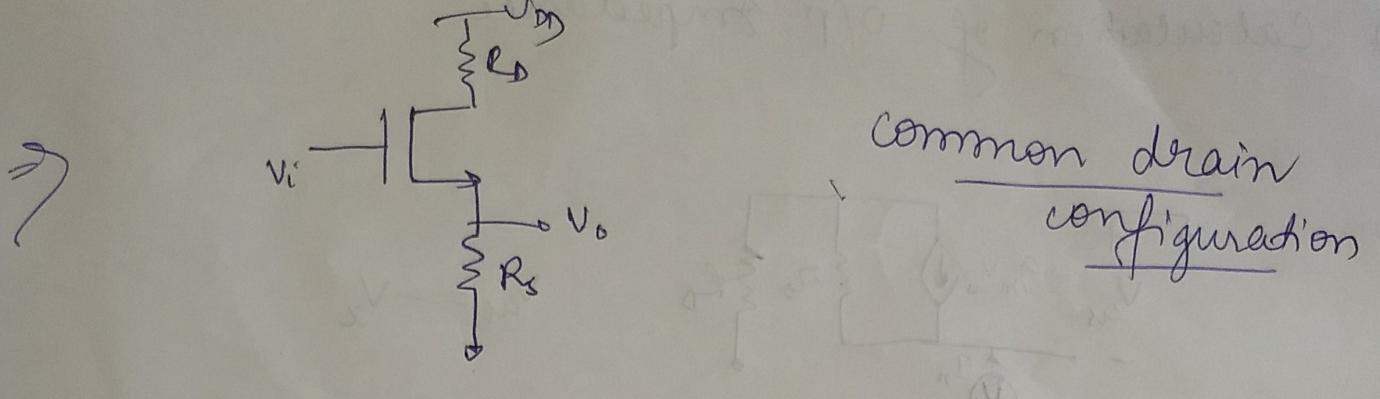

$$V_x = -\frac{V_o}{R_s} \times R_d$$

$$\frac{V_o}{R_s} = g_m (V_i - V_o) + \frac{(V_x - V_o)}{g_{ro}}$$

$$= g_m (V_i - V_o) + \left(-\frac{V_o}{R_s} \frac{R_d}{R_s} - V_o \right) \frac{1}{g_{ro}}$$

$$V_o \left(\frac{1}{R_s} + g_m + \left(\frac{R_d}{R_s} + 1 \right) \frac{1}{g_{ro}} \right) = g_m V_i$$

a)


$$A_v = \frac{V_o}{V_i} = \frac{g_m}{\frac{1}{R_s} + g_m + \left(\frac{R_d}{R_s} + 1 \right) \frac{1}{g_{ro}}}$$

$$= \frac{lm}{\frac{1}{5K} + lm + \left(\frac{10K}{5K} + 1 \right) \frac{1}{50K}}$$

$$= \frac{lm}{0.2lm + lm + 0.06lm}$$

$$= 0.79365$$

b) Calculation of O/P Impedance.

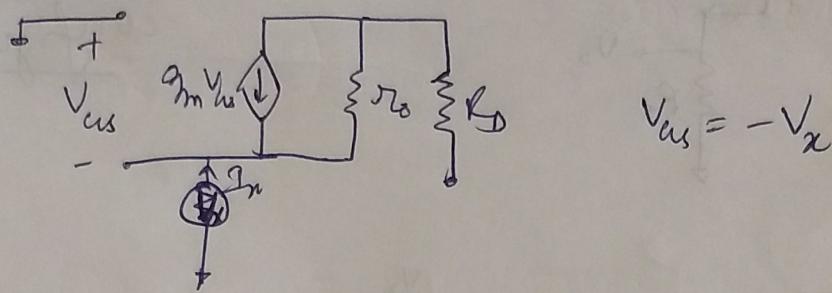

$$V_{cs} = -V_x$$

$$\begin{aligned} I_x &= -g_m V_{cs} + \frac{(V_x - I_x R_d)}{r_o} \\ &= g_m V_x + \frac{(V_x - I_x R_d)}{r_o} \\ &= \left(g_m + \frac{1}{r_o}\right) V_x - I_x \frac{R_d}{r_o} \\ \left(1 + \frac{R_d}{r_o}\right) I_x &= \left(g_m + \frac{1}{r_o}\right) V_x \end{aligned}$$



$$R_{out} = \frac{V_x}{I_x} = \frac{r_o + R_d}{1 + g_m r_o} = \frac{50K + 10K}{1 + 1m \cdot 50K} = 1.1765K\Omega$$

$$R_{out}' = R_{out} // R_s = 1.1364K\Omega$$

c) Input impedance is infinity.

B>

Common Gate Amplifier.

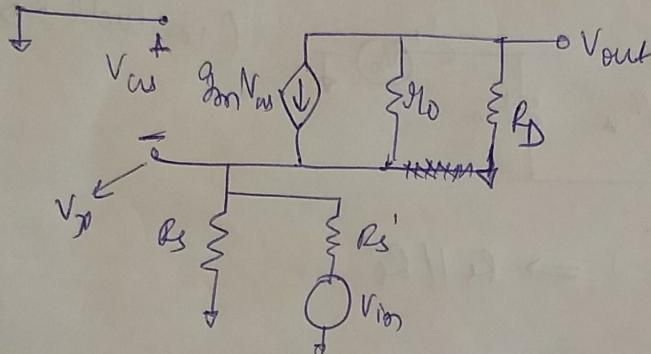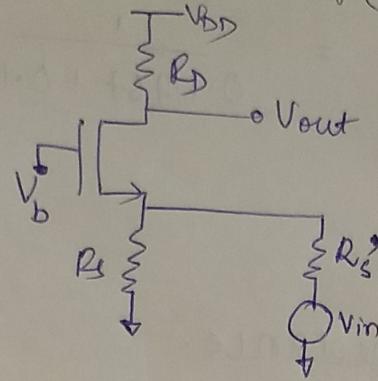

$$\frac{V_x}{R_s} + \frac{V_x - V_{in}}{R_s'} = -\frac{V_{out}}{R_D} \quad \nparallel \quad -\frac{V_{out}}{R_D} = -g_m V_x + \frac{(V_{out} - V_x)}{r_o}$$

$$V_x \left(\frac{1}{R_s} + \frac{1}{R_s'} \right) - \frac{V_{in}}{R_s'} = -\frac{V_{out}}{R_D} \quad \nparallel \quad \left(g_m + \frac{1}{r_o} \right) V_x = \left(\frac{1}{R_D} + \frac{1}{r_o} \right) V_{out}$$

$$V_x = \frac{(R_D + r_o)}{(1 + g_m r_o) R_D} V_{out}$$

$$\left(\frac{(R_D + r_o)}{(1 + g_m r_o) R_D} \right) \left(\frac{1}{R_s} + \frac{1}{R_s'} \right) V_{out} + \frac{V_{out}}{R_D} = \frac{V_{in}}{R_s'}$$

a) $A_V = \frac{V_{out}}{V_{in}} = \frac{\frac{1}{R_s'}}{\frac{(R_D + r_o)}{(1 + g_m r_o) R_D} \left(\frac{1}{R_s} + \frac{1}{R_s'} \right) + \frac{1}{R_D}}$

for $R_s' = 1M\Omega$

$$A_V = \frac{1/10^6}{\frac{60K}{510K} \left(\frac{1}{5K} + \frac{1}{1M} \right) + \frac{1}{10K}} = \frac{10^{-2}}{1.17647K \times \frac{1005K}{5K \times 1M} + 1} = \frac{10^{-2}}{2.365 \times 10^{-4} + 1}$$


$$\approx 9.99763 \times 10^3$$

$$= 8.0873 \times 10^{-3}$$

for $R_s' = 1\Omega$

$$A_v = \frac{1}{\frac{60K}{570K} \left(\frac{1}{5K} + 1 \right) + \frac{1}{10K}} = \frac{1}{0.11767 + 0.1m} = \frac{1}{117.77m} = 8.491126$$

b) Calculation of O/p impedance.

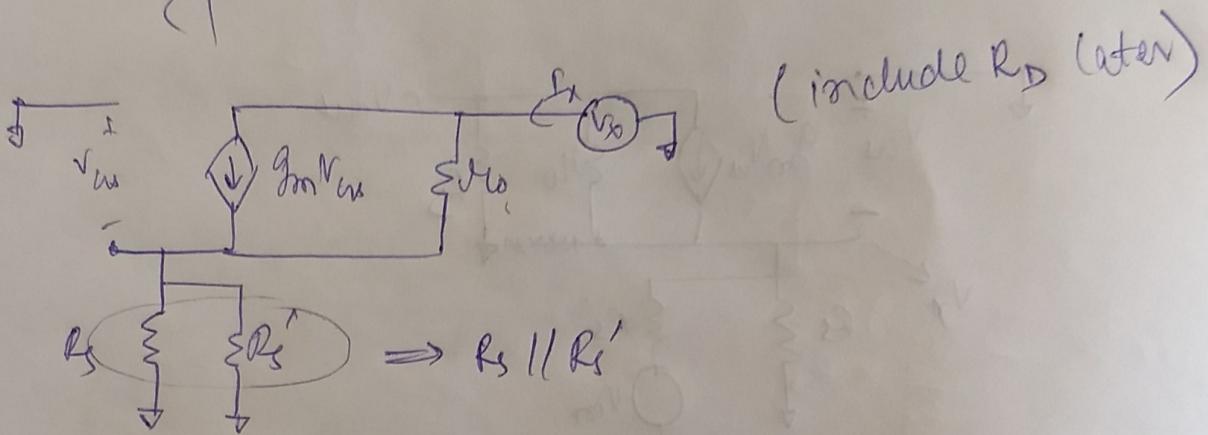

expression similar to that of common source.

$$R_{out}' = R_D \parallel \left[(R_s \parallel R_i' + (1 + g_m (R_s \parallel R_i')) R_o \right]$$


$$\text{for } R_s' = 1M\Omega, R_s \parallel R_i' = 4.975K\Omega$$

$$\begin{aligned} R_{out}' &= 10K\Omega \parallel \left\{ 4.975K + (1 + 1m \times 4.975K) 50K \right\} \\ &= 10K\Omega \parallel 303.725K \\ &= 9.68124 K\Omega \end{aligned}$$

$$\text{for } R_s' = 1\Omega, R_s \parallel R_i' = 5K\Omega \parallel 1 = 0.9998 K\Omega$$

$$\begin{aligned} R_{out}' &= 10K\Omega \parallel [0.9998K + (1 + 1m \times 0.9998K) 80K] \\ &= 10K\Omega \parallel 100.9898K \\ &= 9.099016 K\Omega \end{aligned}$$

c) Calculation of i/p impedance

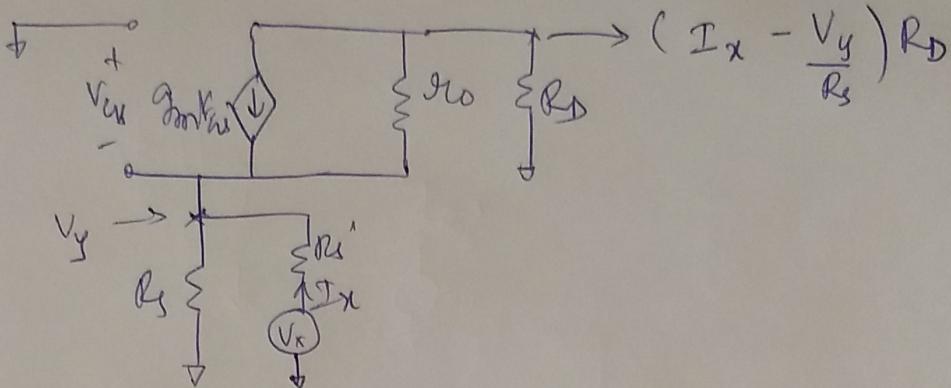

$$\frac{V_y - V_x}{R_s'} = -I_x \quad , \quad -g_m V_y + \left[\left(I_x - \frac{V_y}{R_s} \right) R_d - V_y \right] \frac{1}{R_o}$$

$$\Rightarrow V_y = V_x - I_x R_s' \quad = \frac{V_y}{R_s} - I_x$$

$$I_x \left(\frac{R_d}{R_o} + 1 \right) = \left[g_m + \frac{1}{R_o} \left(1 + \frac{R_d}{R_s} \right) + \frac{1}{R_s} \right] V_y$$

$$= \left[g_m + \frac{1}{R_o} \left(1 + \frac{R_d}{R_s} \right) + \frac{1}{R_s} \right] (V_x - I_x R_s')$$

$$I_x \left\{ \frac{R_d}{R_o} + 1 + R_s \left[g_m + \frac{1}{R_o} \left(1 + \frac{R_d}{R_s} \right) + \frac{1}{R_s} \right] \right\} = \left(g_m + \frac{1}{R_o} \left(1 + \frac{R_d}{R_s} \right) + \frac{1}{R_s} \right) V_x$$

$$R_{in} = R_s' + \frac{\left(\frac{R_d}{R_o} + 1 \right)}{g_m + \frac{1}{R_o} \left(1 + \frac{R_d}{R_s} \right) + \frac{1}{R_s}}$$

for $R_s' = 1M\Omega$

$$R_{in} = 1M\Omega + \frac{\frac{10K}{50K} + 1}{1m + \frac{1}{50K} \left(1 + \frac{10K}{5K} \right) + \frac{1}{5K}} = 1M\Omega + \frac{0.2}{1m + 0.06m + 0.2m}$$

$$= 1M\Omega + 158.7\Omega$$

$$= 1000.1587\Omega$$


for $R_s' = 1\Omega$

$$R_{in} = 1\Omega + 158.7\Omega$$

$$= 159.7\Omega$$

Q.No. 2 (A)

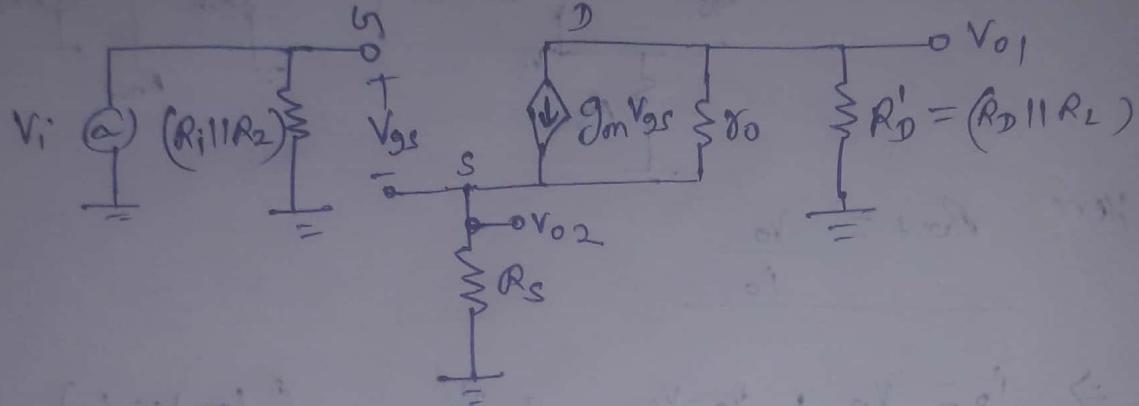→ Small Signal model for the saturation region?



(a) KCL at node S,

$$gmVgs + \frac{V_{01} - V_{02}}{r_o} = \frac{V_{02}}{R_s}$$

$$gm(V_i - V_{02}) + \frac{V_{01} - V_{02}}{r_o} = \frac{V_{02}}{R_s} \quad (\because V_{gs} = V_i - V_{02})$$

$$gmV_i = V_{02} \left(\frac{1}{R_s} + gm + \frac{1}{r_o} \right) - \frac{V_{01}}{r_o} \quad \textcircled{1}$$

and also

$$\frac{V_{02}}{R_s} = - \frac{V_{01}}{R'_D}$$

$$\Rightarrow V_{02} = - \frac{R_s}{R'_D} V_{01}$$

Putting value of V_{02} in equation $\textcircled{1}$

we get

$$gmV_i = - \frac{R_s}{R'_D} \left(\frac{1}{R_s} + gm + \frac{1}{r_o} \right) V_{01} - \frac{V_{01}}{r_o}$$

$$gmV_i = - \left(\frac{1}{R'_D} + \frac{gmR_s}{R_D} + \frac{R_s}{R_D r_o} \right) V_{01} - \frac{V_{01}}{r_o}$$

$$gmV_i = - \frac{(r_o + gmR_s r_o + R_s + R'_D) V_{01}}{R'_D r_o}$$

$$\Rightarrow g_m R'_D r_o V_i = -(r_o + R_S + R'_D - g_m R_S r_o) V_{o1}$$

$$\Rightarrow \frac{V_{o1}}{V_i} = \frac{-g_m R'_D r_o}{r_o + R'_D + R_S (1 + g_m r_o)} \quad \text{--- (2)}$$

gain for
CS amplifier.

and after putting value of V_{o1} in equation (2)

we get

$$-\frac{R'_D \cdot V_{o2}}{R_S V_i} = \frac{-g_m R'_D r_o}{r_o + R'_D + R_S (1 + g_m r_o)}$$

$$\Rightarrow \frac{V_{o2}}{V_i} = \frac{g_m r_o R_S}{r_o + R'_D + R_S (1 + g_m r_o)} \quad \text{--- (3)}$$

gain for
CD amplifier.

as value are given as

$$R_1 = R_2 = R_L = 10\text{ k}\Omega, g_m = 1\text{ mS}, r_o = 50\text{ k}\Omega$$

$$R_S = 5\text{ k}\Omega, R_D = 10\text{ k}\Omega \Rightarrow R'_D = R_D // R_L = 5\text{ k}\Omega$$

after putting values in equation (2) and (3)


$$\boxed{\frac{V_{o1}}{V_i} = -0.806}$$

$$\boxed{\frac{V_{o2}}{V_i} = 0.806}$$

(b)

⑥ Output Impedance Calculation by shorting Source. ③

→ for CS -

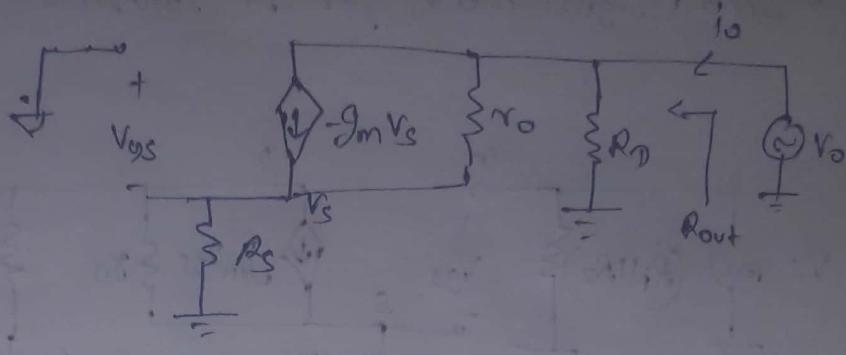

Here $R_{out} = \frac{V_o}{i_o}$

$$\Rightarrow i_o = \frac{V_o}{R_D} + \frac{V_o - V_S}{r_o} - g_m V_S \quad (\text{by KCL})$$

$$i_o = V_o \left(\frac{1}{R_D} + \frac{1}{r_o} \right) - V_S \left(g_m + \frac{1}{r_o} \right)$$

$$V_o \left(\frac{r_o + R_D}{r_o R_D} \right) = i_o + V_S \left(\frac{r_o g_m + 1}{r_o} \right) \quad \text{--- (1)}$$

and

$$\frac{V_S}{R_S} = -g_m V_S + \frac{V_o - V_S}{r_o}$$

$$V_S \left(\frac{1}{R_S} + g_m + \frac{1}{r_o} \right) = \frac{V_o}{r_o}$$

$$V_S = \frac{V_o}{r_o} \left(\frac{R_S r_o}{r_o + g_m r_o R_S + R_S} \right) = \frac{R_S V_o}{r_o R_S + g_m r_o R_S}$$

from equation (1)

$$V_o \left(\frac{r_o + R_D}{r_o R_D} \right) = i_o + \frac{(r_o g_m + 1) R_S V_o}{r_o (r_o R_S + g_m r_o R_S)}$$


$$V_o \left(\frac{r_o + R_D}{r_o R_D} - \frac{R_S (1 + r_o g_m)}{r_o (r_o + R_S (1 + g_m r_o))} \right) = i_o$$

after solving

$$V_o \left(\frac{R_D + r_o + R_s(1+g_m r_o)}{R_D[r_o + R_s(1+g_m r_o)]} \right) = i_o \quad (4)$$

$$R_{out} = \frac{V_o}{i_o} = \frac{R_D(r_o + R_s(1+g_m r_o))}{r_o + R_D + R_s(1+g_m r_o)} \rightarrow \text{for } CS \quad (4)$$

\Rightarrow Similar for CD amplifiers

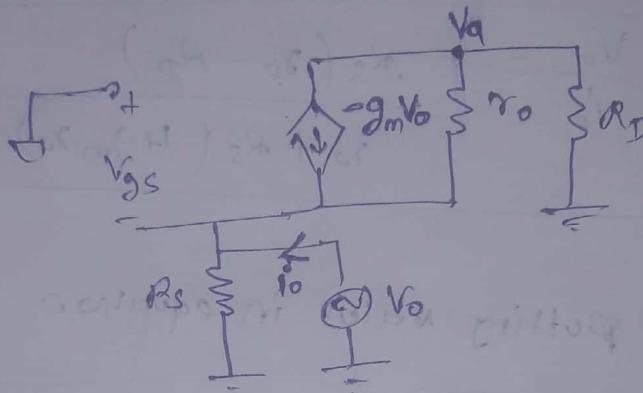

$$R_{out} = \frac{V_o}{i_o}$$

$$\Rightarrow i_o = \frac{V_o}{R_s} + g_m V_o + \frac{V_o - V_a}{r_o} \quad (\text{by KCL}) \quad (1)$$

$$\text{and } \frac{V_a}{R_D} = \frac{V_a - V_o}{r_o} - g_m V_o$$

$$V_a \left(\frac{1}{R_D} - \frac{1}{r_o} \right) = -V_o \left(g_m + \frac{1}{r_o} \right)$$

$$V_a \left(\frac{r_o - R_D}{r_o R_D} \right) = -V_o \left(\frac{1 + g_m r_o}{r_o} \right)$$

$$V_a = \frac{(1 + g_m r_o) V_o \cdot R_D}{(R_D - r_o) \cdot 1000}$$

Putting value of V_a in equation (1)

$$i_o = \frac{V_o}{R_s} \left(\frac{1}{R_s} + g_m + \frac{1}{r_o} \right) - \frac{1}{r_o} \frac{(1+g_m r_o) R_D V_o}{(R_D - r_o)} \quad (5)$$

$$i_o = V_o \left[\frac{r_o + g_m r_o R_s f_{RS}}{r_o R_s} + \frac{(1+g_m r_o) R_D f}{r_o (r_o - R_D)} \right]$$

$$i_o = V_o \frac{r_o + R_s (1+g_m r_o) - R_D}{R_s (r_o - R_D)}$$

$$\boxed{\frac{V_o}{i_o} = \frac{R_s (r_o - R_D)}{r_o + R_s (1+g_m r_o) - R_D}} \rightarrow (5) \text{ for } C_D$$

after putting value in equation (4) & (5)

we get

$$R_{out} = 9.68 \text{ kN} \quad \text{for CS}$$

and

$$R_{out} = 0.677 \text{ kN} \quad \text{for CD amper}$$


(C) input impedance

$$R_{in} = R_1 || R_2 = 5 \text{ kN}$$

2. (B) $R_i = 1 \text{ M}\Omega$

$$R_{eq} = R_1 || R_2 || R_i$$

In a common source eq. circuit is

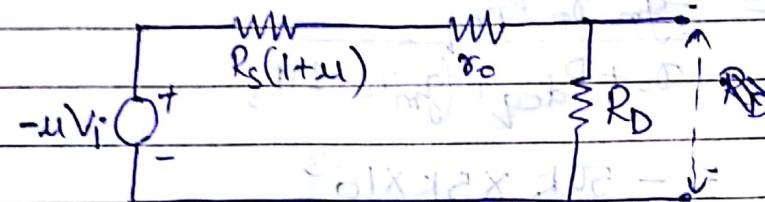


for short circuit gain.

$$\text{Output current} = \frac{uV_i}{R_s(1+u_i) + r_o + R_D}$$

$$\frac{uV_i}{R_s(1+u_i) + r_o + R_D} = \frac{uV_i}{R_s + (1+u_i) + r_o}$$

Small signal equivalent of input,

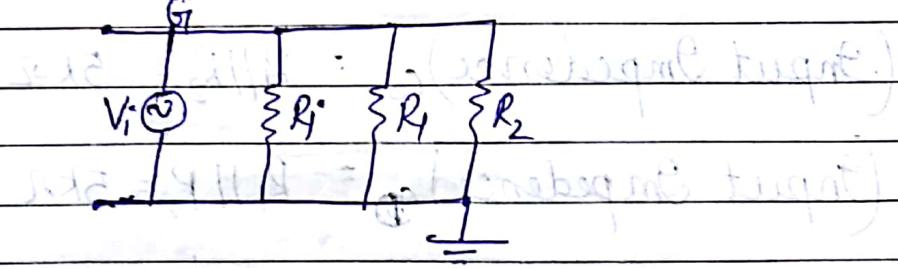

$$\text{Input Current} = \frac{V_i}{R_{eq}}$$

$$\therefore A_{id} (\text{Current Gain}) = \frac{uR_{eq}}{R_s(1+u_i) + r_o}$$

$$\mu = g_m r_o = 50$$

$$\frac{50 R_{eq}}{R_s(51) + 50} = 10 \rightarrow R_s = \frac{5 R_{eq} - 50}{51} = \frac{5(50) - 50}{51} = \frac{250 - 50}{51} = \frac{200}{51}$$

$$\therefore \text{Output Impedance} = R_D \parallel r_o + R_S(1+u) \\ = R_D \parallel 5R_{\text{req}}$$

for Output Impedance to be max.

R_D should be as high as possible

$$\therefore \text{Output impedance} = 5R_{\text{req}}$$

(D configuration)

$$\text{Current Gain} = \frac{uR_{\text{req}}}{r_o + R_D} = 10$$

$$r_o + R_D = \frac{uR_{\text{req}}}{10} = 5R_{\text{req}}$$

$$\text{O/P Imp.} = R_S \parallel \frac{r_o + R_D}{1+u}$$

If R_S is high, we cannot use G-G config.

As Current Gain < 1.

\Rightarrow CS config.

$$\text{O/P Impedance} = 5R_{\text{req}}$$

$$R_S = \frac{5R_{\text{req}} - 50}{51} \quad \text{and } R_D \text{ is as high as poss.}$$

$$(u=10) \boxed{R_D = 250 \text{ k}\Omega}$$

If we don't consider DC biasing

$$R_{\text{req}} = R_i = 1000 \text{ k}\Omega$$


$$R_S = \frac{5000 - 50}{51} = 97 \text{ k}\Omega$$

$$(u=10) R_D = 250 \text{ k}\Omega = 250 \text{ M}\Omega$$

$$\text{O/P Imp.} = 5R_{\text{req}} = 5 \text{ M}\Omega$$

If we consider DC biasing,
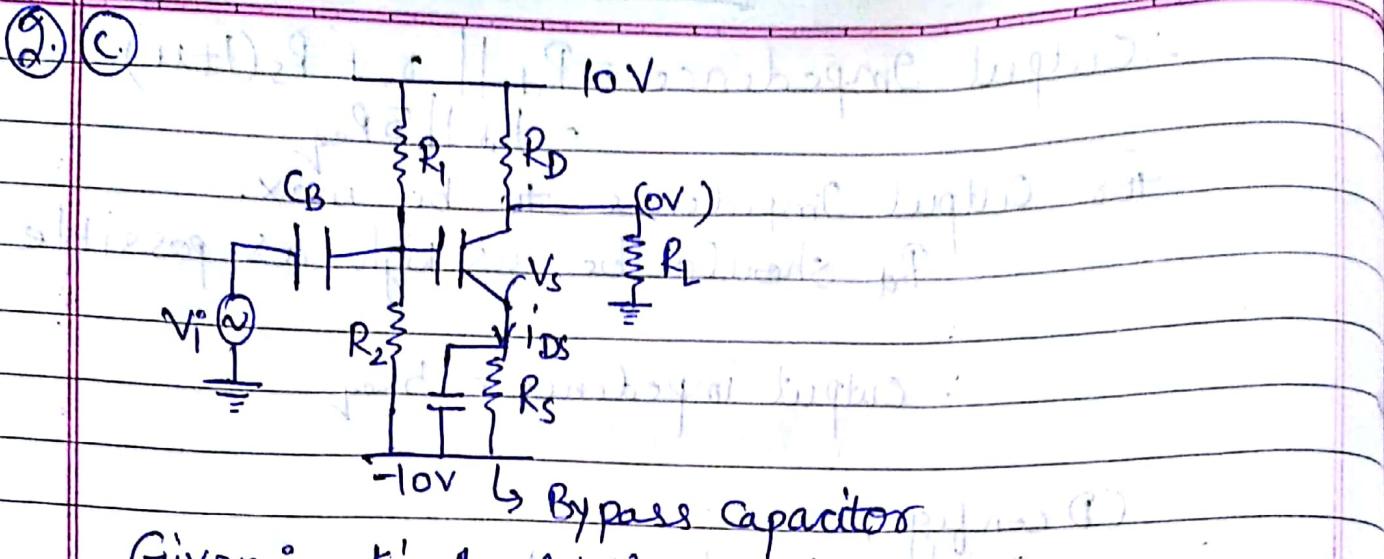
$$R_S = \frac{5R_{\text{req}} - 50}{51} \quad R_D = 250 \text{ k}\Omega$$



Given: $k' = 1 \text{ mA/V}^2$, $V_{GG} = 0$

$$V_T = 0.5V, V_{SS} = -10V$$

$$V_{DD} = 10V, \lambda = 0.01V^{-1}$$

$$V_{GG} = 0, \frac{10}{R_1 + R_2} = \frac{0 - (-10)}{R_1} \Rightarrow R_1 = R_2$$

In DC current I_{DS}

$$10 = i R_D$$

$$i = \frac{10}{R_D} = \frac{10}{10} = 1A$$

$$\text{Gain} = \frac{u(R_D || R_L)}{g_o + (R_D || R_L) + R_s(1+u)}$$

$$u = g_m r_o = \sqrt{2i k'} \cdot \frac{1}{\lambda i} = \frac{1}{\lambda} \sqrt{2k'} = \frac{1}{\lambda} \sqrt{\frac{k' R_D}{5}}$$

$$\text{Gain} = \frac{1}{\lambda} \sqrt{\frac{k' R_D}{5}} (R_D || R_L)$$

$$g_o + (R_D || R_L) + R_s \left(1 + \frac{1}{\lambda} \sqrt{\frac{k' R_D}{5}} \right)$$

for Gain to be max. $R_s \approx 0$

$$g_o = \frac{100}{i}$$

$$R_D = \frac{10}{i} \Rightarrow g_o || R_D = \frac{9.1}{i}$$

$$\text{Gain} = \sqrt{2i k'} \left(\frac{9.1}{i} || R_L \right)$$

$$\text{Gain} = \sqrt{R_L k' (g_i R_L)}$$

$$R_L \sqrt{i} + \frac{g_i}{\sqrt{i}}$$

$$\therefore \text{for max. Gain}, \frac{g_i}{\sqrt{i}} = R_L J_i \Rightarrow i = \frac{g_i}{R_L}$$

$$\text{Gain} = \sqrt{\frac{g_i k'}{2} \times R_L}$$

$$i = \frac{g_i}{R_L} = \frac{k'(-V_s - V_T)^2}{2}$$

$$-V_s > V_T = 0.5 \Rightarrow V_s < 0.5$$

$$\frac{g_i}{R_L} = \frac{k' (0.5)^2}{2}$$


$$R_L \approx 72 \text{ k}\Omega$$

$$\text{Gain} = 18.2$$

$$R_S = g_i = 72 \text{ k}\Omega, R_D = 10 = 80 \text{ k}\Omega$$

$$R_1 = R_2 = 100 \text{ k}\Omega, R_L = 72 \text{ k}\Omega$$

③ @ CS-CS Amp.

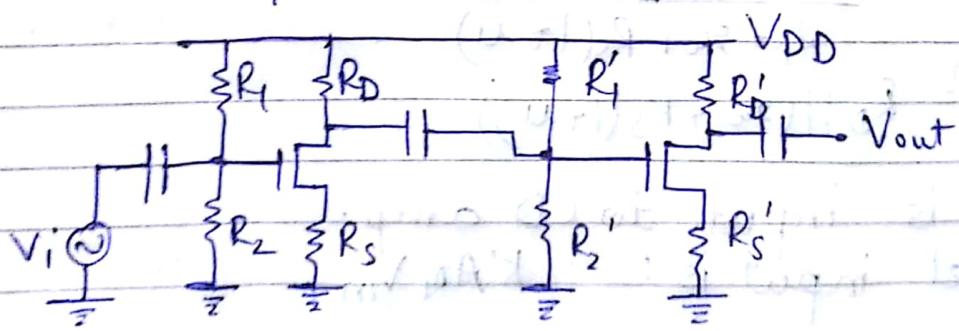

$$A_{v1} = - \frac{g_m r_o R_D}{R_D + r_o + R_s(1+u)}$$

$$Z_{out}^{(1)} = R_D || (r_o + R_s(1+u))$$

At Gate of second, $(R_1' \parallel R_2')$ is $\frac{1}{kA_{T_1}}$

$$A_{T_1} \cdot (R_1' \parallel R_2') = kA_{T_1}$$

$$(R_1' \parallel R_2') + Z_{out}$$

$$V_{out} = kA_{T_1} \cdot A_{T_2}$$


$$AV_2 = \frac{g_m' r_o' R_D'}{R_D' + r_o' + R_s'(1+u)}$$

$$Gain = kA_{T_1} \cdot AV_2$$

$$Z_{in} = R_1 \parallel R_2$$

$$Z_{out} = R_D' \parallel (r_o' + R_s'(1+u))$$

(b) CS-CD Amp.

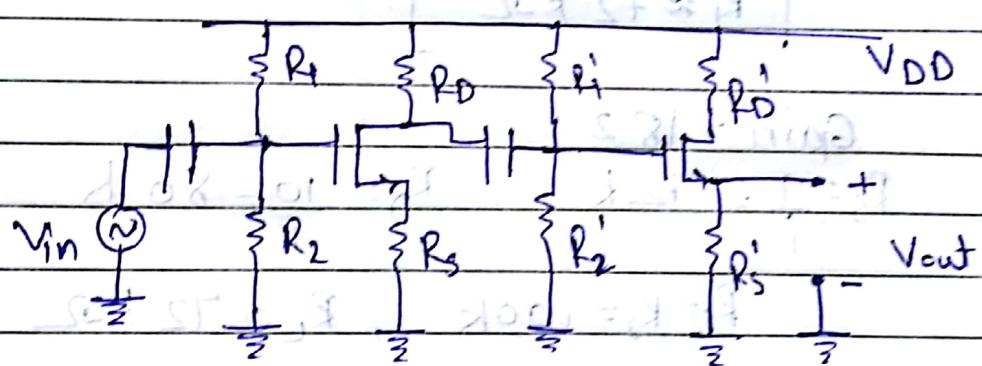

$$A_{T_1} = \frac{-uR_D}{R_D + g_{m0} + R_s(1+u)}$$

$$Z_{out}^{(1)} = R_D \parallel (g_{m0} + R_s(1+u))$$

\therefore It is input to CD amp.

Net input is: $k' A_{T_1} V_{in}$

$$k' = \frac{(R_1' \parallel R_2')}{Z_{out}^{(1)} + (R_1' \parallel R_2')}$$

$$Z_{out}^{(1)} + (R_1' \parallel R_2')$$


$$\frac{\text{Output}}{F' A_{\text{v}}, \tau_{\text{in}}} = \frac{+ u R_D}{R_D + r_o + R_s(1+u)} = A_{\text{v}2}$$

$$\text{Gain} = \frac{A_{\text{v}1}}{\tau_{\text{in}}} \cdot \frac{V_o}{V_{\text{in}}} = F' A_{\text{v}1} \cdot A_{\text{v}2}$$

$$Z_{\text{in}} = (R_1 || R_2)$$


$$Z_{\text{out}} = R_s' || \frac{R_D + r_o}{1+u}$$

(c) CS-CG Amp.

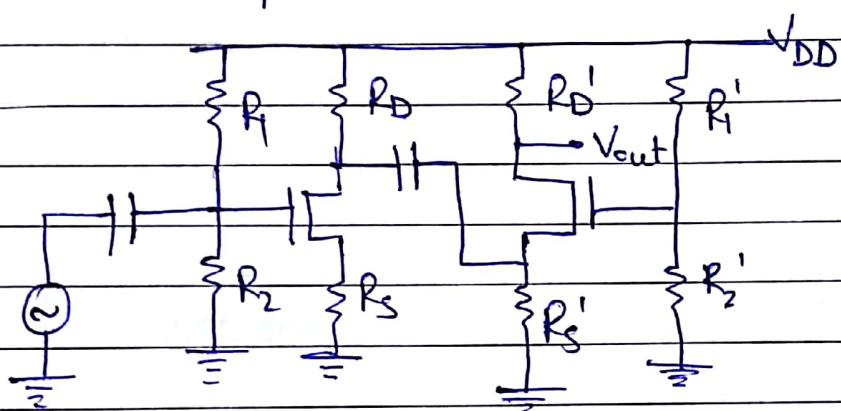

$$A_{\text{v}} = \text{Gain} = \frac{-u R_D}{R_D + r_o + R_s(1+u)}$$

$$Z_{\text{out}} = R_D || (r_o + R_s(1+u))$$

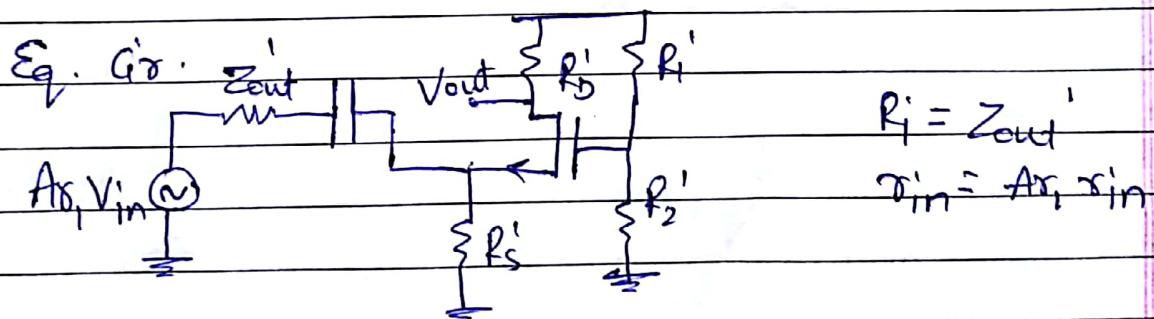

$$A_{\text{v}} = A_{\text{v}1} \cdot A_{\text{v}2}$$

$$Z_{\text{out}} = R_D || (r_o + (1+u)(R_i || R_s))$$

$$Z_{\text{in}} = R_1 || R_2$$