

Review :

1) Features of DC-AC converters are

(a) Constant V & F

(b) $V.V.V.F$ till rated voltage & constant V
variable F above rated

2) $V.S.I \rightarrow$ Input is a voltage source

\Rightarrow I can reverse


\Rightarrow Anti-parallel diodes are essential

\Rightarrow Switching signals for devices


of the same leg are complimentary

\Rightarrow Dead time required

\Rightarrow Fast devices are used

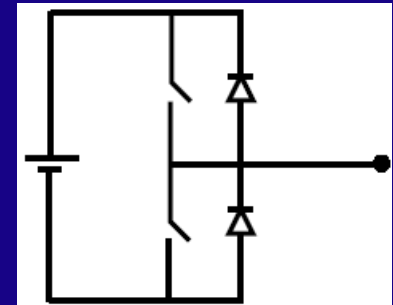

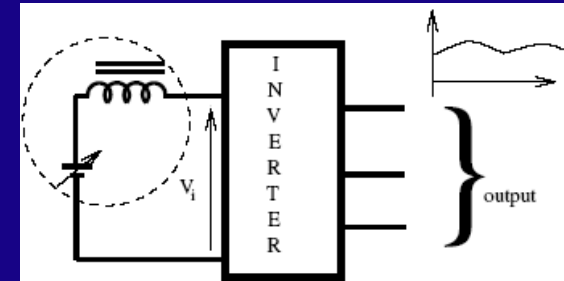- 3) C.S.I → Input is a current source
→ Input 'V' to the inverter can change



- ⇒ Due to the presence of a large 'L', there is no possibility of a shoot through fault. Easier to protect the device against any shoot through fault
- ⇒ Circuit is rugged & reliable
- ⇒ Device having anti parallel diode cannot be used

$\frac{1}{2}$ Bridge Inverter

⇒ Input is V_{DC} without any Z

⇒ O/P is a square wave with $\frac{1}{2} V_{DC}$

⇒ Has all odd harmonics

⇒ T.H.D. → 48%

⇒ Time for which S_1 / S_2 is ON will determine o/p 'F'

⇒ Switch may not carry I for π radians

Case 2 : Load = L

γ for D = γ for S = $\frac{\pi}{2}$ radians



average power = 0

input power = 0 (neglect loss)

⇒ replace battery by 'C'

⇒ VSI can supply reactive power

⇒ active input = inverter losses

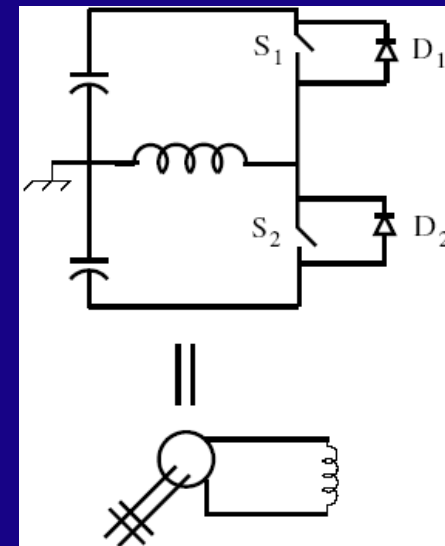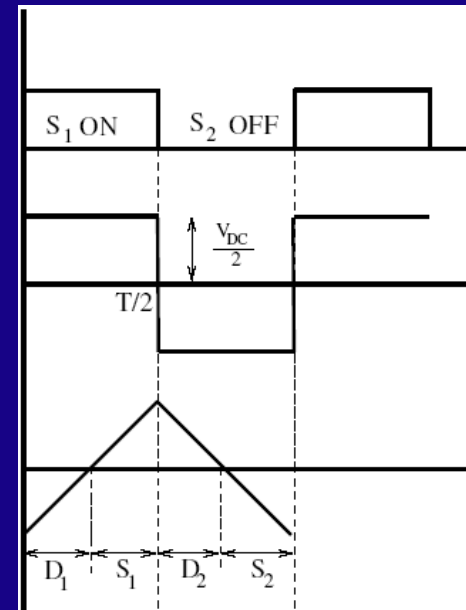

load : R-L-C

⇒ Series R-L-C with $\omega < \omega_r$

$$X_c > X_L$$

⇒ P.F. is leading



⇒ i_L is sinusoidal

⇒ 'i' through the device has become zero much before it is turned

⇒ Device is turned off of its own

⇒ Reason: Load I is leading

⇒ Load Commutation

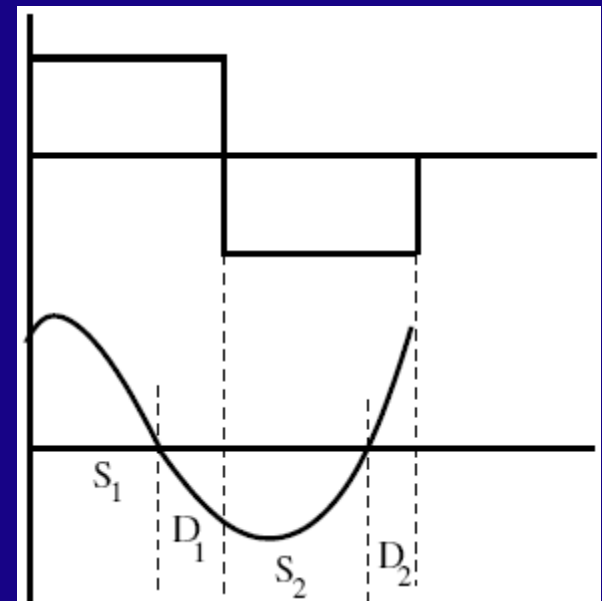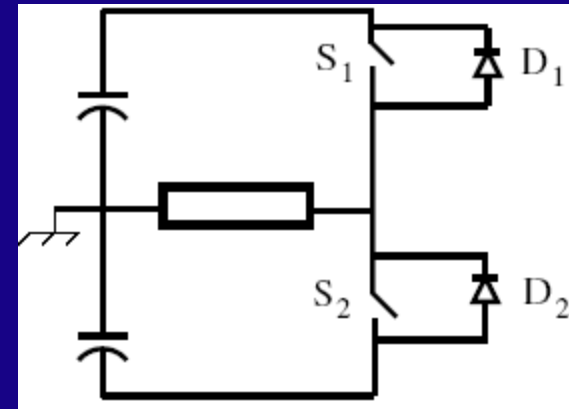



If all switches are SCR's & load is R-L

Input to DC: SCR cannot be turned OFF through Gate

$$i_{\text{DEVICE}} < i_{\text{HOLDING}}$$

Reverse voltage should be applied to turn it OFF

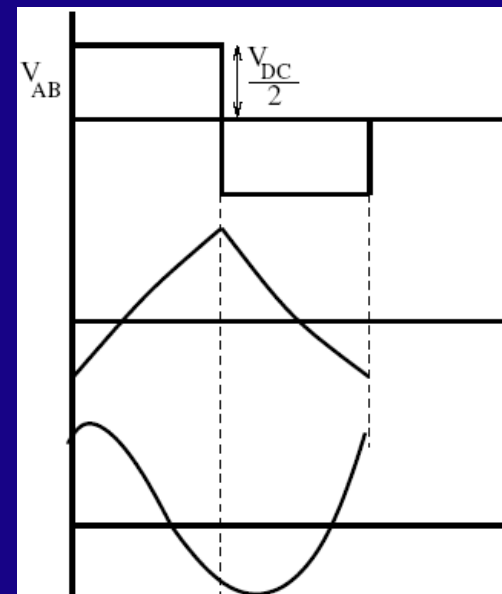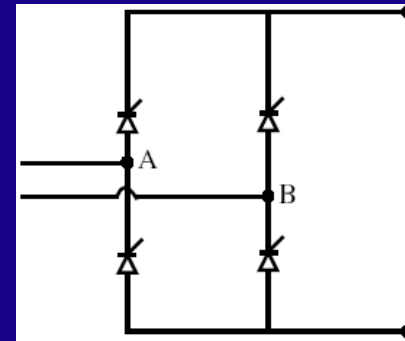- ⇒ Separate L & C
- ⇒ Forcibly turned OFF
- ⇒ Forced Commutation



⇒ Bulky & Noisy

⇒ Inverter grade SCR's are required


If P.F. is leading

'i' through the device = 0 & flows through the diode of its complimentary switch before the voltage is reversed

⇒ SCR has turned OFF

⇒ No external L-C circuit is required

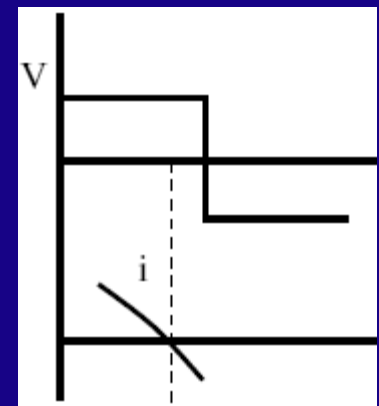⇒ Inverter using SCR's feeding a leading P.F. load is quite attractive.




- ⇒ Inverter feeding over-excited synchronous motor
- ⇒ Large power
- ⇒ Load commutated inverter fed synchronous motor

Limitations of $\frac{1}{2}$ Bridge :

$$\text{Input} = V_{DC}$$

$$\text{Output} = \frac{V_{DC}}{2}$$

- ⇒ One device is conducting at a time.

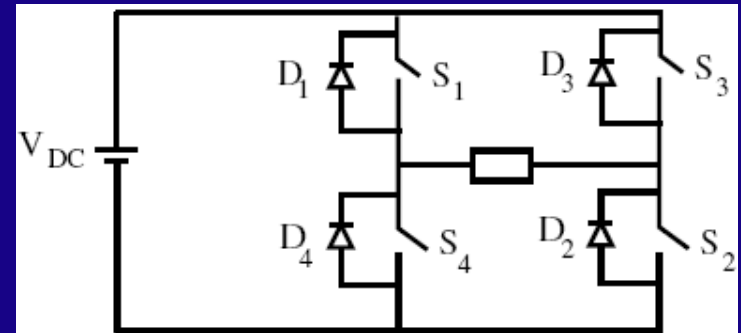

Instead use a Full Bridge

⇒ 2 devices are conducting at a time

⇒ Center point of DC link is not required

