

EE230: Experiment 1

Differential Amplifier and Current Mirrors

Devesh Kumar, 16d070044

March 10, 2018

1 Overview of the experiment

1.1 Aim of the experiment

In this experiment we try to design a differential amplifier i.e. a circuit that amplifies the difference between the two inputs supplied to it. Study, how to use current mirrors and how to find CMRR of differential amplifier

1.2 Methods


To design a differential amplifier we use CMOS. For our experiment CMOS should be in saturation mode. To achieve this we try to fix $I_{SS} = 1\text{mA}$. Instead of using a current source to achieve this we use a current mirror with a variable resistance. We adjust the resistance such a way that I_{out} is 1mA . Both the CMOS will now be in saturation mode and will amplify their respective gate source voltage. We will take the difference in the output of these two CMOS to get the differential output

2 Design

Current Mirror

To design a current mirror we take two NMOS $M1$ and $M2$ and connect their gate terminals. We further connect gate of $M1$ with its drain, this ensures that the MOS will always be in saturation as $V_{gs} = V_{ds}$, so $V_{gs} - V_t < V_{ds}$. We control the current in $M1$ by changing the resistance connected to drain of

 M1. the current in the M1 gets mirrored in M2 as the terminals of both the mos are equi potential.



Current mirror

differential amplifier with resistive loads

We amplify both the input signal by the same amount i.e. $-G_m * R_d$ and then take the difference between V_{o1} and V_{o2} to get the desired result.

expression for gain.

considering small signal model for the mos


$$V_{o1} = -G_m \times R_d \times V_{in1}$$

$$V_{o2} = -G_m \times R_d \times V_{in2}$$

$$V_{o1} - V_{o2} = -G_m \times R_d (V_{in1} - V_{in2})$$


$$A_d = -G_m \times R_d$$

 We ensure that the mos is in saturation by a current source made of current mirror. it is important that same drain current flows through both the mos



passive load

 Active Load To increase the gain and $CMRR$ we replace the resistance R_d with a current mirror setup. This ensures that resistance offered by both mos are equal and same current flows through the mos.



3 Simulation results

3.1 Code snippet

for part 1(passive load)

```

*Model file for ALD1106 and ALD1107
*SPICE Level 1
*Created by: Debapratim Ghosh, IIT Bombay
*Date: 12 Dec 2013

.MODEL ALD1106 NMOS (LEVEL=1 CBD=0.5p CBS=0.5p CGD0=0.1p CGS0=0.1p GAMMA=.85
+ KP=479u L=10E-6 LAMBDA=0.029 PHI=.9 VTO=0.8 W=20E-6)

.MODEL ALD1107 PMOS (LEVEL=1 CBD=0.5p CBS=0.5p CGD0=0.1p CGS0=0.1p GAMMA=.45
+ KP=206u L=10E-6 LAMBDA=0.0304 PHI=.8 VTO=-0.82 W=20E-6)

M1 1 2 3 7 ALD1106
M2 4 6 3 7 ALD1106
M3 8 8 7 7 ALD1106

```

```

M4 3 8 7 7 ALD1106
VSS 7 0 -4.5v
VDD 5 0 4.5v
rd1 1 5 9.7k
rd2 4 5 9.7k
rvar 8 5 6.923k

```

```

Vin 2 0 SIN(0 50m 1k)
r3 0 6 0k

```


```

.TRAN 0.05m 2m
.control
run
plot v(1)-v(4)
plot v(2)
.endc
.end


```

for active load


3.2 Simulation results

 


input when load is passive

 

output when load is passive

 

input when load is active

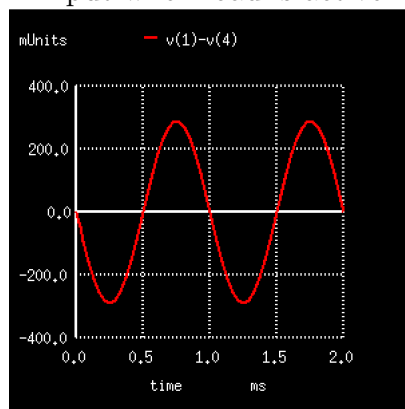


output when load is active

4 Experimental results

 4.1 Current mirror

In this part we varied r through potentiometer such that the current in the main circuit comes to be 1mA .




current mirror

4.2 Differential amplifier with resistive load

We connected the input between V_{in1} and V_{in2} . Measured the V_{o1} in one probe and V_{o2} on other probe. to get the final output we subtracted the two output using the math function of the DSO. we then find out the ratio of amplitude of input and $M(\text{output of the math function})$ to get the differential gain.

To measure the swing we increased the amplitude and saw its variation in the DSO. the swing will be the maximum and minimum amplitude for which the output does not distort.

 To get the Common mode gain we sorted both V_{in1} and V_{in2} and then applied input voltage on V_{in1} . We then measured the output i.e V_{o1} and V_{o2} on the Dso. Found out their difference with the math funtion. the common mode gain will be the ratio of amplitude of $M(\text{output of the math})$ and input voltage



passive load



differential gain at 1Khz

[differentialgain2.jpeg](#)

maximum amplitude for which ouput does not distort

frequency	Ad
1000	8.24
10000	8.32
100000	6.96
500000	2.62
1000000	1.52

1. What value of resistive load did you apply? What gain did you measure, vs what you expected? Explain why there are discrepancies, if any. Was the output swing symmetric?

We used 10kohms as the resistive load. from the data sheet of ALD1106 which came out to be $0.52 * 10^{-3}$ SI units
Gm from this K came out to be $0.72 \times 10^{-3} SI units$

$$Rd = \frac{gain}{(Gm)} = 9.7kohms \quad (1)$$

2. Was there distortion? How did you tweak the circuit to address this challenge?

Yes there was distortion in the output when we increase the amplitude of the input. this can be removed when we decrease the amplitude. Also the distortion can be due to loose connections and can be removed by checking the wire.

3. Maximum symmetric output swing at 1kHz.

1.14V

4. Measured common mode gain, and CMRR.

frequency	Acm	CMRR(db)
1000	0.085	40.14884386
10000	0.09	39.41466639
100000	0.093	37.38962772
500000	0.097	28.81155372
1000000	0.099	23.90143707

5. Measured offset voltage of differential amplifier.
80mv
6. Comparison with 2 other groups - mention which groups you compared to (names and roll numbers), and comment on any differences in observations - why are the answers different?
Anhad Bhati(16d070045)

frequency	Gain	ACM	CMRR(db)
1000	7.6	0.08	39.55447211
10000	7.04	0.08	38.88965344
100000	6.08	0.224	28.67311122
500000	2.28	0.128	25.01449755
1000000	1.28	0.128	20

Nisha Brahmankar(16d070019)

frequency	gain	ACM	CMRR(db)
1000	7.52	0.12	35.94073189
10000	7.68	0.32	27.60422483
100000	6.64	0.56	21.47960105
500000	2.44	0.64	11.62419705
1000000	1.48	0.4	11.36403448

Our gain was larger than rest of the groups the reason could be human error or loose connections. There was difference between common mode gain which could be due to the efficiency of the moss that each group had. This could also depend DSO. The difference in the value of the CMRR was not much

5 Questions for reflection

1. What difficulties did you face in performing the experiment?
Ans. The circuit was quite big on the breadboard so it was very difficult to debug the circuit. There was also noise in the circuit.
2. What advantages or disadvantages did you notice for the diff-amp with active load, as compared to resistive load?
Ans. Active load has greater gain and its CMRR value is also High

3. If you increase the supply voltage magnitude for the diff-amp, would the maximum output swing increase or decrease? Explain your answer.

Ans. the swing would increase as we use this differential amplifier on the assumption that

$$V_{gs} - V_t > v_{gs}$$

as we increase V_{gs} so the approximation becomes more valid hence swing increases.

4. In the simple current mirror, one can introduce "current gain" by sizing the two transistors differently. Assuming different W/L ratio for the transistors, obtain a value for this current gain. Can you suggest why this might be a better way to distribute currents in a circuit, as compared to setting up separate reference branches with separate resistors?

Ans. the current distributes according to the relation K_2 / K_1

If we need more than one current source in our circuit then we do this by only one I_{ref} when we use a current mirror.

Is better than a resistance as it is very hard to find a pair of resistance whose ratio remains constant. Moreover resistance is a function of temperature.

5. In class you learnt that a cascode configuration is better for large gain and low output resistance. Propose a possible circuit diagram using cascode differential amplifier, and active load, with appropriate biasing network for providing bias currents. (Only the circuit diagram made in xcircuit is expected)

Ans.

