

Problem 1 :


Find the turns ratio such that o/p V required is 100V at 0.5 for nominal i/p V = 12V

a. Compute min & max value of D, if i/p varies from 10–14V. Keep V_0 constant

b. Compute the value of L_s on sec. side so that i_2 is just continuous at the min. value of D.

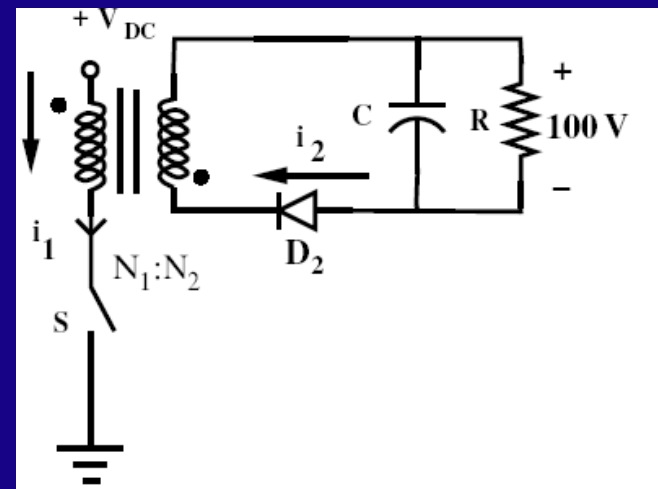c. Find the value of 'C' for o/p voltage ripple of 1% at $D = D_{\max}$

Take $V_s = 0.8V$, $V_D = 0.8V$,
 $f_s = 2KHz$



Solution :

a. Volt.sec / turn $\left(d\phi = \frac{V.DT}{N} \right)$

Balance is a must

$$\frac{1}{N_1} (V_{DC} - V_s) T_{ON} = \frac{1}{N_2} (V_0 + V_d) T_{off}$$

At nominal i/p V, $V_0 = 100V$ at $D = 0.5$

$$\therefore \frac{N_2}{N_1} = \frac{100 + 0.8}{12 - 0.8} = 9$$

Variation in D :

$$\frac{D}{(1-D)} = \frac{V_0 + V_d}{V_{DC} - V_s} \times \frac{N_1}{N_2}$$

$$\therefore D = \frac{V_0 + V_d}{(V_{DC} - V_s) \frac{N_2}{N_1} + (V_0 + V_d)}$$

If V_{DC} varies from the nominal value

so will \underline{D}

$$\begin{aligned} \therefore \text{At } V_{DC} = 12V \quad D &= 0.5 \\ &= 10V \quad D = 0.55 \\ &= 14V \quad D = 0.46 \end{aligned}$$



\Rightarrow Controller should do this function

b. Value of L_s

$$\Rightarrow Av I_2 = Av I_0$$

neglecting ΔV_0 ,

$$I_2 \Big|_{av} = \frac{V_0}{R}$$

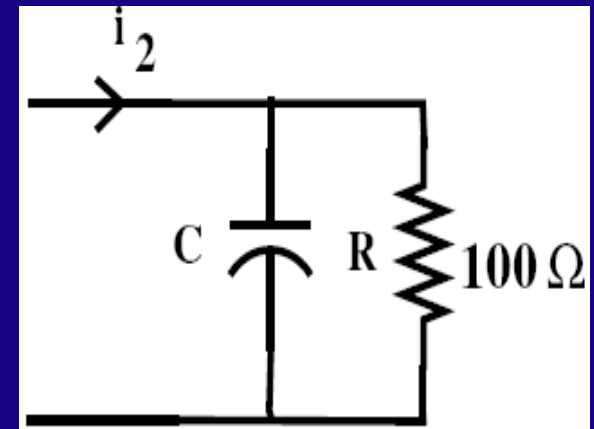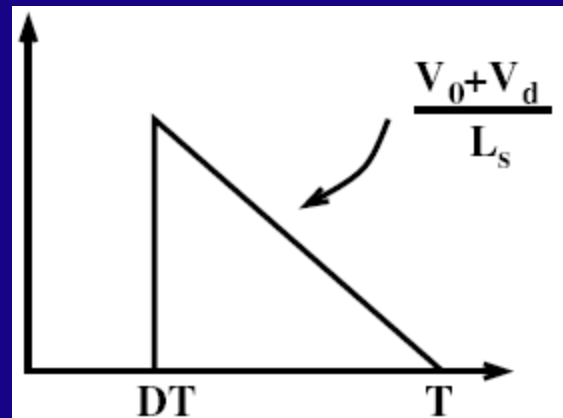

$$\frac{1}{2} I_p \frac{(1-D)T}{T} = \frac{V_0}{R}$$

$$\therefore I_p = \frac{2V_0}{R(1-D)}$$

$$\Rightarrow I_p = \frac{V_0 + V_d}{L_s} (1-D)T$$

$$\therefore L_s = \frac{V_0 + V_d}{2V_0} (1-D)^2 T R$$

' V_0 ' is held constant. I_2 should be just continuous
at $D = D_{\min} = 0.46$

$$\therefore L_s = 612\mu\text{H}$$

c. Duration for which

'C' is charging ($i_2 > I_0$)


Peak value of $i_2 = I_p$

i_2 ↓ at the rate of $\frac{V_0 + V_d}{L_s}$

∴ Peak value of $i_c = I_p - I_0$

$$\therefore t_c = \frac{I_p - I_0}{\left(\frac{V_0 + V_d}{L_s} \right)}$$
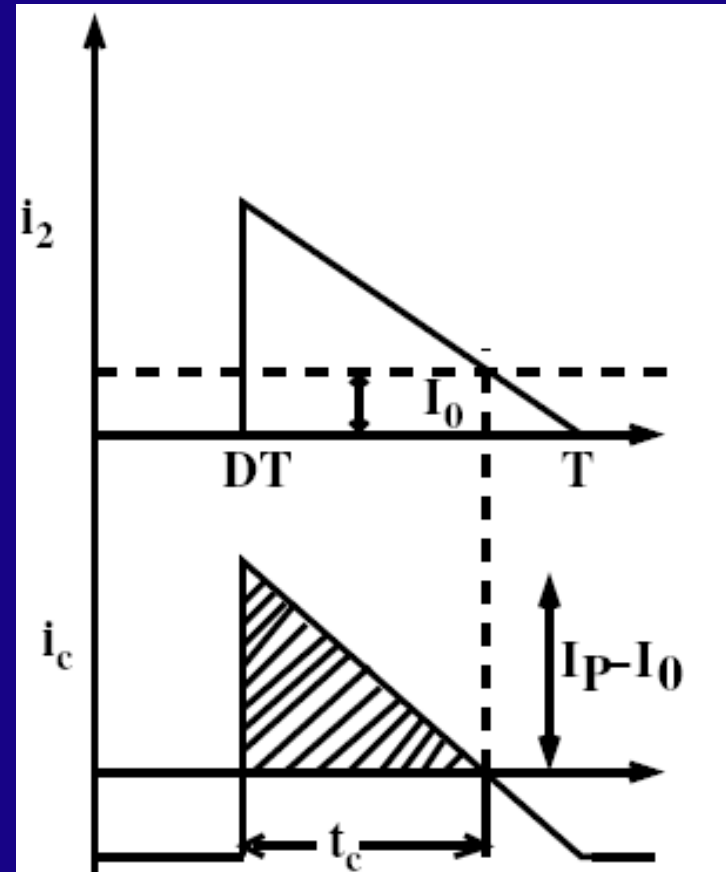
$$\Delta q = C \Delta V_0 = \frac{1}{2} \{ I_p - I_0 \} t_c$$



$$\Rightarrow \Delta q = \frac{1}{2} \{I_p - I_0\} \frac{I_p - I_0}{(V_0 + V_d)} \cdot L_s$$

we know, $I_0 = \frac{V_0}{R}$, $I_p = \frac{2V_0}{R(1-D)}$

$$\Rightarrow \Delta q = \frac{1}{2} \left[\frac{2V_0}{R(1-D)} - \frac{V_0}{R} \right]^2 \frac{L_s}{V_0 + V_d}$$

$$\Rightarrow C \Delta V_0 = \frac{1}{2} \left[\frac{V_0}{R} \right]^2 \frac{1}{V_0 + V_d} L_s \left(\frac{1+D}{1-D} \right)^2$$

$$\therefore \frac{\Delta V_0}{V_0} = \frac{L_s V_0}{2R^2 C (V_0 + V_d)} \times \left(\frac{1+D}{1-D} \right)^2 = 0.01$$

$$\Rightarrow C = 36 \mu F$$


Problem 2 :

A Forward converter is operating at the boundary of continuous / discontinuous conduction. Switching frequency is 100 kHz.

Assume $\mu \rightarrow \infty$ so that energy recovery winding is ignored

A load of 10A at 20V is being supplied

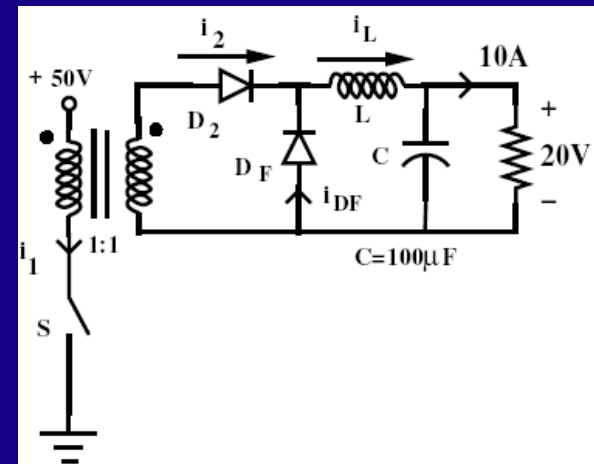- Determine the value of 'L' &
- Determine peak to peak ripple in output voltage



Solution:

$$\text{a. } V_0 = V_{\text{DC}} \left(\frac{N_2}{N_1} \right) D$$

$$\therefore D = 0.4$$

$$\therefore T_{\text{on}} = 4 \mu\text{sec}, T_{\text{off}} = 6 \mu\text{sec}$$


$$\text{av. } i_L = I_0 = 10 \text{ A}$$

$$\therefore I_p = 20 \text{ A}$$

$$L = ?$$

$$\frac{di}{dt} = 5 \text{ A} / \mu\text{sec}$$
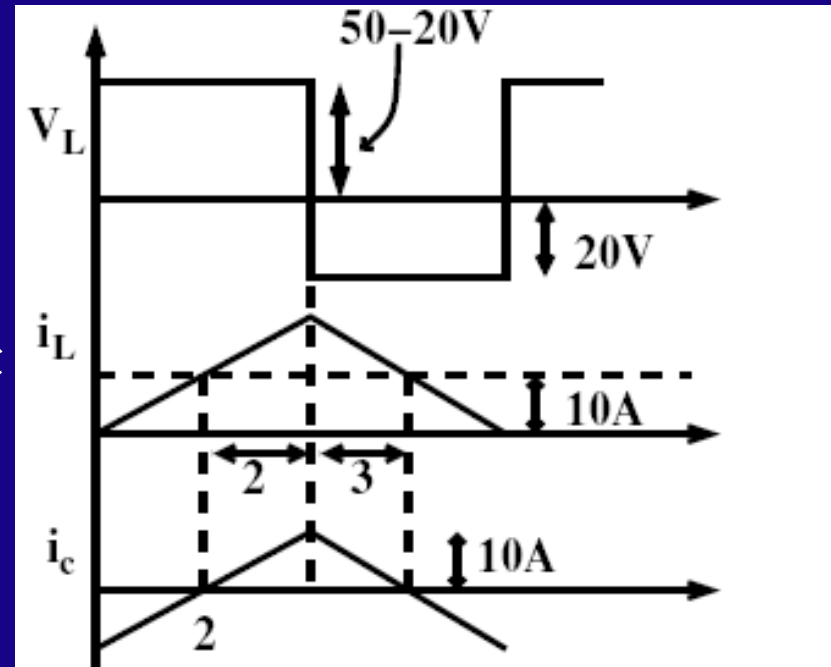
$$\therefore L = \frac{V}{\left(\frac{di}{dt} \right)} = \frac{30}{5} = 6 \mu\text{H}$$



$$\text{b. } C dV_0 = dq = \frac{1}{2} \times 10 \times 5 = 25 \mu\text{C}$$

$$\therefore \Delta V = \frac{25 \mu\text{C}}{100 \mu\text{F}} = 0.25 \text{V}$$

$$\therefore \frac{\Delta V}{V_0} = \frac{0.25}{20} = 1.25 \%$$

Flyback, Forward converter →

Operation in 1st quadrant only

⇒ Current through transformer is DC

⇒ Use 2 forward converters working in anti – phase

⇒ Bi – directional core excitation

⇒ AC current through transformer

⇒ Both converters deliver power to the load
in each half cycle

⇒ Both of them pushing power to the load

⇒ Push – Push converter

⇒ Push – Pull converter has prevailed