

Buck: $V_0 = D V_{DC}$

Boost: $V_0 = \frac{V_{DC}}{1-D}$

Buck – Boost & CUK: $\frac{D V_{DC}}{1-D}$


True only if ' i_L ' is continuous

(independent of i_L)

If it is discontinuous ' V_0 ' is higher than the above value

→ I/P, O/P are not isolated

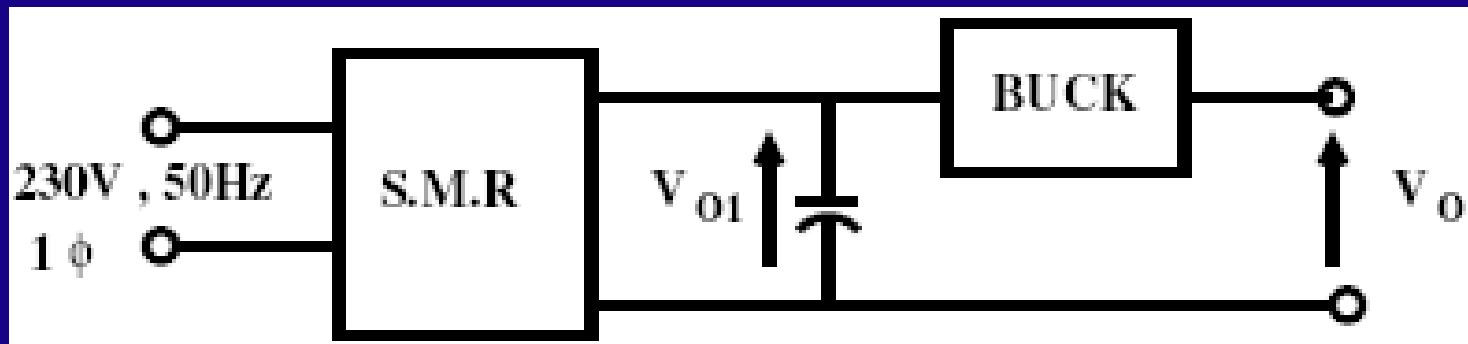i) Consider: $V_0 = 5V$, I/p is 230V, 1 ϕ , P.F. ≈ 1



$$(V_{o1}) > 325V, V_o = 5V \quad \therefore D \rightarrow \frac{5}{325} \rightarrow \underline{\underline{0.01}}$$

230 is the RMS value whereas the capacitor will give peak value

$$\text{If } F_s = 100\text{kHz}, T = 10 \mu\text{s} \quad \therefore DT = 0.1 \mu\text{s} \neq 100 \text{ ns}$$

Assumption : All ckt elements are ideal, T_{on} & T_{off} of devices = 0

'DT' itself comparable with T_{on} .

ii) As $D \rightarrow 1$, ΔV_o & Δi_L in Boost, Buck – Boost & CUK inverter \uparrow

$\Rightarrow \uparrow$ device V & I rating

\Rightarrow Assumption made during analysis are not valid for high values of 'D'

$V_o \rightarrow 0$ & not to ∞ as $D \rightarrow 1$ & V_o depends on $\frac{r}{R}$ ratio

$\therefore |V_{DC}|$ can not be greatly different from $|V_o|$

\Rightarrow Use a transformer

\Rightarrow Do not allow it to saturate

If there is $\frac{d\phi}{dt}$, 'V' will be induced in the secondary.

Recovery of trapped energy

L & S are ideal


$i \uparrow$ linearly

$$i = \frac{V}{L} t$$



⇒ Can the switch be opened ?

⇒ If opened a large 'V' spike will appear across the device.


⇒ May get damaged.

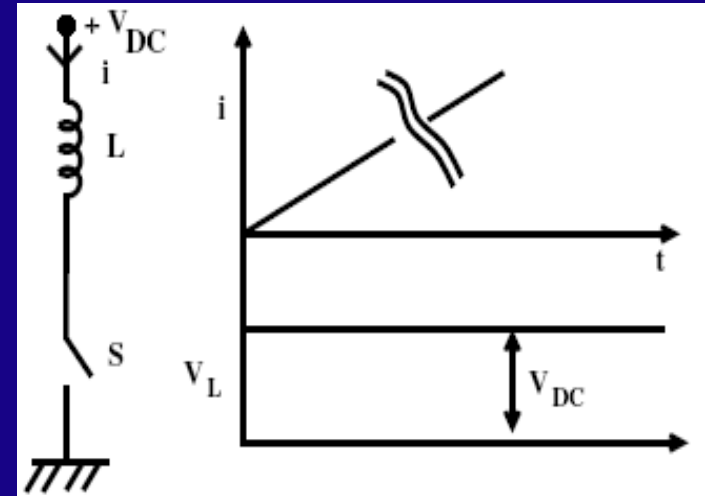

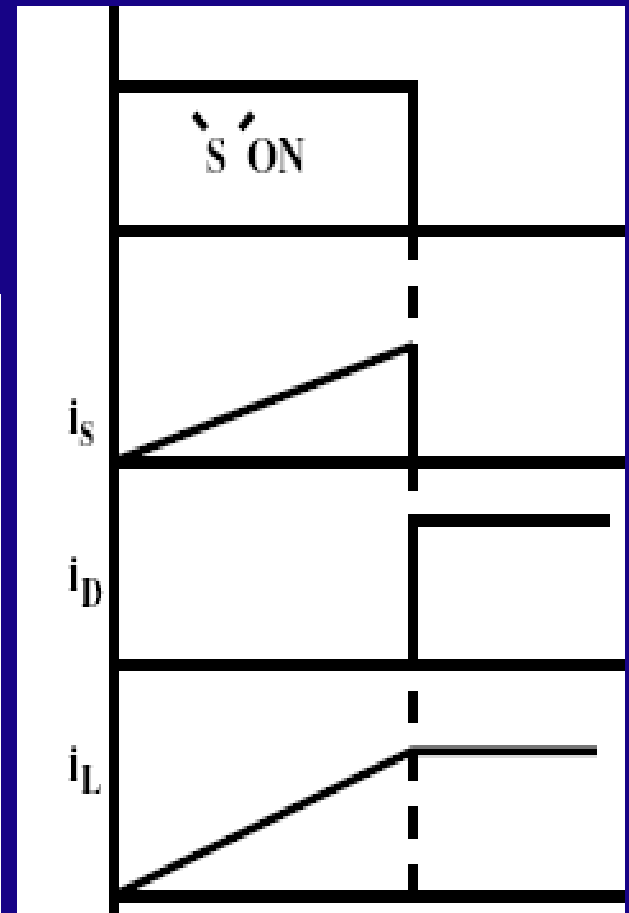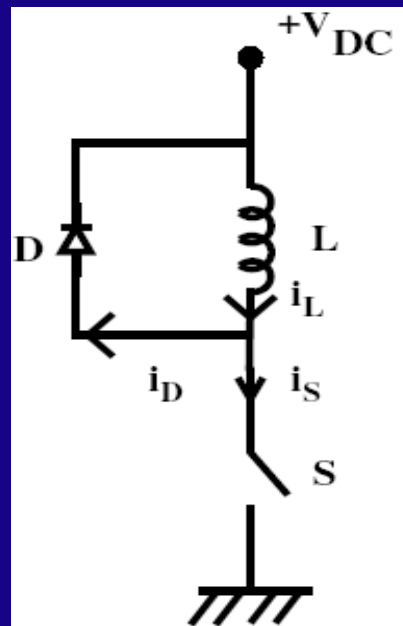- ⇒ Connect a diode 'D' across 'L'
- ⇒ 'i' will flow through 'D'
- ⇒ Circuit is lossless
- ⇒ Same 'i' continues to flow




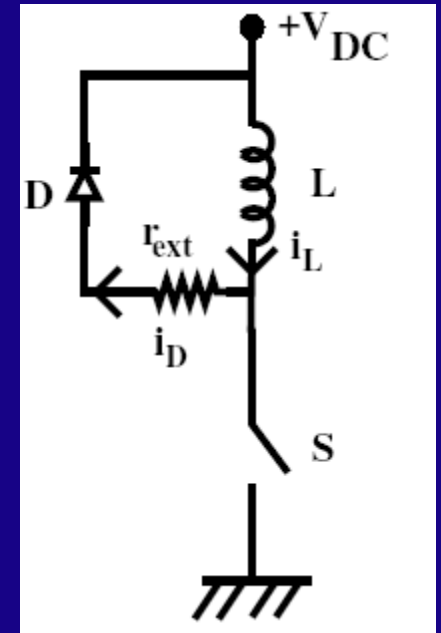- ⇒ In non-ideal circuit, both 'L' and 'D' have finite resistance
- ⇒ Stored energy is dissipated as heat in the internal 'r' of 'L' and 'D'
- ⇒ Rate of decay can be \uparrow by connecting r_{ext} in series with 'D'
- ⇒ All the energy is dissipated as heat




Can it be fed back to the source or some other load?

- ⇒ YES

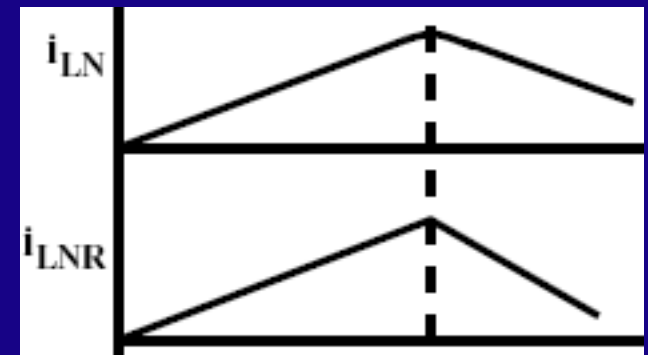

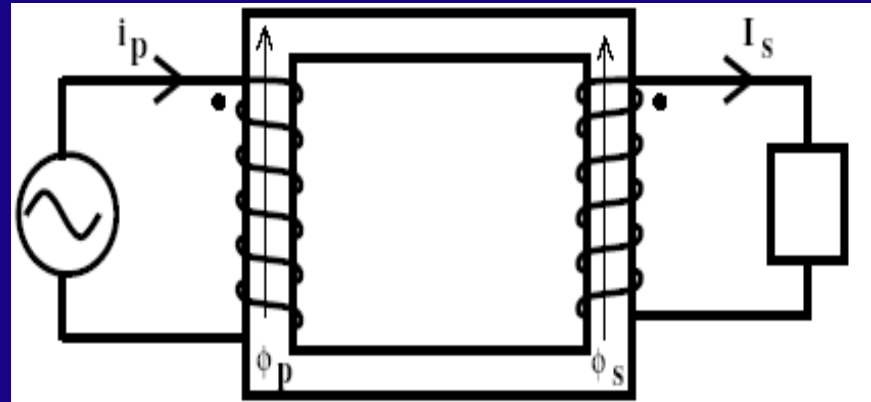
Consider a transformer.
Both coils are carrying 'I'.





Direction of ' ϕ ' due to I_p is opposite to that of the direction of ' ϕ ' due to I_s .

\therefore If i_p enters the dot, I_s will leave the dotted terminal at the secondary. (In that case ϕ_s opposes ϕ_p)

What if only one winding carries 'I'?

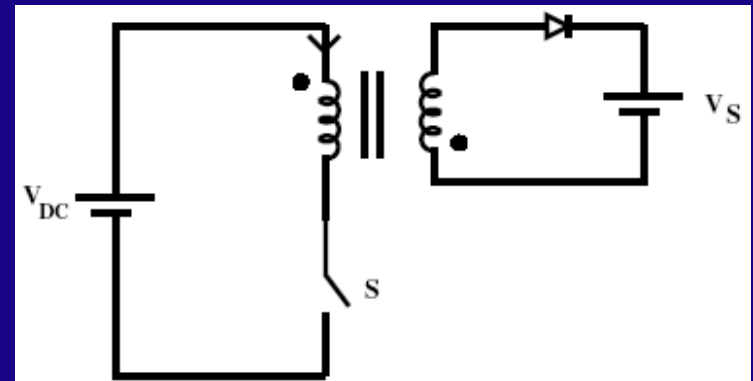

Close 'S' for 'DT' duration:

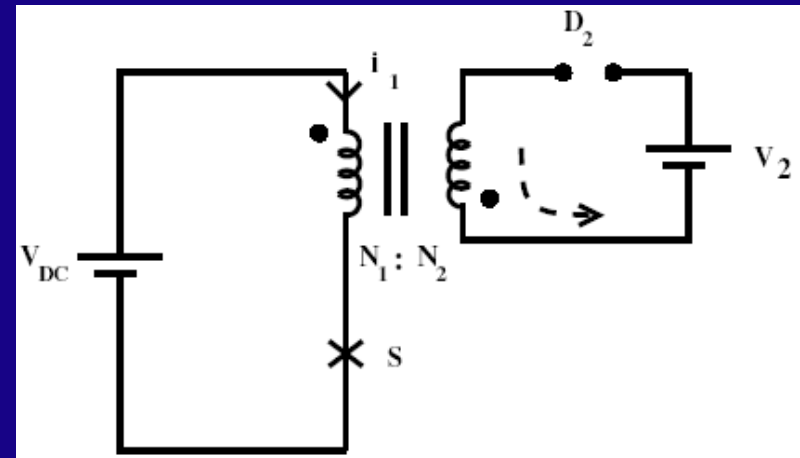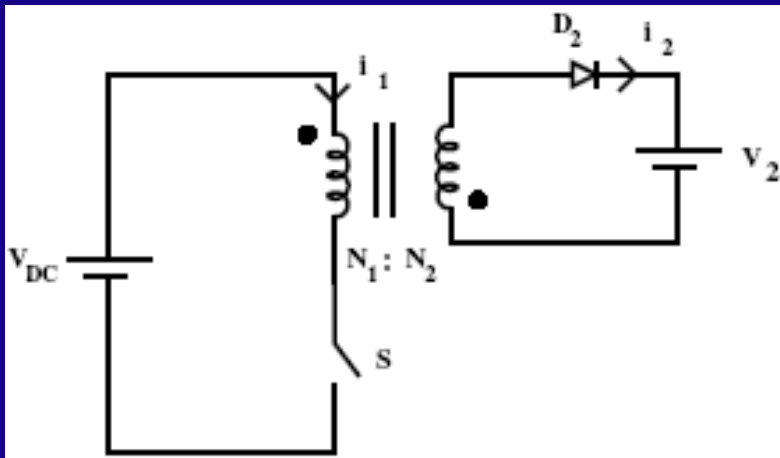

' i_1 ' starts flowing \Rightarrow Enters the dot in the primary

\Rightarrow Correct direction of ' i_2 ' is to leave the dot.

Not possible due to diode D_2 .

\therefore No current flows in the secondary when ' i_1 ' is flowing in the primary. ' \bullet ' is +ve.

'V' applied to primary winding of N_1 turns = V_{DC}

\therefore 'V' induced in the secondary winding of N_2 turns = $V_{DC} \frac{N_2}{N_1}$

with ' \bullet ' as +ve.

Anode pot. of D_2 w.r.t ' \bullet ' terminal = $-V_{DC} \frac{N_2}{N_1}$

Cathode pot. of D_2 w.r.t ' \bullet ' terminal = V_2

\therefore 'V' across D_2 = $-V_{DC} \frac{N_2}{N_1} - V_2 = -(V_{DC} \frac{N_2}{N_1} + V_2)$


No $i_2 \therefore i_1 = i_m$ source supplying as the magnetising current.

Flux is established in the core.

Neglect winding resistance & leakage reactance.

$\Rightarrow V_{DC}$ is applied to L_m

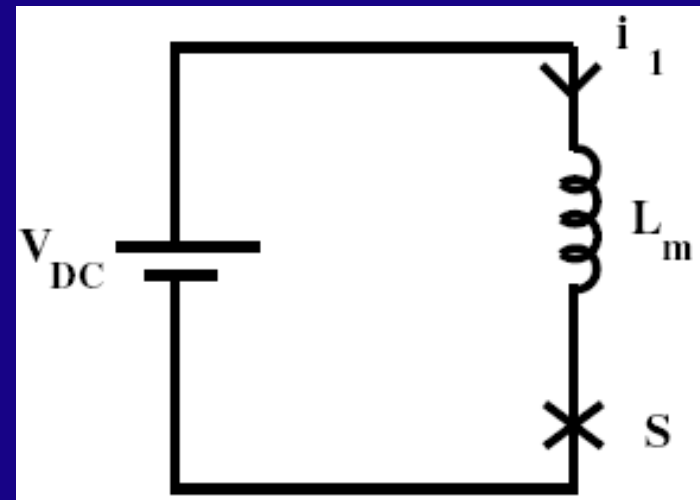$\rightarrow 'i_m' \text{ \& } \therefore '\phi' \text{ in the core } \uparrow \text{ linearly.}$



'S' is opened after DT seconds.

' ϕ ' in the core must be continuous .

$\Rightarrow '\phi' \text{ can not collapse i.e cannot become zero instantaneously.}$

' ϕ ' tries to \downarrow .

$\rightarrow \frac{d\phi}{dt} \rightarrow -ve \therefore '\bullet' \text{ becomes -ve}$

\therefore Other polarity (anode terminal) becomes +ve.

⇒ D_2 starts conducting

⇒ i_2 starts flowing, charges the source V_2

⇒ ' ϕ ' due to i_2 should be in the same direction

as that due to i_1 (they are not produced at the same time).

If it is in the opposite direction, ' ϕ ' in the core, collapses.

⇒ If i_1 enters the ' \bullet ', then i_2 also enters the ' \bullet '


'V' across N_2 turns = V_2 , with ' \bullet ' as -ve.

'V' induced in N_1 turns = $V_2 \frac{N_1}{N_2}$

∴ 'V' across 'S' = $\left(V_{DC} + V_2 \frac{N_1}{N_2} \right)$

OR : Neglecting all leakage 'L' & resistance 'r'.

$$n = \frac{N_1}{N_2}$$

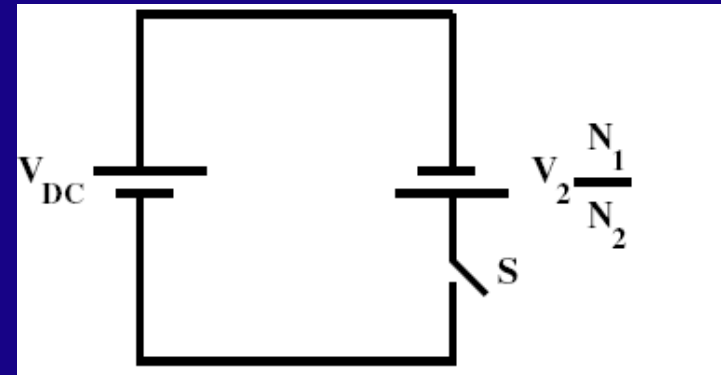

'S' is closed

' i_1 ' \uparrow linearly (flows in $L_m \therefore i_1 = i_m$)

No i_2 flows in the secondary due to D_2

\therefore 'V' induced in the secondary winding of N_2 turns = $V_{DC} \frac{N_2}{N_1}$

with ' \bullet ' as +ve.

Open 'S'

$i_1 = i_m$ should be continuous.


\Rightarrow Starts flowing in the secondary

\Rightarrow Stored energy in L_m is transferred to nV_2

Assume nV_2 is constant.

$\therefore i_2 \downarrow$ linearly.

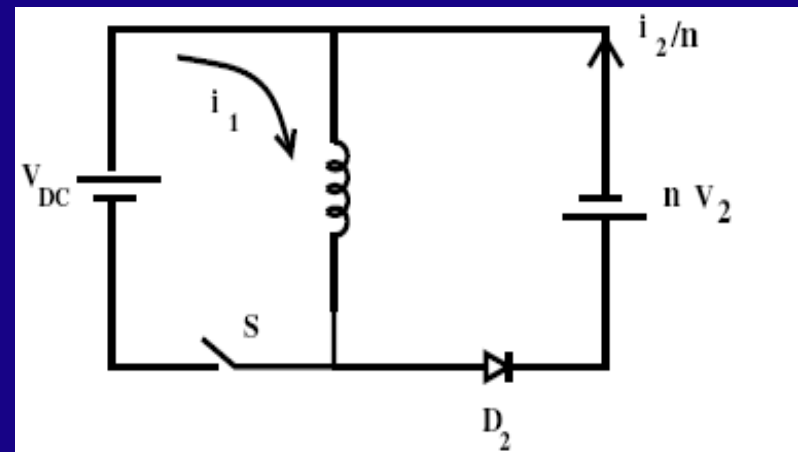i_2 may not be zero ,when 'S' is closed again.



If $i_2 = 0$

\Rightarrow flux in the core = 0

$\Rightarrow i_1$ again starts from zero.

Flux resetting (DC flux).

Operation in 1st quadrant only.

If $i_2 \neq 0$

\Rightarrow flux in the core $\neq 0$

$\Rightarrow i_1$ starts from finite value.

\therefore Energy stored in L_m can be fed back to the another source.

\Rightarrow Or to a capacitor feeding a load

\Rightarrow Fly back converter

