

# Power Electronics



**B.G.Fernandes**

Dept. of Electrical  
Engineering,

I.I.T. Bombay

[bgf@ee.iitb.ac.in](mailto:bgf@ee.iitb.ac.in)

## Outline of the course

⇒ Introduction

⇒ Power semi-conductor devices

⇒ AC-DC converters

⇒ DC-DC converters

⇒ DC-AC converters

⇒ AC-AC converters

## Reference Books:

1. M.H.Rashid, "Power Electronics: Circuits, Devices & Application" Prentice hall of India, (III<sup>rd</sup> Ed.), 2004.
2. Ned Mohan, "Power Electronics, Applications & Design", John Wiley & Sons., (III<sup>rd</sup> Ed.) 2002.
3. Cyril Lander, "Power Electronics", McGRAW Hill Co., (III<sup>rd</sup> Ed.), 1993.
4. B.K.Bose, "Modern Power Electronics & A.C. Drives", Pearson Education Inc., 2002.

## Introduction :

Quotes from IEEE papers :

We now live in a truly global society.

In the highly automated industrial front with economic competitiveness of nations, in future two technologies will dominate :

Computers and power electronics - the former providing intelligence as to "what to do" and the latter - "the means to do it".

- ⇒ "Modern computers, communication and electronic systems get their life blood from power electronics"
- ⇒ "Solid state electronics brought in the first electronics revolution, whereas solid-state power electronics brought in the second electronics revolution"



## Energy scenario :

Globally □ 87% of total energy from  
fossil fuel (coal, oil & natural gas)  
□ 6% nuclear

Remaining from renewable  
(hydro, wind, solar)

[In India □ 70% coal]

⇒ World has limited fuel

**Projected that natural uranium fuel is  
expected to last □ 50 years**


**Oil for □ 100 years**

**Natural Gas □ 150 years and**

**Coal □ 200 years**

**Will the wheels of civilization come to  
a halt at the end of the 22<sup>nd</sup> century?**

## How to solve / mitigate the problem?

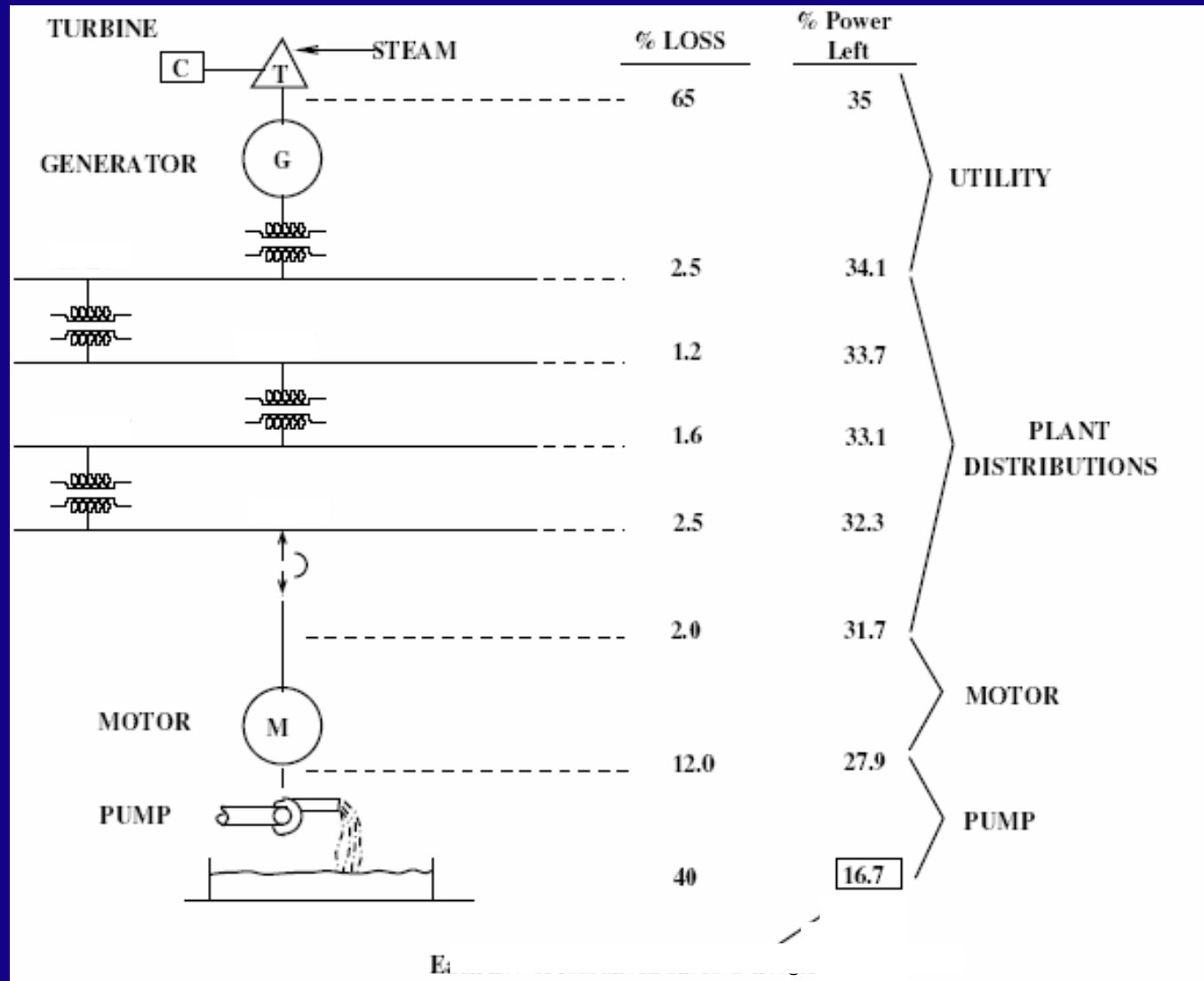



If i/p is 100 KW of fuel energy, output is around 15-20 KW of useful work,

⇒ Why spend much effort on motors and their equipment when losses are the front end?

⇒ Answer : Every KW of loss saved in the process drive, 6KW of fuel energy gets saved on the front end.

Can power from renewables (wind, solar) be explored?

**Nuclear power plant  $\Rightarrow$  Safety**

**$\Rightarrow$  Waste handling**

**Burning fossil fuel  $\Rightarrow$   $\text{CO}_2$ ,  $\text{NO}_2$ ,  $\text{O}_3$ , CO etc.**

**$\Rightarrow$  Fly ash**

**$\Rightarrow$  Global warming**

**$\Rightarrow$  Climatic changes**

**In 1997, conference at Kyoto, Japan**

**Protocol : Developed countries agreed to specific targets for cutting their emissions of gases.**

**[Mt. Everest losing height  $\square$  10cm every year]**

**$\Rightarrow$  Affects agriculture & vegetation**

**Urban pollution  $\Rightarrow$  IC engine vehicles**

- ⇒ Use electrical energy very efficiently
- ⇒ Increase the conversion efficiency
- ⇒ Estimated that 15-50% electricity consumption can be saved by extensive use of power electronics.

Bulk of the power is consumed by

- ⇒ Electric motors ⇒ majority are IM (constant speed m/c)
  - ⇒ Common loads (fans, pump)
- ⇒ Lighting

$$\underline{\text{Fan}} : T_L \propto \omega^2 ; P \propto \omega^3$$

$$\text{If } \frac{\omega_1}{\omega_2} = \frac{1}{2} ; \quad \frac{P_1}{P_2} = \frac{1}{8}$$

⇒ Frequency converter


⇒ ∴ Input 'F' can be ↓,  $N_s - N_r = N_s$  at  $s=1$  ↓

⇒ ∴  $N_s$  is low, magnitude of inrush current ↓.

⇒ Voltage dip can be eliminated

⇒ Stress on cable ↓ & life of m/c ↑.

 
⇒ Machine is being fed by constant  $V$  &  $F$  supply.



⇒  $V$  is constant  $\Rightarrow \Phi$  and  $\therefore$  core loss remains constant.




- ⇒ Assume that the load in the m/c is varying.
- ⇒ As the load  $\downarrow$ , variable loss  $\downarrow$ .  
 $\eta = \eta_{\max}$  when core loss = variable loss
- ⇒ 'V' should be  $\downarrow$  as load  $\downarrow$ .
- ⇒ Auto-transformer  $\Rightarrow$  Not a solution.  
Fan Regulator - Old rugged Vs New  
Elegant and small in size
- ⇒ In Japan, 70% of air-conditioners use variable speed drives.
- ⇒ Smooth control.

 

Slip ring IM  $\Rightarrow$  High Power motor  
 $\Rightarrow sP_{in}$  is rotor copper loss  
 $\Rightarrow$  can this be fed back to the source?  
 $\Rightarrow$  can the starting torque  $\uparrow$   
and starting current  $\downarrow$   
electronically?


D.C. machine  $\Rightarrow$  superior control characteristics

$$T = k I_a I_f$$

 

$$\text{I.M. machine} = \bar{I}_s = \bar{I}_m + \bar{I}_r$$

 Is it possible to independently  
control  $T$  &  $\Phi$  (similar to that of  
S.E. m/c)?



Sync motor  $\Rightarrow$  High power motor,  
 $\Rightarrow$  Speed depends of  $F_s$   
 $\Rightarrow$  Not a self starting m/c  
 $\Rightarrow$  Stability problem

Is it possible to make  $F_s \propto$  rotor speed ?  
 $\Rightarrow$  no stability problem?


Can the speed of the machine be  $\downarrow$  faster  
& the power be fed back to the source?

$$\frac{d\omega}{dt} = \frac{T_e - T_L}{J} \quad \text{During motoring,}$$
$$\frac{d\omega}{dt} = \frac{-(T_e + T_L)}{J} \quad \text{During regeneration}$$

$\Rightarrow$  Power conservation & faster  
deceleration
 
## Power supply :

50Hz step down transformer  
⇒ can the size and weight of  
transformer be reduced?



Speed of PC ↑

IC's ⇒ TTL, CMOS

As clock  $F$  ↑, biasing voltage ↓

⇒ 0.9V, 100A DC power supply  
will be required 2 years from now

⇒ Can this be designed?



## Applications in Power Systems :



- ⇒ If lagging VAR, demand  $\uparrow |V_R| \downarrow$ .
- ⇒ Desired that  $|V_R|$  should remain constant.
- ⇒ Provide reactive power support.

⇒ If 'C' is connected at the receiving end

$$\Rightarrow Q = \frac{V_R^2}{X_C} \downarrow \text{ as } V_R \downarrow .$$

⇒ "Unreliable" friend.



⇒ Smooth control of Q is not possible.

⇒ Can a circuit be designed which supplies  $\pm Q$  VARS & independent of  $|V_R|$ ?
  
## Case 1:

$$P = \frac{V_1 V_2}{X_s} \sin \delta = \frac{\sin \delta}{X_s}, \text{ assuming } V_1 = V_2 = 1 \text{ p.u.}$$



Is it possible to  $\uparrow$  P through line securely?



Now provide Q support as at the mid-point such that


$$|V_m| = 1 \text{ p.u.}$$
  
$$P = \frac{V_1 V_m \sin\left(\frac{\delta}{2}\right)}{\left(\frac{X}{2}\right)}$$



In long distance AC power transmission

- 1) Voltage drop
- 2) Stability problem

 

Can the bulk power be transformed  
by converting it to DC?



## Lighting :

(lumen/watt) for incandescent lamp <  
(lumen/watt) for fluorescent lamp

⇒ needs a ballast (lamp has -ve resistance characteristic once the arc has been struck)

⇒ operate at 50 Hz ⇒ size & noise


⇒ lossy

⇒ overall p.f. is poor

⇒ stroboscopic effect

(lamp is turned off and ignited at 100 Hz)

 - ⇒ Found that lumen output  $\uparrow$  if operating  $F$  is  $\uparrow$
- ⇒ If  $F$  is high, size of energy storage element  $\downarrow$
- ⇒ If  $F > 20$  Khz  $\Rightarrow$   $>$  audible range
- ⇒ Source side p.f. can also be improved.



## Energy from alternate source:

### Clean Technology.

#### Today's energy source

Advanced technology  
using oil, coal,  
nuclear

#### Future energy source

High technology  
generator using  
renewable resources  
like solar, wind power,  
biomass, hydro

#### Historic energy source

Simple technology  
using wind power,  
wood, hydro

→ Solar  $\Rightarrow$  o/p is DC


$\Rightarrow$  Expensive, but decreasing

→ Wind  $\Rightarrow$  cheapest, environmental clean

Wind energy now provides more than 31,000 MW of power around the world. In India Installed capacity 1900 MW

( target = 6000 MW by 2012 )

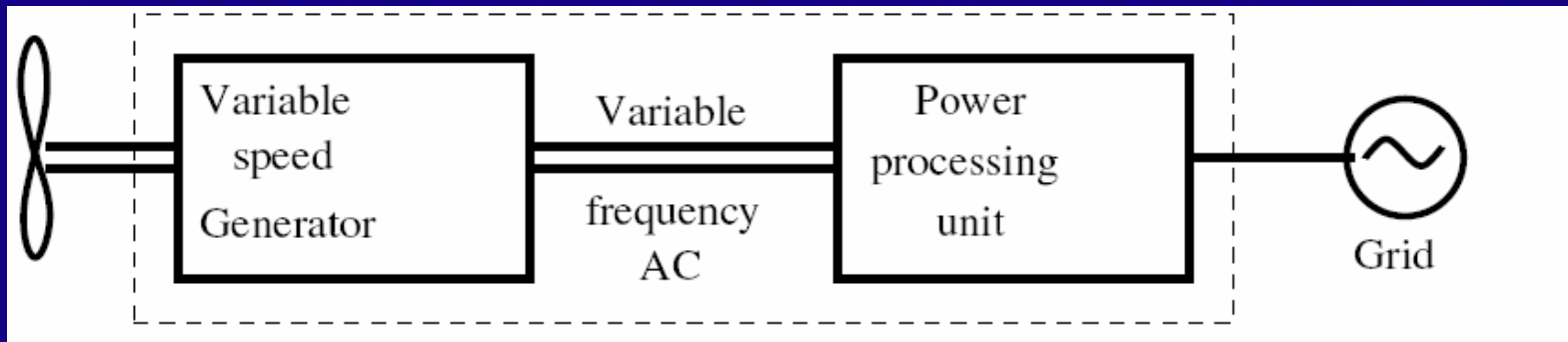It is estimated that the wind could supply 12% of the world's electrical demand by 2020



⇒ O/p is AC

⇒ Variable speed wind turbines with permanent magnet m/c are gaining popularity

⇒ O/P frequency of variable speed wind turbine is a function of speed.

⇒ If the power is to be fed to the grid, frequency should be constant

⇒ Frequency converter is required.



**Urban pollution  $\Rightarrow$  Can be  $\downarrow$  by wide spread use of electric vehicle**

**$\Rightarrow$  Use electric vehicles / hybrid EV**

**$\rightarrow$  I.C. engine + energy storage**

**Gasoline based vehicles are efficient at particular speeds.**


**$\Rightarrow$  At other speeds, motor driving the wheels**

## Power Electronics :
 
### Definition & Goal :

Power Electronics is the technology associated with efficient conversion and control of electric power by power semiconductor devices.

Goal of P.E. : To control the flow of energy from electric source to electric load.



- ⇒  $\eta$  and reliability should be high
- ⇒ size, weight and cost should be low
- ⇒  $\eta$  is a good measure of the success of any technology

As  $\eta \uparrow$ ,

- ⇒ Power loss &  $\therefore$  cooling requirement  $\downarrow$
- ⇒ Packaging density can be increased
- ⇒ Size  $\downarrow$ .

How can the circuit change the voltage level, yet dissipate low power?

---

Circuit elements = R, L, C  $\Rightarrow$  passive

Transistors, MOSFETS  $\Rightarrow$  active


L & C  $\rightarrow$  do not consume power

Power loss in the BJT =  $V_{CE} * I_C$

In the active region,  $V_{CE}$  is high

In saturation,  $V_{CE} = (V_{CE})_{SAT}$   
 $\Rightarrow$  very low

Power loss  $\square 0$

 


⇒ Resistor and active elements operated in the active region result in power dissipation


For high  $\eta$  ⇒ active elements should be operated either in saturation region or cut-off.

In addition, use only L & C elements  
e.g.: Input is 30V DC, O/P is 5V DC

⇒ Use potential divider

 

 ⇒ operate transistor in active region  
( $V_{CE} \leq 25V$ )







⇒ close to 1 for some time & then transfer it to 2

$$V_0 = V_{dc} \frac{T_1}{T_1 + T_2}$$

⇒ Power loss ⇒ 0

  ∴ Voltage drop across the device during ON period = 0



Power electronics is extensively used in

- ⇒ In motor drives
- ⇒ Power supplies (both AC & DC)
- ⇒ Lighting
- ⇒ High frequency induction heating
- ⇒ Electric welding
- ⇒ Active filters
- ⇒ Bulk power transmission
- ⇒ Electric vehicles
- ⇒ To process power from non-conventional sources

Progress in PE is primarily due to advances in power semiconductor devices.

Fast processors, dedicated chips, circuit configurations, control and estimation techniques.


## Significant events in the past history of PE

- 1783 : Concept of semiconductor (VOLTA)
- 1830 : Rectification effect of copper oxide (OHM)
- 1876 : Selenium rectifier (SIEMENS)
- 1896 : Single phase rectifier bridge circuit (POLLAK)
- 1897 : 3 phase bridge circuit
- 1901 : Invention of glass bulb mercury arc rectifier
- 1948 : Invention of the transistor
- 1953 : Germanium power diode
- 1954 : Silicon power diode
- 1957 : Thyristor (SCR) ; blocking voltage capability  
500V to 6.5KV

## Power Semiconductor Devices:

⇒ Is the heart and soul of modern P.E. equipment

⇒ Used as switches.

 

## Properties of ideal switches :

⇒ When switch is OFF (open),  $I_S = 0$ .

Should be able to withstand any  $V$  across it.

$$-\infty \leq V_{SW(OFF)} \leq +\infty$$

⇒ When ON, 'V' across it = 0 ( $V_{SW(ON)} = 0$ ) & it is capable of passing any  $I$  through it.






⇒ 'P' dissipated in the switch when ON or OFF = 0  
(conduction & blocking loss)

⇒ Switch can be turned ON  
& OFF instantaneously.

$$t_{\text{ON}} = t_{\text{OFF}} = 0$$

   ⇒ turn-on and turn-off losses  
(switching loss=0)





Characteristics of practical devices are very close to the ideal switches.


⇒ OFF state,  $I \neq 0$  &  $V \neq \infty$  in the OFF state.

⇒  $V_{SW(ON)} \neq 0$ , ON state current carrying capacity is limited.

⇒ 'P' loss in OFF state (blocking loss) & ON state (conduction loss)  $\neq 0$ .

⇒  $t_{ON} \neq 0$  ;  $t_{OFF} \neq 0$

 
- ⇒ Takes finite time to switch from one state to another
- ⇒ switching loss
- ⇒ operating point should lie within safe operating area (SOA)



Device characteristics are thermally unstable

$P_{\text{dissipated}} \neq 0$

 - ⇒ Heat and  $\therefore$  temperature rise
- ⇒ Cooling requirement




## Power switching devices :

Uncontrolled switch  $\Rightarrow$  only two terminal device.

$\Rightarrow$  ON/OFF determined by state of the circuit in which the device is connected.

'D' is ON

$$i = \frac{10 - 0.7}{10} \text{ A}$$

 

## Semiconcontrolled switch :


⇒ 3 terminal device

Switch may be turned to ONE of its state (either ON/OFF)

⇒ Other state is reachable only through the circuit.

⇒ It is possible to turn-on silicon controlled rectifier (SCR) by +ve  $I_g$

⇒ Cannot be turned OFF through GATE.

 


## Controlled Switch :

Both the states On/OFF are reachable through appropriate control signals applied to the control terminal

BJT = Bipolar Junction Transistor

Diode = 2 Terminal Device

 



$V_{AK} \rightarrow$  should be +ve

$\rightarrow 0.7V$

$\rightarrow 1.5V$  for high power diodes

Current in ON mode is limited by load.

  'V' across diode when it is reverse biased  $< V_{BD}$





⇒ ON state (conduction loss) =  $V_F * I_A$

$V_F \rightarrow V$  across the diode when it is ON


⇒ Heat sink is required as the loss  $\uparrow$

⇒ Reaches ON state with some delay  
when forward biased.


⇒ Goes to OFF state after  $t_{rr}$  when forward current goes to zero.

The minority carriers require certain time to recombine with opposite charge and to get neutralized.

 ⇒ This is reverse recovery time ( $t_{rr}$ )




 - ⇒  $t_{rr}$  → time from 1<sup>st</sup> initial zero crossing of diode current to 25% of maximum reverse recovery current ( $I_{rr}$ )
- ⇒ During  $t_{rr}$ , -ve  $I$  flows through the device.
- ⇒ Decides the maximum frequency of operation.



## Important specification : –

 - 1) Average forward current  
(to assess suitability with a power circuit)
- 2) Reverse blocking voltage (-----do-----)
- 3) ON state voltage  $\Rightarrow$  to determine conduction loss
- 4)  $t_{rr} \Rightarrow$  to assess high frequency switching capability
- 5)  $I^2t$  rating  $\Rightarrow$  short time surge energy that the diode can withstand.



## Type of diode :

- 1) Rectifier diode or slow diode:  
suitable for line frequency applications.  
Recovery time is not specified.  
6 KV, 4500A diodes are available.
  
- 2) Fast recovery diode: In high frequency  
switching application, 6 KV, 1.1KA diodes  
are available.  
 $t_{rr}$  could be  $0.1 \mu\text{sec}$ .

3) Schottky diode : They have low ON state voltage drop

V rating  $\square$  100V, I = 300A

4) Silicon Carbide Diode :

$\Rightarrow$  Ultra low power loss



$\Rightarrow$  Ultra fast switching behaviour


$\Rightarrow$  Highly reliable (no temperature influence on the switching behaviour)


  
## Thyristor or Silicon Controlled Rectifier (SCR)

- ⇒ Three element device
- ⇒ Anode (A), Cathode (K) & Gate (G)
- ⇒ A & K ⇒ power circuit terminals
- control signal is applied to the Gate w.r.t K.
- ⇒ 4 layers



 

$N_2 \rightarrow$  Layer is very thin & highly doped

$P_2 \rightarrow$  Layer is thicker & less highly doped

$N_1 \rightarrow$  (Blocking layer) is thickest & less doped

$P_1 \rightarrow$  is similar to  $P_2$

Junction  $J_3$  has low breakdown  $V$  in either direction

$J_3 \rightarrow$  cannot support high reverse voltage

When  $V_{AK} > 0$  & device current = 0


$\Rightarrow$  forward blocking mode




$J_1$  &  $J_3$  are Forward Biased (F.B)

$J_2$  is reverse biased (R.B)

When  $V_{AK} < 0$ ,  $J_2$  is F.B. &  $J_1$ ,  $J_3$  are R.B.

 $\Rightarrow J_1$  should block the entire  $V$  when R.B.



   

PQ (or  $PQ_1$  or  $PQ_2$ ) → forward blocking mode.

$i_A \approx 0$  (mA) Forward leakage I

QR (or  $Q_1R$  or  $Q_2R$ ) → negative resistance region  
→ unstable

RS → forward conduction mode.



When F.B., SCR goes into conduction mode  
when  $V_{\text{applied}} > V_{B0}$  if  $I_G = 0$ .

$V_{B0}$  → forward breakover voltage

→ forward blocking voltage

capacity is determined by  $J_2$

  - i) If  $I_G \neq 0$ , 'V' at which device goes into conduction mode ↓.  
(  $I_G$  reduces the depletion layer around  $J_2$  )





For any transistor

$$I_C = \alpha I_E + I_{CBO}$$


$\alpha \rightarrow$  common base current gain

$$\square \frac{I_C}{I_E},$$

$I_{CBO} \rightarrow$  leakage current of the C-B junction.

$$\therefore \text{ for } T_1, I_E = I_A \quad I_{C1} = \alpha_1 I_A + I_{CBO1}$$
 
$$\text{ for } T_2, I_E = I_K \quad \therefore I_{C2} = \alpha_2 I_K + I_{CBO2}$$



Now,  $I_E = I_C + I_B$

$I_{E1} = I_A$  and  $I_{B1} = I_{C2}$

$\therefore I_{C1} + I_{C2} = I_A = \alpha_1 I_A + I_{CBO1} + \alpha_2 I_K + I_{CBO2}$

$I_K = I_{B2} + I_{C2}$


for finite  $I_G$ ,

$$I_K = I_{C1} + I_G + I_{C2}$$

$$= I_A + I_G$$

$$\therefore I_A = \frac{\alpha_2 I_G + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$


$\alpha \uparrow$  with  $I_E$

 

## Review :

1)  $t_{rr} \rightarrow$  reverse recovery time

 2) Reverse recovery charge,  $Q_{rr} = \frac{1}{2} t_{rr} I_{rr}$



3) S.C.R  $\Rightarrow$  minority carrier device

$J_3 \rightarrow$  cannot block high reverse voltage


When forward blocking mode  $\rightarrow J_1, J_3 = \text{F.B.}$   
and  $J_2 = \text{R.B.}$


Entire 'V' appears across  $J_2$ .

$\Rightarrow$  Breakdown 'V' of  $J_2$  can be  $\downarrow$  by  $+I_G$ .

When R.B. : entire reverse 'V' is blocked by  $J_1$

 $\because J_2$  is F.B. &  $J_3$  cannot block high 'V'.




 


$$I_A = \frac{\alpha_2 I_G + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$

$I_{CBO}$  → reverse current  
flowing from collector  
to base with emitter open  
circuited.

↑ with temperature

 

 



$\alpha$  increases with  $I_E$

$\therefore \alpha_1$  also increases with  $I_A \because I_{E1} = I_A$


Similarly  $\alpha_2$  varies with  $I_K \because I_{E2} = I_K = I_A + I_G$

If  $I_G$  is suddenly  $\uparrow$ ,  $I_A \uparrow \because I_A = \frac{\alpha_2 I_G + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$

As  $I_A \uparrow$ ,  $\alpha_1 \uparrow$  and  $\therefore \alpha_2 \uparrow$ .

$\Rightarrow \uparrow$  in  $\alpha_1$  and  $\alpha_2$  further increases  $I_A$

$\Rightarrow$  +ve feedback.

 

If  $(\alpha_1 + \alpha_2) \rightarrow 1$ ,  $I_A$  is large (determined by load)

$\Rightarrow$  Requires a small  $I_G$

If  $\frac{dV}{dt}$  is large,  $i_{j2}$  would be


large and this may

increase  $I_{CBO1}$  and  $I_{CBO2}$ .

$\Rightarrow$  gets amplified by transistor action


$\Rightarrow (\alpha_1 + \alpha_2) \text{ may } \rightarrow 1$

□ device may turn ON.

 



 
- 3) If  $\frac{dV}{dt}$  is above a certain rate
- 4) Temperature effect  $\Rightarrow$  At high temperature, leakage  $I$  of transistor  $\uparrow$ .
- 5) By direct light radiation.


 
## Switching characteristics:

In forward blocking mode, when  $I_G$  starts flowing, there is a finite delay time ( $t_d$ ) before device current builds up

After  $t_d$ , device current builds up attains a value determined by load



If  $\frac{di}{dt}$  is very high  $\Rightarrow$  device may fail.

Initially turn ON of the device occurs near the gate-cathode periphery & then it spreads across the entire junction with a finite velocity

If  $\frac{di}{dt}$  is high

$\Rightarrow$  Current is confined to small area of the device

$\Rightarrow$  Overheating of the junction  $\Rightarrow$  destruction of the device



- ⇒ During turn-ON,  $\frac{di}{dt}$  has to be controlled
- ⇒ In conduction mode  $J_2$  is highly saturated with minority carriers
- ⇒ Gate has no further control
- ⇒ 'V' across the device  $\approx 1.5 \text{ V}$

SCR can be turned OFF by temporarily applying a -ve voltage across it

- ⇒ When reverse voltage is applied,  $I_A$  becomes zero & then reverses.

⇒  $V_{AK}$  is still +ve until  $J_1$  &  $J_3$  starts to become R.B.

⇒ When this reverse current reaches maximum junctions begin to block.

$J_1$  blocks just before  $J_3$


( $\because N_1$  is less heavily doped than  $N_2$ )

⇒ Reverse I starts decaying

⇒ Fast decay of recovery current causes a voltage overshoot across the device due to leakage L effect.

Reverse recovery current stabilizes to very low value

 
- ⇒  $J_2$  is still F.B.
- ⇒ There are still residual charge carriers trapped in  $P_2$  &  $N_1$  layer
- ⇒ Charge carriers must be given time for recombination
- ⇒ Takes considerable time



⇒ Reapplied  $\frac{dv}{dt}$  should be within a safe limit

else it may turn ON

 $t_q$  → Minimum time interval between ON state  
( $I_A$ ) current becomes zero & the instant when  
thyristor is capable of withstanding forward  
voltage without  
turning ON



## Important parameters

⇒ Average forward current (to assess suitability with a power ckt)

⇒ Reverse blocking voltage

⇒ ON state voltage drop

⇒ OFF state current

⇒  $\frac{di}{dt}$  during turn-ON &  
during turn-OFF

⇒ Reapplied  $\frac{dv}{dt}$

To design protection  
ckt (snubber ckt)

⇒  $I^2R$  rating

⇒ Device turn-OFF time ' $t_q$ ' → to assess high frequency switching capability

How to limit  $\frac{di}{dt}$  &  $\frac{dv}{dt}$  ?

High  $\frac{dv}{dt}$  → Device may turn ON with

$$I_G = 0 \text{ \& \; } V_{AK} < V_{BO}$$

Also protection against voltage spike due




to stray inductance  $\left( L \frac{di}{dt} \right)$



⇒ Connect RC ckt (snubber) across the thyristor





R → Rated such that discharge current is controlled during turn ON

   ⇒  $\frac{di}{dt}$  can be controlled by connecting a small L in series with the device



    
## Gating requirement

- ⇒  $I_G$  should be present till  $I_A > I_{\text{Latching}}$
- ⇒ One of the requirements is control ckt should be isolated from power ckt
- ⇒ Use a pulse transformer



 → One pulse may not be sufficient to turn ON the SCR



## Re view :

1) During turn – OFF

When  $J_1$  &  $J_3$  have recovered blocking capability

⇒ -ve 'V' is applied across thyristor.


In addition 'V' spike due to

$\frac{di}{dt}$  in 'L' in series with thyristor

⇒ Use RC snubber

2) If  $\frac{di}{dt} > \frac{di}{dt} \Big|_{\text{rated}}$  device will get damaged

 3) High frequency pulses are used to trigger the thyristor



## Types of SCR :-

1) Converter grade SCR  $\Rightarrow$  slow

2) Inverter grade SCR  $\Rightarrow$  fast

$\Rightarrow$  suitable for high frequency application

TT 46 F 08...13

## Electrical properties

### *Maximum rated values*

repetitive peak forward off-state and reverse voltages	$V_{DRM}, V_{RRM}$	800, 1000, 1100 1200, 1300	V <sup>1)</sup>
non-repetitive peak forward off-state voltage	$V_{DSM}$	800, 1000, 1100 1200, 1300	V
non-repetitive peak reverse voltage	$V_{RSM}$	900, 1100, 1200 1300, 1400	V
RMS on-state current	$I_{TRMSM}$	120	A
average on-state current	$I_{TAVM}$	45	A
		76	A
surge current	$I_{TSM}$	1300	A
		1150	A
$I^2 t$ -value	$I^2 t$	8450	A <sup>2</sup> s
		6600	A <sup>2</sup> s



critical rate of rise of on-state current	$(di_T/dt)_{cr}$	120	A/ $\mu$ s
gate trigger current	$I_{GT}$	max. 150	mA
gate trigger voltage	$V_{GT}$	max. 1,4	V
holding current	$I_H$	max. 250	mA
latching current	$I_L$	max. 1000	mA

## TRIAC: (1964-General Electric)



⇒ TRIAC has a complicated structure

⇒ Functionally equivalent to two thyristors connected antiparallel


⇒ Bidirectional device

⇒ Can be triggered when  $MT_2$  is +ve w.r.t.  $MT_1$  & +ve  $I_G$  w.r.t. to  $MT_1$

  ⇒ Can also be triggered when  $MT_2$  is -ve w.r.t.  $MT_1$  & -ve  $I_G$  w.r.t. to  $MT_1$



 ⇒ Used in fan regulators, Light intensity controller, Temperature controller



V – I characteristics

## Limitations :

In the case of thyristor,


$\frac{dv}{dt}$  during OFF state is as shown.

⇒ Device may go to conduction mode due to  $\frac{dv}{dt}$  during turn-OFF

⇒ When  $i=0$ , 'V' across is very different from zero

⇒ Has less time than thyristor to recover its blocking power

⇒  $\frac{dv}{dt}$  rating is lower

 

**SCR is nearly an ideal switch**

→ **Requires a sharp pulse to turn-ON**  
**(No continuous gate drive)**


→ **Block +ve as well as -ve 'V'**

→ **High V & high I devices are available**

→ **Rugged**

⇒ **Inability to turn -OFF by application of a control signal at the thyristor gate.**

 ⇒ **Inclusion of turn-OFF capability in thyristor requires device modification with some compromise in operational capability**





## Gate Turn-OFF Thyristor (GTO)

(1961-Small power GTO -GE)

(1981-2.5kV, 1kA - Hitachi, Toshiba)

⇒ can be turned-ON by +ve  $I_G$ ,

can be turned-OFF by -ve  $I_G$

  



## Description :


Four layer structure  $\Rightarrow$  similar to SCR


$\Rightarrow$  Thickness of  $P_2 <$  that in SCR

$\Rightarrow N_2$  layer is removed by itching in place  
where gate contacts are situated

$\Rightarrow$  These cells are surrounded by  
gate, they are brought together  
by a cathode plate

 
$\Rightarrow$  GTO can be seen as a large  
number of GTO's in parallel



 

Vertical cross section & perspective view of a GTO.

 ii) At regular intervals  $n^+$  region penetrates  $P_1$  layer to make contact with  $n^-$  region ( $N_1$  base layer)




⇒ Used to speed up the turn-OFF process

## ⇒ No reverse blocking capability

**(only  $J_3$  can now block -ve V. It is very low)**

 **⇒ GTO without anode short can block -ve V**



Vertical cross section & perspective view of a GTO.



High level of gate interdigitation results in


⇒ Even a remote part of cathode region is very near to a gate edge since

⇒ Fast turn-ON speed



⇒ Like SCR only the area of cathode adjacent to gate electrode is turned ON initially & then it spreads

⇒ Turn-ON area is large

⇒ High  $\frac{di}{dt}$

 

  $\Rightarrow \therefore$  GTO can be brought into conduction very rapidly





## ON – state characteristics:

⇒ They are similar to SCR

⇒ Gate signal can be removed if

$$I_A > I_{\text{latching}}$$

⇒ Recommended that +ve  $I_G$  is not removed.

⇒  $I_{\text{Holding}}$  for GTO  $>$   $I_{\text{Holding}}$  of SCR

⇒ Under transient condition if  $i_A \downarrow$  below  $I_{\text{Holding}}$   
some regions may turn off.


⇒ Anode  $I$  now  $\uparrow$  at a high rate

⇒ Could be destructive.

During turn ON,  $\frac{di_G}{dt}$  peak value of  $I_A$  should be large enough to ensure that all cathode islands begin to conduct & there is a sharing of anode current

⇒ Else hot spots & could damage the device

⇒  $I_{GM} \approx 10 I_{GT}$

 

## Turn – off of GTO:

When thyristor (or GTO) is ON, both  $T_1$  &  $T_2$  are in saturation.


By  $\downarrow I_{B2}$ ,  $T_2$  can be brought out of saturation.

The total saturation current of the GTO

$$i_A = \frac{a_2 I_G + i_{CBO}}{1 - (a_1 + a_2)} \text{ --- (A)}$$

$$i_{CBO} = i_{CBO1} + i_{CBO2}$$

 When GTO is in ON state,  $i_G$  is very small.



$$\therefore i_{A(ON)} = \frac{i_{CBO}}{1 - (a_1 + a_2)}$$

Is the current to be turned OFF

From eqn. (A),  $i_A = 0$  if there is a large gate current

such as  $i_G = \frac{-i_{CBO}}{a_2}$

$$\therefore \frac{i_{A(ON)}}{i_G} = \frac{a_2}{(a_1 + a_2) - 1}$$

$a_2 \rightarrow$  Should be as high as possible

transistor  $N_1 P_2 N_2 \Rightarrow$  should have a


high current gain

$\Rightarrow P_2$  layer should be very thin &  $N_2$  should be heavily doped.
 
## To turn – OFF a GTO:

- ⇒ Gate is reversed biased w.r.t. cathode
- ⇒ Holes from anode are extracted from P-base ( $P_2$ )
- ⇒ 'V' drop is developed in P-base region
- ⇒ Eventually reversed biases G-K junction & cut-off injection of electrons
- ⇒ As the holes extraction continues,  $P_2$  is further depleted.
- ⇒ Conduction area ↓

- ⇒ Anode current flows through the area which is far away from gate.
- ⇒ May form high current density filaments
- ⇒ May lead to localised heating
- ⇒ Should be controlled
- ⇒ Device may fail
- ⇒ Eventually device turns-OFF





## Turn – OFF :

Performance is generally influenced by the characteristics of gate turn-OFF circuit.

⇒ Turn-OFF gain is low (around 6-15 )

⇒ If  $i_A = 100\text{A}$ ,  $i_G = 10\text{A}$  (but for a short period)

As -ve  $I_G$  is established, anode

$I$  starts  $\downarrow$  after a time  $t_s \rightarrow$  storage time



Turn-OFF process can not be studied without taking the snubber into account.

(Turn on: Small L is sufficient compared to that used in SCR because of interdigitated structure.)

$t_s \rightarrow$  Storage time is of the order of few  $\mu s$ .

Application of  $-I_G$  brings about a fast & sudden  $\downarrow$  in  $I_A$ .

( $di/dt$  could be  $10^9$  A/S)

  

After  $t_s$  anode I starts  $\downarrow$  steeply to a tail current in  $t_f$  (fall time)

$\Rightarrow$  start flowing through the snubber 'c'

$\Rightarrow$  A large 'V' spike due to stray inductance in the loop formed by C, D & GTO.


$\Rightarrow$  Should be controlled

$\Rightarrow$  Loop L should be very low

$\Rightarrow$  Snubber ckt layout is very important.

$\Rightarrow$  After the spike capacitor

$$\text{limits } \frac{dv}{dt}$$

 

Tail current : ( $I_K = 0 \therefore I_G = I_A$ )


Corresponding to the free charge carriers which exist in blocking layer  $N_1$  (very thick & lightly doped).

Carriers are numerous & they recombine slowly (Higher the forward  $V$  to be blocked, thicker the  $N_1$  layer, & longer the tail current period).

$t_t$  is relatively long compared to  $t_s$  &  $t_f$ .

⇒ During  $t_f$   $V_{AK}$  is ↑

⇒ Turn-OFF losses are significant

 

Anode short : It produces a short circuit between anode &  $N_1$

⇒ Heavily doped 'N' cells make the minority carriers trapped in  $N_1$  recombine more quickly

⇒ Structure is no longer symmetrical.



## BJT (1948)

In 1975  $\Rightarrow$  300V, 400A, giant Transistor by Toshiba.

Power transistor are normally of NPN type.

N layer which forms the collector is thickest.


Reverse blocking capability is small.

$\Rightarrow$  Emitter is heavily doped to increase  $\beta$ .

Operated in quasi-saturation

& cut-off
 
$$\text{In saturation } I_c = \frac{V_{cc} - V_{CE(sat)}}{R} \\ \neq \beta I_B$$





⇒ For high voltage BJT, current gain is low when operated in saturation.

⇒ Use Darlington circuit


⇒ Requires a low base current

⇒  $\beta_1$  &  $\beta_2$  are current gains of transistors.

$$i_C = i_{C1} + i_{C2}$$

$$i_C = \beta_1 i_{B1} + \beta_2 i_{B2}$$
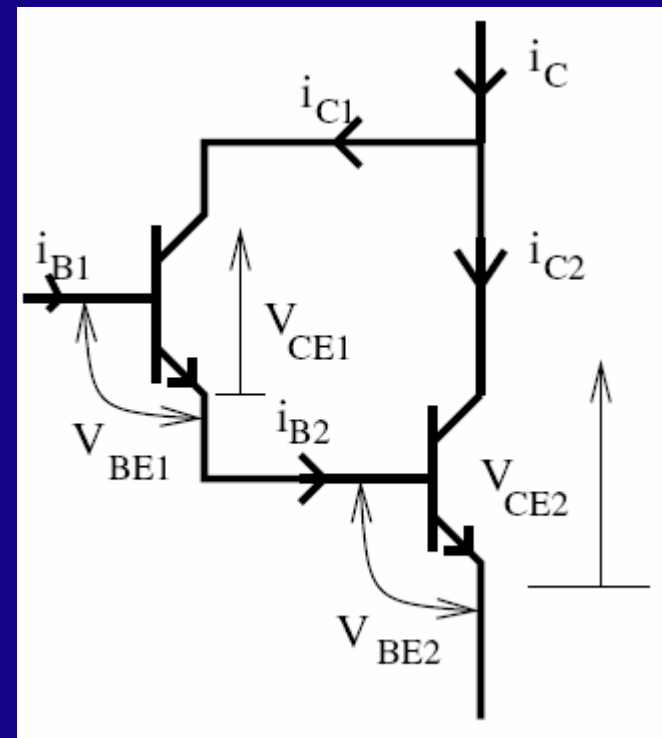
$$\text{But } i_{B2} = i_{E1} = (\beta + 1) i_{B1}$$



$$i_C = \beta_1 i_{B1} + \beta_2 (1 + \beta_1) i_{B1}$$

$$= (\beta_1 + \beta_2 + \beta_1 \beta_2) i_{B1}$$

$\Rightarrow$  Over all gain =  $\beta_1 + \beta_2 + \beta_1 \beta_2$

$\Rightarrow$  Cannot operate  $T_2$  in saturation

since  $V_{CE2} = V_{CE1} + V_{BE2}$

$\Rightarrow T_2$  may be in quasi-saturation

## On – State Safe operating Area (FBSOA)

(2) if transistor is ON for a very small time.

AB → admissible current  $I_C$


in steady state

BC → Maximum power that  
transistor can dissipate


CD → Secondary breakdown

$P_{\max}$  limitation (or  $T_{j(\max)}$ )

 assumes a uniform current density  
in the various transistor region.



 - ⇒ Difficult to achieve
- ⇒ BJT is a minority carrier device
- ⇒ Have a -ve resistance coefficient.
- ⇒ Resistance  $\downarrow$  as temp  $\uparrow$   
( $\because$  Minority carrier density  $\propto$  to intrinsic current density which increases exponentially with temperature)
- ⇒ Power dissipation  $\uparrow$  as  $R \downarrow$



- ⇒ Temp ↑
- ⇒ Goes ON till device fails  
(Thermal runaway)
- ⇒ Paralleling the devices is difficult.

DE = corresponding to max. voltage limit.

- ⇒ If BJT is ON for very small period  
boundaries of SOA expand.

## Turn-ON:


Requires  $+I_{\beta}$  to turn on

$$t_{ON} = t_d + t_r$$

$t_d \rightarrow$  delay time

$t_r \rightarrow$  rise time

 During turn-on, there is a progressive accumulation of charge in the base which increases  $i_c$ .





$t_d \rightarrow$  Corresponding to charging  
of B-E capacitance

$t_r \rightarrow$  should be very small

In order to reduce  $t_{ON}$ , supply  $I_B = 1.5I_{B(\text{required})}$

$\Rightarrow$  Transistor is operated in quasi saturation  
mode.

On state loss  $= V_{CE(sat)} * I_C$

Turn – off :

$$t = t_s + t_f$$

$t_s \rightarrow$  Storage time

= delay between the change of base current & the instant when  $I_C$  starts  $\downarrow$ .

$\Rightarrow$  Limits the upper frequency of operation


$t_f \rightarrow$  Fall time of  $I_C$

Storage time : If transistor is in saturation/quasi

saturation, width of base region  $\uparrow$

$\Rightarrow$  Equivalent to as if a part of collector is transformed to base.  $I_C$  remains constant.

 $I_C$  does not fall even though  $I_B$  has reversed.



- When excessive number of charges are injected into the base,  
 $\Rightarrow$  they are diffused in  $N^-$  layer of the collector.

- ⇒ equivalent to P-type doping & to an extension of base thickness, with a corresponding  $\downarrow$  in  $N^-$ .
- ⇒ due to a  $\downarrow$  in  $N^-$  (highly resistive layer),  $V_{CE} \downarrow$  for a given  $I_C$ . Also  $\beta \downarrow$ .
- ⇒ Quasi saturation.
- ⇒ As  $I_B \uparrow$  further,  $N^-$  is completely changed to P-type.

Highly doped  $N^+$  layer of collector prevents the base region from extending further.

## Turn-off

Involves removing all of the stored charge in the transistor

⇒ Could be accomplished by making  $I_B = 0$

⇒ Takes long time

⇒ Instead make  $I_B$  -ve

What should be the value of  $I_B$  during turn off ?

If prior to turn off, the transistor is over saturated state, if large  $I_B$  is applied


⇒ Rapid evacuation of the carriers at the base

⇒ Results in rapid cut-off of B-E junction

⇒ Holes in collector region requires certain time to recombine and -ve  $I_B$  has negligible effect on this time.



 - ⇒ From the time B-E junction is in cut-off and base collector current continuous to flow, operation is equivalent to diode during  $t_{rr}$
- ⇒ Also known as current tail
- ⇒ During this period, in most cases  $V_{CE}$  is already high
- ⇒ High losses
- ⇒ Risk of thermal runaway
- ⇒  $\uparrow i_b$  gradually in the -ve direction



## Anti Saturation network(Baker clamp)

Operating the transistor in  
Quasi saturation region  
increases  $V_{CE}$  slightly.


But  $t_s$  is greatly reduced.

Prevent the BJT from over saturating.


$$\text{Now, } V_{CE} = V_{BE} + V_{D2} + V_{D3} - V_{D1}$$

$$\Rightarrow V_{CE} \text{ is maintained at } V_{BE} + V_{D1}$$

 By connecting additional diodes in  
series with  $D_2$  or  $D_3$ ,  $V_{CE}$  can be  $\uparrow$



 - Assume Transistor is off.  
+ve  $I_B$  applied at point x  
Till  $V_{CE} = V_x + V_{D1}$   
 $D_3$  is off.  
All  $I_B$  will flow through  
 $D_2$  &  $D_3$  & into the base.



Assume that load has ↓

Since  $I_B$  is held constant corresponding to rated load, transistor might get saturated.

⇒  $V_{CE}$  ↓

⇒ When  $V_{CE} = V_x + V_{D1}$ ,  $D_1$  turns on.

Part of  $I_B$  flows through  $D_1$

$I_B$  flows into the base ↓

Transistor comes out of saturation

⇒ -ve feedback or 'control value'

⇒  $D_4$  provides a path for -ve  $I_B$

## Review :



**TRIAC** :→ Functionally equivalent to 2 thyristors connected anti-parallel.

Can be triggered by

$MT_2 + ve$   
 $I_G +ve$  || W.R.T.  $MT_1$

$MT_2 - ve$   
 $I_G -ve$  || W.R.T.  $MT_1$

  ⇒  $\frac{dv}{dt}$  rating < than that of SCR



GTO: → High power device  
(6KV, 6KA by MITSUBISHI)

Turn ON → by  $+I_G$

OFF → by  $-I_G$

⇒ 4 layer structure

⇒ Thickness of  $P_2$  layer is reduced by  $\uparrow \underline{a_2}$



thereby increasing gain during turn-off.

⇒ Gate cathode structure is highly interdigitated



⇒ High  $\frac{di}{dt}$  rating



  - ⇒ Gate current to turn-off the GTO is high  $\approx 10\%$  of  $I_A$
- ⇒ Though it is a latching device,  $I_G$  is maintained during ON period.
- ⇒ Turn-off loss is high. Can be  $\downarrow$  by reducing tail current.
- ⇒ Tail current is due to minority carriers in  $N_1$  layer.




  - ⇒ Duration of tail current  $\uparrow$  with thickness of  $N_1$  layer
- ⇒ This duration can be  $\downarrow$  by using anode short structure
- At regular intervals  $N^+$  region penetrates  $P_1$  layer to make contact with  $N^-$  region.
- ⇒ Cannot block -ve  $V$



Inductance in GTO & turn-off snubber loop should be very small.

A large voltage spike due to loop 'L'.

 

## BJT (1948)

In 1975  $\Rightarrow$  300V, 400A, giant Transistor by Toshiba.

$\Rightarrow$  Power transistors are normally of NPN type.

$\Rightarrow$  N layer which forms the collector is thickest.


$\Rightarrow$  Reverse blocking capability is small.

$\Rightarrow$  Emitter is heavily doped to increase  $\beta$ .

$\Rightarrow$  Operated in quasi-saturation

& cut-off
 
$$\text{In saturation } I_c = \frac{V_{cc} - V_{CE(sat)}}{R} \\ \neq \beta I_B$$



⇒ For high voltage BJT, current gain is low when operated in saturation.

⇒ Use Darlington circuit


⇒ Requires a low base current

⇒  $\beta_1$  &  $\beta_2$  are current gains of transistors.

$$i_C = i_{C1} + i_{C2}$$

$$i_C = \beta_1 i_{B1} + \beta_2 i_{B2}$$
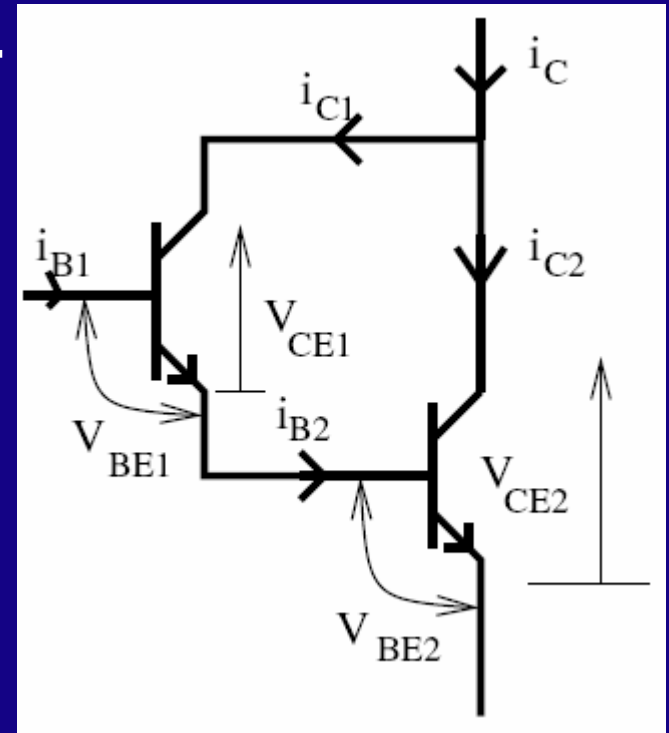
$$\text{But } i_{B2} = i_{E1} = (\beta + 1) i_{B1}$$



$$i_C = \beta_1 i_{B1} + \beta_2 (1 + \beta_1) i_{B1}$$

$$= (\beta_1 + \beta_2 + \beta_1 \beta_2) i_{B1}$$

$$\Rightarrow \text{Overall gain} = \underline{\beta_1 + \beta_2 + \beta_1 \beta_2}$$

$\Rightarrow$  Cannot operate  $T_2$  in saturation

$$\text{since } V_{CE2} = V_{CE1} + V_{BE2}$$

$\Rightarrow T_2$  may be in quasi-saturation



## On – State Safe operating Area (FBSOA)

(2) if transistor is ON for a very small time.

AB → admissible current  $I_C$


in steady state

BC → Maximum power that  
transistor can dissipate


CD → Due to secondary  
breakdown.

$P_{\max}$  limitation (or  $T_{j(\max)}$ )

 assumes a uniform current density  
in the various transistor regions.



 - ⇒ Difficult to achieve
- ⇒ BJT is a minority carrier device
- ⇒ Has a -ve resistance coefficient.
- ⇒ Resistance  $\downarrow$  as temp.  $\uparrow$   
( $\because$  Minority carrier density  $\propto$  to intrinsic current density which increases exponentially with temperature)
- ⇒ Power dissipation  $\uparrow$  as  $R \downarrow$



- ⇒ Temp ↑
- ⇒ Goes ON till device fails  
(Thermal runaway)
- ⇒ Paralleling the devices is difficult.

DE = corresponds to max. voltage limit.

- ⇒ If BJT is ON for a very small period,  
boundaries of SOA expand.

## Turn-ON:


Requires  $+I_{\beta}$  to turn on

$$t_{ON} = t_d + t_r$$

$t_d \rightarrow$  delay time

$t_r \rightarrow$  rise time

 During turn-on, there is a progressive accumulation of charge in the base which increases  $i_c$ .



$t_d \rightarrow$  delay time.

$t_r \rightarrow$  should be very small

In order to reduce  $t_{ON}$ , supply  $I_B = 1.5I_{B(\text{required})}$

$\Rightarrow$  Transistor is operated in quasi saturation mode.

On state loss =  $V_{CE(sat)} * I_C$

Turn – off :

$$t = t_s + t_f$$

$t_s \rightarrow$  Storage time

= delay between the change of base current & the instant when  $I_C$  starts  $\downarrow$ .

$\Rightarrow$  Limits the upper frequency of operation


$t_f \rightarrow$  Fall time of  $I_C$

Storage time : If transistor is in saturation/quasi

saturation, width of base region  $\uparrow$

 $\Rightarrow$  Equivalent to as if a part of collector is transformed to base.  $I_C$  remains constant.





- ⇒ When excessive number of charges are injected into the base,
- ⇒ They are diffused in  $N^-$  layer of the collector.

- ⇒ equivalent to P-type doping & an extension of base thickness, with a corresponding  $\downarrow$  in  $N^-$ .
- ⇒ due to a  $\downarrow$  in  $N^-$  (highly resistive layer),  $V_{CE} \downarrow$  for a given  $I_C$ . Also  $\beta \downarrow$ .
- ⇒ Quasi saturation.
- ⇒ As  $I_B \uparrow$  further,  $N^-$  is completely changed to P-type.

Highly doped  $N^+$  layer of collector prevents the base region from extending further.

## Turn-off

Involves removing all of the stored charge in the transistor

⇒ Could be accomplished by making  $I_B = 0$

⇒ Takes a long time

⇒ Instead make  $I_B$  -ve

What should be the value of  $I_B$  during turn off ?


If prior to turn off, the transistor is in over-saturated state and a large  $I_B$  is applied

⇒ Rapid evacuation of the carriers at the base

⇒ Results in rapid cut-off of B-E junction

⇒ Holes in collector region requires certain time to recombine and -ve  $I_B$  has negligible effect on this time.

 - ⇒ From the time B-E junction is in cut-off and base collector current continues to flow, operation is equivalent to a diode during  $t_{rr}$
- ⇒ Also known as current tail
- ⇒ During this period, in most cases  $V_{CE}$  is already high
- ⇒ High losses
- ⇒ Risk of thermal runaway
- ⇒  $\uparrow i_B$  gradually in the -ve direction



## Anti-Saturation network (Baker clamp)

Operating the transistor in  
Quasi saturation region  
increases  $V_{CE}$  slightly.


But  $t_s$  is greatly reduced.

Prevent the BJT from over saturating.

$$\text{Now, } V_{CE} = V_{BE} + V_{D2} + V_{D3} - V_{D1}$$


$$\Rightarrow V_{CE} \text{ is maintained at } V_{BE} + V_{D1}$$

 By connecting additional diodes in  
series with  $D_2$  or  $D_3$ ,  $V_{CE}$  can be increased.





 Assume Transistor is off.  
+ve  $I_B$  applied at point x  
Till  $V_{CE} = V_x + V_{D1}$   
 $D_1$  is off.  
All  $I_B$  will flow through  
 $D_2$  &  $D_3$  & into the base.



Assume that load has  $\downarrow$

Since  $I_B$  is held constant corresponding to rated load, transistor might get saturated.

$\Rightarrow V_{CE} \downarrow$

$\Rightarrow$  When  $V_{CE} = V_x - V_{D1}$ ,  $D_1$  turns on.

Part of  $I_B$  flows through  $D_1$

$\Rightarrow$  Current flowing into the base  $\downarrow$

$\Rightarrow$  Transistor comes out of saturation

$\Rightarrow$  -ve feedback or 'control value'

$\Rightarrow D_4$  provides a path for -ve  $I_B$

## Review :

1) B.J.T  $\Rightarrow$  Should not be driven into saturation

$\Rightarrow$  Storage time  $\uparrow$



$\Rightarrow$  Operated in quasi-saturation

$\Rightarrow$  Supply  $I_B$  ;  $1.5I_{B(st)}$  to  $\downarrow T_{ON}$

$\Rightarrow$  Supply -ve  $I_B$  to turn off BJT.


$\Rightarrow$  Should be gradually increased.

  $\Rightarrow$  Use Baker clamp to prevent the transistor operating in saturation.


 
## 2) Minority carrier device

- ⇒ -ve resistance coefficient
- ⇒ paralleling is difficult
- ⇒ SOA has secondary breakdown limit.







Isolation: In latching devices, pulse transformer is used.

⇒ BJT requires continuous base drive.

⇒ Use OPTO ISOLATOR


⇒ Transistor requires supply voltage.

    


As the no. of devices  $\uparrow$ , base drive circuit may become bulky.



## BU208D

 

### INTERNAL SCHEMATIC DIAGRAM

 

### ABSOLUTE MAXIMUM RATINGS


Symbol	Parameter	Value	Unit
$V_{CE0}$	Collector-Emitter Voltage ( $I_B = 0$ )	700	V
$V_{EBO}$	Emitter-Base Voltage ( $I_C = 0$ )	10	V
$I_C$	Collector Current	8	A
$I_{CM}$	Collector Peak Current ( $t_p < 5$ ms)	15	A

### ELECTRICAL CHARACTERISTICS ( $T_{case} = 25^\circ C$ unless otherwise specified)


Symbol	Parameter	Test Conditions	Min.	Typ.	Max.	Unit
$V_{CE(sat)*}$	Collector-Emitter Saturation Voltage	$I_C = 4.5$ A $I_B = 2$ A			1	V
$t_s$ $t_f$	INDUCTIVE LOAD Storage Time Fall Time	$I_C = 4.5$ A $h_{FE} = 2.5$ $V_{CC} = 140$ V $L_C = 0.9$ mH $L_B = 3$ $\mu$ H		7 550		$\mu$ s ns



## Safe Operating Area (TO-3)

 

## DC Current Gain

 

BU208D-BJT:  $V_{CEO} = 700V$ ,  $I_C = 8A$ ,  $t_s = 7\mu s$ ,  $t_f = 500ns$

$h_{FE}$  at 5A ; 5



$\therefore I_B = \underline{1} A$

$I_{B(START)} = \underline{1.5} A$

$\Rightarrow$  A small PT to drive another PT!
 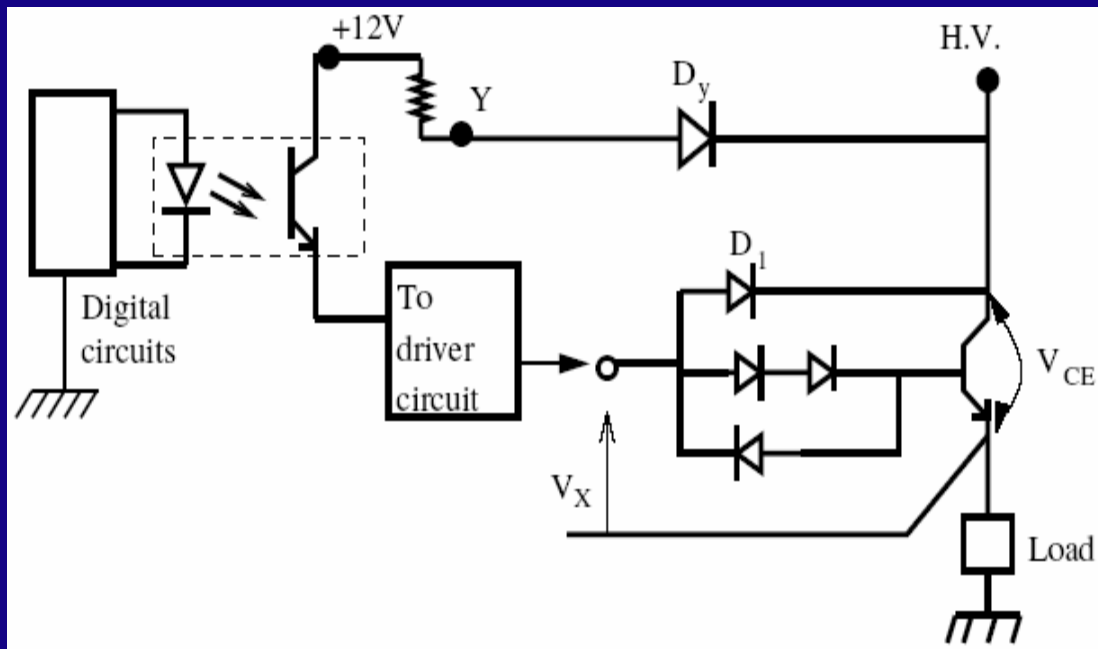
## Overload protection :

- ⇒ Cannot be protected using a fuse.
- ⇒ Fuse is not fast enough
- ⇒ Overload capacity is not much higher than rated steady state capacity.
- ⇒ Necessary to detect an overcurrent condition & remove the base drive immediately.



⇒ Sense  $V_{CE}$  during conduction.

⇒  $V_{CE}$  drops to  $V_X - V_{D1} = \text{Pot. of } Y$ , after  $T_{ON}$ .

If pot. of  $Y \uparrow$  above this limit during conduction period

→ Overload condition.

⇒ Withdraw +ve base drive & supply  $-I_B$

⇒ Signals are applied w.r.t emitter.

Pot. of emitter  $\square$  Pot. of collector, when ON.

When it is OFF = 0.


⇒ Reference point is floating.

## Power MOSFET:


(1978 : 100V, 25A power MOSFET)

MOSFET : [200V, 500A – SEMIKRON],  
[60V, 1000A - SEMIKRON]

 - ⇒ Generally low  $V$ , high  $I$  devices
- ⇒ Very popular in DC-DC conversion.
- ⇒ Metal – Oxide – Semiconductor Field Effect Transistor
- ⇒ Fast device
- ⇒ Majority carrier device
- ⇒ Unipolar device
- ⇒ Non-latching device
- D → Drain G → Gate S → Source





 

Appears as though there cannot be any I flow between D & S.

Gate is insulated from the rest of the device

⇒ No steady I


⇒ Only displacement current (like in a parallel plate capacitor).

MOSFET is in cut-off when  $V_{GS} < \text{threshold value}$ .

When  $V_{GS} > \text{threshold value}$ ,

⇒ Converts silicon surface below the gate into an N-type channel

 - ⇒ Connects source to drain
- ⇒  $I$  starts flowing.
- ⇒ Threshold value  $V_{TH}$  depends on thickness of oxide layer
- ⇒  $V_{TH}$  can be reduced by  $\downarrow$  the thickness




⇒ when  $V_{GS} > V_{GS(Th)}$  ;

⇒ Device is driven into ohmic region

$$V_{GS} - V_{GS(Th)} > V_{DS} > 0$$

⇒ Power loss is low

 ⇒ In the active region,  $I_D$  depends only on  $V_{GS}$  ; Current is said to have saturated (saturation region).



In ON state the 'channel'  
of the device behaves  
like a resistance


$$R_{DS(ON)}$$

$$R_{DS(ON)} = \left. \frac{\partial V_{DS}}{\partial i_D} \right|_{V_{GS} \text{ (constant)}}$$

$$\Rightarrow \text{Conduction power loss} = I_D^2 R_{DS(ON)}$$

BJT requires a base current for  $I_C$  to flow

 $\Rightarrow$  BJT has substantially lower voltage  
drop than MOSFET





## Internal Body Diode

Has a internal Body Diode

Connected between source & drain

→ MOS can block +ve 'V'



(junction P-N<sup>-</sup> determines this V)

→ 'i' can be either +ve or -ve.

→ -ve I through diode

→ This diode has adequate I  
& switching speed rating

→ Some applications  
require fast diode

  

## Safe Operating Area

No secondary breakdown region

SOA is limited by

AB-maximum drain  $I$  at  
steady state


CD-Maximum  $V_{DS}$  that the device  
can sustain

BC-Maximum power dissipation

⇒ Imposed by  $R_{DS(ON)}$

⇒ Has +ve resistance coefficient.

⇒ Paralleling is easy

 


## Internal Capacitor (Parasitic capacitance)

⇒ limits the switching speed
 
### 3 types

$C_{GS}$  → Dielectric is the oxide  
layer isolating G &  
source

Almost independent of  
variation in  $V_{DS}$



## Gate – Drain capacitance : ( $C_{GD}$ )

Varies considerably with  $V_{DS}$

$\Rightarrow$  ;  $C_{GS}$  when  $V_{DS}$  is low

$\Rightarrow$  Negligible when  $V_{DS}$  is high


$\Rightarrow C_{DS} \rightarrow$  Less important

$\Rightarrow C_{GD} + C_{GS} \rightarrow C_i$

$\Rightarrow C_i \rightarrow$  Input capacitance

in pico Farads

 $\Rightarrow$  During turn-ON,  $C_{GD}$  &  $C_{GS}$  must be charged through gate



## Review :

### 1) Power MOSFET

Metal Oxide Semiconductor Field  
Effect Transistor



⇒ Fast Device

⇒ Gate is insulated from source

⇒ Input I ;  $\underline{0}$

⇒ Input Z  $\rightarrow \infty$  ; it is capacitive.

  ⇒ If  $V_{GS} > V_{TH}$ , a n channel is formed,  
which connects drain and source.







## V-I characteristics

⇒ In ohmic region MOS can be represented by Resistance ( $R_{DS}$ )

⇒ BJT has substantially lower voltage drop than MOSFET.

⇒ One of the drawbacks of MOSFET.

  



⇒ Input  $C_i = C_{GD} + C_{GS}$

$C_{GD} \rightarrow$  varies with  $V_{DS}$

$C_{GD}$  ;  $C_{GS}$  when  $V_{DS} = V_{DS(ON)}$


$C_{GD}$  is very low when  $V_{DS}$  is high

$C_{GS} \rightarrow$  almost independent of  $V_{DS}$

⇒ majority carrier device.


⇒ +ve temperature coefficient

⇒ paralleling is easy

 


SOA has

 - $I_D$  limit,  $V_{DS}$  limit.
- Max. power dissipation limits.



Increase in  $V_{GS}$  as a function of charge carried to the Gate:

 $Q_G \rightarrow$  Charge carried to the gate by current  $i_G$  during turn-ON  
OA  $\rightarrow$  Corresponding to the charging of  $C_i$  under full  $V_{DS}$   
 $C_i$  ;  $C_{GS}$   
 $\rightarrow$  Charge supplied depends on drain I .




AB → Corresponds to  $V_{DS}$  decrease from the supply voltage to  $V_{DS(ON)}$ .  $V_{GS}$  remains constant.

Charge supplied is used to vary the 'V' across  $C_{GD}$ .


BC → Corresponds to input capacitance charge when the device is ON

$$C_i = C_{Gs} + C_{GD(ON)}$$

 

 
## During turn-OFF

Removal of excess charge (EF), discharge of  $C_{GD}$  during voltage rise (FH), &  $C_{GS}$  discharge during current fall (HJ).




## IRF640

 

$$V_{DSS} = 200V$$

$$R_{DS(on)} = 0.18\Omega$$

$$I_D = 18A$$

 

TO-220AB


### Absolute Maximum Ratings

	Parameter	Max.	Units
$I_D @ T_C = 25^\circ C$	Continuous Drain Current, $V_{GS} @ 10 V$	18	A
$I_D @ T_C = 100^\circ C$	Continuous Drain Current, $V_{GS} @ 10 V$	11	
$V_{GS}$	Gate-to-Source Voltage	$\pm 20$	V




## Electrical Characteristics @ $T_J = 25^\circ\text{C}$ (unless otherwise specified)

	Parameter	Min.	Typ.	Max.	Units	Test Conditions
$V_{(BR)DSS}$	Drain-to-Source Breakdown Voltage	200	—	—	V	$V_{GS}=0V, I_D=250\mu A$
$R_{DS(on)}$	Static Drain-to-Source On-Resistance	—	—	0.18	$\Omega$	$V_{GS}=10V, I_D=11A$ ④
$V_{GS(th)}$	Gate Threshold Voltage	2.0	—	4.0	V	$V_{DS}=V_{GS}, I_D=250\mu A$
$Q_{gs}$	Gate-to-Source Charge	—	—	13	nC	$V_{DS}=160V$
$Q_{gd}$	Gate-to-Drain ("Miller") Charge	—	—	39	nC	$V_{GS}=10V$ See Fig. 6 and 13 ④
$t_{d(on)}$	Turn-On Delay Time	—	14	—	ns	$V_{DD}=100V$ $I_D=18A$ $R_G=9.1\Omega$ $R_D=5.4\Omega$ See Figure 10 ④
$t_r$	Rise Time	—	51	—		
$t_{d(off)}$	Turn-Off Delay Time	—	45	—		
$t_f$	Fall Time	—	36	—		

 


**Fig 5.** Typical Capacitance Vs. Drain-to-Source Voltage

 

**Fig 6.** Typical Gate Charge Vs. Gate-to-Source Voltage
 
## Switching characteristics :

$t_d \rightarrow$  time required to  
charge  $C_{GS}$  to  $V_{Th}$   
 $t_r \rightarrow$  Charging time to  
drive the gate for  
full conduction of  
the device



Rise in  $i_D$  with time (hatched area) is decided by internal circuit

$t_{d(off)}$  → Time required for the gate to discharge from the overdriven voltage to the threshold voltage corresponding to active region.

$t_f$  → Time required for the gate voltage to move through the active region before entering cut-off.

## Difference between BJT & MOSFET

### BJT

- 1) Current controlled device
- 2) Minority carrier device  
∴ has -ve resistance  
co-efficient.
- 3) Has secondary breakdown
- 4) Paralleling device is  
difficult
- 5) On state power loss  
( $V_{CE(sat)} I_C$ ) is low
- 6) Turn-off time is higher

### MOSFET

- 1) Voltage controlled device
- 2) Majority carrier device  
has +ve resistance  
co-efficient.
- 3) No secondary breakdown
- 4) Easy
- 5)  $I_D^2 R_{DS(ON)}$  is higher than on  
state losses of BJT
- 6) Very fast device

COOLMOS: On state resistance is low.

∴ conduction losses are low.

IGBT (1983-by Jayant Baliga)

(Insulated Gate Bipolar Transistor)

⇒ Prior to advent of IGBT,

⇒ BJTs & MOSFET were used in high frequency application

⇒ BJT has excellent on-state characteristics

⇒ Current controlled device



MOSFET : – Requires very small gate current.

Is it possible to use both?

⇒ BJT & MOSFET have characteristics that  
compliment each other in some respects.

IGBT ⇒ Insulated gate → similar to MOS  
→ control stage

BJT ⇒ Power stage




## Modify the structure

$P^+$  layer forms the drain.

When +ve potential applied to the gate  
& exceeds threshold voltage  
n channel is formed  $\rightarrow$  similar  
to MOS

 $\Rightarrow$  Electron flow into  $N^-$  region  
 $N^-$  layer receives electrons from  
source ( $N^+$ ) & holes from drain ( $P^+$ )




If  $P^+ N^+ (J_1)$  junction is forward biased  
holes are injected into the  $n^-$  region  
 $\Rightarrow$  Some electrons recombine with holes  
 $\Rightarrow$  Remaining holes are collected at source  
 $\Rightarrow J_1$  can now block -ve V.

In comparison to MOSFET, IGBT has no inverse body diode.



⇒ Most IGBTs contain inverse diode

⇒ Built-in which is optimized to match the IGBT switching operation.

 V-I characteristics look similar to BJT  
except control parameter is  $V_{GS}$



During conduction,  $R_{DS}$  is lower.

  

⇒  $N^+$  layer between  $P^+$  (drain)  $N^-$  drift layer is not essential for operation of IGBT

⇒ Some have just  $N^-$  layer



⇒ Non punch through (NPT) IGBT


If both are present, is known as punch through IGBT (PT-IGBT)




When reverse voltage is applied  $J_1$  should block -ve  
Due to heavy doping on both sides this  $V \downarrow$

  $\Rightarrow$  PT IGBT has low -ve  $V$   
blocking capability  
(Non-symmetrical IGBT)  
 $\Rightarrow$  Non-punch through IGBT  
 $\rightarrow$  symmetrical IGBT



 

NPT

 

PT

Turn – ON of IGBT is ; same as that of power MOS

Turn-off :-


There are two distinct time interval during turn off:

1) The channel disappears & MOSFET blocks quickly

$\Rightarrow i_D$  drops

$\Rightarrow$  Minority carriers in  $N^-$  layer gradually recombine.

 $i_D \downarrow$  relatively slowly  
(Tail current)




This period should be small since  $V_{DS}$  has attained reasonably a high value

⇒ Losses high


⇒ Punch through IGBT has smaller tail time

⇒ Has  $N^+$  layer

 (Almost similar to  $N^+$  layer in GTO anode short structure)



## SOA of IGBT

 

## Smart Power Module:

⇒ Power module + Driver circuit + Protection circuit

- Over temperature protection
- Over current protection
- Over voltage protection

