

A first look at CMOS logic gates

Madhav Desai

January 11, 2018

Logic Gate?

 


Figure: AND logic gate

Other two input logic gates

- ▶ OR2: $z = x + y$.
- ▶ NAND2: $z = \overline{x.y}$.
- ▶ NOR2: $z = \overline{x + y}$.
- ▶ XOR2: $z = (x + y).(\overline{x} + \overline{y})$.
- ▶ etc..

The CMOS inverter

 


Figure: CMOS inverter

Inverter characteristics: Transfer characteristics

 


Figure: CMOS inverter transfer characteristic (with capacitive load)

Inverter characteristics: Output characteristics

 


Figure: CMOS inverter output characteristic with input tied low

Inverter characteristics: Output characteristics

 


Figure: CMOS inverter output characteristic with input tied high

Inverter characteristics: Delay

 


Figure: CMOS inverter delay

Inverter characteristics: I_{DD}

 


Figure: CMOS inverter power supply current

Other CMOS logic gates: NAND2

 


Figure: CMOS NAND2

Other CMOS logic gates: NOR2

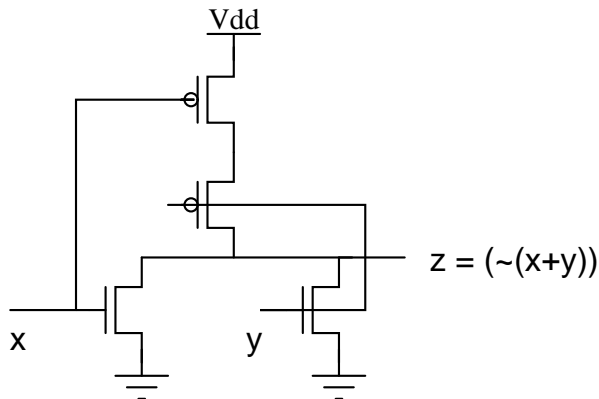


Figure: CMOS NOR2

Static Complementary CMOS logic gate construction

 


Figure: CMOS NOR2

Summary

- ▶ Easy to construct logic gates using CMOS technology.
- ▶ CMOS inverter is prototype for more complex CMOS gates.
- ▶ CMOS inverter characteristics
 - ▶ Transfer characteristic.
 - ▶ Output characteristics.
 - ▶ Delay characteristics.
 - ▶ Supply current characteristics.
- ▶ Characterization necessary for predicting delay, power dissipation, cost of final logic circuit.