

Review :

1) One of the applications of fully controlled bridge in HVDC

(preferred for bulk power transmission).

2) Main limitations of line commutated bridges are

a. Low power factor.



b. Harmonics.

$$3) \text{ P.F} = \frac{I_{s1}}{I_{\text{rms}}} \times \text{D.F}$$

D.F = 1 ; for 1- Φ uncontrolled bridge.


How to improve the P.F ?



P.C.C → Point of common coupling

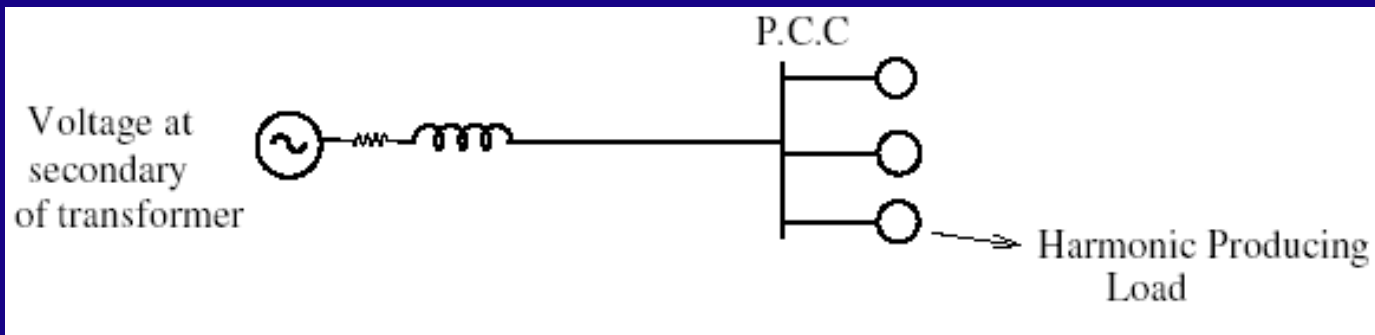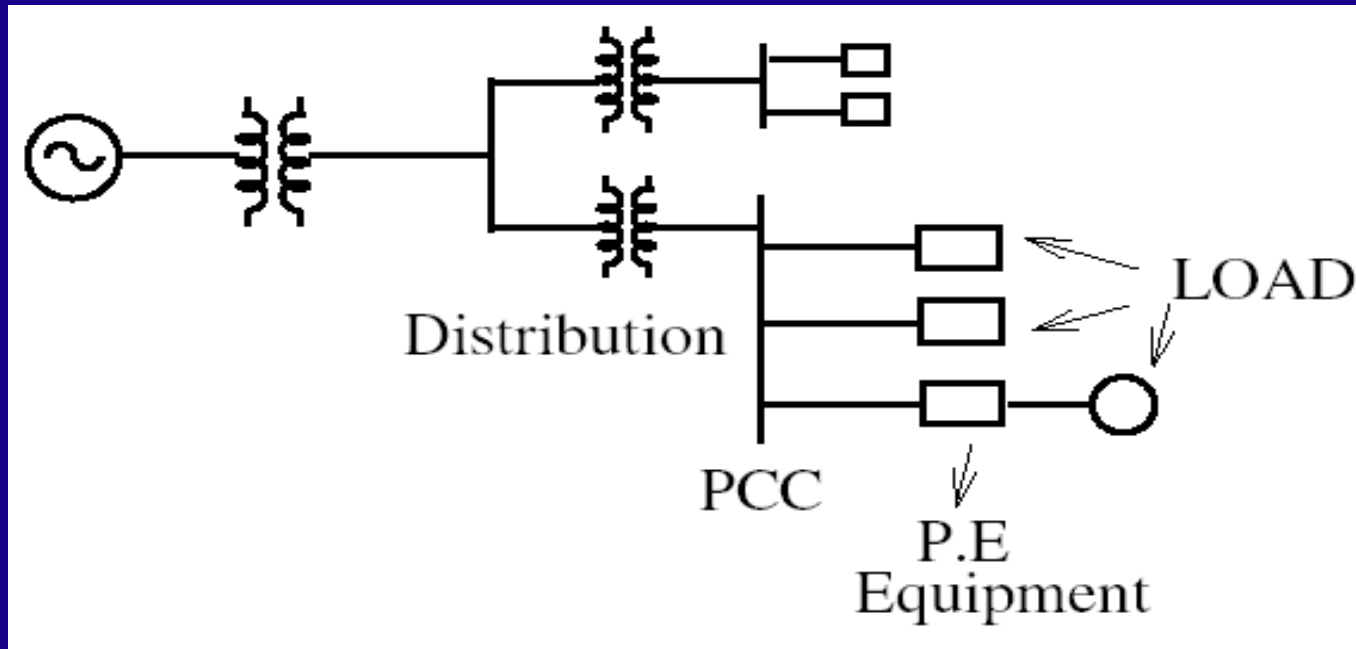

Current drawn by the load fed from P.E. equipment flows through system impedance.

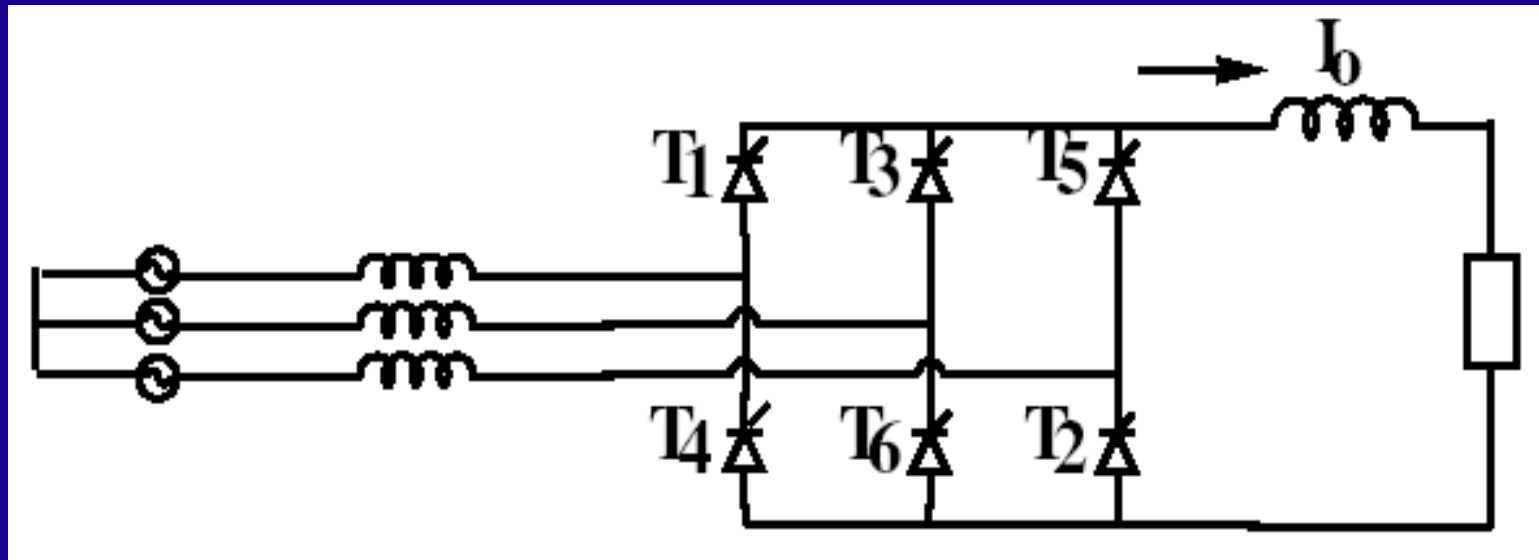Voltage at P.C.C is non-sinusoidal
(We had assumed that 'V' is sinusoidal).



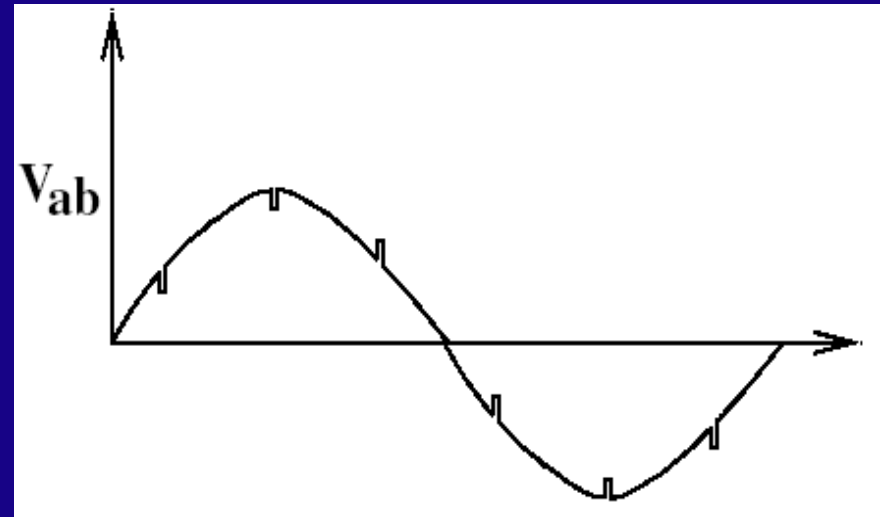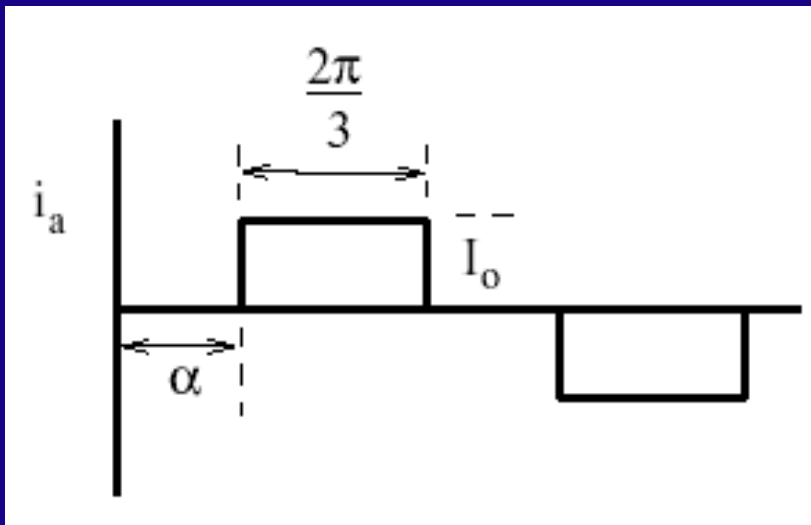

$$i_a = \frac{2\sqrt{3}}{\pi} I_o \left[\sin \omega t - \frac{1}{5} \sin 5\omega t + \frac{1}{7} \sin 7\omega t - \dots \right]$$

= $6N \pm 1$, Harmonics

⇒ Line Commutated converter → causes notches in the source voltage waveform.

→ Source current has harmonics.

Effect of harmonics:

A. In the Rotating machine

- Increases heating.
- They produce noise.
- Torque pulsations.

B. In Transformers

- Cu losses \uparrow .
- Audible noise & heating.

C. In Cables

- Additional heating.

D. P.F correction capacitors.

- Thermal voltage stress.

E. Electronic Equipments

- Affects control system.
- Maloperation of relays.

Various IEEE & IEC standards (International Electro Technical commission) impose specific limits on the level of current harmonics & voltage notches.

Philosophy - "Prevents harmonic currents travelling back to power system and affecting other customers".

Voltage distortion at P.C.C. is of concern.

⇒ Depends on the short circuit current capacity at P.C.C.

⇒ Stricter limits for low value of S.C. current capacity.

IEEE 519

Bus voltage	Max. Individual harmonic component(%)	Max. THD(%)
69kV	3	5


How to filter the source current :

1- Φ 3rd – 150Hz

5th – 250Hz

3- Φ 5th – 250Hz

7th – 350Hz

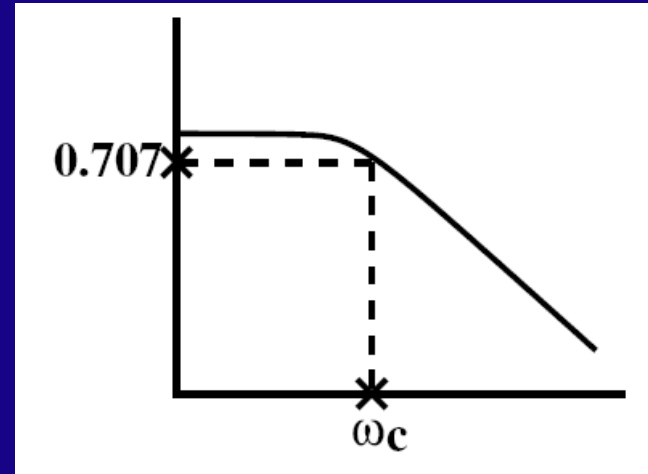


Use of L-C filter (2nd order, -40 dB/decade), Fundamental should not get attenuated (1st order is not possible).

$$\Rightarrow \omega_c = \frac{1}{\sqrt{LC}}$$

As $\omega_c \uparrow$, Size of L & C \downarrow .

⇒ There is only one pulse/ $\frac{1}{2}$ cycle in input source current.

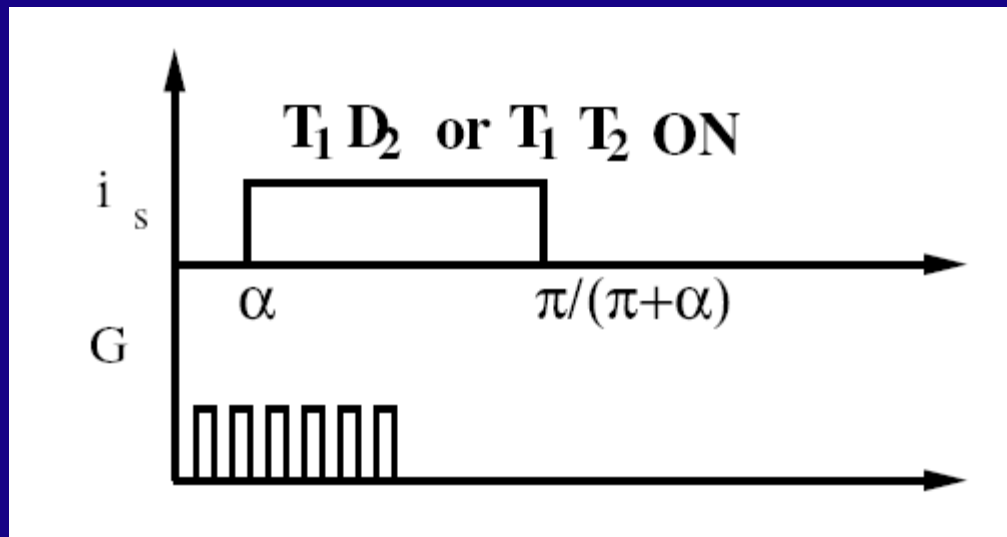
⇒ If there are large number of pulses/ $\frac{1}{2}$ cycle, frequency of the predominant harmonic can be \uparrow .



⇒ To have large number of pulses / $\frac{1}{2}$ cycle

Devices should be turned ON/OFF

several times / $\frac{1}{2}$ cycle.

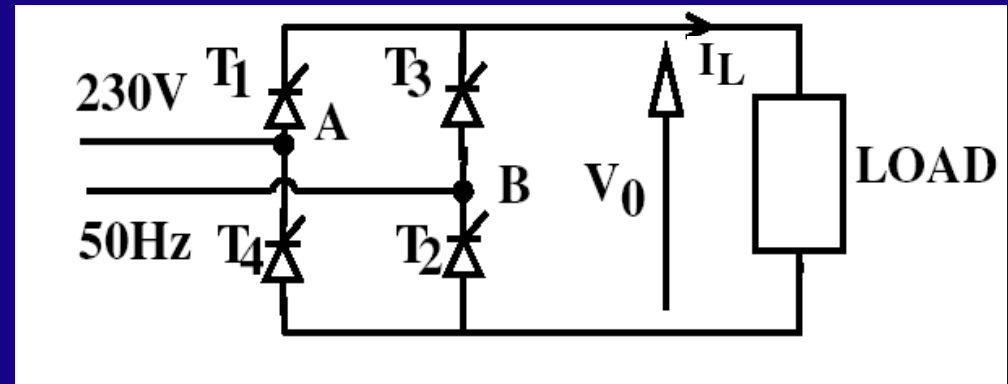

⇒ In the +ve half having triggered T₁ & T₂.

They cannot be turned off by triggering

T₃ T₄ till $\omega t = \pi^+$


(T₃ & T₄ cannot be turned ON).

- ⇒ Either apply – ve voltage across the conducting thyristor using additional voltage source & other passive elements (L & C) or use devices having Gate Turn – OFF capability. (They should be able to withstand – ve voltage)
- ⇒ Self commutating devices
- ⇒ First option → Forced commutation
 - ⇒ Size, Noise ↑
- ⇒ Second option ⇒ Elegant, costly.

How many Pulses / $\frac{1}{2}$ cycle & what are the instants of turn ON/OFF.

\Rightarrow Conduction should begin at $\omega t = 0^+$

So that $\phi_1 = 0$ or D.F. = 1

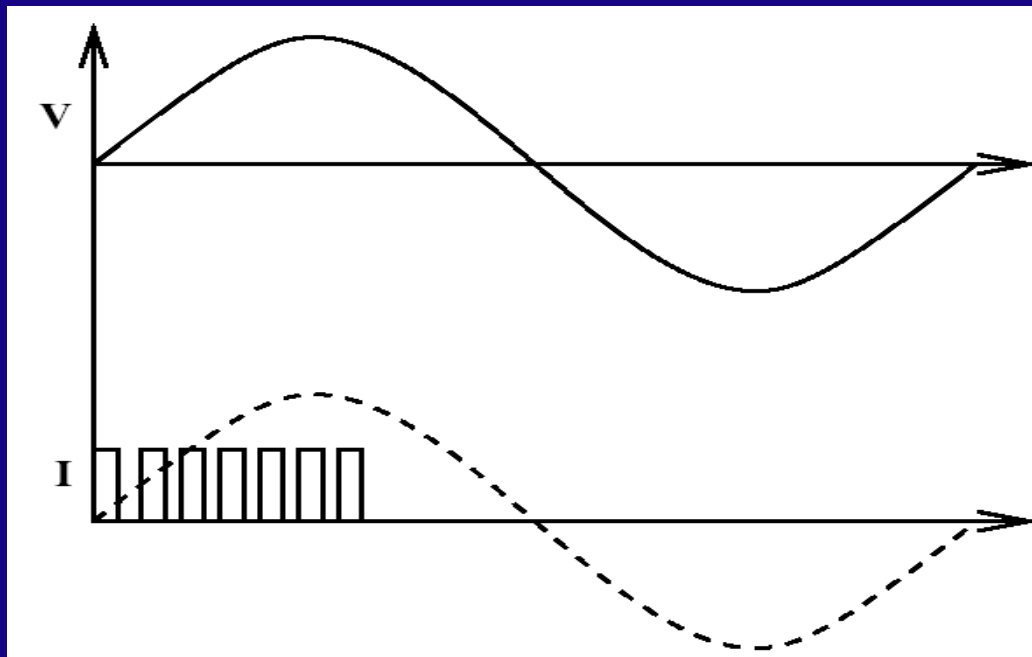

Use Sinusoidal Pulse Width Modulation Technique to generate large No. of pulses.

*** Magnitude of lower order harmonics ↓ or → 0**

*** Magnitude of predominant harmonics ↑**

∴ Frequency of predominant harmonics is high.

Size of filter component ↓

$$\omega_c = \frac{1}{\sqrt{LC}}$$

Sinusoidal PWM Techniques:


A. Full wave rectified sine wave of $2 \times$ supply frequency
& variable magnitude (A_m).

→ Known as modulating wave.

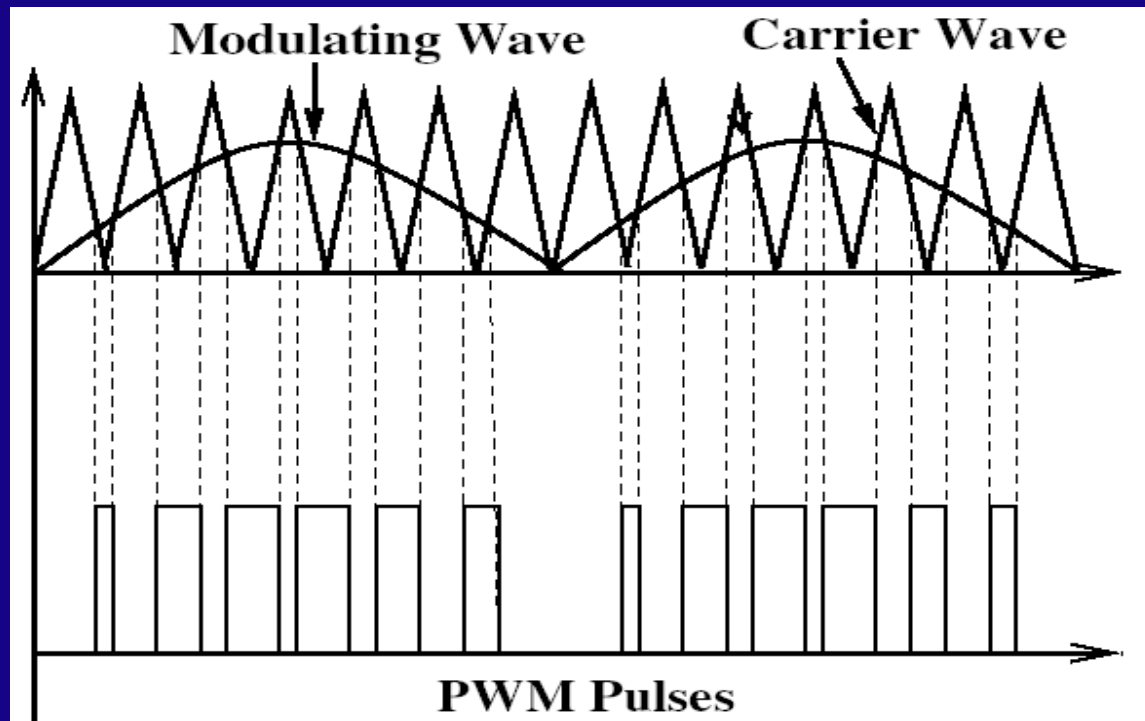B. High frequency triangular wave of fixed amplitude

→ Known as carrier wave.

→ Compared, intersection of sine wave with triangular wave determines the switching instants.



- o/p of the comparator has large number of pulses of varying width.
- How to distribute them $S_1 - S_4$?
- Modulating wave should be synchronized with the mains.

In the +ve half of input supply if S_1 & S_2 are ON, source supplies power to the load.

⇒ Current is established in the load.


⇒ Assume load current is constant & ripple free
Alternative path for the load current should be provided while opening S_1 & S_2 .

⇒ Either have a freewheeling diode across the load


OR

Open S_1 only & close S_3

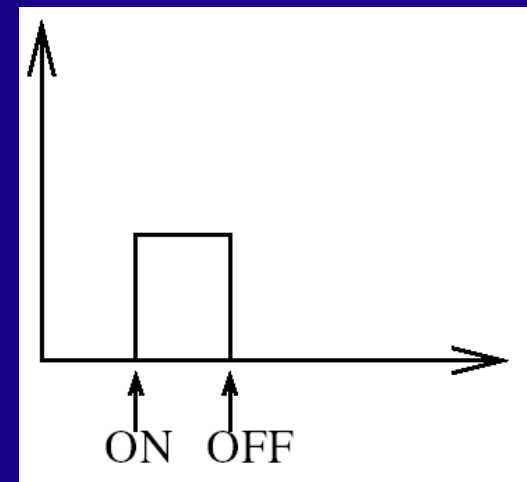⇒ Load 'I' freewheels through S_2 - S_3 .



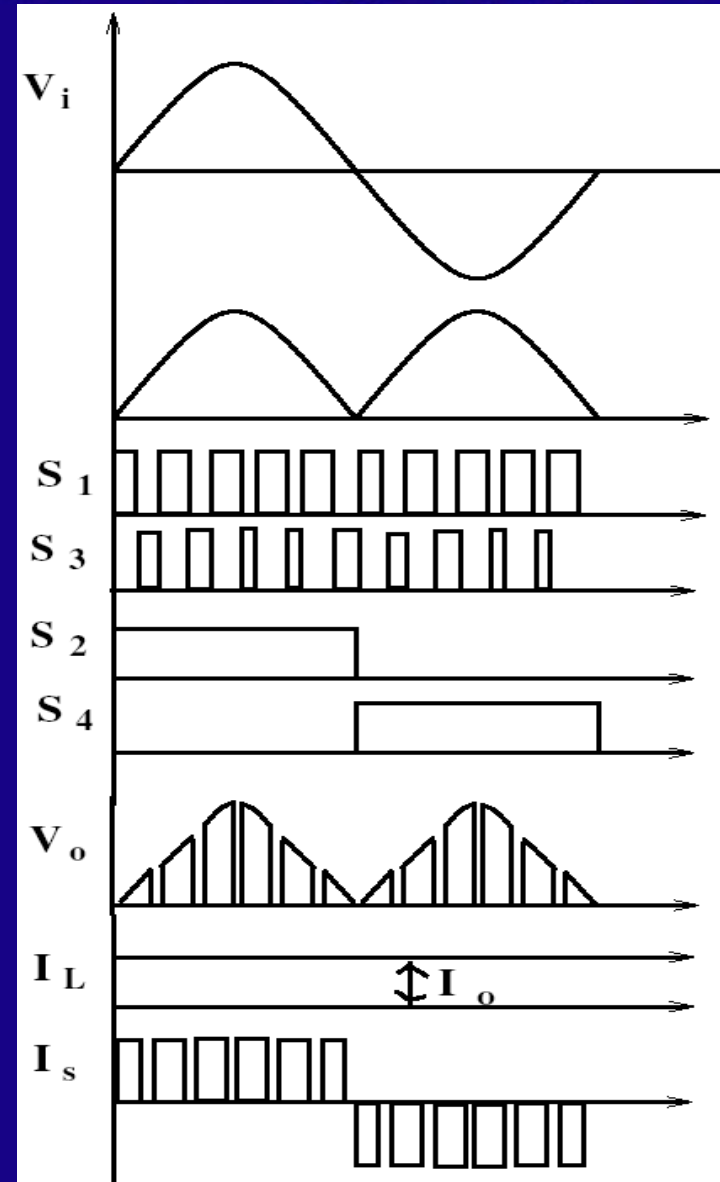- ⇒ In the +ve half keep S_2 permanently closed & switching signals for S_1 & S_3 are complimentary. When S_1 S_2 are ON $V_o = V_i$, $i_s = i_L$ & S_2 S_3 are ON $V_o = 0$
- Similarly in the -ve half closing of S_3 & S_4 results in power transfer to the load.
- ⇒ While opening S_3 close S_1 .
- ⇒ S_4 closed for entire π radians.



How to choose the no. of pulses/ $\frac{1}{2}$ cycle

No. of pulses/ $\frac{1}{2}$ cycle depends on frequency of triangular wave (Carrier wave).

⇒ It can be proved that if there are 'N' pulses/ $\frac{1}{2}$ cycle,

Frequency of predominant harmonic = $(N+1)F$,

Where $F \rightarrow$ Frequency of the modulating wave or supply.

As $N \uparrow$, Frequency of predominant also \uparrow

⇒ Easier to Filter.

⇒ Switching loss \uparrow (& \therefore converter $\eta \downarrow$)

⇒ As $N \uparrow$ fast switching devices are required.