

REVIEW

1. **FULL WAVE RECTIFICATION:** Using centre tap transformer
 - ➡ one diode conducts at a time
 - ➡ V rating of diode = $2 V_{(\text{peak})}$
2. **Common Cathode Configuration :-** Diode whose Anode potential is maximum will conduct
3. **Common Anode Configuration :-** Diode whose Cathode potential is least will conduct
4. **Uncontrolled bridge** ➡ 2 diodes conduct at a time
 - ➡ V rating of diode = peak of input voltage

Single Phase Semiconverter

α to $\pi \Rightarrow T_1 D_2$ Conduct


π to $\pi + \alpha \Rightarrow D_2 D_3$ Conduct

$\pi + \alpha$ to $2\pi \Rightarrow D_3 T_4$ Conduct

2π to $2\pi + \alpha \Rightarrow D_2 D_3$ Conduct

γ for $T = \pi - \alpha$

γ for $D = \pi + \alpha$

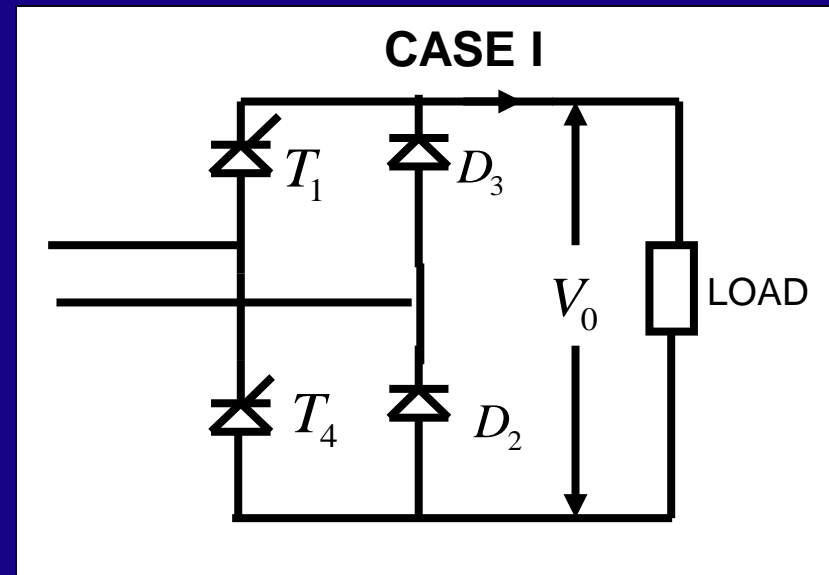

Case II

α to $\pi \Rightarrow T_1 D_2$ Conduct

π to $\pi + \alpha \Rightarrow T_1 D_4$ Conduct

$\pi + \alpha$ to $2\pi \Rightarrow T_3 D_4$ Conduct

2π to $2\pi + \alpha \Rightarrow T_3 D_2$ Conduct

γ for $T = \pi = \gamma$ for D


$A_v V_0 = \frac{V_m}{\pi} (1 + \cos \alpha)$ is always +ve

Instantaneous value of o/p V is either +ve or 0

Displacement Factor = $\cos \left(-\frac{\alpha}{2} \right)$

I/p Line voltage is used to turn off the thyristor

\Rightarrow LINE COMMUTATED CONVERTER

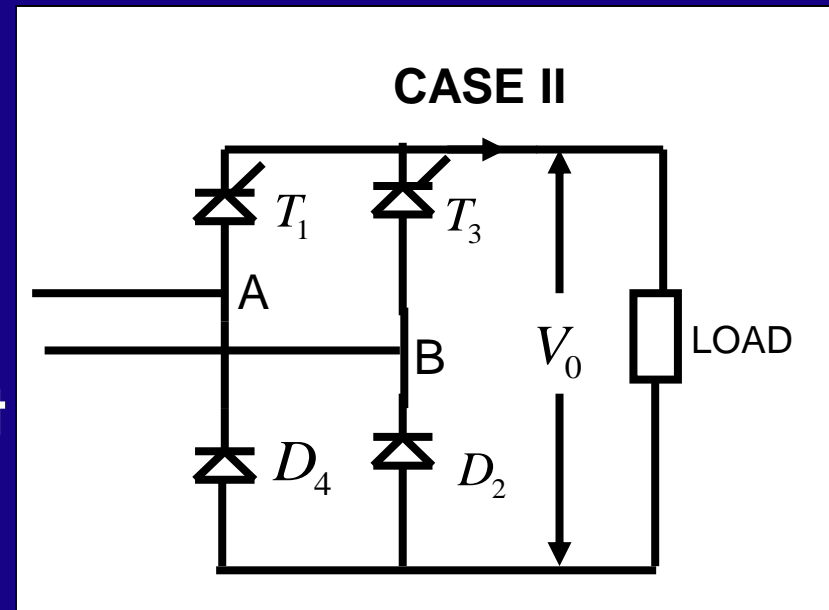

R-L-E Load :

Load current is continuous

$$\alpha_{\min} = 0$$




When T_1 & D_2 are conducting

$$V_i = Ri + L \frac{di}{dt} + E$$

$$\frac{di}{dt} = \frac{V_i - E - Ri}{L}$$

$$= \frac{V_i - E}{L} \quad (\text{If } R \rightarrow 0)$$
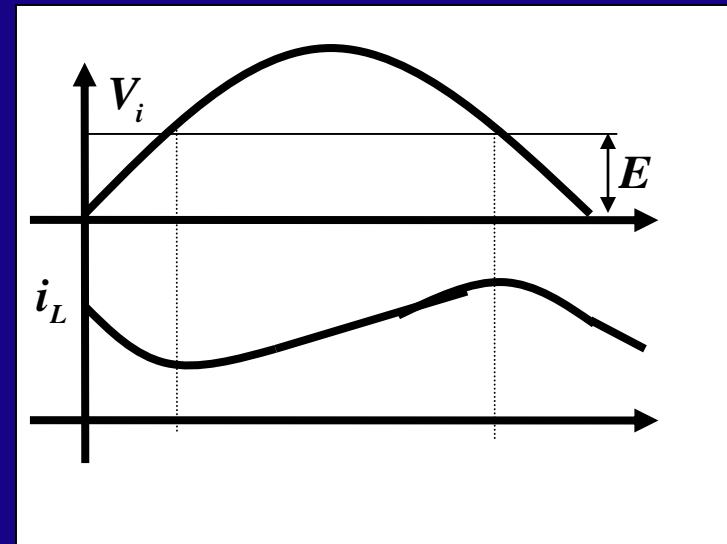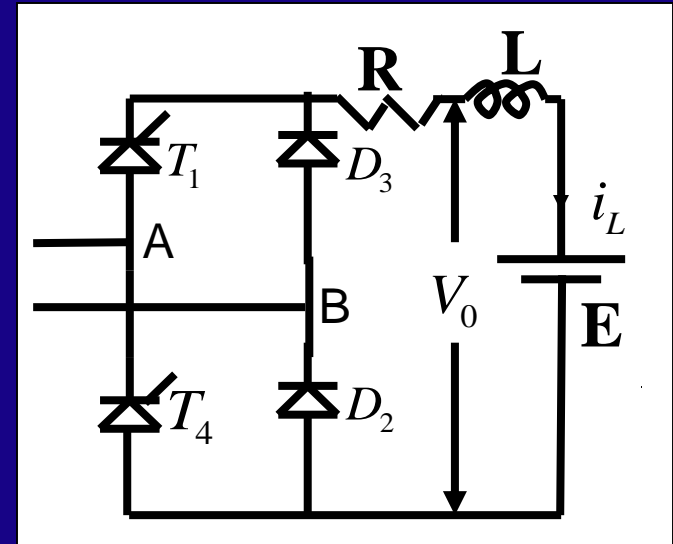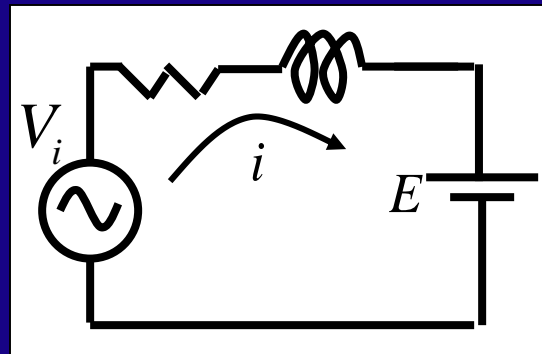
$$\therefore \text{till } \omega t = \sin^{-1} \left(\frac{E}{V_i} \right), E > V_i$$



$\Rightarrow i$ is flowing through ckt=Due to $L \frac{di}{dt}$

\Rightarrow Though T_1 & D_2 are conducting in the +ve half

$\Rightarrow \frac{di}{dt}$ is -ve

it becomes +ve when $\sin^{-1}\left(\frac{E}{V_i}\right) < \omega t < \left(\pi - \sin^{-1}\left(\frac{E}{V_i}\right)\right)$

if $R \rightarrow 0$

Load I is discontinuous ($R-L-E$)

→ Assume that load I becomes zero after π

→ Also assume that SCR's are triggered at


$$\alpha > \sin^{-1} \left[\frac{E}{V_m} \right]$$

Recall : If I is continuous $\alpha = 0$
(independent of type of Load)

If it is discontinuous $\alpha_{\min} = \sin^{-1} \left[\frac{E}{V_m} \right]$

→ Depends very much on load

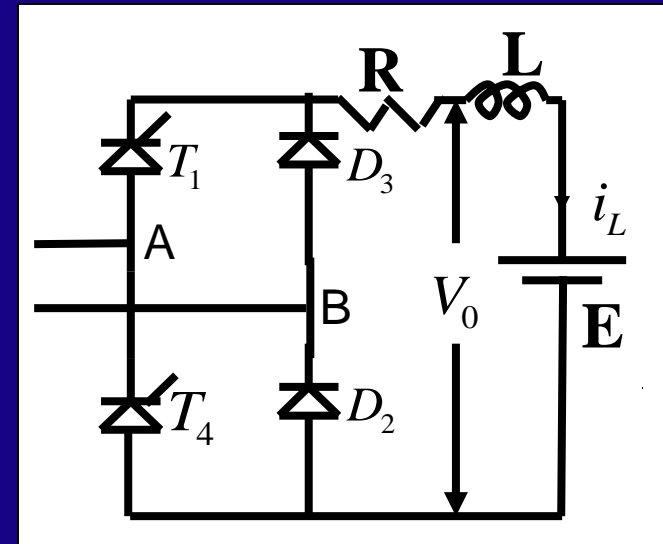→ SCR gets F.B at $\omega t = \sin^{-1} \left[\frac{E}{V_m} \right]$.





\therefore It is triggered at $\alpha > \sin^{-1} \left[\frac{E}{V_m} \right]$???????

$\rightarrow T_1$ and D_2 start conducting

$\rightarrow V_0 = V_{in} = V_m \sin \omega t$ till $\omega t = \pi$

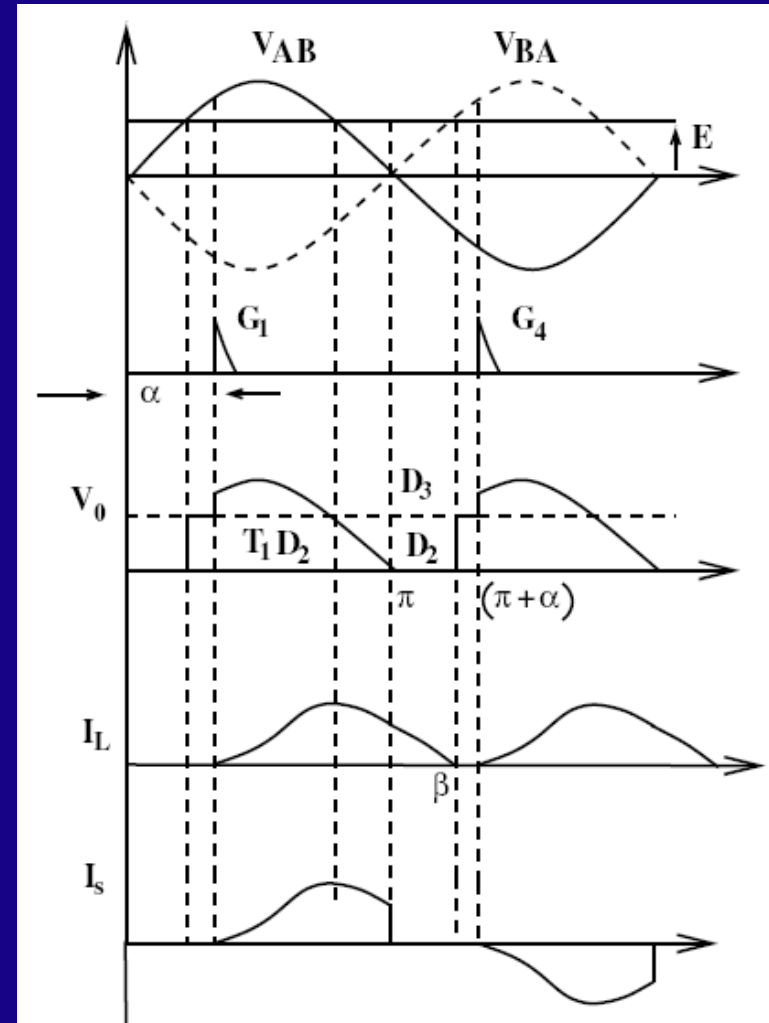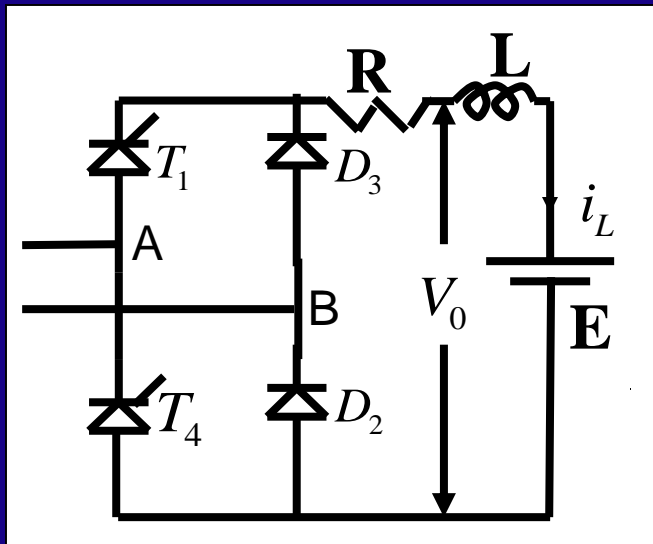at $\omega t = \pi^+$, D_3 D_2 start conducting $V_0 = 0$




Till $i = 0$ at β

$\rightarrow \beta$ to $\pi + \alpha \rightarrow i_L = 0$


$V_0 = E$ (If load is $R-L$, $V_0 = 0$)

at $\pi + \alpha$, T_4 is triggered $\left(\text{is F.B. at } \pi + \sin^{-1} \frac{E}{V_{in}} \right)$

CASE I

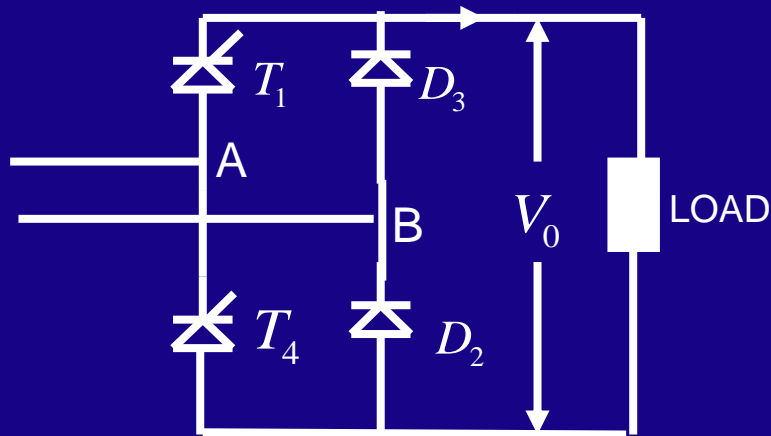

CASE II

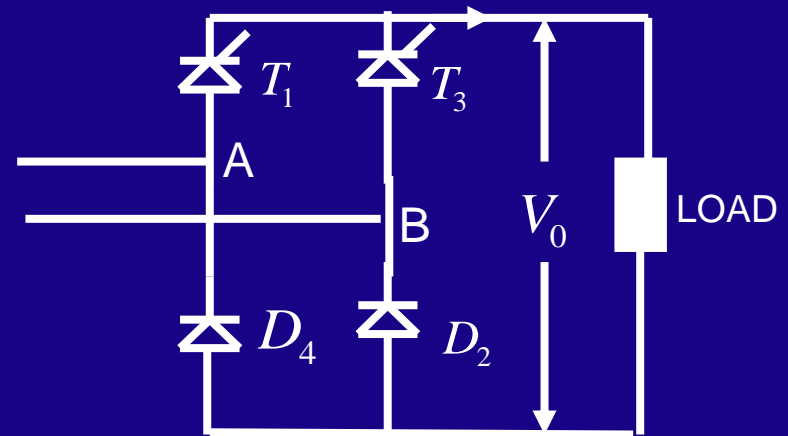

➡ DEVICE SHOULD TURN OFF BEFORE IT IS FORWARD BAISED

- OTHERWISE IT WILL NOT TURN OFF

➡ COMMUTATION FAILURE

IN CASE I

AT $\omega T = \pi^+$, T_1 IS TURNED OFF

BECAUSE DIODE STARTS CONDUCTING

→ CASE II

→ T_1 CONTINUES TO CONDUCT TILL T_3 IS TRIGGERED

T_3 CAN BE TURNED OFF ONLY BY TURNING ON T_1

→ IF $\alpha \rightarrow \pi$

→ At $\omega t = \pi^+ \rightarrow T_3$ GETS FORWARD BAISED


→ T_3 SHOULD ATTAIN ITS F.B.
CAPABILITY BEFORE $\omega t = \pi^+$

→ REQUIRES FINITE TIME

→ IF AVAILABLE TIME < THE ABOVE TIME

T_3 CONTINUOUS TO CONDUCT

→ $\frac{1}{2}$ WAVE EFFECT

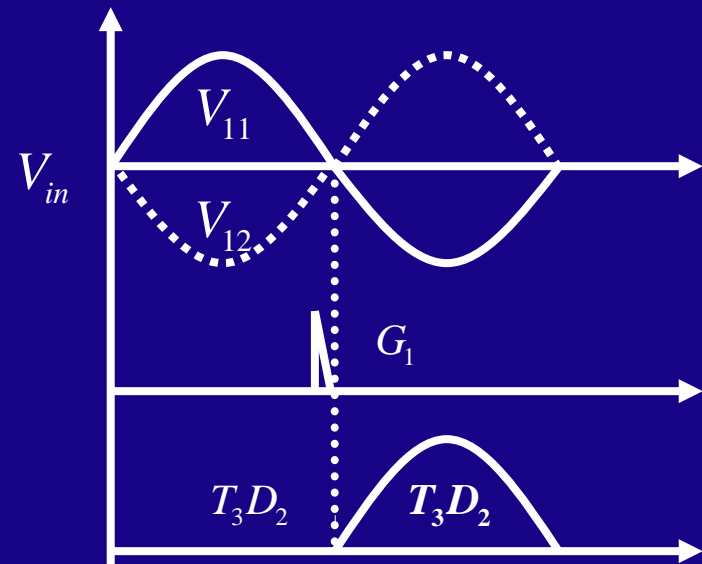

1 If L is large, find the value of α if the av. value of $i = 100\text{A}$

$\Rightarrow L$ is large

$\Rightarrow i$ is continuous



$\Rightarrow \alpha_{\min}$ can be 0

(independent of type of load)

When SCR is ON $V_0 = V_i$

Let α be the triggering angle

\therefore SCR conducts for α to π

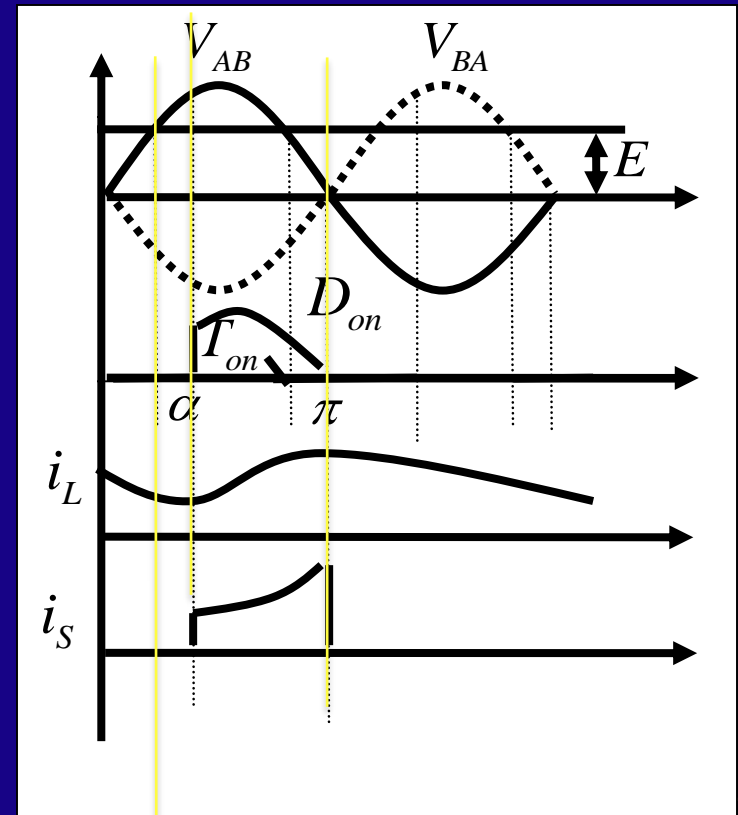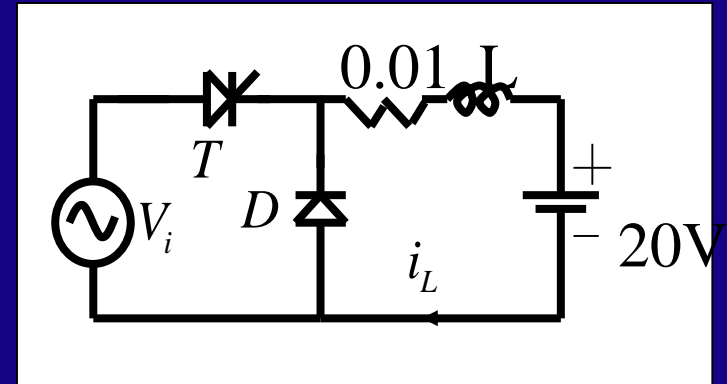

At $\omega t = \pi^+$

**Freewheeling diode turns on
when SCR is off D is ON**

$$V_0 = 0$$

$$\text{Av. value of } I = \frac{\text{Av. voltage across } R}{0.01}$$

$$\therefore V_{av} \text{ across } R = 1V$$

(No instantaneous -ve voltage across load)

$$V_{av} \text{ across } L = 0$$

$$\therefore V_{av} = i_{av} R + E$$

$$\therefore V_{av} = 21$$

$$\therefore V_{av} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$21 = \frac{230\sqrt{2}}{2\pi} [1 + \cos \alpha]$$

$$\therefore \alpha = 53^{\circ}$$



2. For the circuit shown in fig. determine average value of load current for $\alpha = 60^\circ$

What is the new value of average current flowing through load if a large 'L' is connected in series with the load

Neglect the device drop

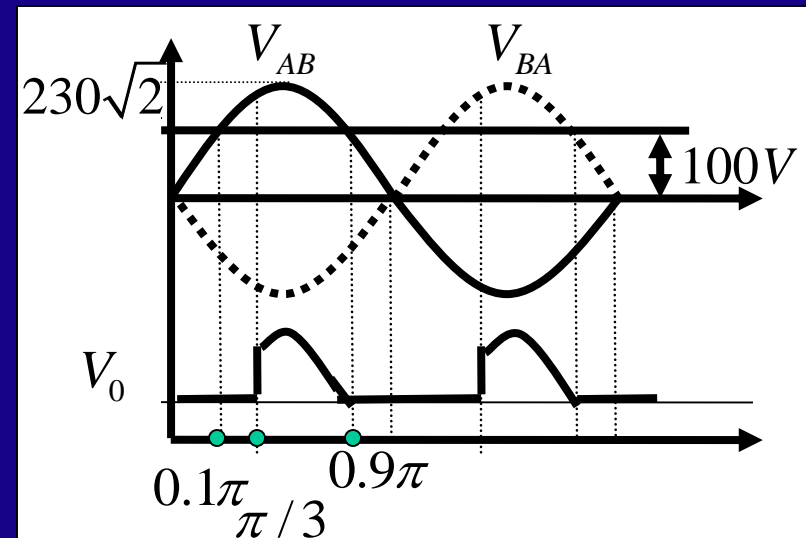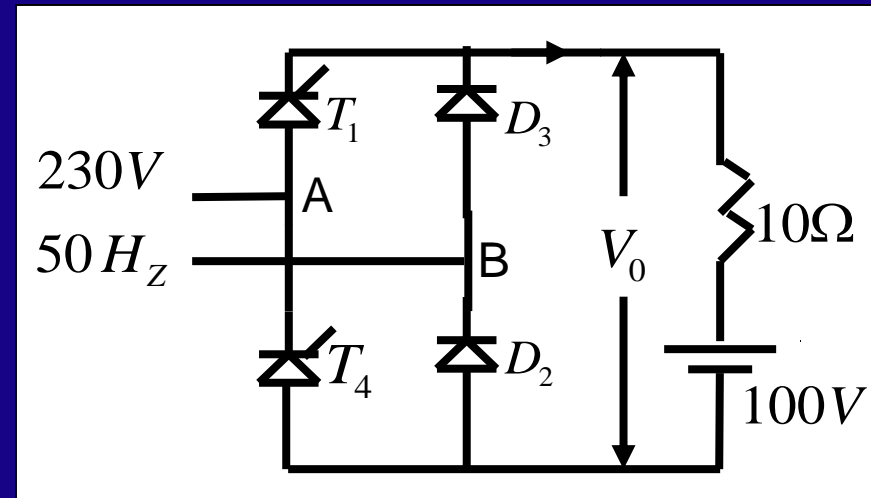a) R-E Load:

$$\alpha_{\min} = \sin^{-1} \left(\frac{100}{230 * \sqrt{2}} \right) = 18^\circ = 0.1\pi^c$$



Minimum value of α can be 18°

But it is triggered at 60°

It will turn off $= \pi - \alpha_{\min} = 162^\circ$

$\Rightarrow 0 \text{ to } 60^\circ :- V_0 = E$

$60^\circ \text{ to } 162^\circ :- V_0 = V_m \sin \omega t$

$162^\circ \text{ to } 360 :- V_0 = E$

\therefore Av. line voltage

$$= \frac{1}{\pi} \left[\int_0^{\pi/3} E d\omega t + \int_{\pi/3}^{0.9\pi} V_m \sin \omega t d\omega t + \int_{0.9\pi}^{\pi} E d\omega t \right]$$

$$= 193.45 \text{ V}$$

$$\therefore \text{Av. value of load current } I_{av} = \frac{193.45 - 100}{10} = 9.345 \text{ A}$$

- b **With large inductance in series with the load current becomes continuous.**

$$\alpha = 60^\circ$$

$$\begin{aligned} \text{Av. value of o/p Voltage} &= \frac{230\sqrt{2}}{\pi} (1 + \cos\alpha) \\ &= 155 \text{ V} \end{aligned}$$



$$\text{Av. value of } I = \frac{155 - 100}{10} = 5.5 \text{ A}$$

3. Av. value of $I_L = 1.8A$

Triggering angle is maintained at 110°
current seems zero at 50° beyond the
zero crossing.

Sketch the load current and
applied average voltage
waveform.
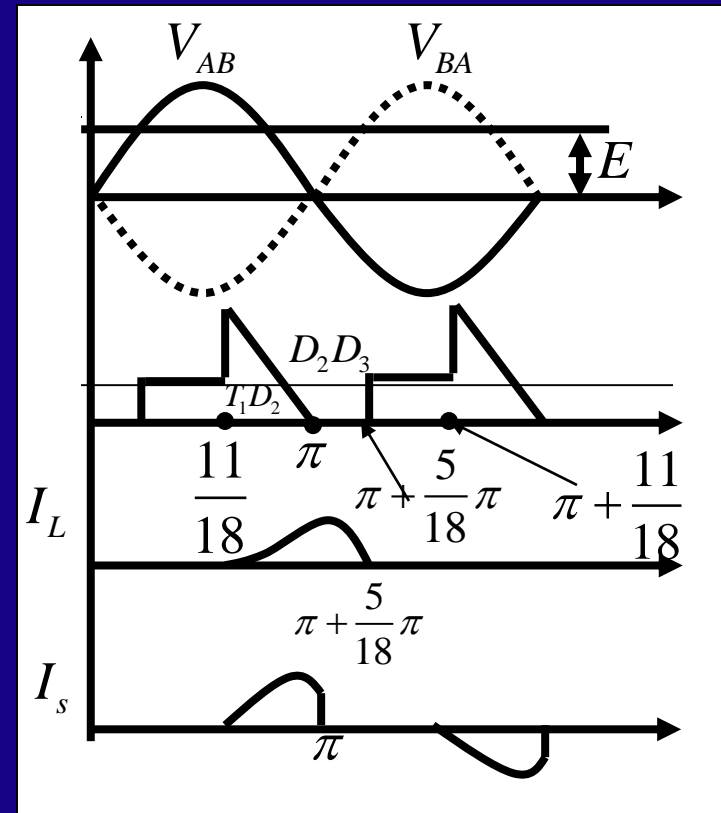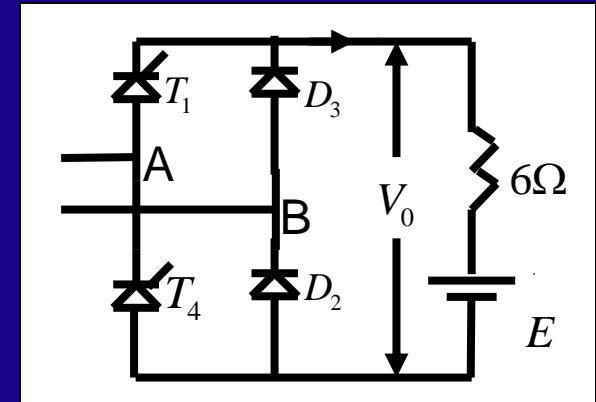
$$\alpha_{\min} = \sin^{-1} \left[\frac{E}{V_m} \right]$$



From $\frac{11}{18}$ to π radian T_1 & D_2 conduct

$$V_0 = V_i$$

From π to $\left(\pi + \frac{5}{18}\pi\right)$

$V_0 = 0 \because D_2$ & D_3 conducting


$$V_{av} = \frac{1}{\pi} \left[\int_{\frac{11\pi}{18}}^{\pi} V_m \sin \omega t d\omega t + \int_{\pi}^{\pi + \frac{5\pi}{18}} 0 d\omega t + \int_{\pi + \frac{5\pi}{18}}^{\pi + \frac{11\pi}{18}} E d\omega t \right]$$
$$= \frac{1}{\pi} \left[230\sqrt{2} \left(\cos \frac{11\pi}{18} + 1 \right) + \frac{\pi}{3} E \right]$$

$$\therefore V_{av} = 68.12 + \frac{E}{3}$$

$$\therefore I_{av} = \frac{V_{av} - E}{R}, \quad I_{av} = 1.8A, R = 6\Omega$$

$$\therefore E = 85.9V$$

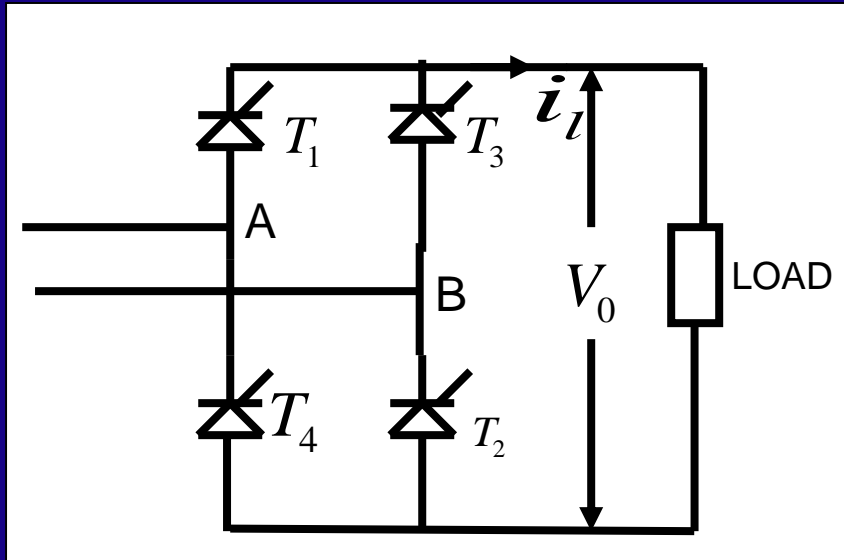
FULL CONTROLLED BRIDGE (Two Quadrant Conf.)



➡ LOAD CURRENT IS CONSTANT & RIPPLE FREE

➡ IN THE +VE HALF T_1T_2 ARE F.B. & -VE HALF T_3T_4 ARE F.B.

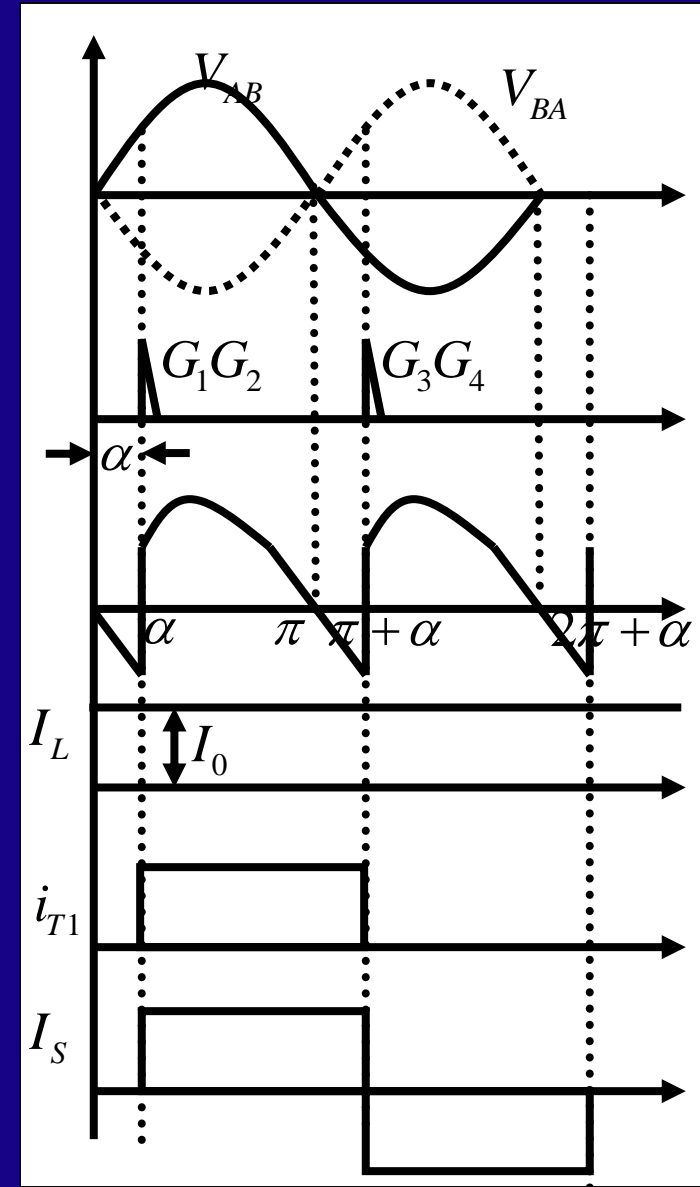T_1T_2 CONTINUE TO CONDUCT TILL T_3T_4 ARE TRIGGERED
($\because I_0$ IS CONTINUOUS)



α to $(\pi + \alpha)$

$$V_0 = V_i = V_m \sin \omega t$$

$$i_s = I_L$$

at $\omega t = \pi + \alpha$ T_3 & T_4 ARE TRIGGERED

POT. OF A < POT. OF C

WHEN T_3 STARTS CONDUCTING

$$V_K = POT. C$$

\Rightarrow -VE 'V' APPEARS ACROSS T_1



\Rightarrow TURNS OFF

\Rightarrow SIMILARLY T_2 TURNS OFF IN THE LOWER ARM

$$i_s = i_L$$

γ for each device is π rads

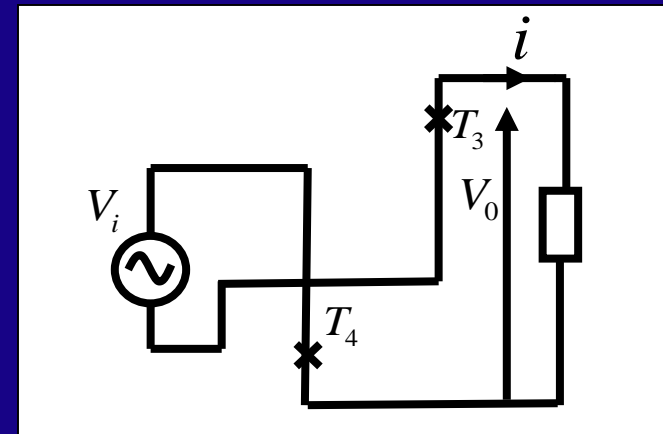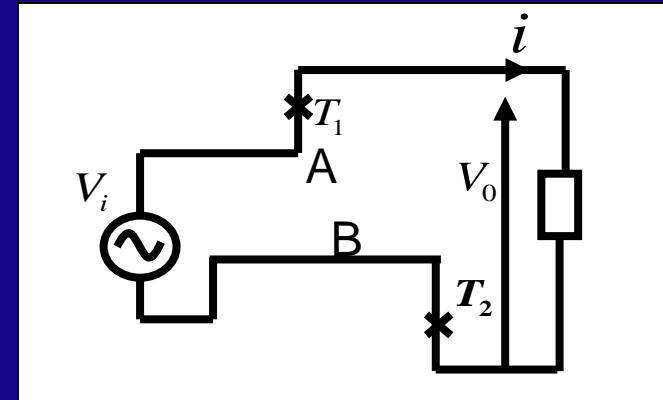There are 2 pulses per cycle \rightarrow Two pulse converter



$$V_0 = \frac{2}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t d\omega t = \frac{2V_m}{\pi} \cos \alpha$$

$\Rightarrow V_0$ +ve For $0 < \alpha < \pi/2$

-ve For $\pi/2 < \alpha < \pi$



$\Rightarrow I_L$ is unidirectional

\Rightarrow 2quadrant converter

$\Rightarrow 0 < \alpha < \pi/2 : 1^{st}$ quadrant operation

Input Power = +ve \rightarrow Converter

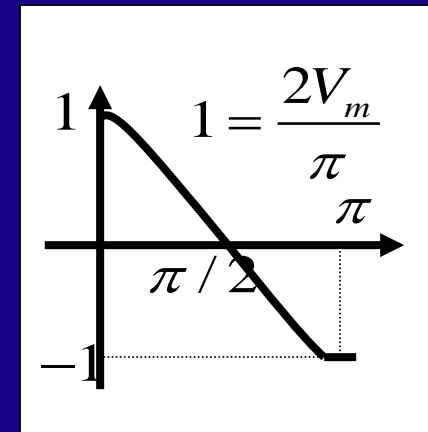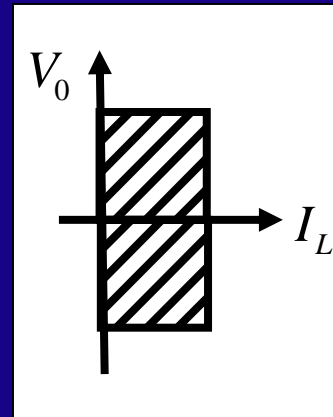$\Rightarrow \pi/2 < \alpha < \pi : 4^{th}$ quadrant operation



Input Power = -ve \rightarrow Inversion

$$\theta_1 = \alpha$$

$$\cos \theta_1 = \cos(-\alpha) \text{ (lagging)}$$

$$I_{rms} \text{ of } I_{s1} = \frac{2\sqrt{2}}{\pi} I_0 \quad 4/1.44\pi$$

$$\text{RMS value of } I_s = I_0$$

$$P.F. = \frac{2\sqrt{2}}{\pi} \cos \alpha = \frac{V_{s1} I_{s1} \cos \alpha}{V_{rms} I_{rms}} = \frac{2\sqrt{2}}{\pi} \cos \alpha$$

\rightarrow lagging

