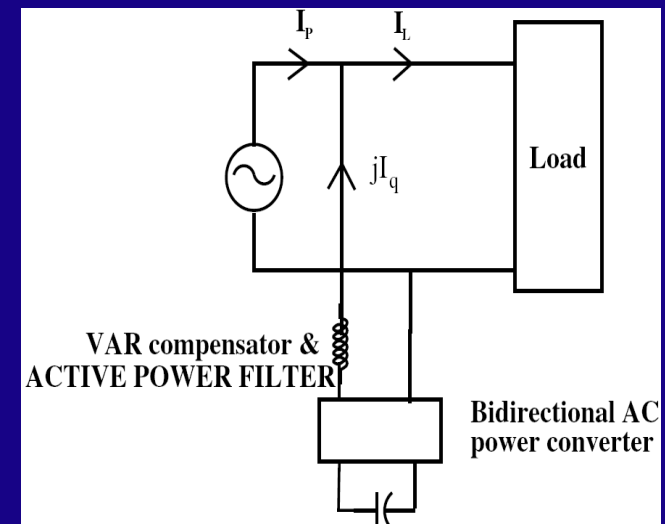


Review :

- 1) Self commutating devices should be used in V.S.I. feeding lagging P.F.
- 2) If the P.F. is leading, S.C.R's can be used as switching elements
- 3) If V.S.I is feeding a pure 'L' load, input batteries can be replaced by 'C'
- 4) Under non-ideal condition, even if inverter is fully loaded by pure 'L' load, Input power ≈ 0



3 – Φ Inverter :

Required Output : 3 - Φ AC

Phase Displacement between S_1 & $S_3 = 120^\circ$


$$S_1 \text{ ON } V_{A0} = \frac{V_{DC}}{2}$$

$$\text{OFF} = \frac{-V_{DC}}{2}$$

$$V_{AB} = V_{A0} - V_{B0}$$

$$0 \text{ to } \frac{2\pi}{3}$$
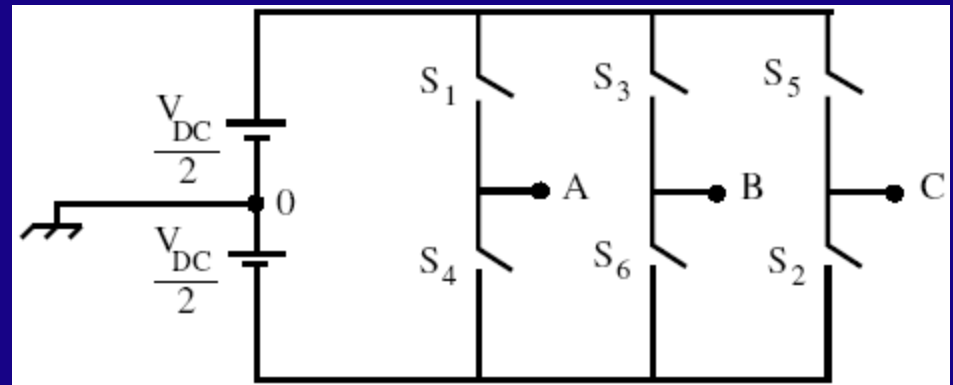
$$V_{A0} = \frac{V_{DC}}{2} \quad V_{B0} = \frac{-V_{DC}}{2} \quad \therefore V_{AB} = V_{DC}$$



$$\frac{2\pi}{3} \text{ to } \pi$$

$$V_{A0} = V_{B0} = \frac{V_{DC}}{2}$$

$$\therefore V_{AB} = 0$$


Pot. of A = Pot. of B


\Rightarrow Either +ve DC Bus
or -ve DC Bus

$$V_{CA}:$$

$$0 - \frac{\pi}{3} = 0$$


$$\frac{\pi}{3} - \pi = -V_{DC}$$

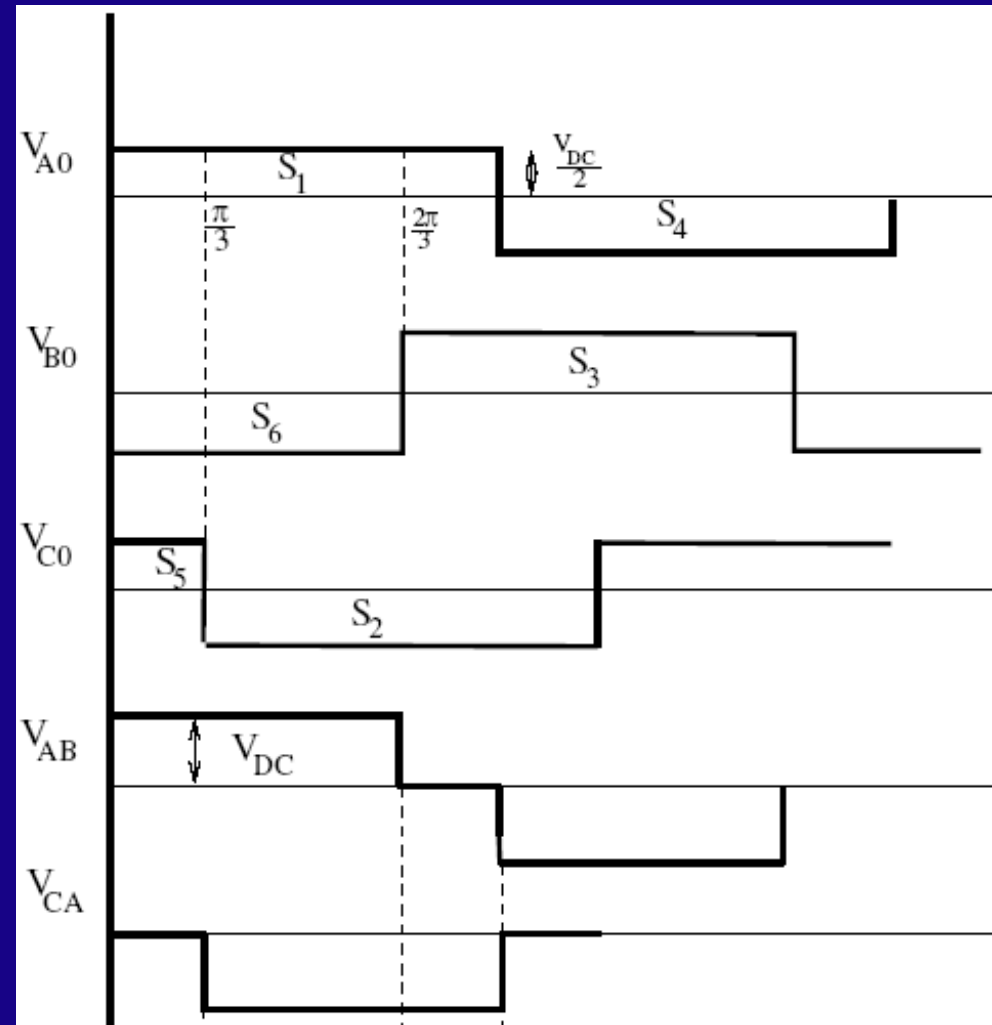

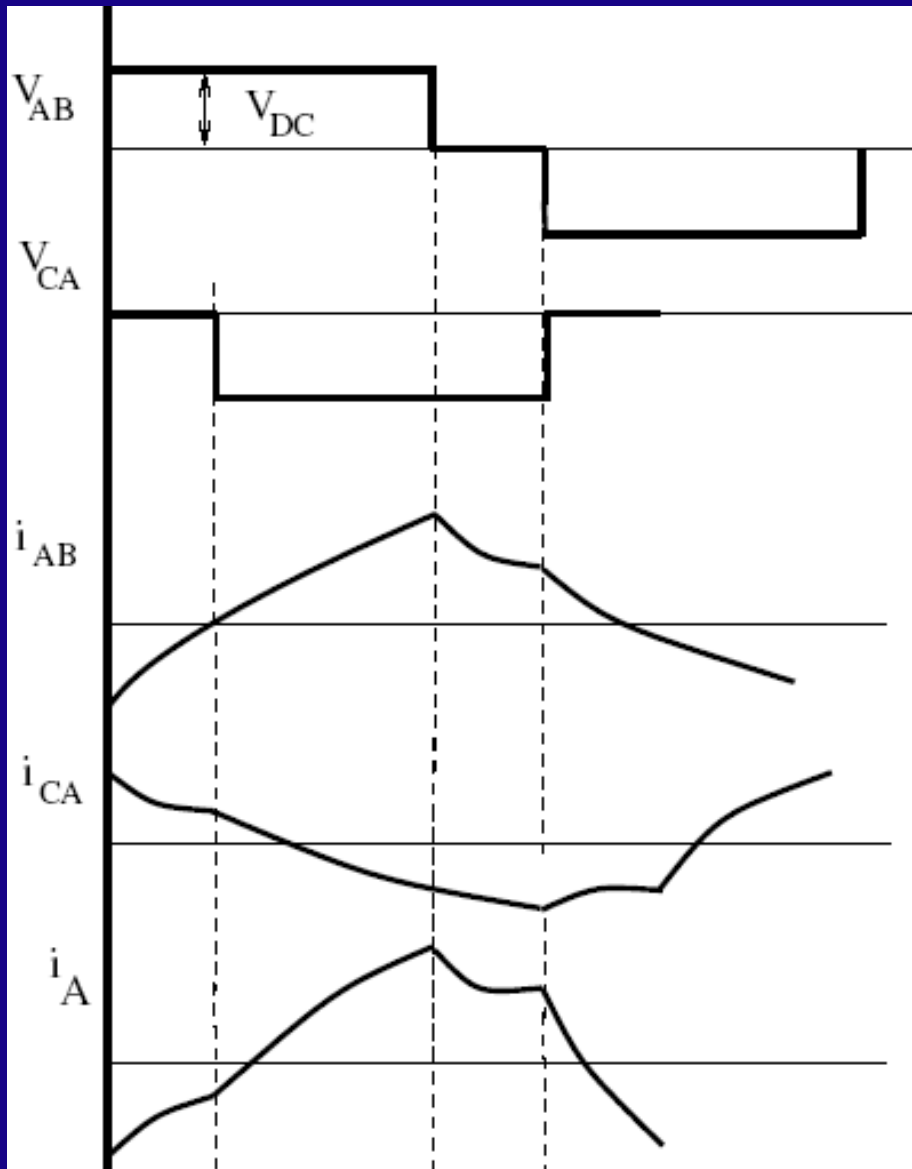

Δ connected load
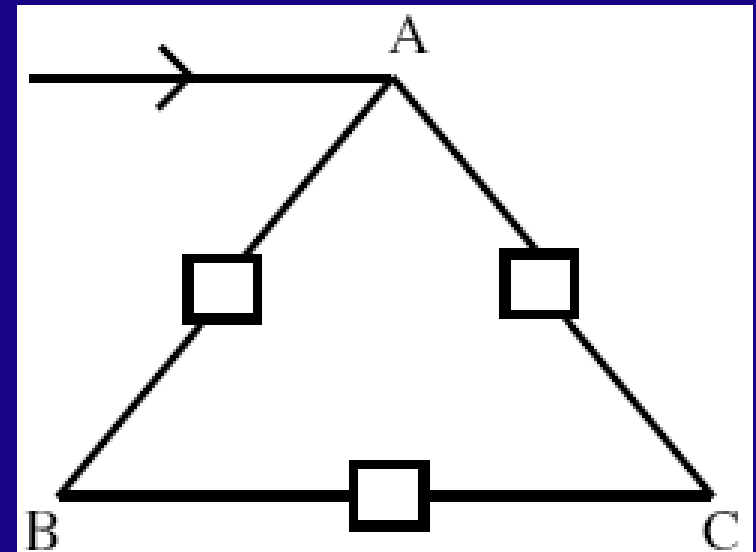
$$i_{AB} = \frac{V_{AB}}{Z} \quad i_A = i_{AB} - i_{CA}$$



⇒ Observations :

There are 6 steps/cycle in load current


⇒ Six Step Inverter

⇒ $V_{A0}, V_{B0}, V_{C0} \rightarrow$ pole voltage


$V_{AB}, V_{BC}, V_{CA} \rightarrow$ predominant harmonic is $5^{\text{th}},$
 $7^{\text{th}}, \dots$

$$= (6N \pm 1)$$
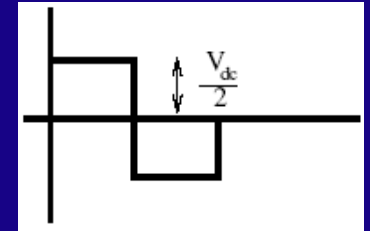
$$V_{A0} = \frac{4}{\pi} \frac{V_{dc}}{2} [\sin \omega t + \frac{1}{3} \sin 3\omega t + ...]$$


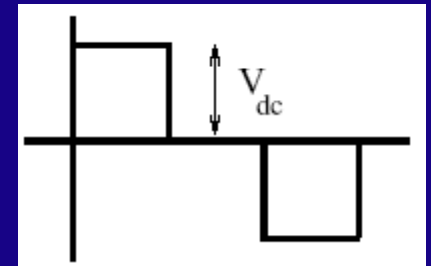
$$V_{AB} = \frac{2\sqrt{3}}{\pi} V_{dc} [\sin \omega t - \frac{1}{5} \sin 5\omega t - ...]$$



$$\text{R.M.S of L-L is } \sqrt{\frac{2}{3}} V_{dc} = 0.816 V_{dc}$$

RMS value of the whole wave = $V_{dc} \cdot (1/3 + 0 + 1/3)^{0.5}$

$$\text{Fundamental} = \frac{\sqrt{6}}{\pi} V_{dc} = 0.78 V_{dc}$$



Rms value
of sin is 1/ROOT(2)

Y Connected Load :

Phase voltage waveform is required

S_1 is ON \rightarrow 'V' w.r.t '0' is known

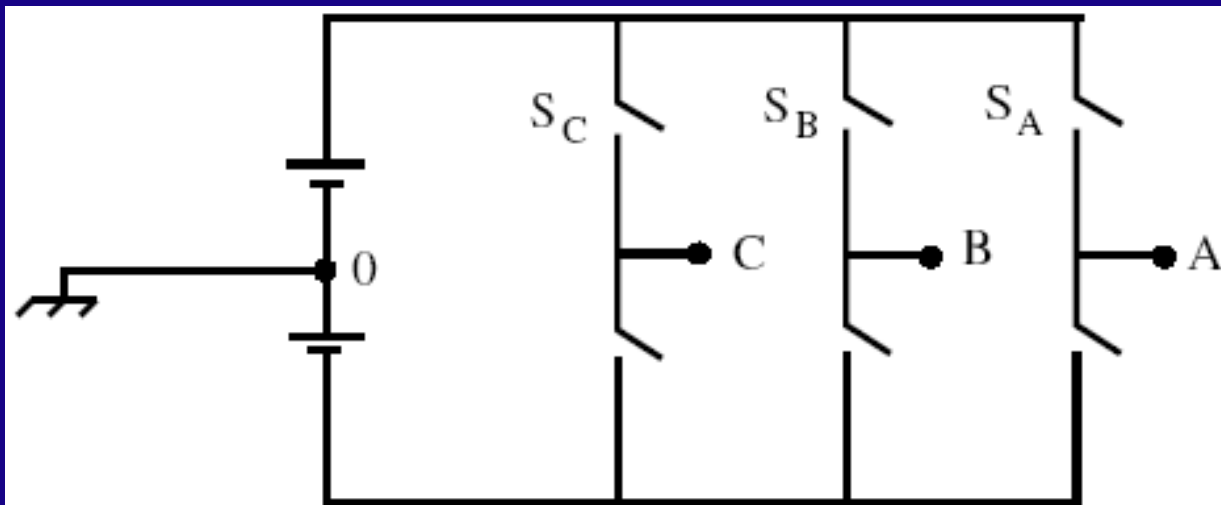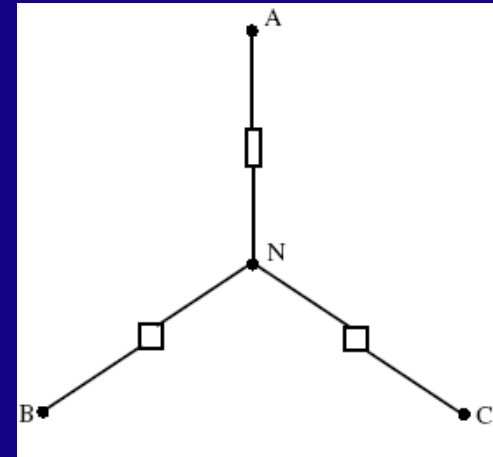V.S.I \rightarrow switching signals for the leg of the inverter are complimentary



If status of S_A , S_B , S_C are known, the status of the other switches will also be known.

8 possible combinations (0,0,0) - (1,1,1)

0,0,0 $\rightarrow S_A$, S_B , S_C are off

\rightarrow Points A, B and C are connected to -ve DC bus

$\rightarrow I_L$ is freewheeling through -ve DC bus

$\Rightarrow V_{AB} = V_{BC} = V_{CA} = 0$

\Rightarrow True for (1,1,1)

\Rightarrow Known as "0 Voltage Vectors"

$$s_C, \quad s_B, \quad s_A$$

$$0 \quad 0 \quad 1$$

$$\therefore V_{AN} = \frac{2}{3} V_{dc}$$


$$V_{BN} = V_{CN} = -\frac{1}{3} V_{dc}$$

$$s_C, \quad s_B, \quad s_A$$

$$0 \quad 1 \quad 0$$

$$\therefore V_{BN} = \frac{2}{3} V_{dc}$$

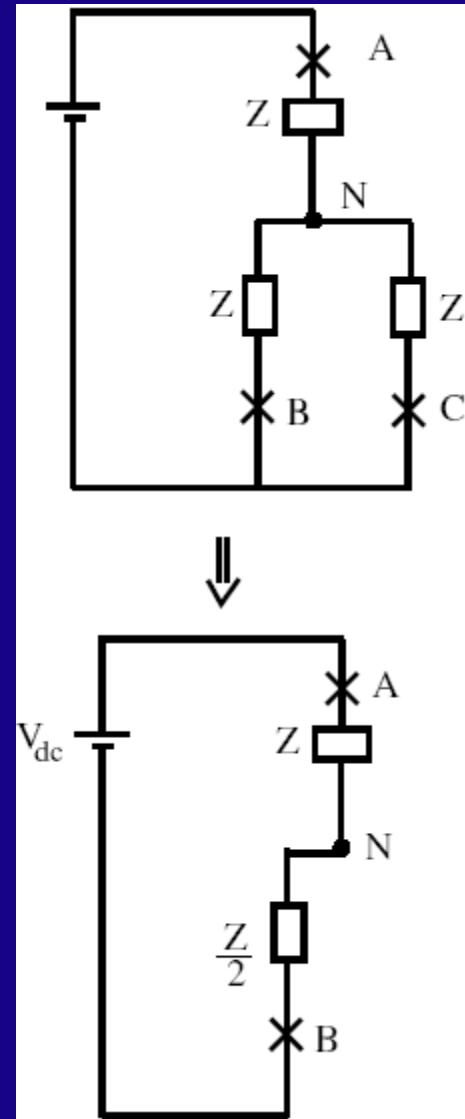
$$V_{CN} = V_{AN} = -\frac{1}{3} V_{dc}$$



$$\begin{matrix} S_C, & S_B, & S_A \\ 0 & 1 & 1 \end{matrix}$$

$$\therefore V_{CN} = -\frac{2}{3} V_{dc}$$

$$V_{AN} = V_{BN} = \frac{1}{3} V_{dc}$$

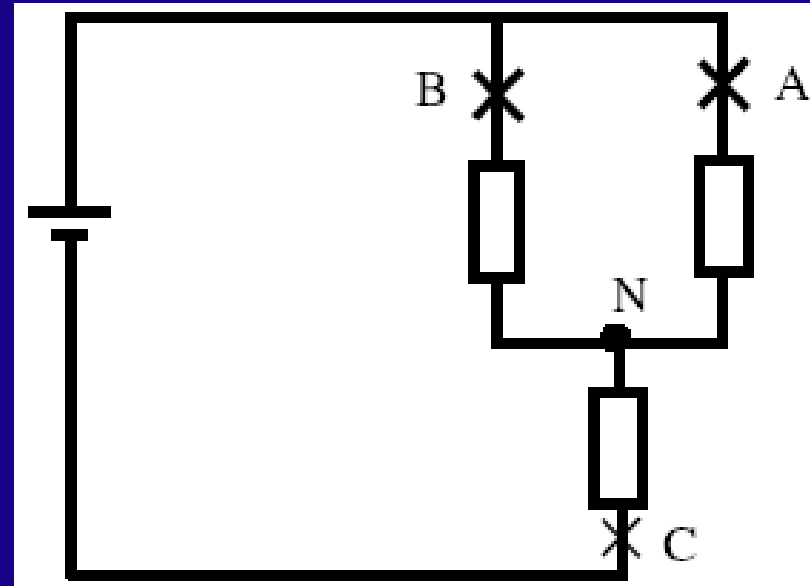

$$\underline{0 - \frac{\pi}{3} : S_A = 1, S_C = 1, S_B = 0}$$

$$\therefore V_{AN} = \frac{1}{3} V_{dc}$$


$$\underline{\frac{\pi}{3} - \frac{2\pi}{3} : S_A = 1, S_C = 0, S_B = 0}$$

$$\therefore V_{AN} = \frac{2}{3} V_{dc}$$

$$\underline{\frac{2\pi}{3} - \pi : S_A = 1, S_C = 0, S_B = 1}$$

$$\therefore V_{AN} = \frac{1}{3} V_{dc}$$

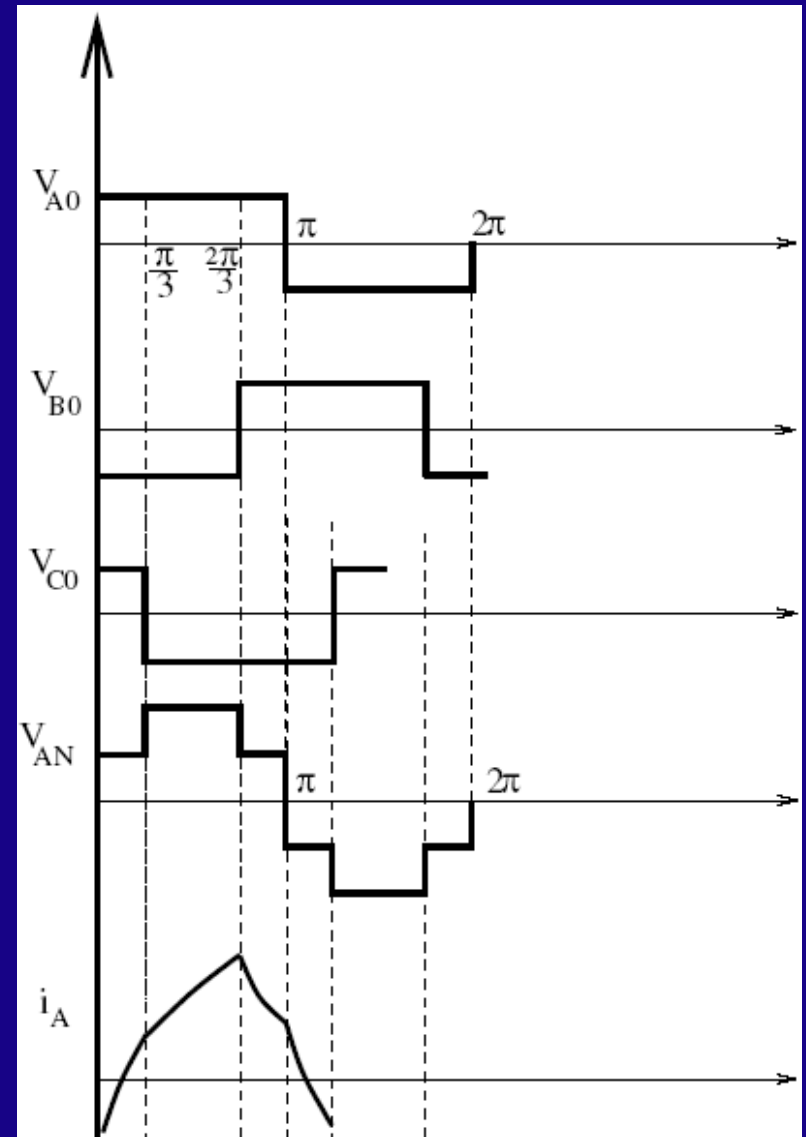$\Rightarrow V_{AN} \rightarrow 6 \text{ steps/cycle}$
 $\rightarrow 6 \text{ step inverter}$



⇒ Both phase voltage & line current has
6 step/cycle

⇒ 6 step inverter

⇒ Frequency of harmonics = $(6N \pm 1)F_1$

F_1 → Frequency of the fundamental

⇒ This could change

⇒ could be 1Hz, 10Hz or 50Hz

under these condition frequency of
predominant harmonics

⇒ 5Hz, 50Hz, 250Hz

⇒ Impossible to filter