

## Problem 1 :

Find the turns ratio such that o / p V required is 100V at 0.5 for nominal i / p V = 12V


a. Compute min & max value of D, if i / p varies from 10 – 14V. Keep  $V_o$  constant

b. Compute the value of  $L_s$  on sec. side so that  $i_2$  is just continuous at the min. value of D.

c. Find the value of 'C' for o / p voltage ripple of 1% at  $D = D_{\max}$

Take  $V_s = 0.8V$ ,  $V_D = 0.8V$ ,

$f_s = 2KHz$

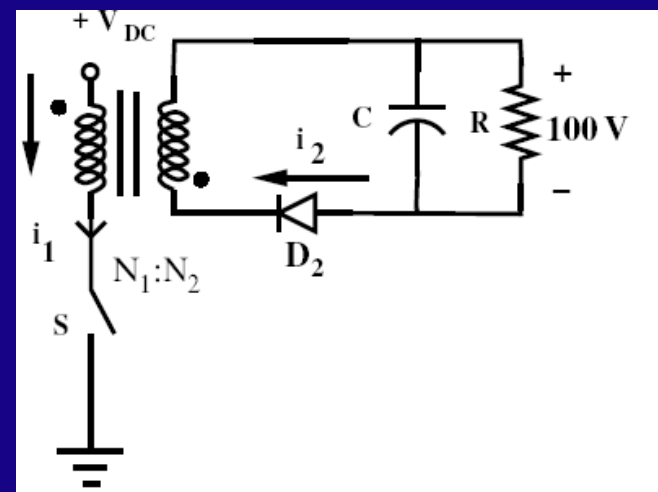

## Solution :

a. Volt.sec / turn  $\left( d\phi = \frac{V.DT}{N} \right)$

**Balance is a must**

$$\frac{1}{N_1} (V_{DC} - V_s) T_{ON} = \frac{1}{N_2} (V_0 + V_d) T_{off}$$

**At nominal i/p V,  $V_0 = 100V$  at  $D = 0.5$**

$$\therefore \frac{N_2}{N_1} = \frac{100 + 0.8}{12 - 0.8} = 9$$

## Variation in D :

$$\frac{D}{(1-D)} = \frac{V_0 + V_d}{V_{DC} - V_s} \times \frac{N_1}{N_2}$$

$$\therefore D = \frac{V_0 + V_d}{(V_{DC} - V_s) \frac{N_2}{N_1} + (V_0 + V_d)}$$

If  $V_{DC}$  varies from the nominal value

so will  $\underline{D}$

$$\therefore \text{At } V_{DC} = 12V \quad D = 0.5$$

$$= 10V \quad D = 0.55$$

$$= 14V \quad D = 0.46$$



$\Rightarrow$  Controller should do this function

b. Value of  $L_s$

$$\Rightarrow Av I_2 = Av I_0$$

neglecting  $\Delta V_0$ ,

$$I_2 \Big|_{av} = \frac{V_0}{R}$$

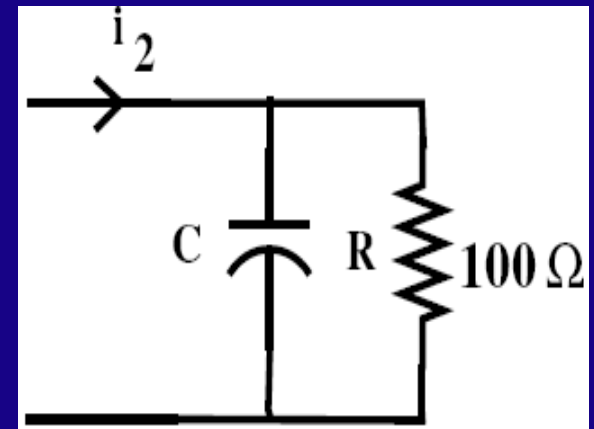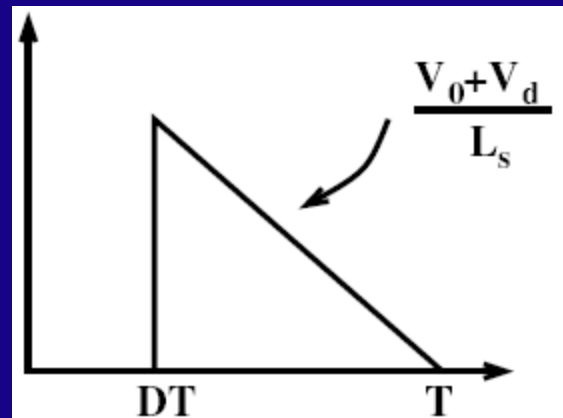

$$\frac{1}{2} I_p \frac{(1-D)T}{T} = \frac{V_0}{R}$$

$$\therefore I_p = \frac{2V_0}{R(1-D)}$$

$$\Rightarrow I_p = \frac{V_0 + V_d}{L_s} (1-D)T$$

$$\therefore L_s = \frac{V_0 + V_d}{2V_0} (1-D)^2 T R$$

**'V<sub>0</sub>' is held constant. I<sub>2</sub> should be just continuous  
at D = D<sub>min</sub> = 0.46**

$$\therefore L_s = 612\mu\text{H}$$

c. Duration for which

'C' is charging ( $i_2 > I_0$ )


Peak value of  $i_2 = I_p$

$i_2$  ↓ at the rate of  $\frac{V_0 + V_d}{L_s}$

∴ Peak value of  $i_c = I_p - I_0$

$$\therefore t_c = \frac{I_p - I_0}{\left( \frac{V_0 + V_d}{L_s} \right)}$$
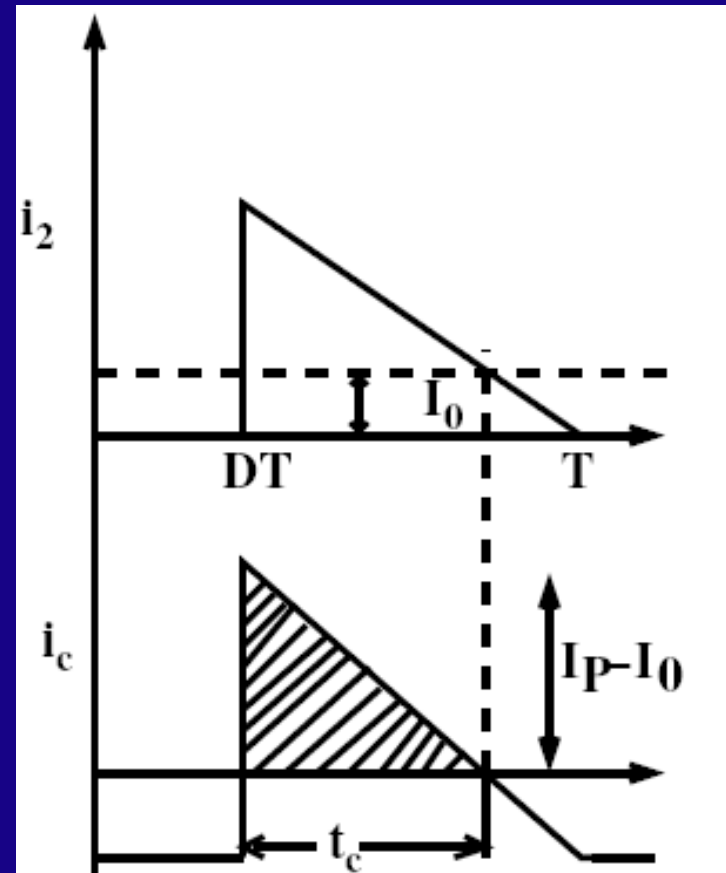
$$\Delta q = C \Delta V_0 = \frac{1}{2} \{ I_p - I_0 \} t_c$$



$$\Rightarrow \Delta q = \frac{1}{2} \{I_p - I_0\} \frac{I_p - I_0}{(V_0 + V_d)} \cdot L_s$$

we know,  $I_0 = \frac{V_0}{R}$ ,  $I_p = \frac{2V_0}{R(1-D)}$

$$\Rightarrow \Delta q = \frac{1}{2} \left[ \frac{2V_0}{R(1-D)} - \frac{V_0}{R} \right]^2 \frac{L_s}{V_0 + V_d}$$

$$\Rightarrow C \Delta V_0 = \frac{1}{2} \left[ \frac{V_0}{R} \right]^2 \frac{1}{V_0 + V_d} L_s \left( \frac{1+D}{1-D} \right)^2$$

$$\therefore \frac{\Delta V_0}{V_0} = \frac{L_s V_0}{2R^2 C (V_0 + V_d)} \times \left( \frac{1+D}{1-D} \right)^2 = 0.01$$

$$\Rightarrow C = 36 \mu F$$




## Problem 2 :

A Forward converter is operating at the boundary of continuous / discontinuous conduction. Switching frequency is 100 kHz.

Assume  $\mu \rightarrow \infty$  so that energy recovery winding is ignored

A load of 10A at 20V is being supplied

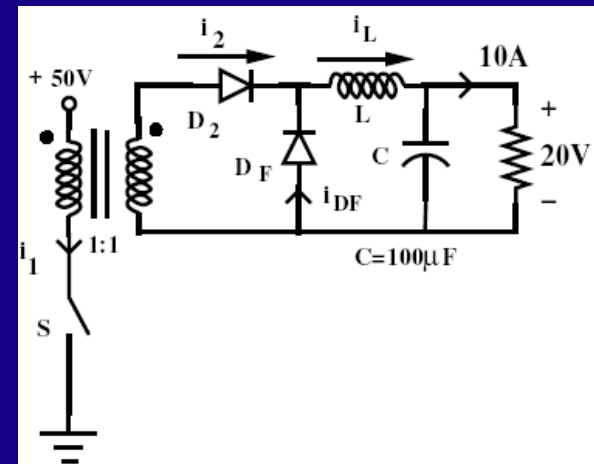- Determine the value of 'L' &
- Determine peak to peak ripple in output voltage



## Solution:

$$\text{a. } V_0 = V_{\text{DC}} \left( \frac{N_2}{N_1} \right) D$$

$$\therefore D = 0.4$$

$$\therefore T_{\text{on}} = 4 \mu\text{sec}, T_{\text{off}} = 6 \mu\text{sec}$$


$$\text{av. } i_L = I_0 = 10 \text{ A}$$

$$\therefore I_p = 20 \text{ A}$$

$$L = ?$$

$$\frac{di}{dt} = 5 \text{ A} / \mu\text{sec}$$
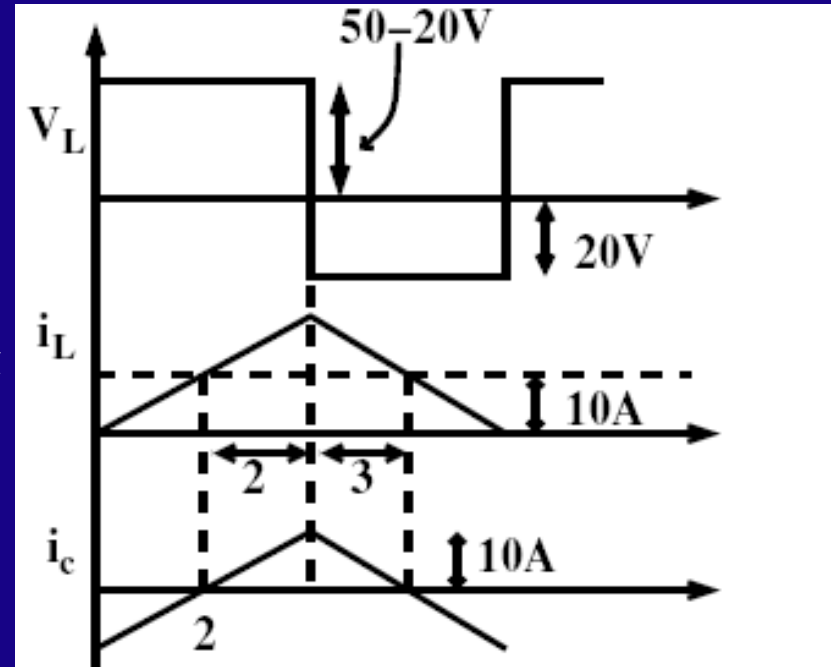
$$\therefore L = \frac{V}{\left( \frac{di}{dt} \right)} = \frac{30}{5} = 6 \mu\text{H}$$





$$\text{b. } C dV_0 = dq = \frac{1}{2} \times 10 \times 5 = 25 \mu\text{C}$$

$$\therefore \Delta V = \frac{25 \mu\text{C}}{100 \mu\text{F}} = 0.25 \text{ V}$$

$$\therefore \frac{\Delta V}{V_0} = \frac{0.25}{20} = 1.25 \%$$

**Flyback, Forward converter →**

**Operation in 1<sup>st</sup> quadrant only**

**⇒ Current through transformer is DC**

**⇒ Use 2 forward converters working in anti – phase**

**⇒ Bi – directional core excitation**

**⇒ AC current through transformer**

**⇒ Both converters deliver power to the load  
in each half cycle**

**⇒ Both of them pushing power to the load**

**⇒ Push – Push converter**

**⇒ Push – Pull converter has prevailed**