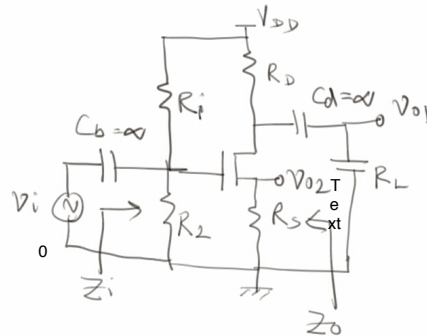


Assignment-4	EE204 - Analog Circuits	6 th Feb 2018
Submission Deadline-17.00 12th Feb, 2018.	Submission Protocol: Drop hardcopy in the EE office	Comment: None

1.



Assume the following parameters: $g_m = 2 \text{ mS}$, $r_o = 100 \text{ k}\Omega$, $R_D = 20 \text{ k}\Omega$, $R_S = 5 \text{ k}\Omega$, $R_L = 20$, $R_1 = R_2 = 10 \text{ k}\Omega$, $C_{gs} = 10 \text{ pF}$, $C_{gd} = 0.1 \text{ pF}$. Assume input signal has an internal resistance of $100 \text{ }\Omega$. Draw Bode plot for gain and phase i) from analytical expression and ii) using Miller's theorem with approximation for the following cases.

- I. $C_b = 100 \text{ pF}$ and $C_d = \infty$
- II. $C_b = \infty$ and $C_d = 100 \text{ pF}$
- III. $C_b = 100 \text{ pF}$ and $C_d = 100 \text{ pF}$
- IV. An additional capacitor $C_S = 1 \text{ nF}$ is connected in parallel with R_S along with III.