

No class on 8th Jan.
Make-up on 10th Jan. @ 7

Page No.	
Date	

EML (Power electronics)

* Why laptop power is so light?

India, avg Power generating 300 Gigawatts.
abt 70% consumed by motors (industrial) (Induction Machines).

$$T_L \propto \omega_r^2 \quad (\text{Pump \& fan, Load Torque})$$
$$P \propto \omega_r^3 \quad (I \omega)$$

* 4 pole, 50Hz, 1485 rpm.

↳ Speed of motor at full load

IM can't run at synchronous speed.

$$N_s = \frac{120f}{P} = 1500 \text{ rpm.}$$

At no load, it may run at 1485 rpm.

From No load to full load, red in speed just 30 rpm.
almost 2%.

For practical purposes, IM have almost constant speed, doesn't depend on load.

* How to convert variable freq. & voltages to constant freq. & voltage.

* Transformer & rectifier. 230V \rightarrow 3V DC.


If $f \uparrow$, $N \downarrow$, copper req. \downarrow .

but if $f \uparrow$, loss \uparrow , eddy loss core loss $\propto f, f^2$


* If connecting a IM to 3-phase,
initial current is very high, $I = 6 I_{\text{full load}}$.

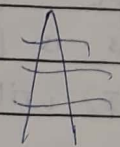- i) How to vary Nr. of IM or SE (separately excited) DC.
- ii) Reduce weight of Power Supply.
- iii) Limitation of Led lamp.
- iv) Consumer return product.
- v) How to use power from renewable source.
- vi) How to transmit bulk power.



Chandrapur (near Nagpur). Bulk power supply. halogen rectifier. Power transfered as H.Voltage DC.



3phase towers.

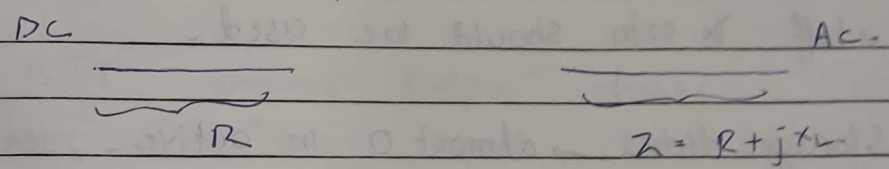


voltage drops.

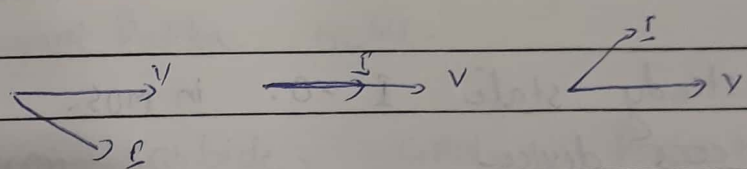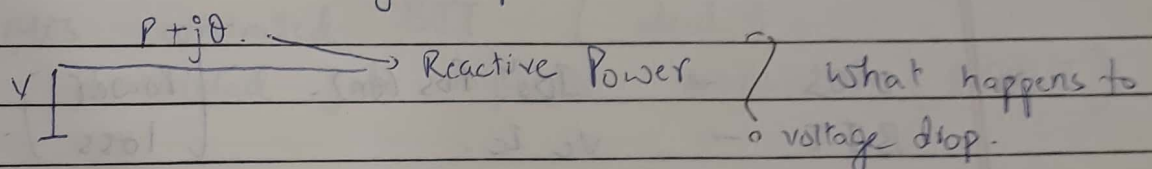


lagging power factor case.


* Fan Regulator

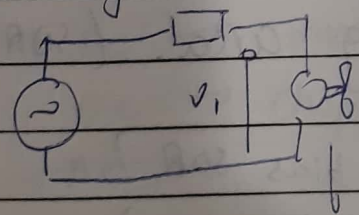

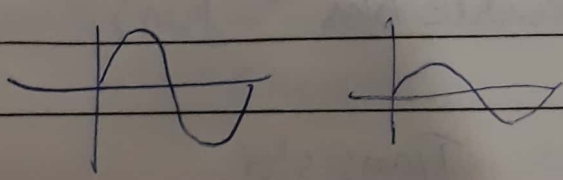load, speed same. \therefore R.M value of voltage should be same.



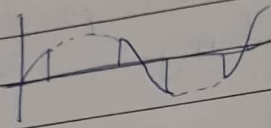Output voltage should be A i.e. Avg is 0. (need not be sinusoidal)



off state \rightarrow Power loss 0.
on-state \rightarrow " " low
 R is very low.

* No BJT in AC, as β_{FE} is highly doped, will not withstand high voltage.

* Active cutoff & saturation.

If in active, Power loss high (β_{FE}).

If in satn, low Power loss is low.

turn off time if saturate BJT will \uparrow .

Cutoff & satn should be used.

Storage time \rightarrow almost 0 in active.
"Quasi-saturation mode".

* MOS $\rightarrow I_D^2$ for (on). (Power loss)
BJT $\rightarrow V_C I_C$.

* at steady state $I = 0$ in MOS.

* BJT, cccs device

BC547.

SL100. n-p-n transistor.

$A = 500$, 0.5A rating.

HAU (H \rightarrow) β - current gain.

Diag \rightarrow Safe operating area. (SOA)

FB SOA. (Fwd. bias SOA)

RB SOA (Reverse bias ").

loss 0.
" low
is very low.
will not

safety margin.

$$\frac{I_c}{\beta}$$

gain-6-8.

steady state

$$I_B \approx I_A$$


Fast reg.

faster turn-on & turn-off.

∴ loss during turn on.

can reduce by having fast turn-on.

If I the I_B , turn-on time reduce.

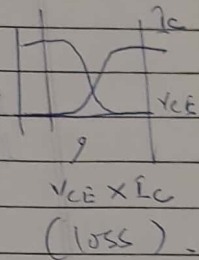

Steady

have to supply 2.5A to I_B . One power transistor to drive another power transistor.

- * BJT excellent Output charac.
- MOS " Input charac.

- * MOS controlled BJT (ideal)
- Insulated gate bipolar transistor (IGBT)

Prof. Jayant Balika. NCSU.

Silicon carbide, GAN. Device + Power
(Self Study).


- * AC → converter → DC (avg. value is finite).
- DC → inverter → AC (" " " 0)
- DC → Chopper → (DC variable).
- AC → → AC (freq. = const)

low power ⇒ (MPS) → switched mode power supply

high " ⇒ Chopper.

chopper fed DC motor.

highly efficient, compact, light-weight, pay-back less
Power electronics.

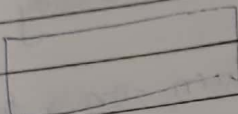
AC → 

→ AC (freq. = const) = Phase
AC (V-V-V-f) - controller
Matrix converter.

- 1 AC (f=c), Phase controller.
- 2 AC (V-V-V-f), Matrix converter.
(variable voltage variable frequency)


New day
*

As $\theta \uparrow$, for a given V,

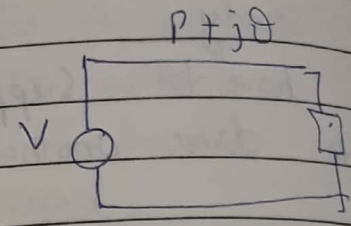

No need to transmit Reactive
Power - can generate locally
by using a capacitor.

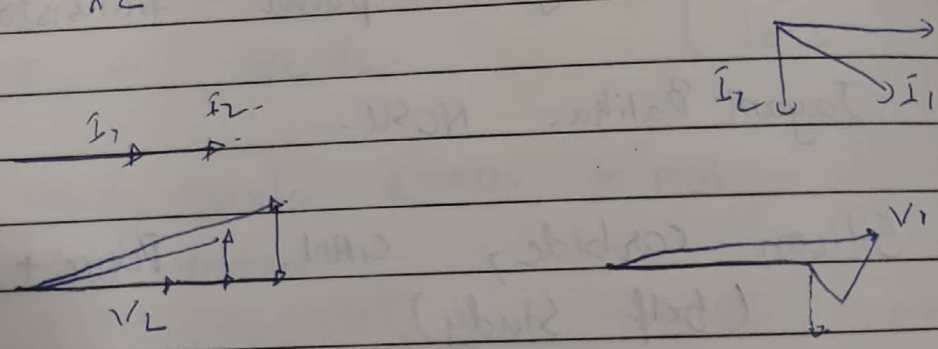$I_c = \frac{V_L}{X_c}$ V is fixed. V_L is \downarrow with θ .



V is fixed, $V_L \downarrow$, $\Rightarrow \theta \uparrow$ (Reactive power demand \uparrow)

As V_L is \downarrow , $I_c \downarrow$,
capacitor expected to supply θ , but not able
to supply. unreliable friend.

System require high I_c .