


Review :

- 1) Device switching varies in S.M.R. with fixed hysteresis band current control.
- 2) Magnitude of reference current / D is determined by comparing the desired output voltage with actual V_0 .
 \Rightarrow Closed loop control is a must.
- 3) D.C. link V_0 has 2nd order ripple.
- 4) In bi-directional power converter, power can be controlled by controlling ' δ '.

$$P = \frac{V_i V_{AB1}}{X} \sin \delta.$$

OR Change the in-phase component of ' i_s ' .

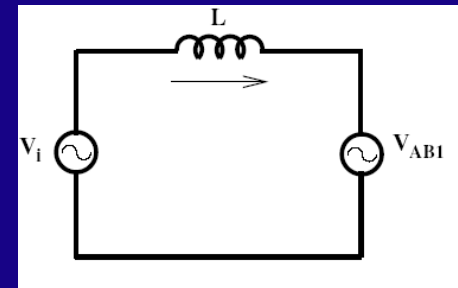\Rightarrow Control philosophy : Sense capacitor 'V' and control ' δ ' or magnitude of ' i_s ' .






If V_i & V_{AB1} are in phase, $|V_i| \neq |V_{AB1}|$.

\Rightarrow Active power transferred = 0.

\Rightarrow If $|V_i| < |V_{AB1}|$, $\angle_{V_i}^{I_s} = 90^\circ$ leading.

and if $|V_i| > |V_{AB1}|$, $\angle_{V_i}^{I_s} = 90^\circ$ lagging.

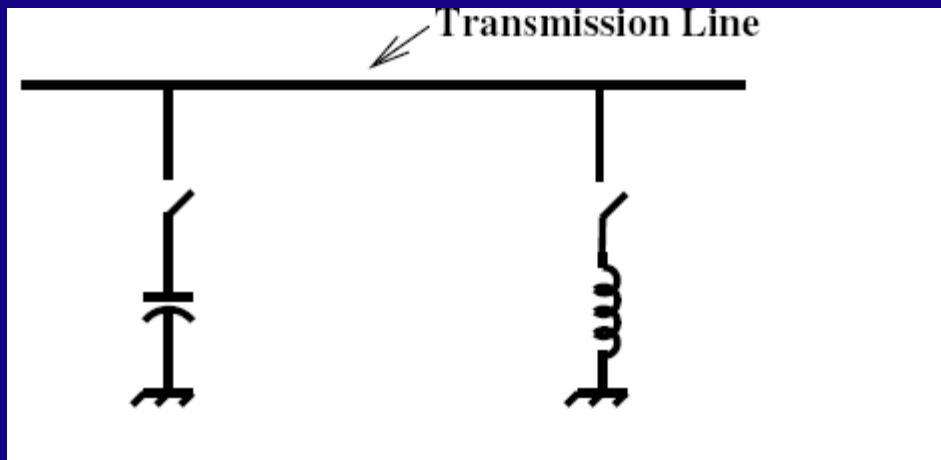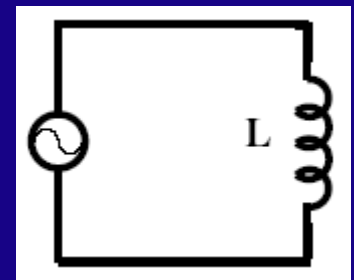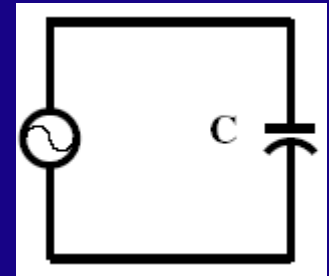

VAR Compensator & Harmonic Filter


$$I_L = I_P - jI_Q$$

Assume load to be
Non – Linear

⇒ Has harmonics

⇒ Source is made to
supply only the
ACTIVE COMPONENT.

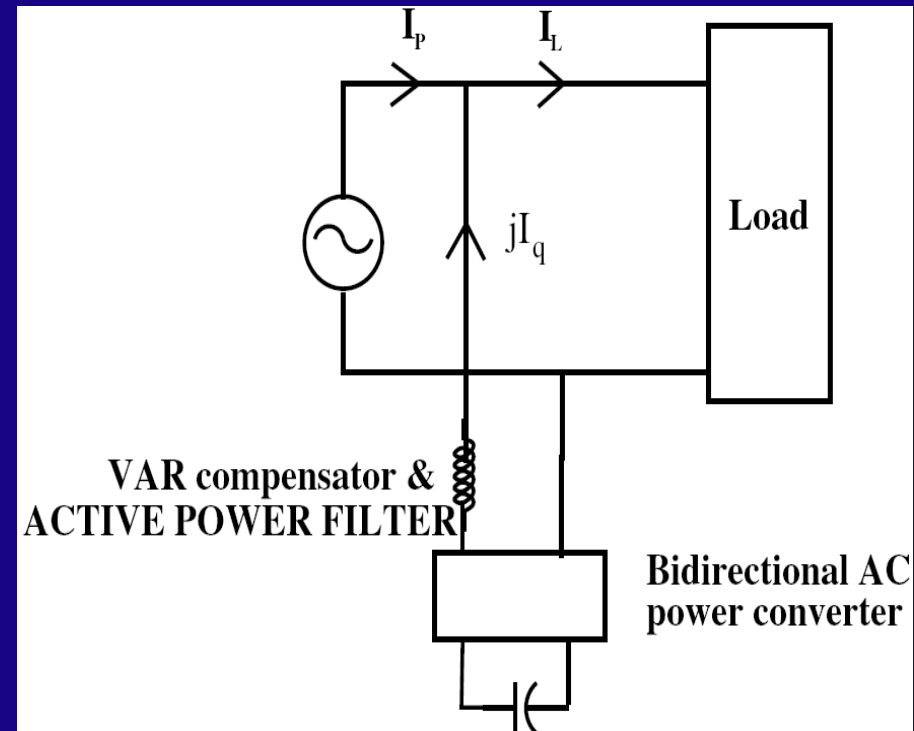⇒ Remaining current has to come
from P.E. converter.





In the previous case
(only S_4 is closed in the +ve half),
Near the Zero crossings,
 v_i is low

$$\frac{di}{dt} = \frac{v_i}{L}$$

⇒ Forcing function is low.

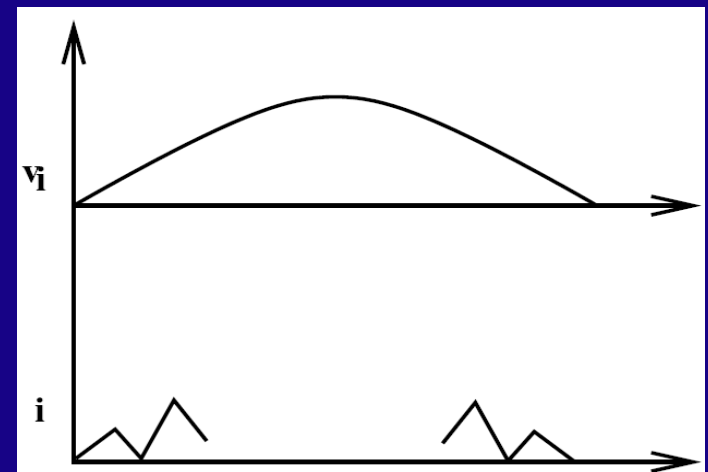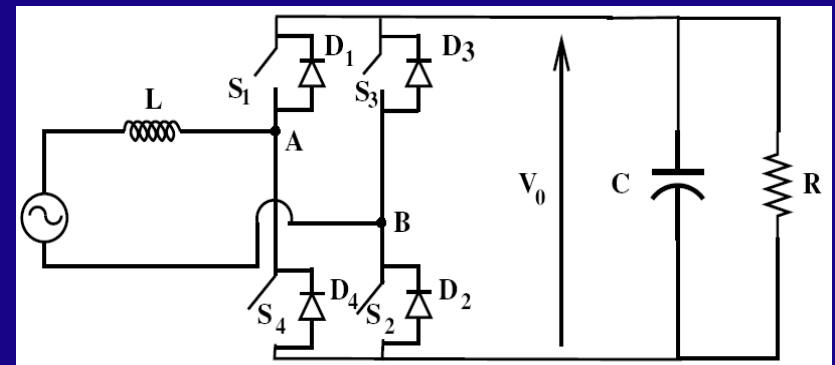
⇒ It may be difficult to
force the current.



Instead :

In the + ve half, close S_4 & S_3
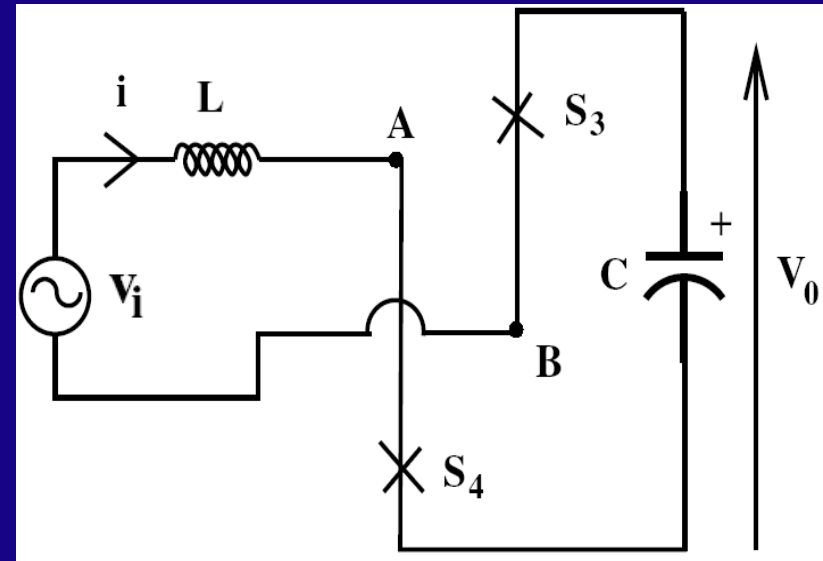
$$\frac{di}{dt} = \frac{v_i + v_0}{L} \quad \& \quad V_{AB} = -V_0$$



⇒ Capacitor voltage aids the current rise.

⇒ Current waveform improves.



⇒ Switching frequency increases if current control is used.

⇒ Open S_1 & S_3 :

EQ. CKT.


$$V_{AB} = V_0$$



In the –ve half
Close S_1 & S_2

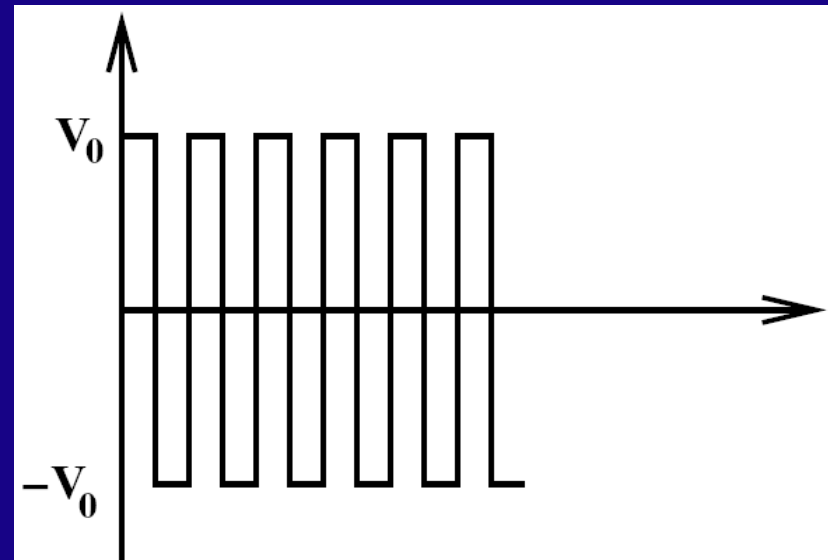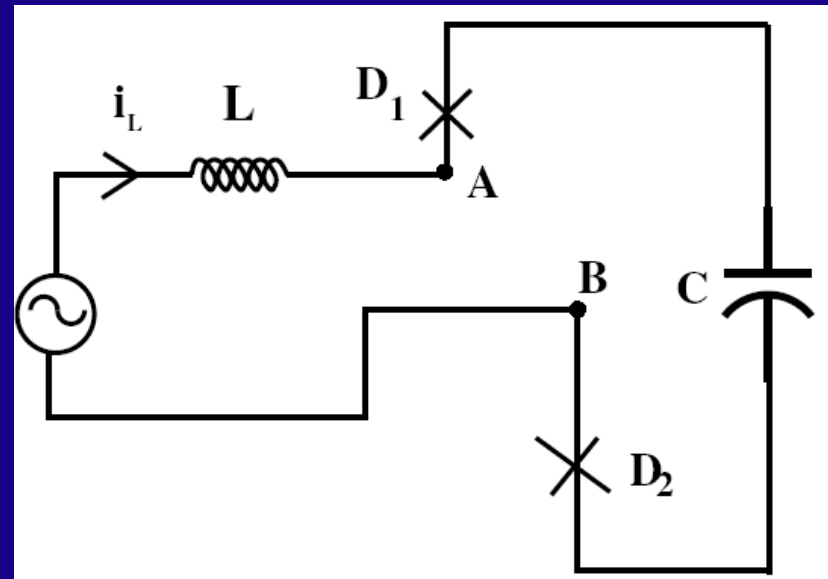

Regenerative mode :

Source is receiving power at UPF.

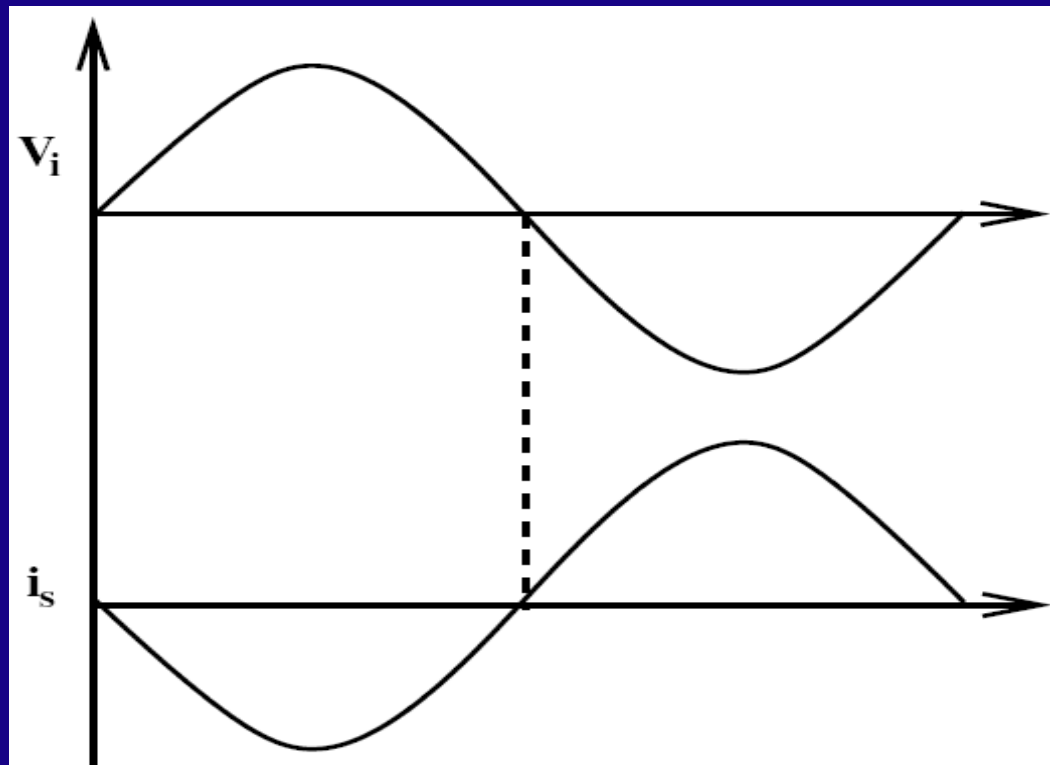

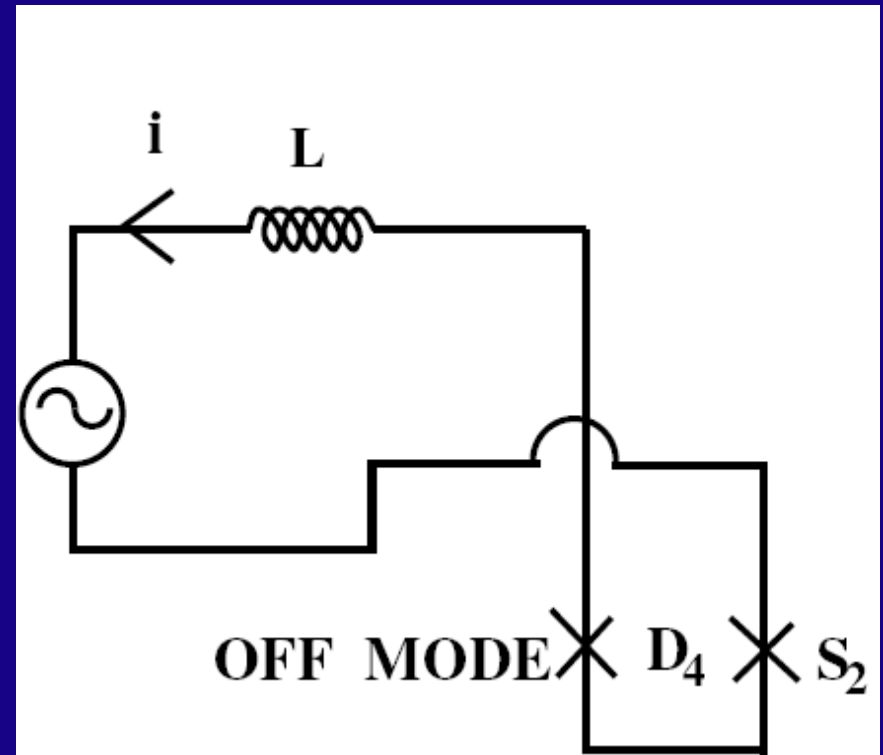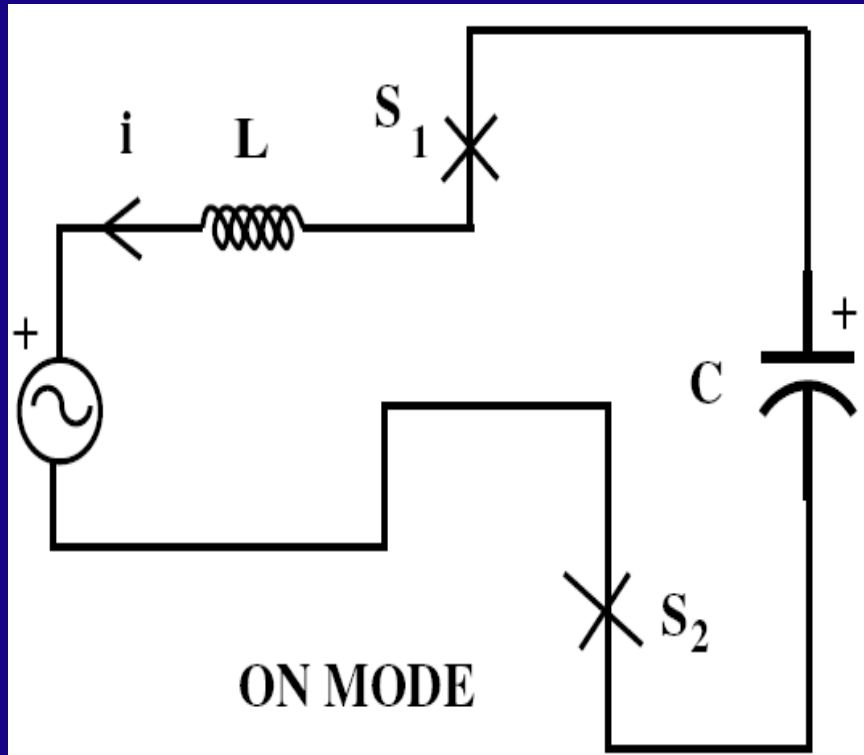

Summary of AC/DC conversion :

1) a. Half wave

b. Half controlled

c. Fully controlled

P.F. & Harmonic Spectrum are poor.

⇒ Only 1 pulse of current / $\frac{1}{2}$ cycle.



V_0 Ripple frequency = $2F$ for 1ϕ Bridge.
= $6F$ for 3ϕ Bridge.

Filtering requirement for $V_0 \downarrow$ in 3ϕ .

2) PWM Converter :

$$V_0 \propto m_i \quad \& \quad |V_0| < |V_m|$$

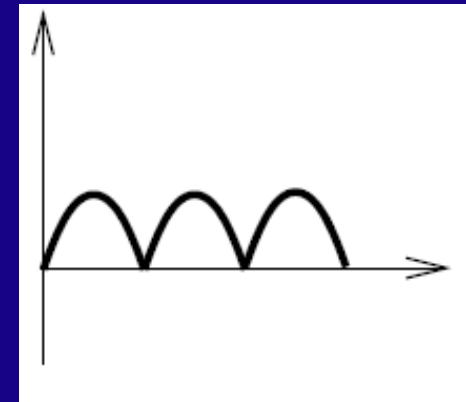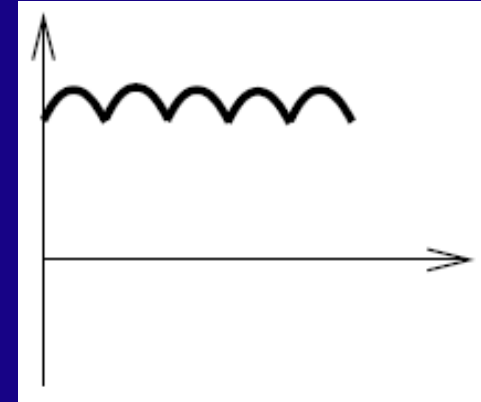⇒ Has large number of pulses in V_0 & I_s .



3) S.M.R (Switched Mode Rectifier) :

$$|V_0| > |V_m|$$

Source $I \approx$ Sinusoidal.

$$\text{P.F.} \approx 1$$

4) Bi – Directional Power Transfer :

Using bridge with self commutating devices

\Rightarrow Bi – Directional power transfer at UPF.

$\Rightarrow \pm \text{VAR}$ supply to the load.

\Rightarrow Active filtering.