
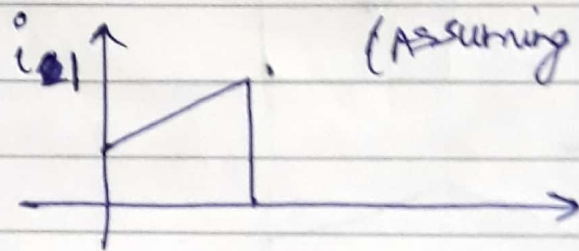



2 leakage impedances  $\rightarrow$  (small,  $\therefore$  voltage spike won't be that high)

# Ideal forward  $\rightarrow$  Acts like a current source

S closed  
 $i_e = i_2$

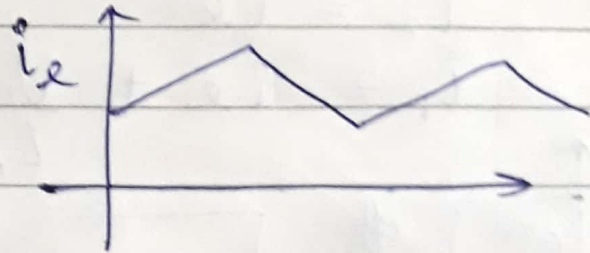


(Assuming leakage = 0)

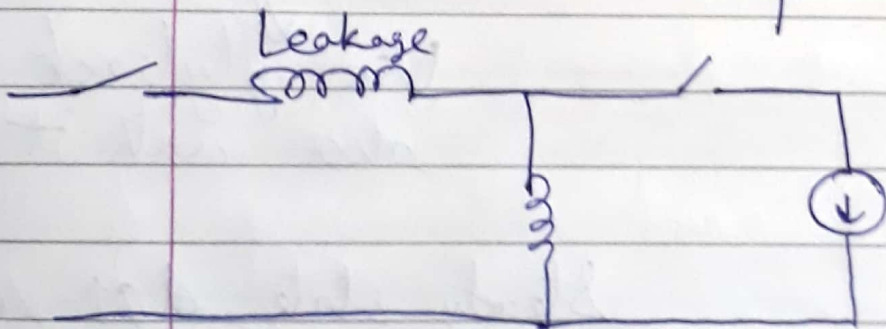

$\therefore$  Leakage won't allow instantaneous  $\uparrow$  in  $i_e$  when S closed

# Non-ideal forward

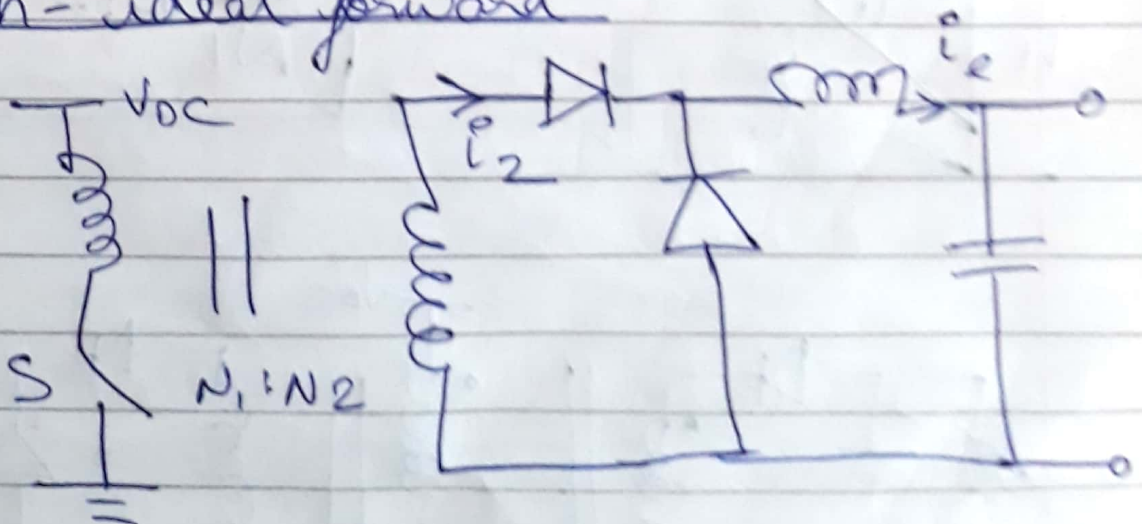



$S_1 \& S_2 \rightarrow \text{same}$

$S_1 \& S_2' \rightarrow \text{comp}$

$S_1 \text{ closed, } S_2' \text{ open}$


$$i_2 = i_2$$

$$i_1 = i_2 + \frac{V_{dc} dt}{L_m}$$



$\phi$  doesn't decay  
problem!

Use flyback  
also with it

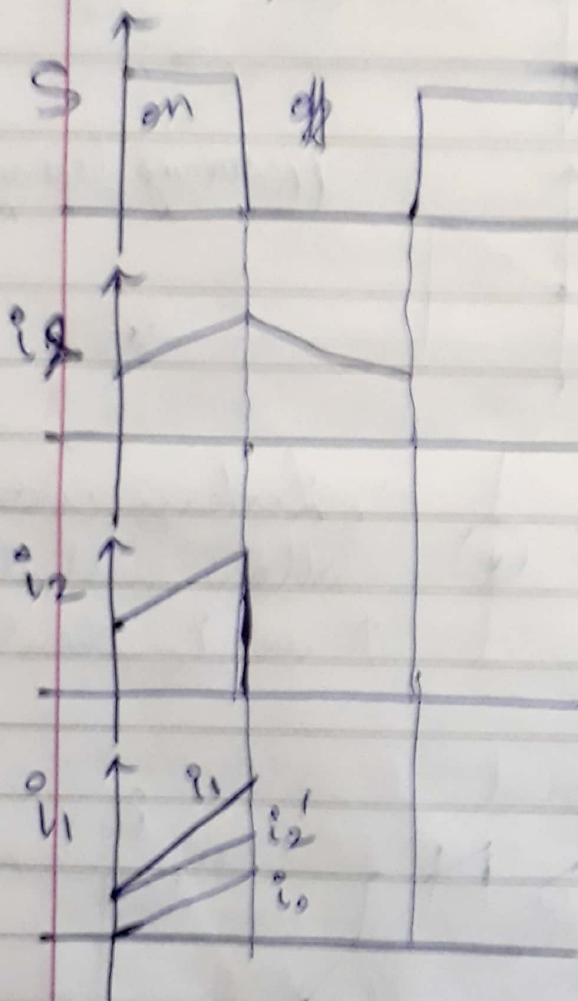

Steady state,  $\Delta \phi = 0$

$$\frac{V_{dc} DT}{N_1} = \frac{V_o'(1-D)T}{N_2}$$




$$V_o' = V_{dc} \frac{N_2 D}{N_1 (1-D)}$$

Flyback

$$V_o = V_{dc} \frac{N_2 D}{N_1}$$



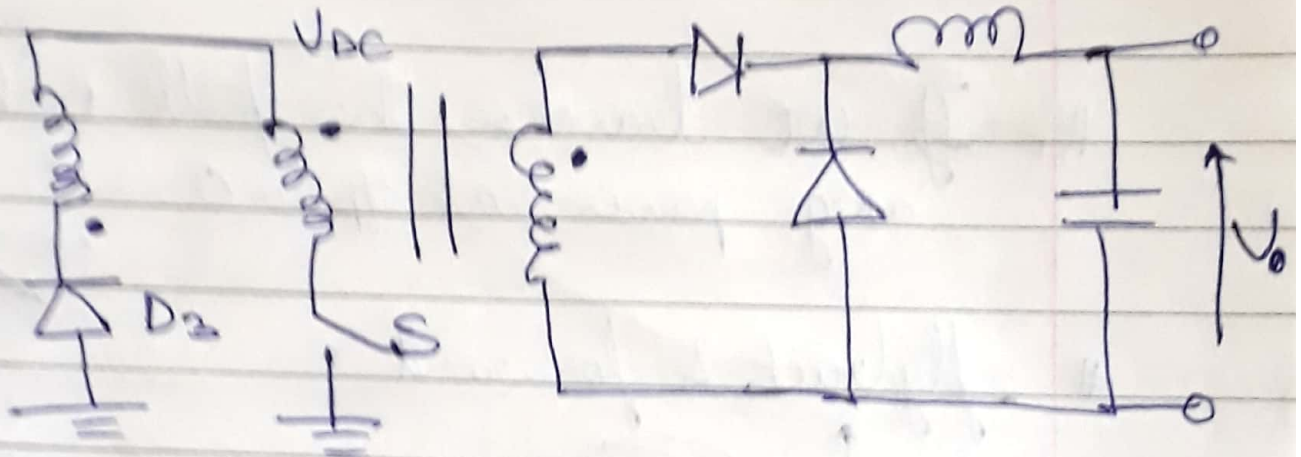We take  $N_1 = N_2 \rightarrow$  Easy for winding  
 $N_2$  has to carry only magnetising current  
 but  $N_1$  has to carry magn. + load current  
 $N_2 \rightarrow$  thin,  $N_1 \rightarrow$  thick.



$$\frac{V_{dc} DT}{N_1} \rightarrow \phi \uparrow$$



$$\frac{V_{dc}(1-D)T}{N_3 \text{ or } N_1} \rightarrow \phi \downarrow$$

$\therefore$  If  $D > 0.5$ ,  $\phi \uparrow$  & will keep  $\uparrow$ .



It is always operated in discont. conduction.

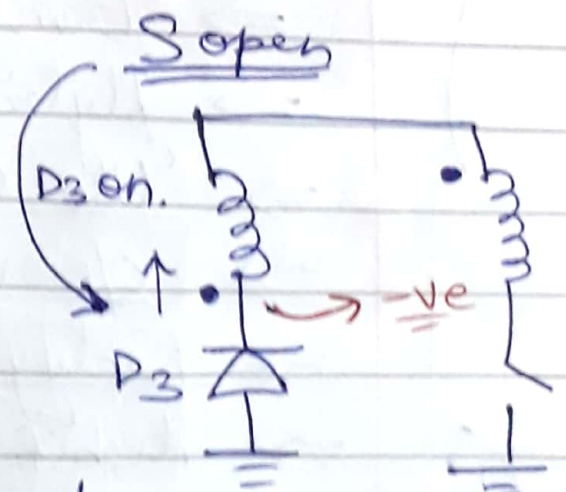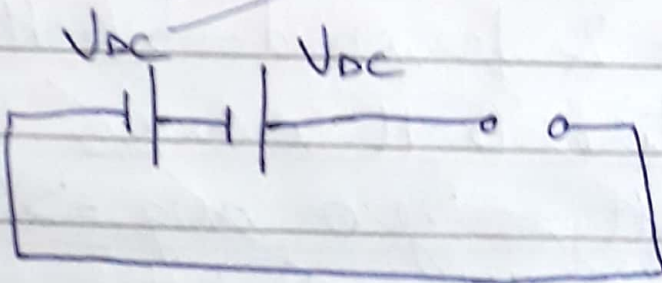5 Voltage  $\rightarrow$  AS  $N_1 = N_3$




We don't take  $V_o$  as  $D_2$  is open, unlike flyback.

# Flyback & forward

Both use transformers, but forward  
conv. use is better.

# If we traverse the full B-H curve,  
avg. power at  $\phi = 0$ .

# Flyback & forward

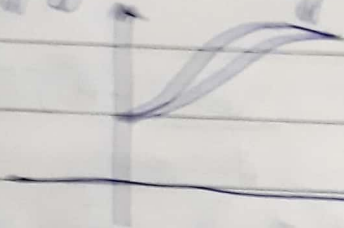

Avg.  $\phi$  will not be 0.

$\Rightarrow$  DC offset.

$\Rightarrow$  core may get sat.

# High Power applications

- # If significant difference in i/p & o/p  
 $\Rightarrow$  Transformer
- $\Rightarrow$  Flyback & forward  $\rightarrow$  B-H loop problem
- $\Rightarrow$  Use entire B-H curve
- $\Rightarrow$  o/p volt = zero avg  $\Rightarrow$  AC
- $\Rightarrow$  Rectify it (small filter cap)
- $\Rightarrow$  High  $f$  AC  $\rightarrow$  DC

High 'f' DC  $\rightarrow$  AC  $\rightarrow$  DC



- Loss =  $s P_2$

$\Rightarrow P_2 = \text{Air gap (rotor) power}$

Cu loss =  $s P_2$

Power developed =  $(1-s) P_2$

Bulk of power  $\rightarrow$  Im, pump & fans.


$$T_e \propto N_s^2$$

$$P.d = \frac{I_a^2 R_a (1-s)}{s}$$

$$T.d = \frac{I_a^2 R_a (1-s)}{N_s (1-s) s}$$

$$\therefore \frac{I_a^2 R_a}{N_s s} = k N_a^2 = k (1-s)^2$$
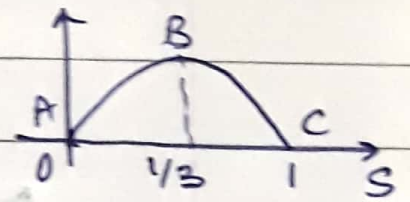
$$\therefore \boxed{I \propto (1-s) \sqrt{s}} \rightarrow$$




$N_s$  &  $N_a$  can't be too diff<sup>n</sup> for fan ( $T_{dw}$ )  
as  $s$  will be high.  $\Rightarrow$   $s P$  losses  $\Rightarrow$  heat

If  $T_e = k$ ,  $\frac{I_a^2 R_a}{N_s s} = k \Rightarrow I \propto \sqrt{s}$

$\therefore s$  should be low

$\therefore I_a^2$  losses  $\uparrow$  with  $\uparrow$  ins.

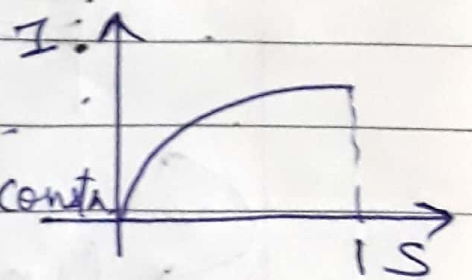As  $T_e$  is const<sup>n</sup>,  $\phi$  is also const<sup>n</sup>




$\rightarrow$  As  $s \uparrow$ ,  $N_a \downarrow$ .

If  $N_a \downarrow$ ,  $T_e \propto N_a^2 \downarrow \Rightarrow$  Input also  $\downarrow$   
&  $T$  also  $\downarrow$  from B-C
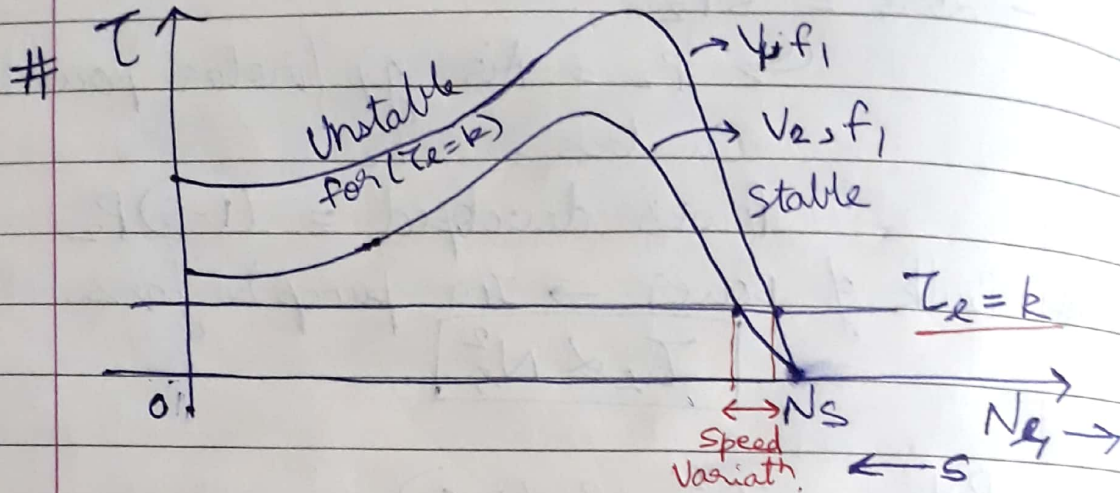
# ∴ If  $T_e = k$ ,  $s$  should be low & we need to change  $N_s$ .

∴ If  $T_e \propto \omega_r^2$ ,  $s$  can be large & no need to change  $N_s$ .



$T_e \propto V_{ph}^2$

$T_e \propto F_s \cdot F_r$

or  $\propto \beta I$


$\beta \propto V_{ph}$

$I \propto \beta \& \text{SN/s}$  (Prod. speed)

$\Rightarrow I \propto V_{ph} \text{ too}$

$\Rightarrow T_e \propto V_{ph}^2$

$I$  in Const.  $\omega_r$

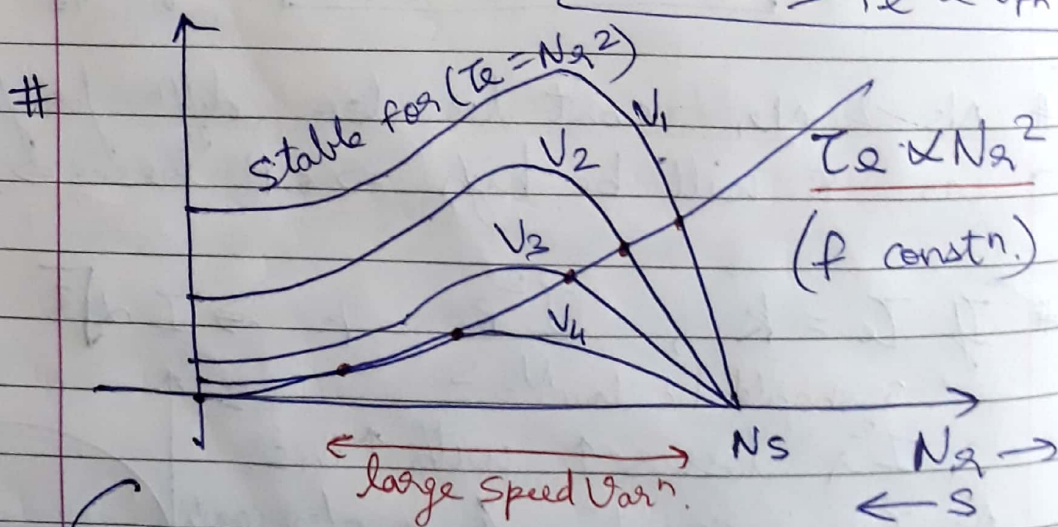


→ We can still make  $\eta = \eta_{max}$  i.e. (variable = constant losses)  
 (Hint: Reduce  $\phi$ , don't keep it const<sup>n</sup>)  
 $\Rightarrow$  Const losses & variable  $\omega_r$  &  $V_{ph}$


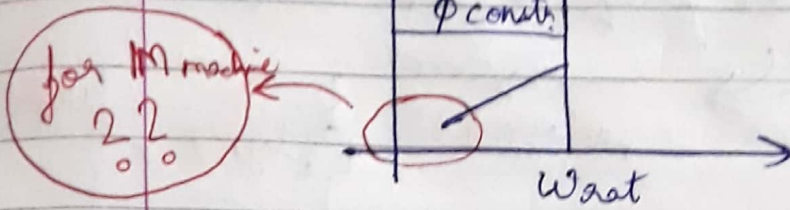
#  $E = k \omega \phi N_a$

~~for~~ keep  $\phi$  const  $\rightarrow \frac{V}{f} = k = (?)$



# To keep rotor current const.,  
 $\phi$  & SNs must be const. (Induced & Induced voltage)

4 pole, 50 Hz, 1455 rpm

At 415 V,  $\phi = \phi_{rated}$

$T = k$ ,  $N_a = 1455 \text{ rpm}$

SNs = 45 rpm

Now to keep  $I_r$  const., SNs = const.

To make  $N_a = 900 \text{ rpm}$ ,


$N_s = 945 \text{ rpm}$  (SNs = const)

$\Rightarrow$  calc.  $f$

Keep  $\frac{V}{f}$  const to keep  $\phi = \phi_{rated}$ .

$\Rightarrow$  Find  $V$ .

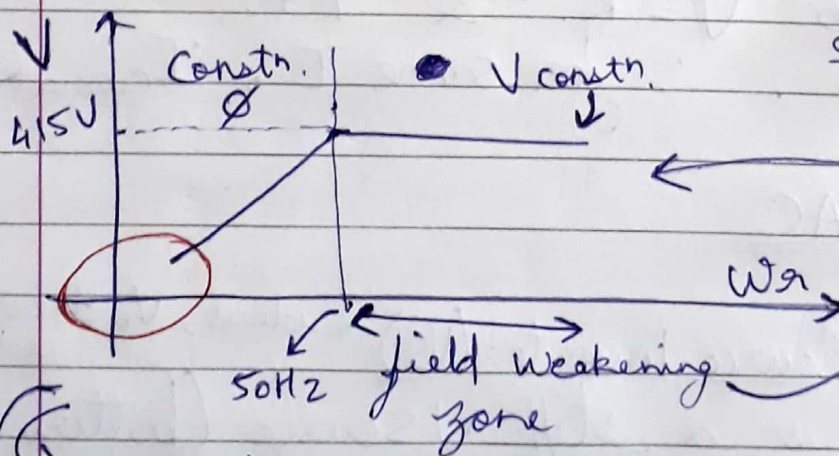$\therefore$  Need to generate 3 phase balanced supply.




$\phi \downarrow$   
 Keep  $V = k$ ,  
 $\uparrow f$ .

Q. Will it work for fan/pump?

A. No,  $V = k$ ,  $f \uparrow \Rightarrow \phi \downarrow \Rightarrow$  for same torque,  $I \uparrow$   
 & on  $\uparrow f$ ,  $T$  of fan needed also  $\uparrow \Rightarrow I \uparrow$ .



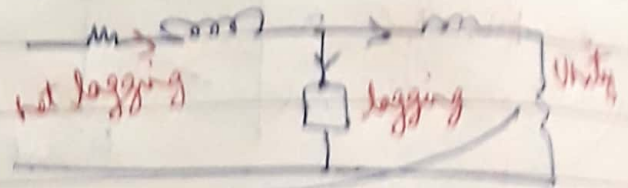
# IM  $\rightarrow$  always lagging.  
 $\hookrightarrow$  Rotor p.f. is almost unity,  
 as rotor freq.  $= s f \approx 0 \Rightarrow$  D.C.



While for transformer,  $(\checkmark)$  could be lead, lag, unity depending on load.

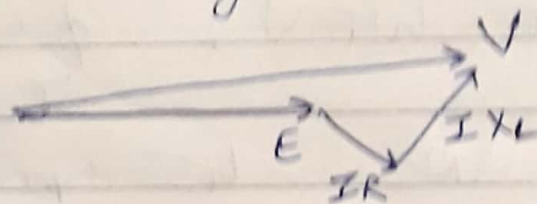At low freq's, magnitude rules,  $E = V - IR$



#  $0 < \omega < \omega_{rated}$


- $\rightarrow$  const.  $\phi$  operatn.  $\Rightarrow E/f$  const.
- $\rightarrow$  motor has capability to develop rated torque  $\Rightarrow$  control SNs.

#  $\omega > \omega_{rated}$  (field weakening)

- $\rightarrow$  keep  $V = k$  &  $\uparrow f$ .
- $\rightarrow \phi \downarrow$ ,  $\therefore$  for same  $T$ ,  $I_{current} > I_{rated}$

# DC - AC


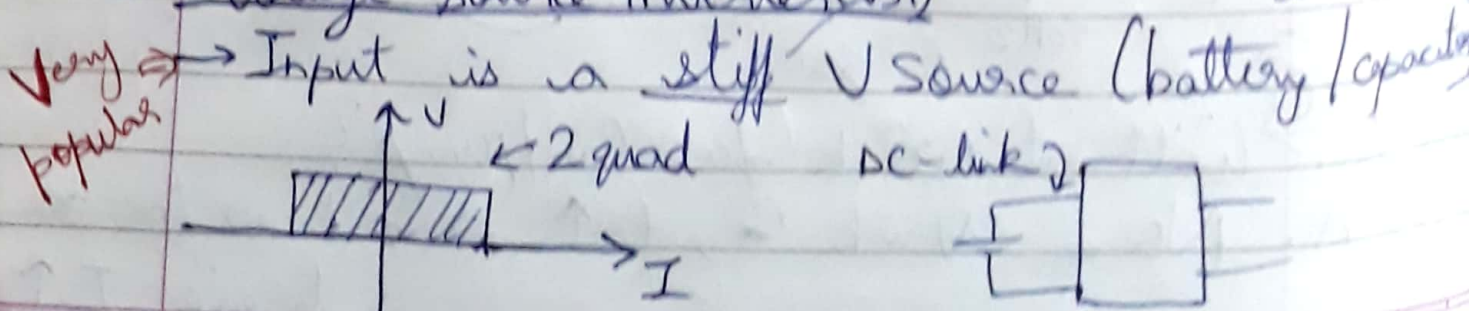
I. Voltage Source Inverter (VSI)  $\rightarrow$  ideal,  $V_o$  doesn't change with load






## II. Current Source Inverter (CSI)


Used at high powers

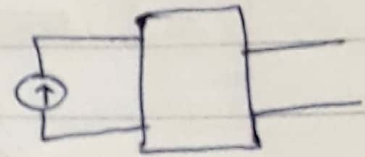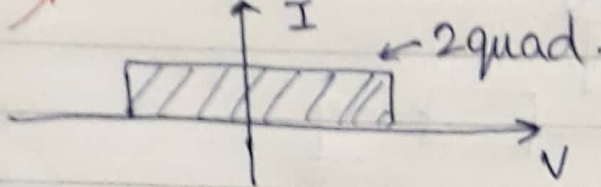

## # Half-Bridge

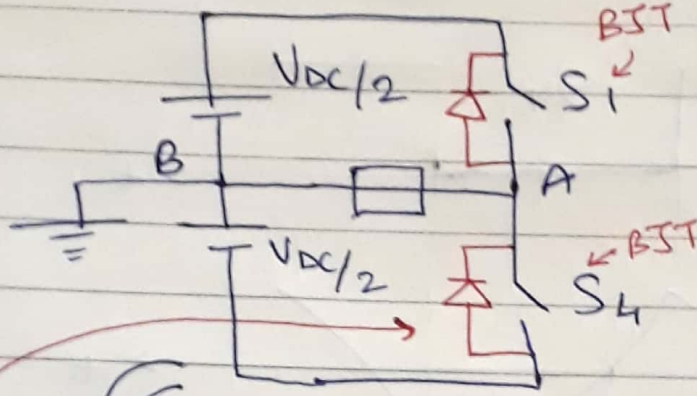

$S_1$  &  $S_4$  are complimentary

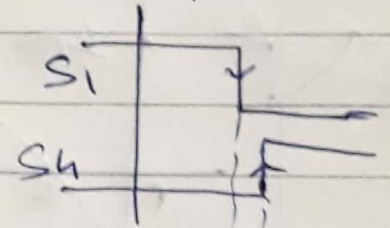


dead time

$S_1$  &  $S_4$  can't be closed at both time as then short circuit of volt. sources.

$\Rightarrow$  At high power (high  $V_{dc}$  too), current source is preferred as it can be shorted.

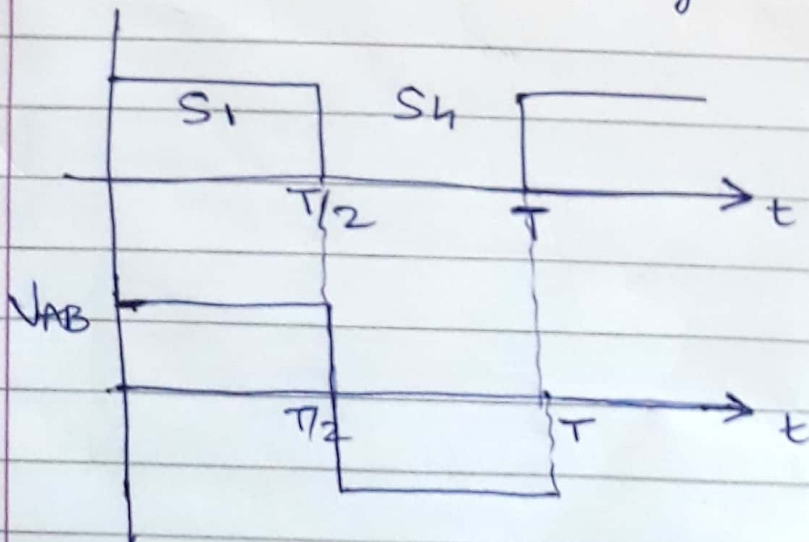We want A.C  $\Rightarrow$  Avg. value = 0  $\Rightarrow$   $D = 0.5$



$$T/2 = 10 \text{ ms} \\ \Rightarrow f = 50 \text{ Hz}$$

If load is inductive & we open  $S_1$ , in transient, we need to provide a path as  $I$  can't change instantaneously.

$\Rightarrow$  Put Diodes

